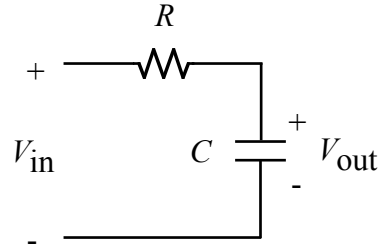


### Laplace Problem #3

In the circuit below,  $R = 4 \text{ k}\Omega$  and  $C = 1 \text{ }\mu\text{F}$ . The network is assumed to have no energy stored at  $t=0^-$



- Find the network function  $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$
- Find the impulse response  $h(t)$
- Find the step response using both the inverse Laplace method and the convolution method.
- Find the response of this network when  $v_{in}(t) = (3e^{-4 \times 10^3 t})U(t)$  [V] using both the inverse Laplace method and the convolution method
- Find the response of this network when  $v_{in}(t) = 2 \cos(2 * 10^3 t)U(t)$  [V] using both the inverse Laplace method and the convolution method