

EECS 212

S.P. 19-A

For the 2-port network below, find the Z parameters and from these show its equivalent “T” network. Note that this equivalent circuit will have no coupled components and no dependent sources.

