

For the parallel and series RC networks shown below:

- For given values of C_p and R_p , find the values of C_s and R_s that make the impedances/admittances of the two networks identical for a given value of ω .
- Show that the Q s of these two networks are the same at that value of ω .

