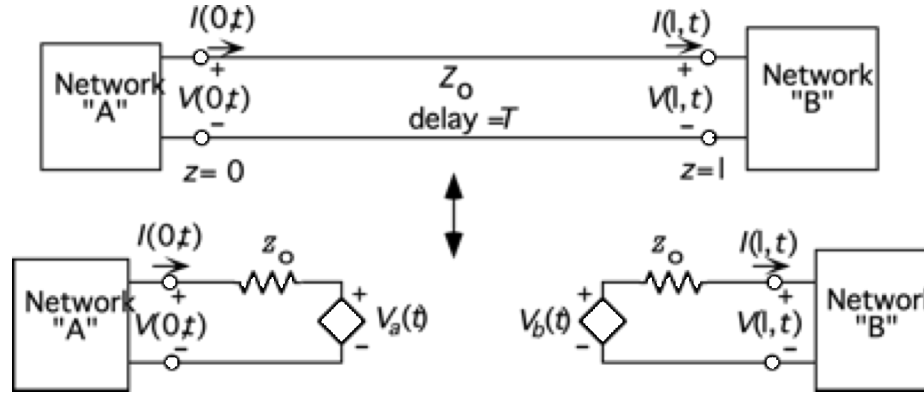


PSpice Model for a Lossless Transmission Line



$$\text{where: } V_a(t) = V(\ell, t - T) - Z_0 I(\ell, t - T) \quad \text{and} \\ V_b(t) = V(0, t - T) + Z_0 I(0, t - T)$$

To prove that Network “A” sees the equivalent circuit shown, we first note that the total voltage and current at any point of a transmission line can be expressed as the sum of forward and backward travelling components:

$$V = V^+ + V^- \quad \text{and} \quad I = I^+ + I^- = \frac{1}{Z_0} [V^+ - V^-] \quad (1)$$

From these, we find:

$$V^+ = \frac{1}{2} [V + Z_0 I] \quad \text{and} \quad V^- = \frac{1}{2} [V - Z_0 I] \quad (2)$$

We can use (1) to expand the total voltage $V(0, t)$ at the left side of the line as:

$$V(0, t) = V^+(0, t) + V^-(0, t)$$

Since $V^-(0, t)$ is backward (left) propagating, its value at the left side at time t is the same as its value at the right side at earlier time $t - T$, so we can write:

$$V(0, t) = V^+(0, t) + V^-(\ell, t - T) \quad ,$$

Next, using (2), we can write both $V^+(0, t)$ and $V^-(\ell, t - T)$ in terms of total voltages and currents, yielding

$$V(0, t) = \frac{1}{2} [V(0, t) + Z_0 I(0, t)] + \frac{1}{2} [V(\ell, t - T) - Z_0 I(\ell, t - T)]$$

From which we finally obtain:

$$V(0, t) = Z_0 I(0, t) + V(\ell, t - T) - Z_0 I(\ell, t - T) \quad ,$$

Which is exactly what we get by doing KVL around the left equivalent circuit at Network A. A similar development proves that right-hand equivalent circuit is indeed “seen” at Network “B”