

EECS 211  
Special Problem 7-1

For the circuit below,  $v_s(t)$  is nonzero *only* between 0 and 20 ms.

- (a) Find an expression for  $i(t)$  that is valid for *all* values of  $t$ .
- (b) Find the value of  $i(t)$  at  $t=8$  [ms],  $t=15$  [ms], and  $t=25$  [ms].

