

EECS 202
Special Problem 5-A

For the comparator circuit shown, plot $v_o(t)$ for a) $v_{\text{ref}} = +3 \text{ V}$, and b) $v_{\text{ref}} = -2 \text{ V}$

