

Figure P15.59 Twin-T RC circuit.

Step and Impulse Response

60. Consider the circuit of figure P15.60.

- Find the transfer function $H(s)$ and the impulse response $h(t)$.
- Tabulate $h(t)$ for $t = 0, 1, 2, \dots, 8$. Use this table to do the next three parts, assuming that $v_C(0^-) = 0$.
- If $v_{in}(t) = 328(t - 2)$ V, find $v_{out}(5)$.
- If $v_{in}(t) = 648(t - 2) + 168(t - 5) + 28(t - 8)$ V, find $v_{out}(8^+)$.
- If the input is a rectangular pulse of duration 1 ms and amplitude 1000 V, and if it is applied at $t = 0$ s, find the values of $v_{out}(t)$ at $t = 1, 2$, and 3 s. Compare with part (b). Note that in this RC circuit, the pulse width is much smaller than the circuit time constant; hence to the circuit this rectangular pulse looks like an impulse, $\delta(t)$.

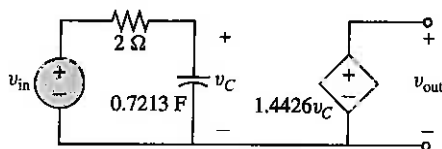


Figure P15.60

61. Consider the circuit of figure P15.61.

- Find the transfer function $H(s)$ and the impulse response $h(t)$.
- Find the response due to a unit step function input by two different methods:
 - Inverse Laplace transformation of $V_{out}(s)$.
 - Integration of $h(t)$.
- Find the response due to a unit ramp function input by two different methods:
 - Inverse Laplace transformation of $V_{out}(s)$.
 - Integration of the unit step response found in part (b).
- Find the maximum value of $|v_{out}(t)|$ due to an input $v_{in}(t) = 200u(t)$ V. Does the answer surprise you?

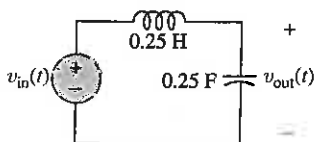


Figure P15.61

62. Consider the circuit of figure P15.62a.

- Find the transfer function $H(s)$ and the impulse response $h(t)$.
- Find the step response.
- Find $v_{out}(t)$ due to a rectangular pulse input, as shown in figure P15.62b, with $\Delta = 2/LC$. Hint: Make use of the result of part (b).
- Find $v_{out}(t)$ in part (c) when $\Delta \rightarrow 0$. Note: The result should agree with part (a), since $i_{in}(t)$ approaches $\delta(t)$.

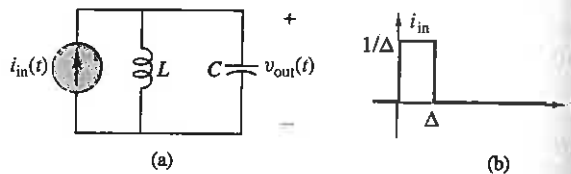


Figure P15.62

- Suppose the zero-state step response of the circuit of figure P15.63 is $i_{out}(t) = e^{-2t}u(t)$ A. Find the zero-state response to $i_{in}(t) = 2\delta(t - 1)$ A.
- Compute the zero-state response for $t \geq 0$ to a ramp input $4r(t)$. Recall that the ramp function is the integral of the step function.

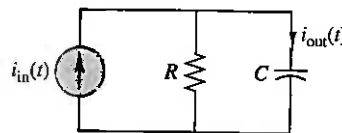


Figure P15.63

- For the circuit of figure P15.64, suppose $i_{in}(t) = Ku(t)$ A. $v_C(0^-) \neq 0$, and the response of the circuit for $t > 0$ is $v_C(t) = 2.5u(t) + 2.5e^{-0.2t}u(t)$ V. Find the values of K and $v_C(0^-)$.

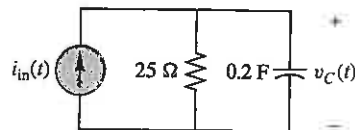


Figure P15.64

65. Suppose the impulse response of the network in figure P15.65 is

$$v_{out}(t) = [2e^{-t} + 3\cos(2t) - 1.5\sin(2t)]u(t) \text{ V.}$$

- Compute the transfer function $H(s)$.
- Find all poles and zeros, and draw the pole-zero plot.
- If there is no initial stored energy in the network i.e., no initial conditions, compute the network response to $v_{in}(t) = \sin(t)u(t)$ V. Does your answer make sense? Why or why not?

(d) 1
that 1
Does
stabl

66. A tir
zero-state
shifted in
 $h(t) = \delta'$
function.
by $f(t)$,
response

ANSWERS
67. The
to a ramp

(a) 1
 $v_2(t)$
(b) 1
 $v_3(t)$
(c) 1
 $v_4(t)$

68. For t
transform
of the im

Find $H_1(s)$
(a)
(b)

Initial- z

69. (a)

Find

- (d) Now suppose $v_{in}(t) = \cos(2t)u(t)$ V. For large t , show that $v_{out}(t) \approx Kt \cos(2t + \phi)$ V for appropriate K and ϕ . Does the response remain finite as $t \rightarrow \infty$? Is the network stable or unstable?

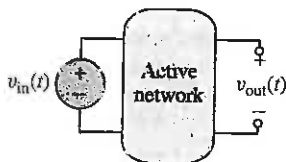


Figure P15.65

66. A time shift differentiator circuit has the property that its zero-state output is always equal to the derivative of its input shifted in time by some $T > 0$. Hence its impulse response is $h(t) = \delta'(t - T)$, a shifted version of the derivative of the delta function. Suppose $T = 1$ and the input to the circuit is given by $f(t)$, as sketched in figure P15.66. Compute the zero-state response $y(t)$ of the circuit at $t = 2.5$ s and $t = 6$ s.

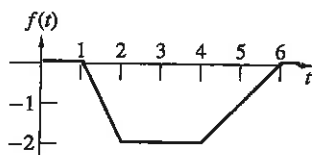


Figure P15.66

ANSWERS: -2, 1

67. The Laplace transform of the response of a relaxed circuit to a ramp $v_1(t) = r(t - 1)$ V is

$$Y(s) = \frac{e^{-2s}}{s^3}$$

- Find the response of this same relaxed circuit to an input $v_2(t) = u(t)$ V.
- Find the response of this same relaxed circuit to an input $v_3(t) = \delta(t)$ V.
- Find the response of this same relaxed circuit to an input $v_4(t) = 5\delta(t - 2)$ V.

68. For this problem you are to use the properties of Laplace transforms as listed in chapter 13. Suppose the Laplace transform of the impulse response $h(t)$ of a circuit is given by

$$H(s) = \frac{s + 2}{(s + 1)(s + 3)}$$

Find $H_1(s)$ and $H_2(s)$ when:

- $h_1(t) = h(4t)$,
- $h_2(t) = e^{-4t}h(4t - 8)$.

Initial- and Final-Value Problems

69. (a) The Laplace transform of a signal $f(t)$ is

$$\frac{(5s - 1)(4s - 5)(6s - 2)}{s(2s + 1)(3s + 2)(5s + 4)}$$

Find the value of $f(0^+)$.

- (b) Repeat part (a) when the Laplace transform of a signal $f(t - 1)u(t - 1)$ is

$$e^{-s} \frac{(10s - 1)(8s - 5)(12s - 2)}{s(2s + 1)(3s + 2)(5s + 4)}$$

ANSWERS: 4, 32.

70. The output $v_{out}(t)$ of a particular circuit is engineered to track a reference signal $v_{ref}(t)$. After the circuit overheated, it was found that

$$V_{ref}(s) - V_{out}(s) = \frac{1}{s} - \frac{1}{s} \ln \left(\frac{s + 1}{s + 0.2865} \right)$$

Find the difference $v_{ref}(t) - v_{out}(t)$ for large t .

ANSWER: -0.25.

71. Given the following functions $F_i(s)$, find $f_i(0^+)$ and $f(\infty)$ for those cases where the initial-value and final-value theorems are applicable (a root-finding program is useful in this endeavor):

$$(a) F_1(s) = \frac{21s + 5}{0.1s^2 + 4s + 3}$$

$$(b) F_2(s) = \frac{2s^3 + 7s^2 + s + 4}{s(s^3 + s^2 + 7s + 6)}$$

$$(c) F_3(s) = \frac{s^2 + 4s + 3}{s(s^4 + 5s^3 + 5s^2 + 4s + 4)}$$

72. (a) If $F(s) = (e^{-s}/s) \ln[(2.7183s + 1)/(s + 3)]$, find $f(1^+)$.

- (b) If $F(s) = (e^{-2s}/s) \ln[(s + 3)/(0.13533s + 1)]$, find $f(2^+)$.

ANSWERS: 1, 2.

73. The capacitor voltages $V_C(s)$ of various networks have Laplace transforms as given. Use only the initial- and final-value theorems to determine $v_C(0^+)$ and $v_C(\infty)$ for each of the transforms. If either theorem is not applicable, explain why.

$$(a) \frac{(14s - 1)^2}{s^2(7s + 2)}$$

$$(b) \frac{(2s - 15)(2 - e^{-6s})}{s(s + 10)(1 - e^{-3s})}$$

$$(c) 200 \frac{(0.1s - 1)(0.2s + 1)}{s(s^2 + 144)}$$

$$(d) \frac{16s - 1}{(2s + 1)^2} \left[1 + \frac{4s - 1}{2s + 1} + \left(\frac{2s - 1}{2s + 1} \right)^2 + \left(\frac{4s - 1}{2s + 1} \right)^3 \right]$$

74. The capacitor voltages $V_C(s)$ of various networks have Laplace transforms as given. Use only the initial- and final-value theorems to determine $v_C(0^+)$ and $v_C(\infty)$ for each of the transforms. If either theorem is not applicable, explain why.

$$(a) 20 \frac{0.1s - 1}{s(2s + 25)}$$

$$(b) \frac{(6s + 1)(3s + 1)(2 - e^{-20s})}{s^2(4 - e^{-2s})}$$

$$(c) \frac{4}{s} - \frac{e^{-\sqrt{s}}}{s(s + 0.5)}$$

$$(d) \frac{Ke^{-2/s}}{s}$$