

Find $v_r(t)$ for all $t > 0$ in the circuit below. Evaluate these expressions at $t = 10$ and $20 \mu\text{s}$.

