Salen-Key Oscillator



$$\frac{V_{-} - V_{g}}{R_{g}} + \frac{V_{-} - V_{0}}{R_{f}} = 0$$

After *a lot* of manipulations, these equations yield:

$$V_{0}(s) = -\frac{R_{f}}{R_{g}}V_{g}(s) \frac{s^{2} + \frac{3}{RC}s + \left(\frac{1}{RC}\right)^{2}}{s^{2} + \left(\frac{3-G}{RC}\right)s + \left(\frac{1}{RC}\right)^{2}}$$

Where $G=1+R_f/R_g$ is the dc gain of the op amp circuit.

We know of course that it's the denominator that determines the nature of the transient response.

Comparing this denominator, the standard form:
$$s^2 + \left(\frac{3-G}{RC}\right)s + \left(\frac{1}{RC}\right)^2 = s^2 + 2\varsigma\omega_0 s + \omega_0^2 s$$

we find: $\varsigma = \frac{1}{2}(3-G)$ and $\omega_0 = 1/RC$. From this, we see that the transient response of this circuit will be of the form: $e^{-\omega_0 \varsigma t} \cos(\omega_0 \sqrt{1-\varsigma^2} t)$.

Clearly, if, $G = \left(1 + \frac{R_f}{R_g}\right) = 3$, $\zeta = 0$, and the output will NOT decay with time so the circuit that produces a sinusoid of frequency $f = \frac{\omega_0}{2\pi} = \frac{1}{2\pi RC}$.