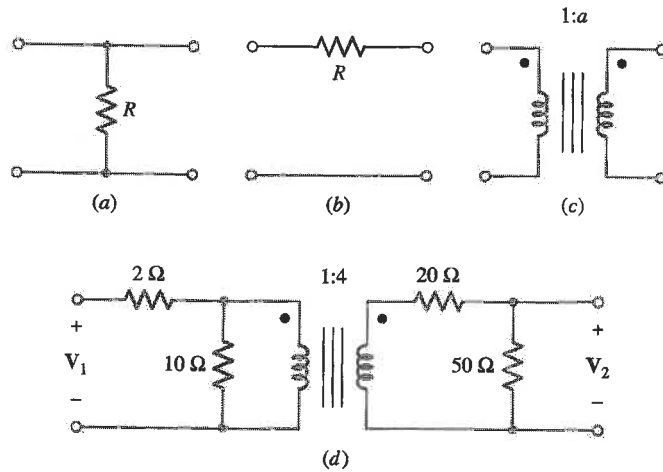


S. P. 19-B

58. (a) Find T_a , T_b , and T_c for the networks shown in Fig. 17.66a, b, and c.
 (b) By using the rules for interconnecting two-ports in cascade, find T for the network of Fig. 17.66d.



■ FIGURE 17.66