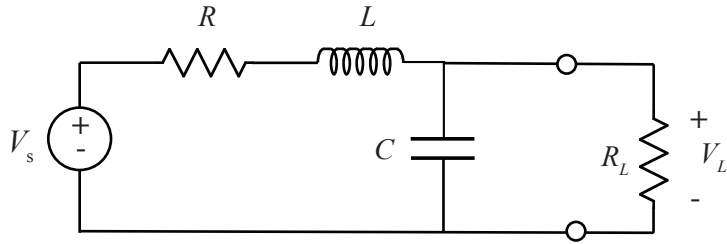


S.P. #14-D

The circuit below is operating as a resonant voltage multiplier.



The source has values:  $V_s = 1$  [V],  $R = 1$   $\Omega$ ,  $L = 15.9$   $\mu\text{H}$ ,  $C = 1.59$  nF. and the operating frequency is 1 MHz.

Find the load voltage  $v_L$  for a)  $R_L \rightarrow \infty$ , b)  $R_L = 10$   $\text{k}\Omega$ , c)  $R_L = 1$   $\text{k}\Omega$ .

Hint: It would make it a lot easier to note that for all values of  $R_L$ , the parallel combination of the load resistor and the capacitor has a high  $Q$ , which means that the parallel combination can be considered as roughly the same  $C$ , in series with a much smaller resistor.