

S.P. #00 (40 pts)

For the circuit shown below, find the steady-state response $v_0(t)$ using:

a) phasor analysis

b) Laplace analysis. (note: you can ignore the transient response)

