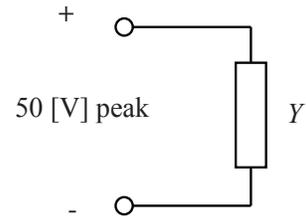


### Special Problem 11.5

A 50 [V] peak sinusoidal voltage is applied to a load with admittance  $Y = 20 + j10$  [mS]

- a) Find the average power  $P$  delivered to the entire load



- b) Consider the load to be the parallel combination of a resistor  $R_p$  and a reactance  $X_p$ . Find this resistance, and find the power delivered to it and show that it is the same as in a).

- c) Now, consider the load to be a series combination of a resistor  $R_s$  and a reactance  $X_s$ . Find this resistance, and show that the power delivered to it is the same as found in a)-c).