
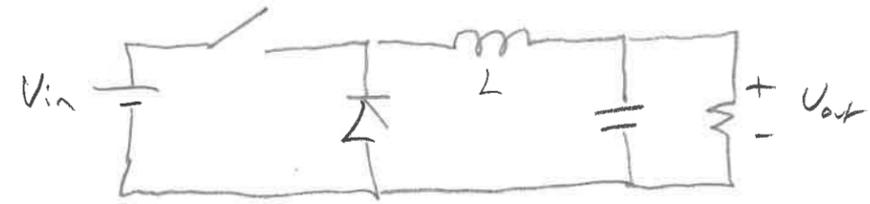


# Buck

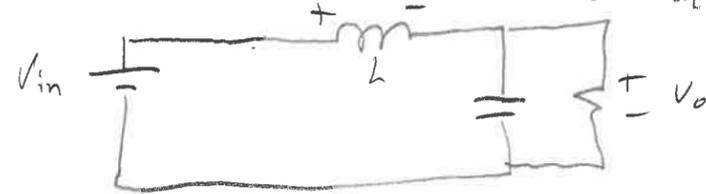



Switch closed

$$V_L = V_{in} - V_o = L \frac{di_L}{dt}$$



Switch open


$$v_L = -v_o = L \frac{di_L}{dt}$$

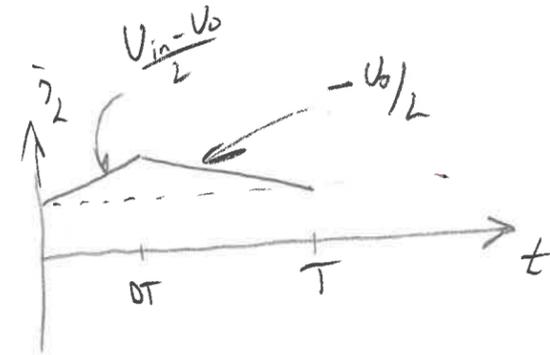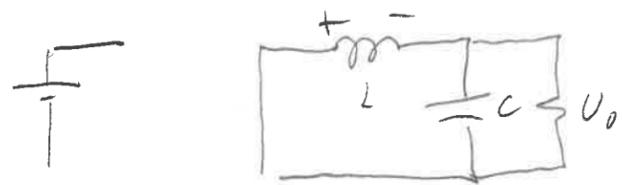


$$\Delta i_L = DT \left( \frac{V_{in} - V_o}{L} \right) + T(1-D) \left( -\frac{V_o}{L} \right) = 0$$

$$\Rightarrow V_o = D V_{in}$$



# Boost

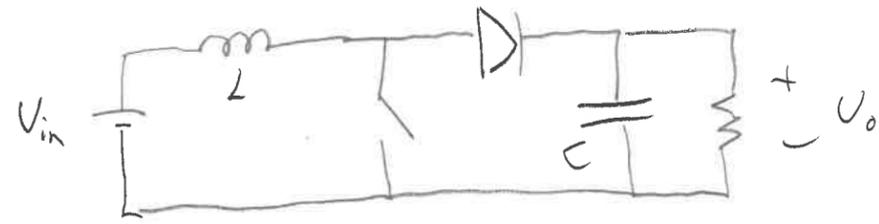

Switch closed

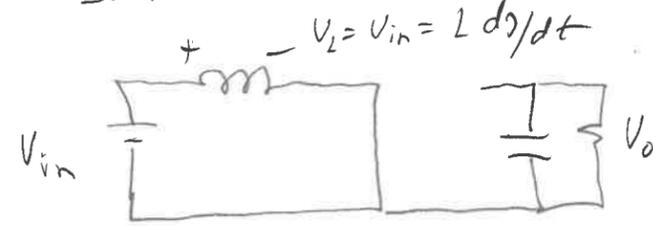


Switch open

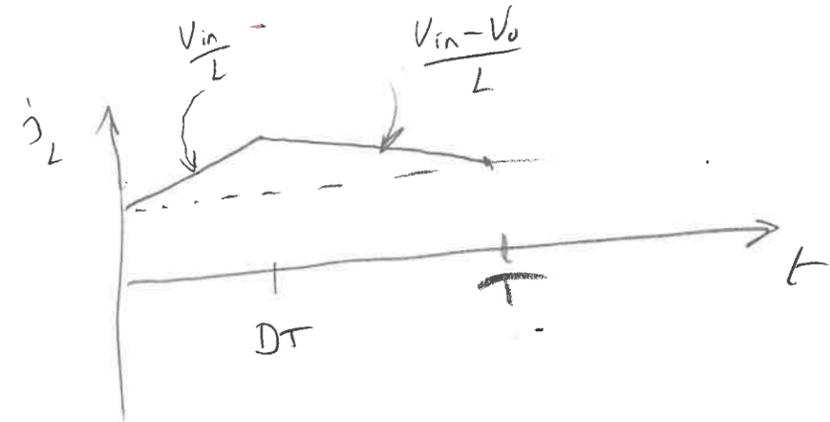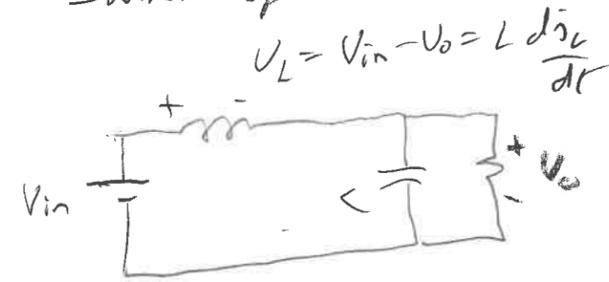



$$\Delta i = DT \left( \frac{V_{in}}{L} \right) + T(1-D) \left( \frac{V_{in} - V_o}{L} \right) = 0$$

$$\Rightarrow V_o = \frac{V_{in}}{1-D}$$


# Buck - Boost

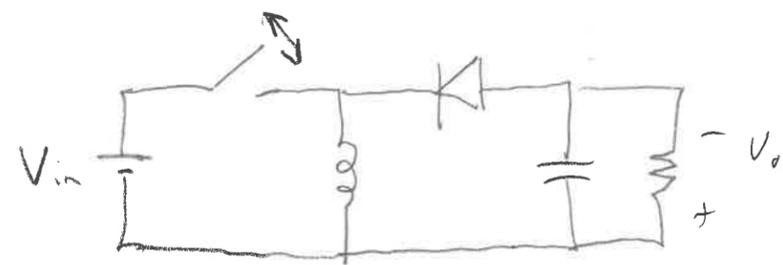

Switch closed

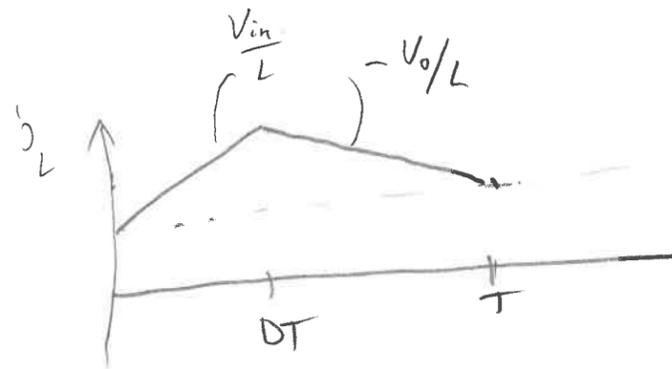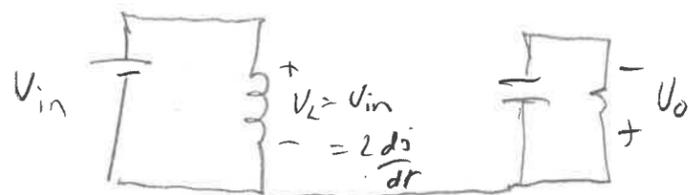



Switch open

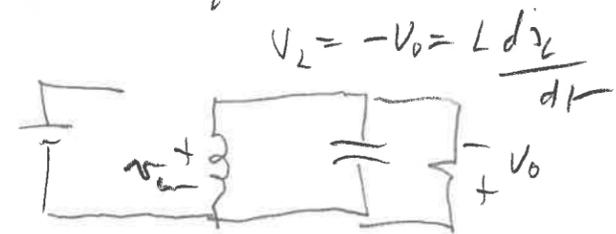


$$\Delta i = DT \left( \frac{V_{in}}{L} \right) + T(1-D) \left( -\frac{V_o}{L} \right) = 0$$

$$V_o = \frac{D}{1-D} V_{in}$$

# Fly Buck

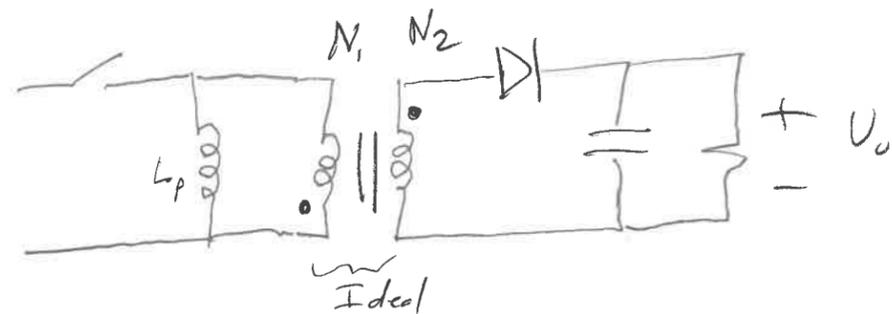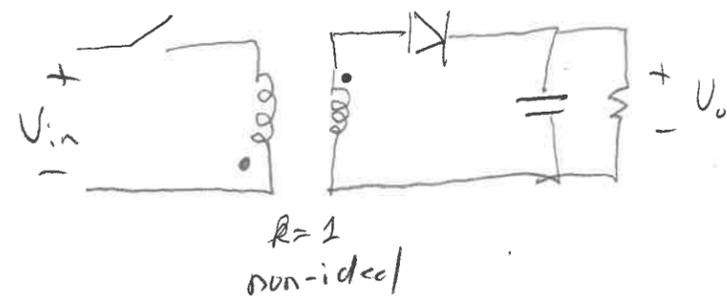

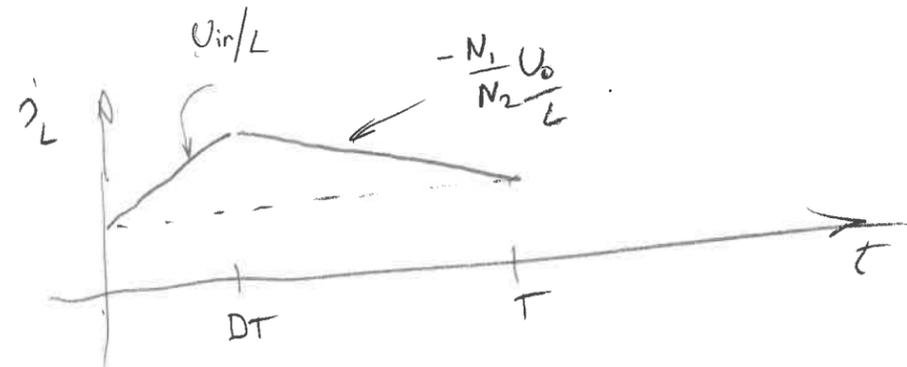Switch - closed  
 $V_2 = V_{in} = L \frac{di_2}{dt}$



Switch open



$$V_2 = -\frac{N_1}{N_2} U_o = L \frac{di_2}{dt}$$

$$\Delta i_2 = DT \left( \frac{V_{in}}{L} \right) + T(1-D) \left( -\frac{N_1}{N_2} \frac{U_o}{L} \right) = 0$$

$$U_o = \frac{N_2}{N_1} \times \frac{D}{1-D} V_{in}$$