

TL-4 Using a bounce diagram, generate a plot of $V_o(t)$ for $0 < t < 8.5$ ns in the circuit. Comparing $V_o(t)$ with $V_s(t)$, what would you say is the effect of the transmission line on the transmitted waveform?

