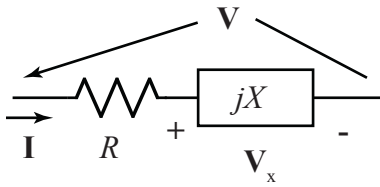


## The Meaning of Q



For the impedance  $Z=R+jX$ ,  $V$  is the (peak) phasor across the entire impedance, and  $V_x$  is the voltage across the reactive part. The complex power delivered to  $Z$  is:

$$S = \frac{1}{2} VI^* = \frac{1}{2} (ZI)I^* = \frac{1}{2} |I|^2 Z = \frac{1}{2} |I|^2 R + j \frac{1}{2} |I|^2 X$$

Thus,

$$P = \text{Re}(S) = \frac{1}{2} I_m^2 R \quad \text{and} \quad Q = \text{Im}(S) = \frac{1}{2} I_m^2 X,$$

Where  $I_m$  is the peak value of the load current. We already know that  $P$  is the average power consumed by the load, so now we ask the question: what kind of power does  $Q$  represent?

Since  $Q$  is clearly associated with the reactive load, let's look at the instantaneous power  $p_x(t)$  delivered to the reactive part of the load. Since  $V_x = jXI = jXI_m \angle \theta_I$ ,  $\theta_I$  are the (peak) phase of the load current. This gives us,

$$v_x(t) = XI_m \cos(\omega t + \theta_I \pm 90^\circ)$$

Where the  $+$  sign is for when  $X > 0$  (inductive) and the  $-$  sign is for when  $X < 0$  (capacitive).

Hence,  $p_x(t)$  is

$$\begin{aligned} p_x(t) &= v_x(t)i(t) = XI_m^2 \cos(\omega t + \theta_m) \cos(\omega t + \theta_m \pm 90^\circ) \\ &= \frac{XI_m^2}{2} [\cos(90^\circ) + \cos(2\omega t + 2\theta_m \pm 180^\circ)] = \frac{XI_m^2}{2} \cos(2\omega t + 2\theta_m \pm 180^\circ) \end{aligned}$$

Thus, the peak value of  $p_x(t)$  is  $\frac{XI_m^2}{2}$ , which is the same as  $Q$ !

**Hence, the quadrature power  $Q$  is the peak power delivered to (and then supplied by) the reactive part of the load.**