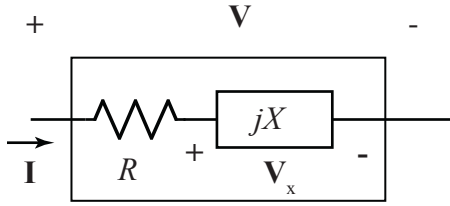


The Meaning of Quadrature Power



For the impedance $Z = R + jX$, V is the (peak) phasor across the entire impedance, and V_x is the voltage across the reactive part. The complex power delivered to Z is:

$$S = \frac{1}{2} V I^* = \frac{1}{2} (Z I) I^* = \frac{1}{2} |I|^2 Z = \frac{1}{2} |I|^2 R + j \frac{1}{2} |I|^2 X$$

Thus,

$$P = \text{Re}(S) = \frac{1}{2} I_m^2 R \quad \text{and} \quad Q = \text{Im}(S) = \frac{1}{2} I_m^2 X,$$

Where I_m is the peak value of the load current. We already know that P is the average power consumed by the load, so now we ask the question: what kind of power does Q represent?

Since Q is clearly associated with the reactive load, let's look at the instantaneous power $p_x(t)$ delivered to the reactive part of the load. Since $V_x = jX I = jX I_m \angle \theta_I$, θ_I are the (peak) phase of the load current. This gives us,

$$v_x(t) = X I_m \cos(\omega t + \theta_I \pm 90^\circ)$$

Where the $+$ sign is for when $X > 0$ (inductive) and the $-$ sign is for when $X < 0$ (capacitive).

Hence, $p_x(t)$ is

$$\begin{aligned} p_x(t) &= v_x(t) i(t) = X I_m^2 \cos(\omega t + \theta_m) \cos(\omega t + \theta_m \pm 90^\circ) \\ &= \frac{X I_m^2}{2} [\cos(90^\circ) + \cos(2\omega t + 2\theta_m \pm 180^\circ)] = \frac{X I_m^2}{2} \cos(2\omega t + 2\theta_m \pm 180^\circ) \end{aligned}$$

Thus, the peak value of $p_x(t)$ is $\frac{X I_m^2}{2}$, which is the same as Q !

Hence, the quadrature power Q is the peak power delivered to (and then supplied by) the reactive part of the load.