
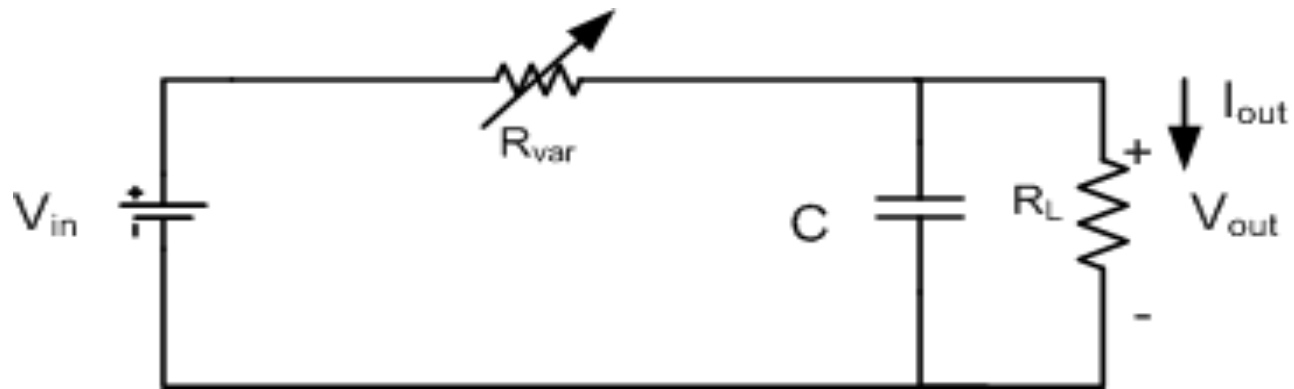


Linear (Step-Down) Converter

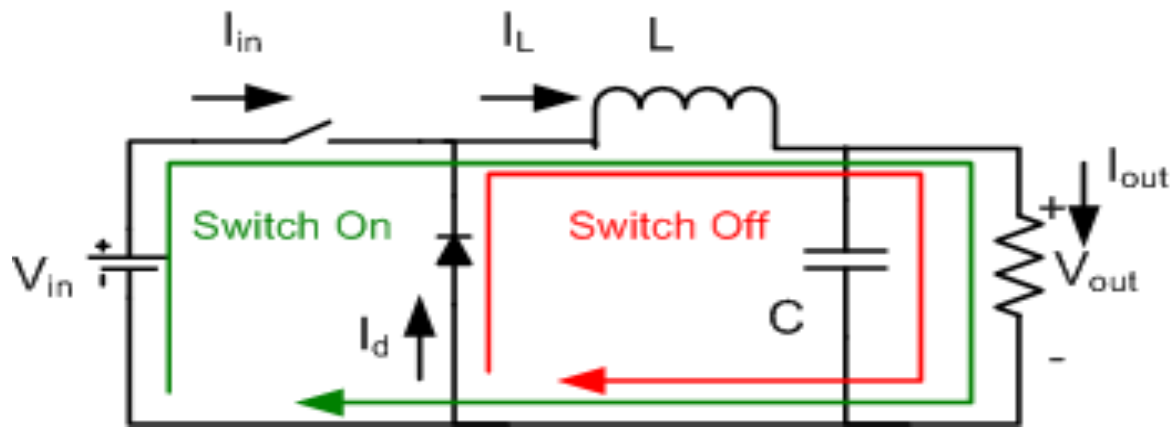


- $V_{out} = V_{in} * R_L / (R_{var} + R_L)$
- Capacitance smoothes out load and source transients



Buck (step-down) Converter



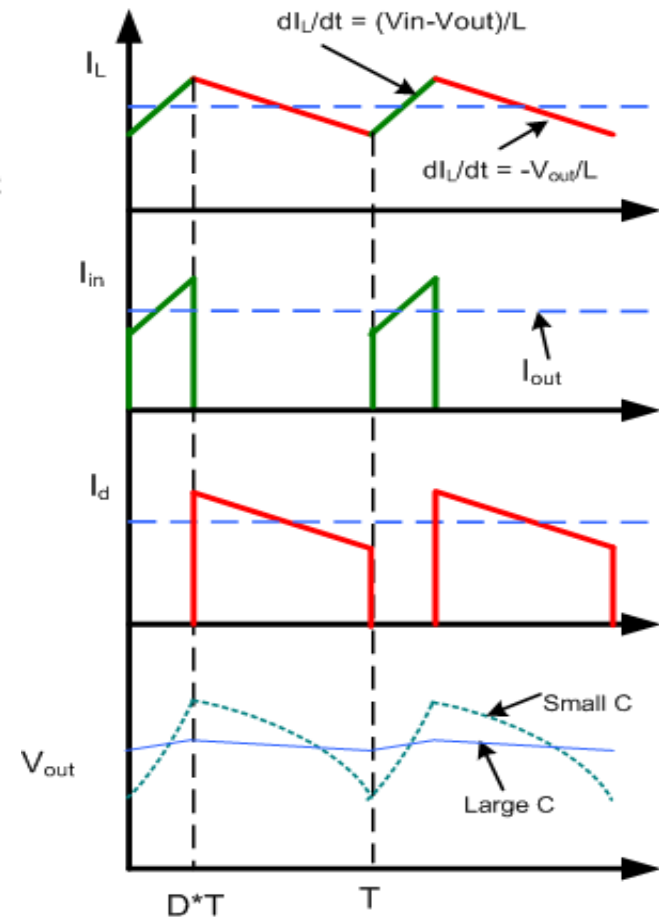- $V_{out} = V_{in} * D$
- Capacitance smoothes out effects of inductor ripple current and load variations




Boost (step-up) Converter

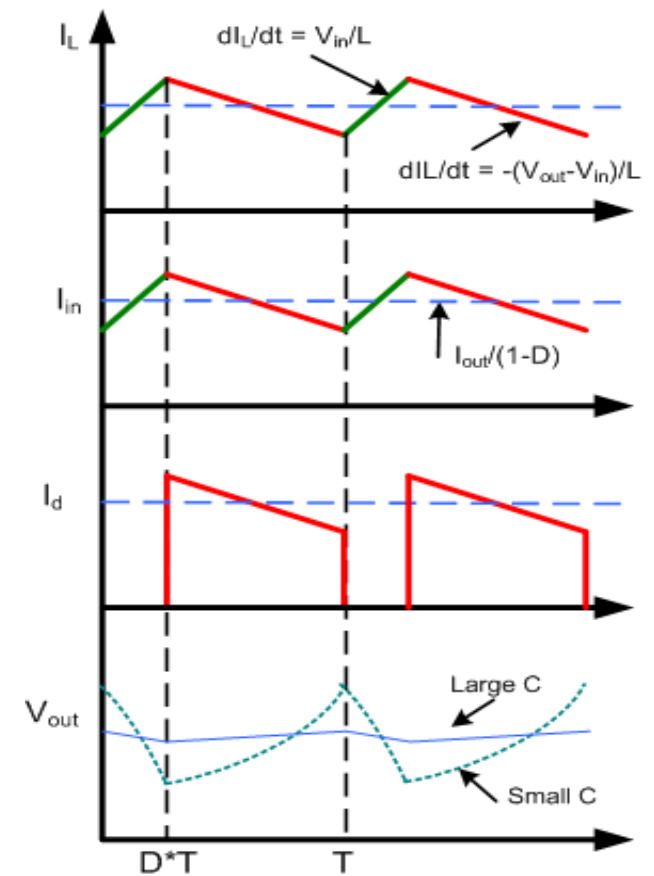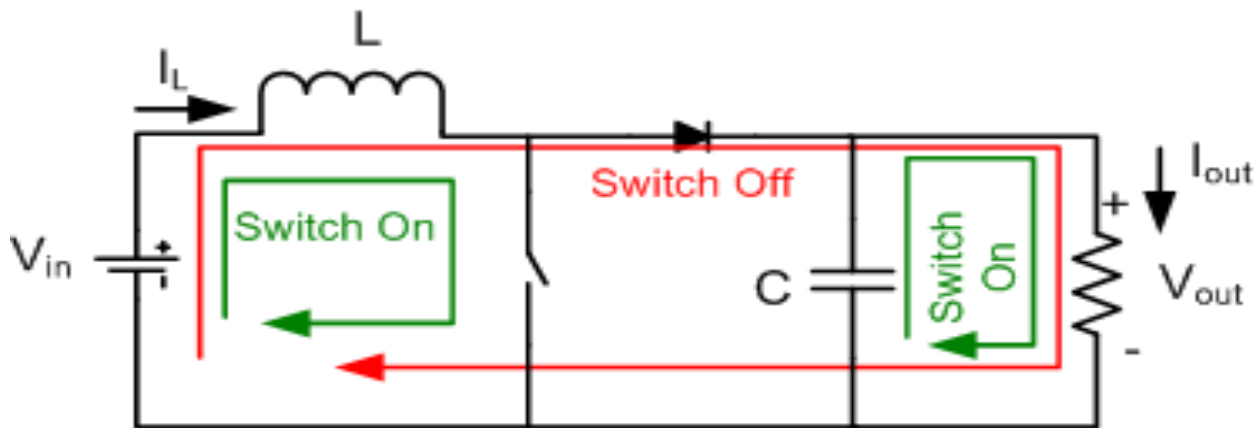


- $V_{out} = V_{in} / (1-D)$
- Capacitor C smoothes out effects of inductor ripple current and load variations


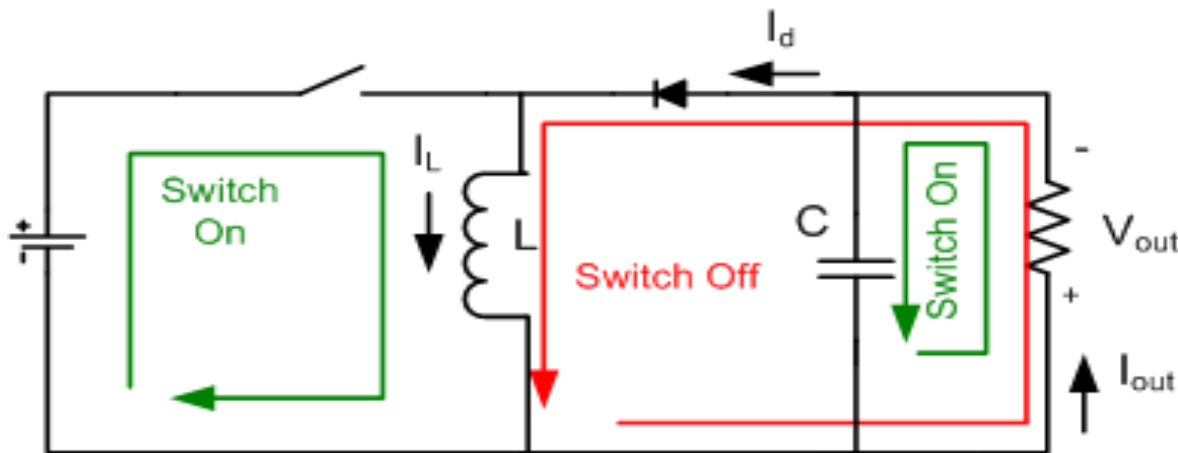
Buck-Boost (invert, step-up/down) Converter



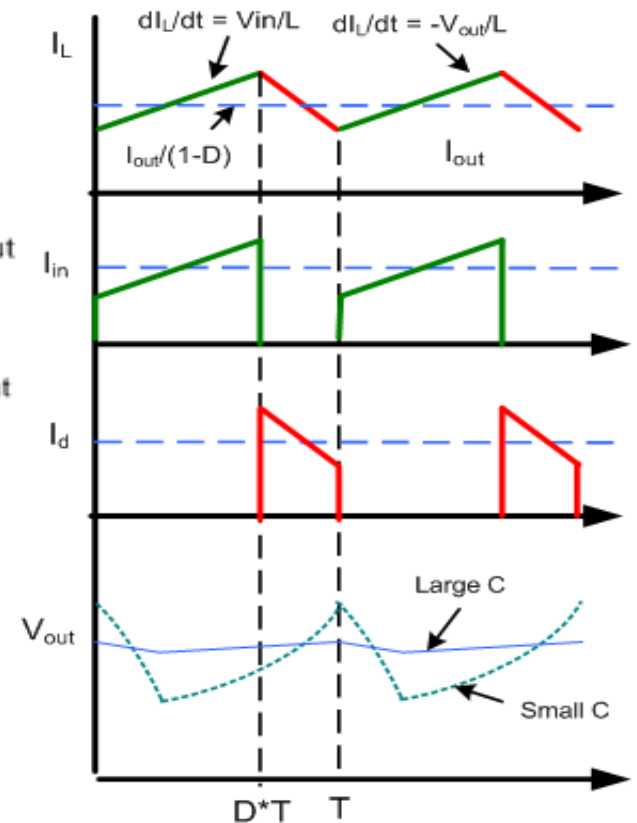- $V_{out} = V_{in} * D / (1-D)$
- Ripple current inversely proportional to inductance L
- Capacitance smoothes out effects of inductor ripple current and load variations
- $V_{out} > V_{in}$ requires $D > 1/2$



Flyback Converter

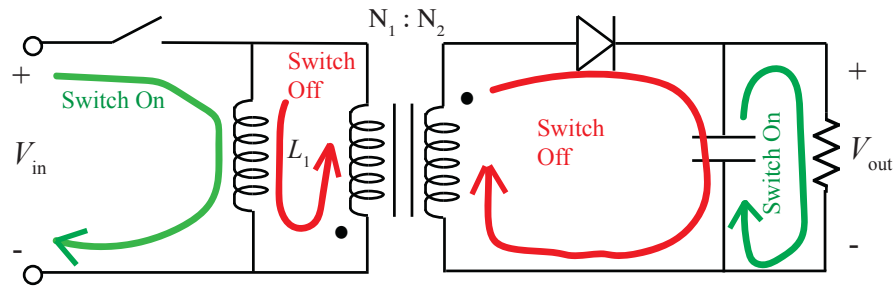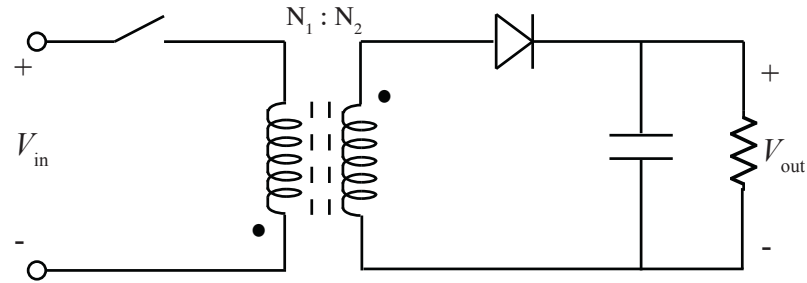

$$V_{out} = V_{in} * (N_2/N_1) * D / (1-D)$$