

**Prerequisites: The class will build on concepts from Circuits I and II.**

**A key skill for success in the course is the ability to analyze electronic schematics (circuits).**

**Primarily containing these three components:**

- 1. Voltage Source.**
  - 2. Current Source.**
  - 3. Resistor.**
  - 4. Some Basic Capacitor and Inductor.**
- \*. We will add others as the semester progresses.**

**Given a circuit – you should be able to:**


- 1. Identify voltages and currents.**
- 2. Determine component values to obtain voltages and currents.**
- 3. Find transfer functions.**

**Need to be capable of conducting both Mesh and Nodal Analysis.**



**Mesh: Currents are unknowns – use KVL to build a set of equations.**

**Nodal: Voltages are unknowns – use KCL to build a set of equations.**




# Example Circuit:

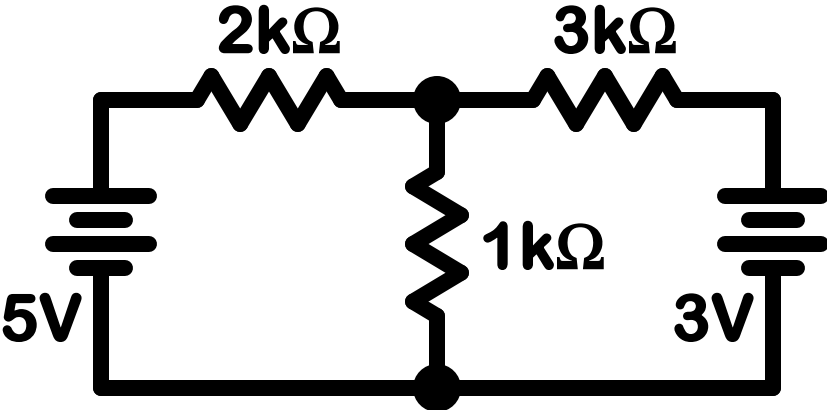


**Example Circuit:**

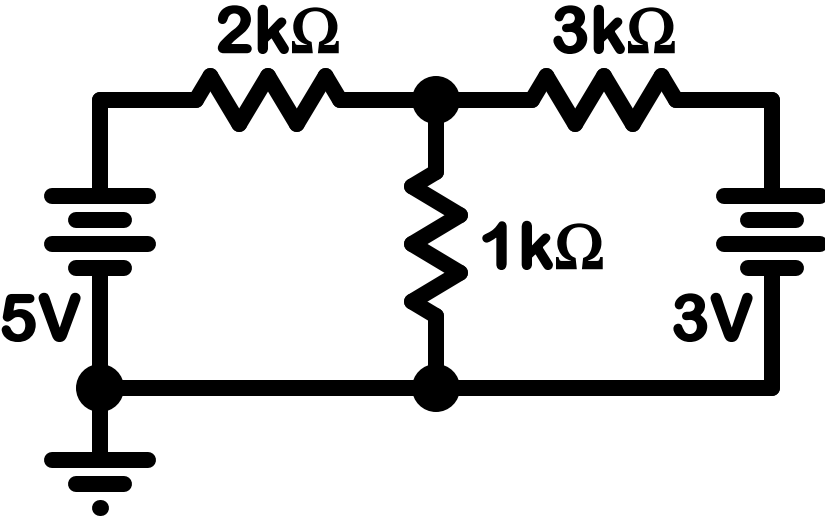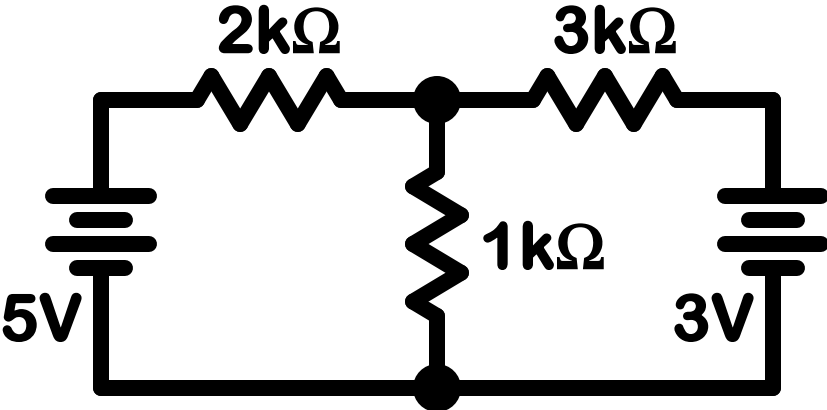




# Example Circuit:

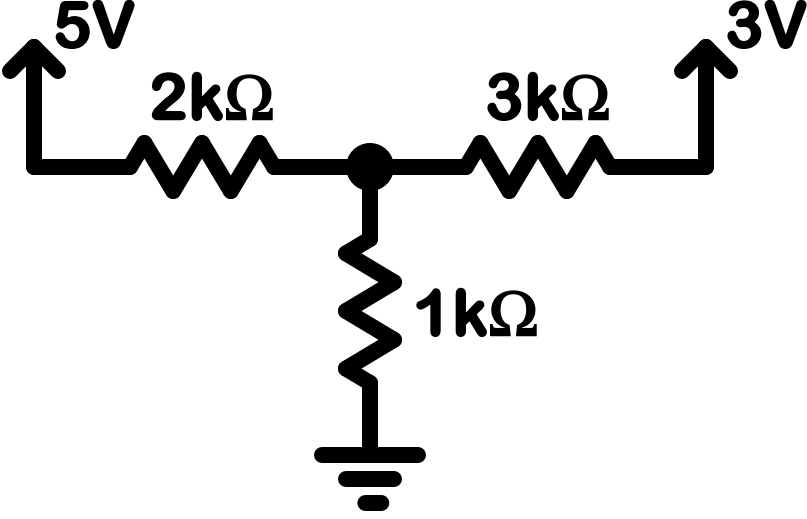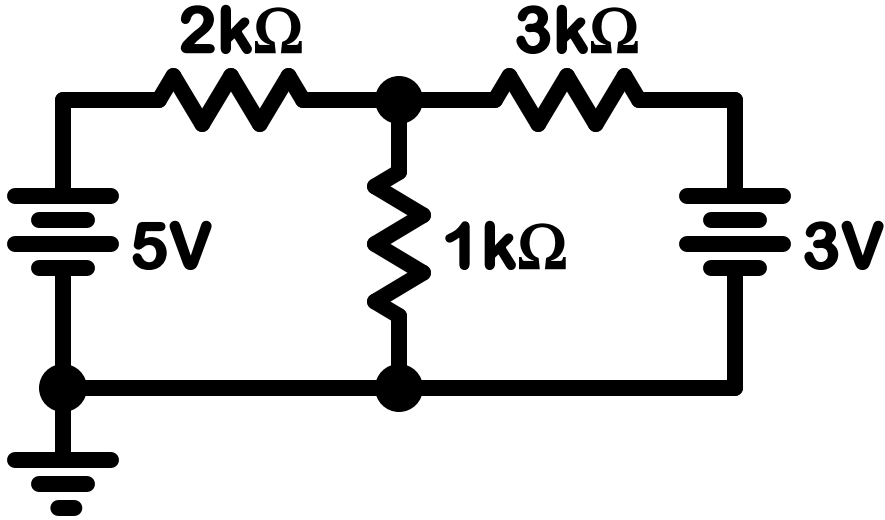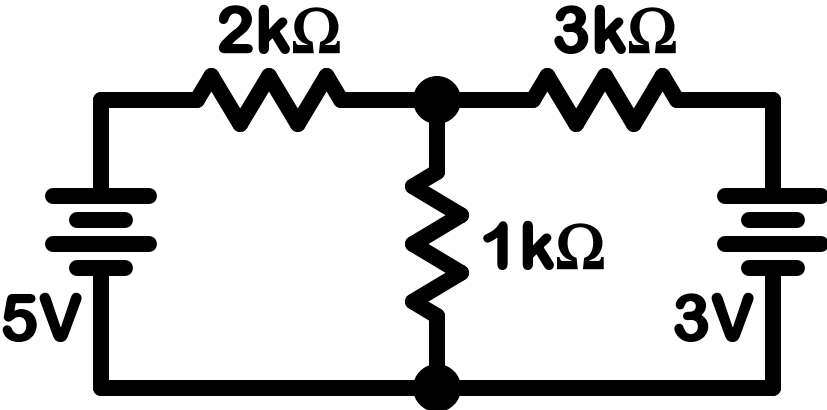

# Superposition (Circuit Math):

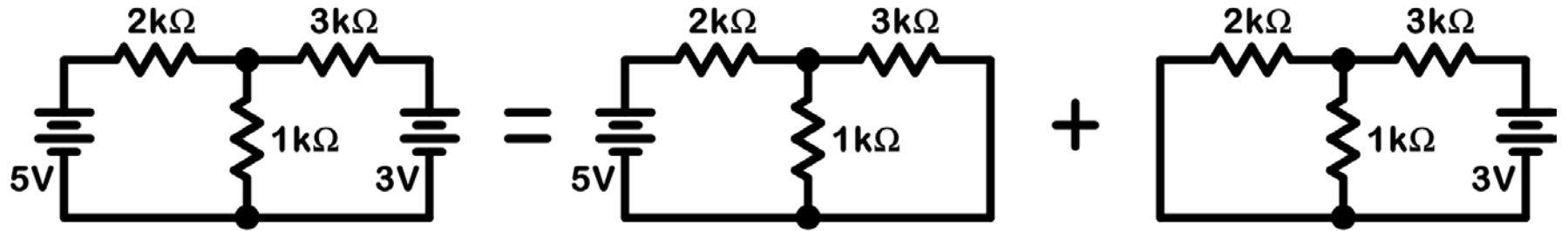

# Example Circuit:

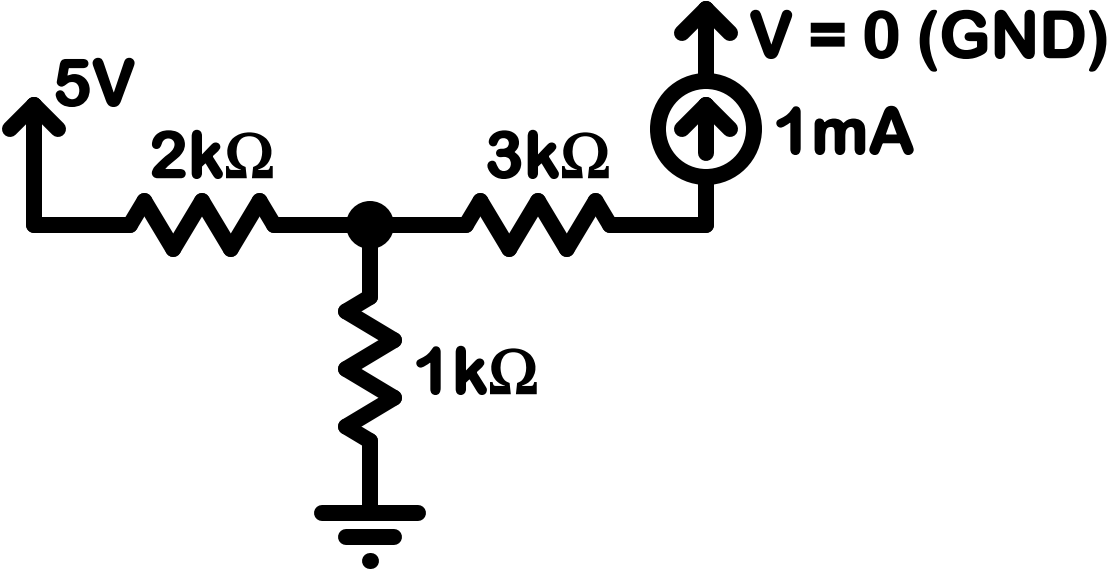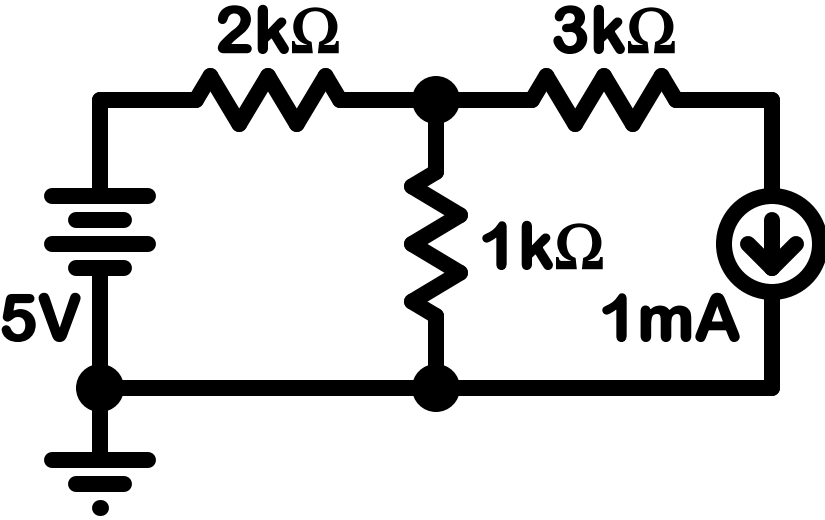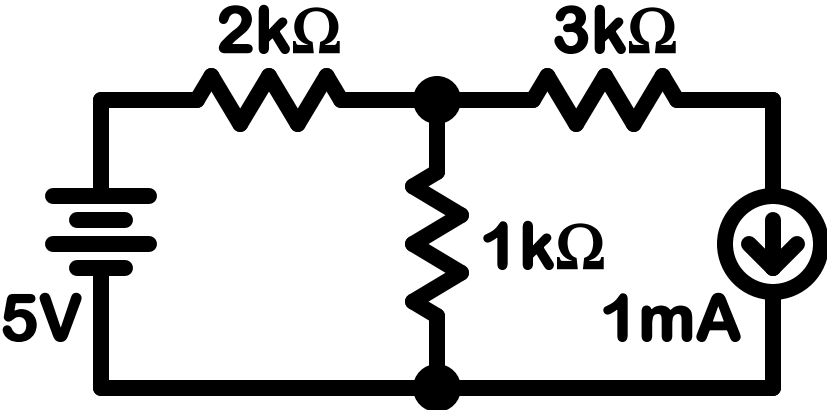

# Example Circuit:

