
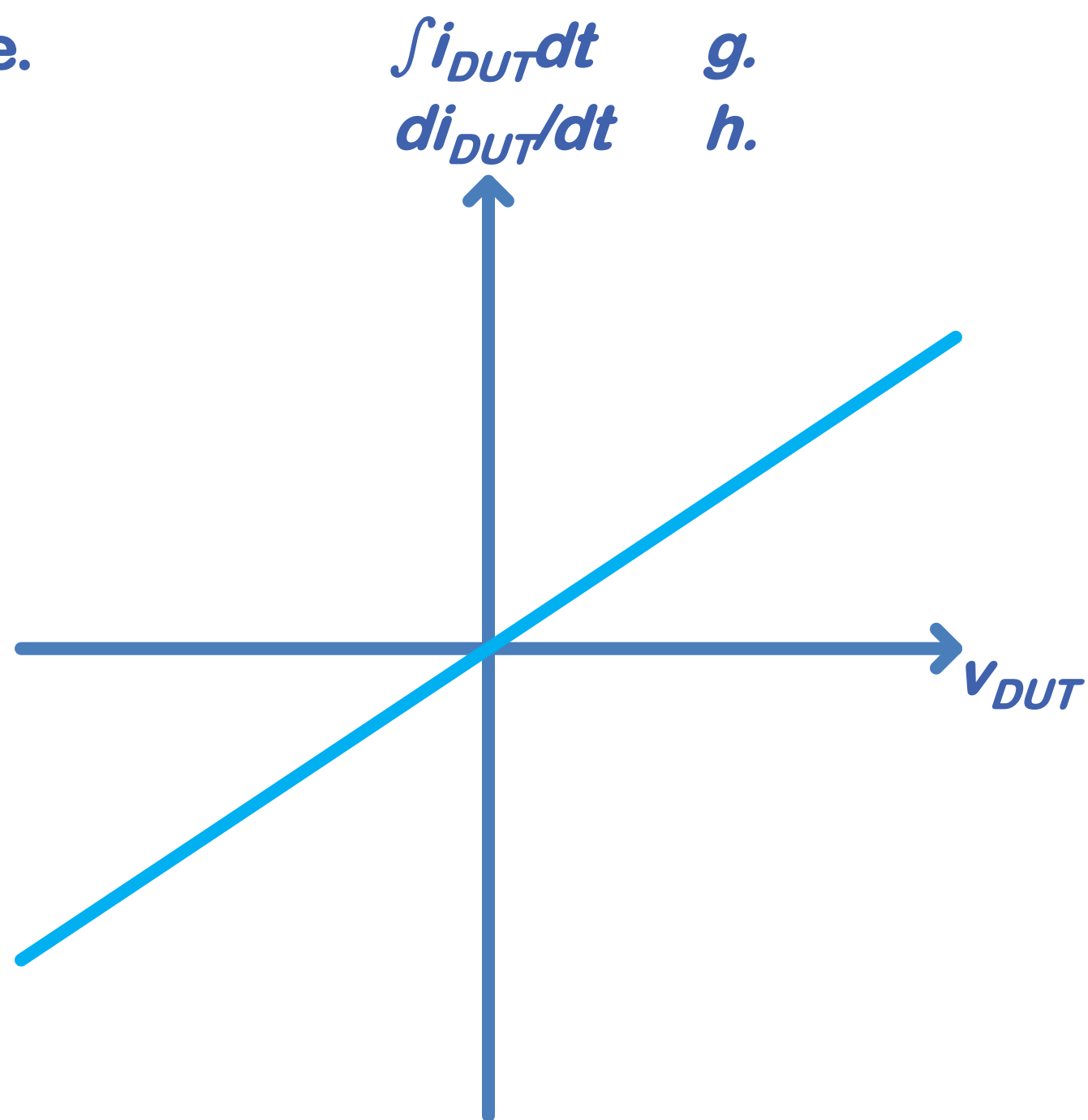


Guess the device from i-v plot

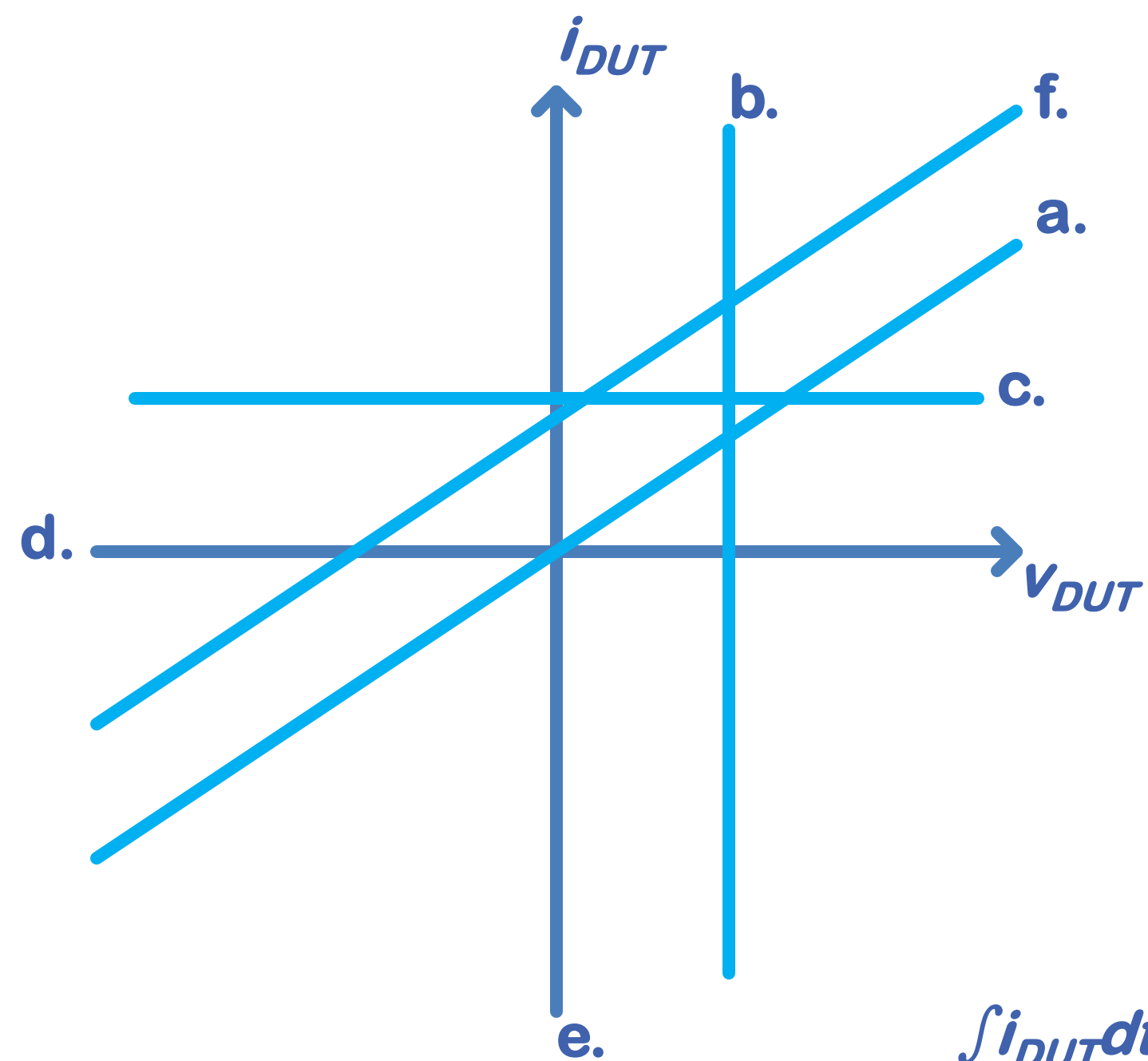

a.

b.

c.

d.

e.


f.

g.

h.

h.

Guess the device from i-v plot

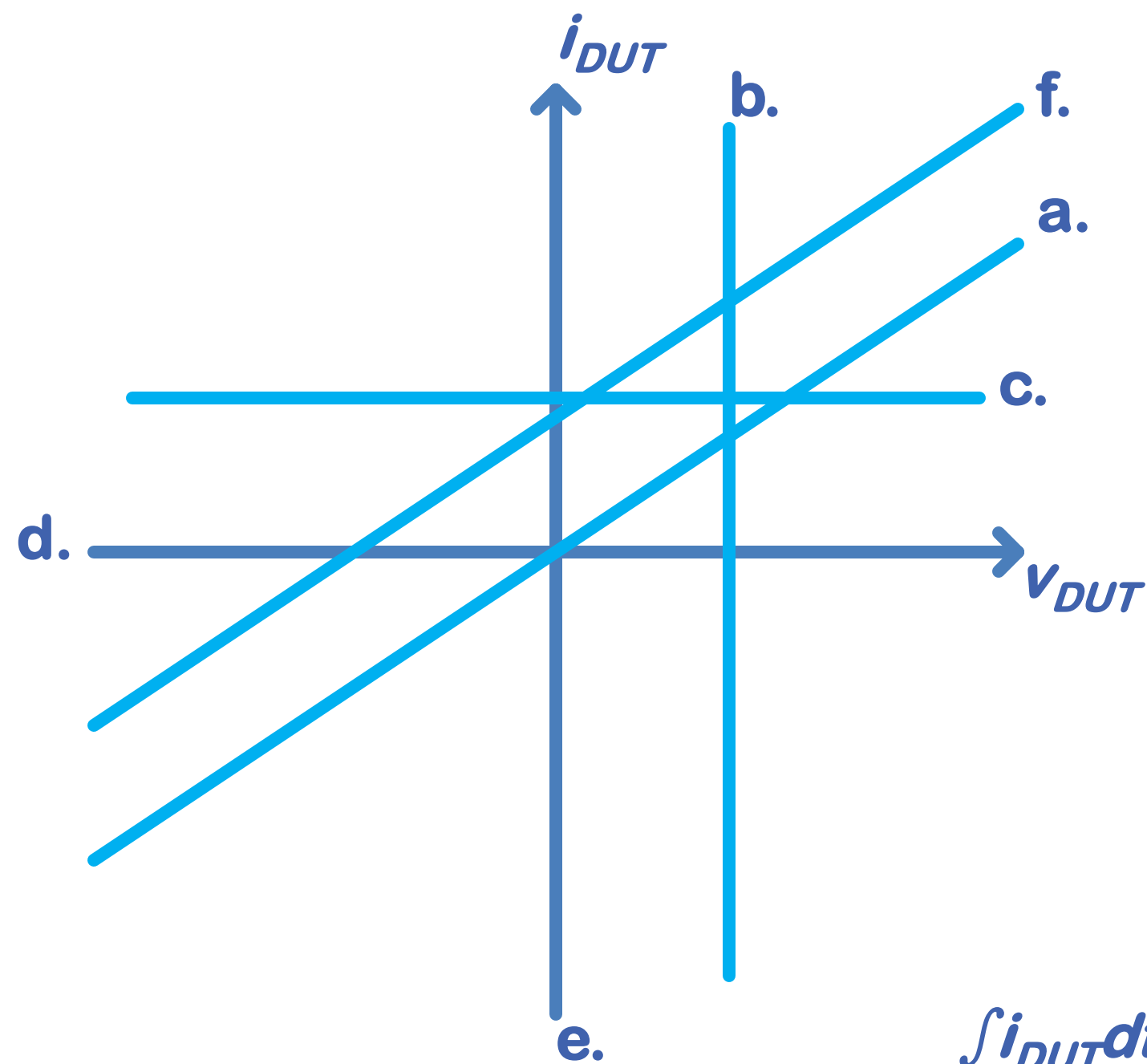

a. resistor


b. voltage source

c. current source

d. open circuit (relates to c and a)

e. short circuit (relates to b and a)

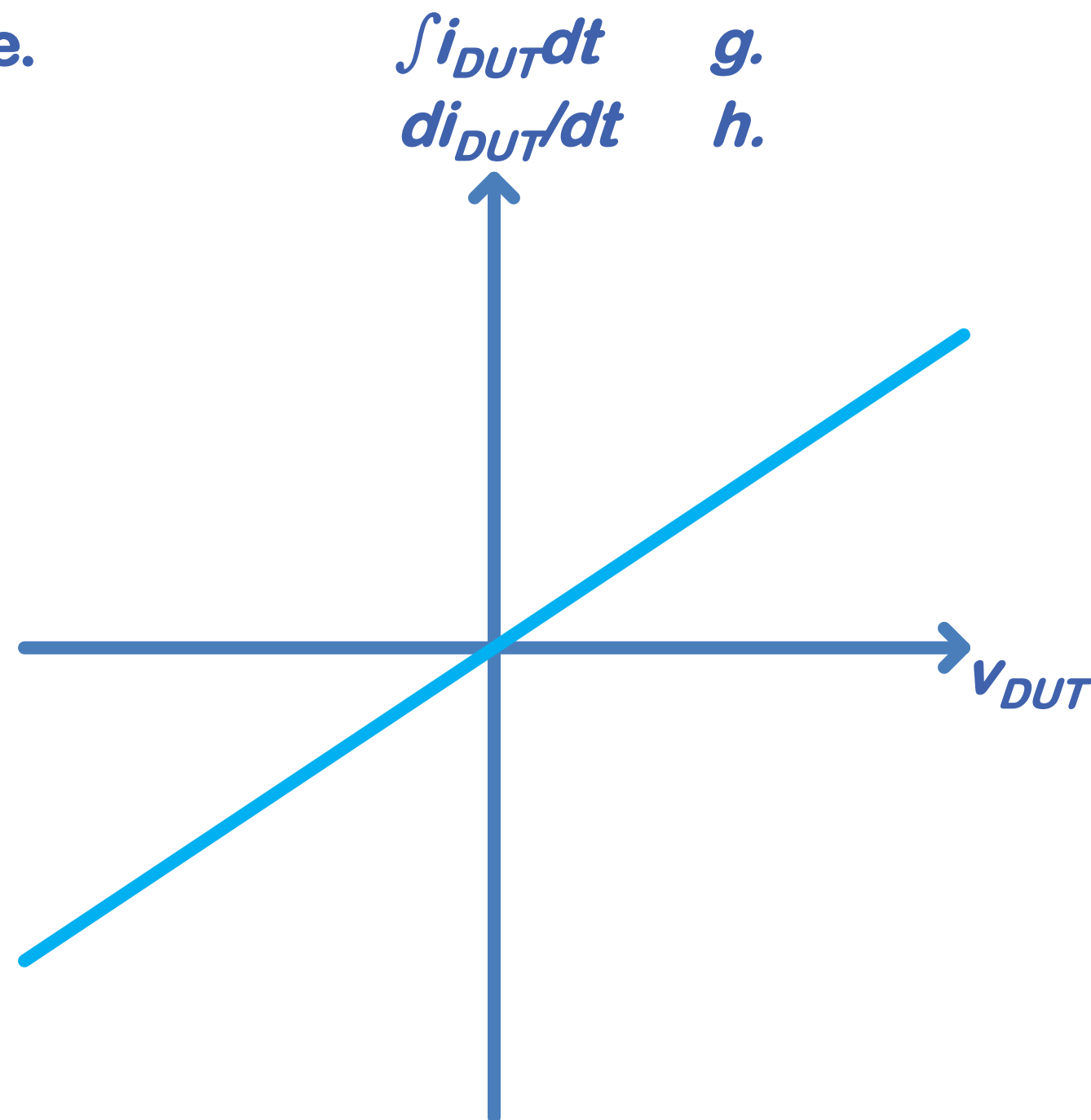**f. voltage source in series w/resistor
current source in parallel w/resistor**




g. capacitor

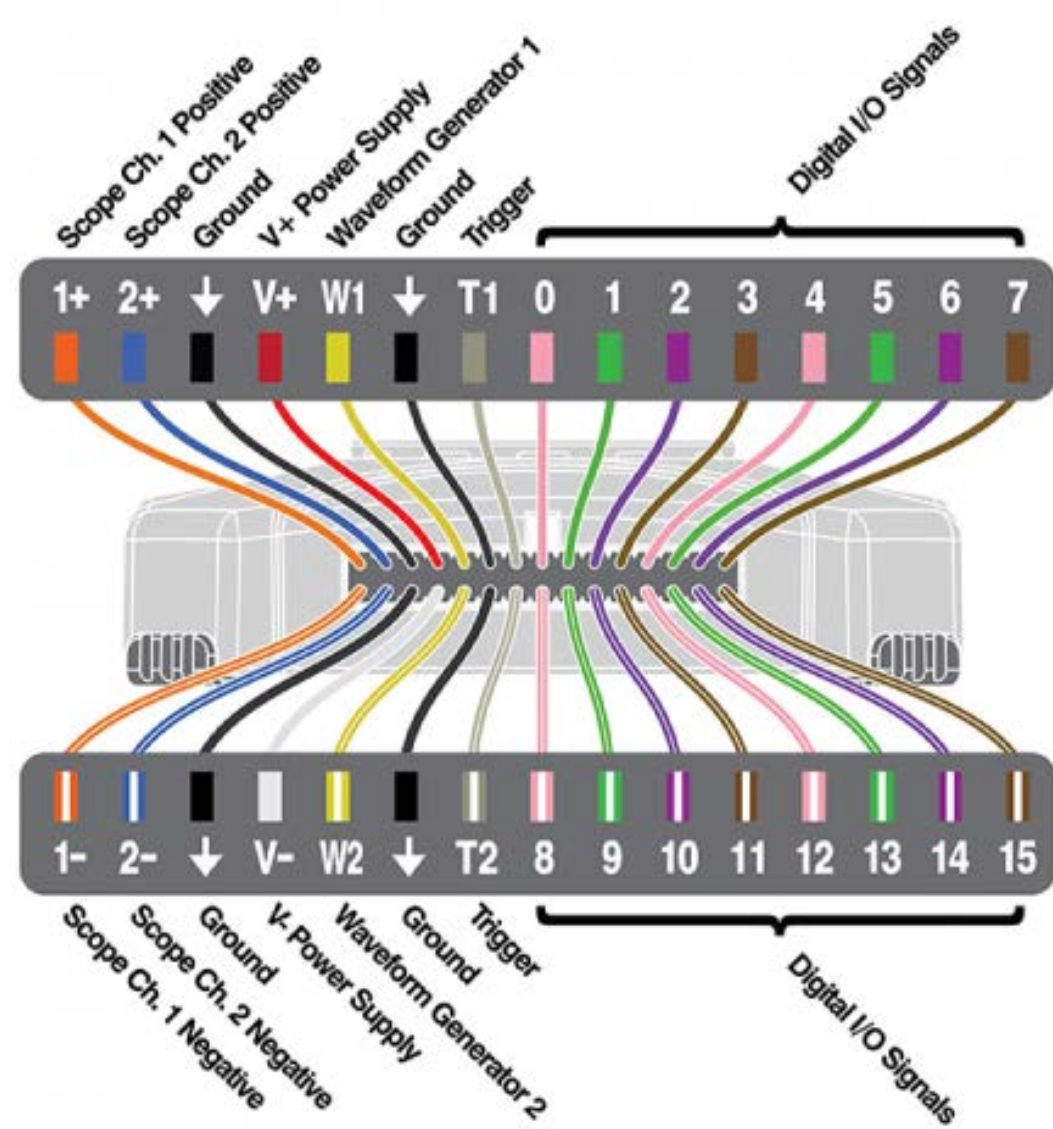
h. inductor


**Guess the device from a physical
unknown component**

Determine the i-v relationship of an unknown device.



DUT, Value Unknown

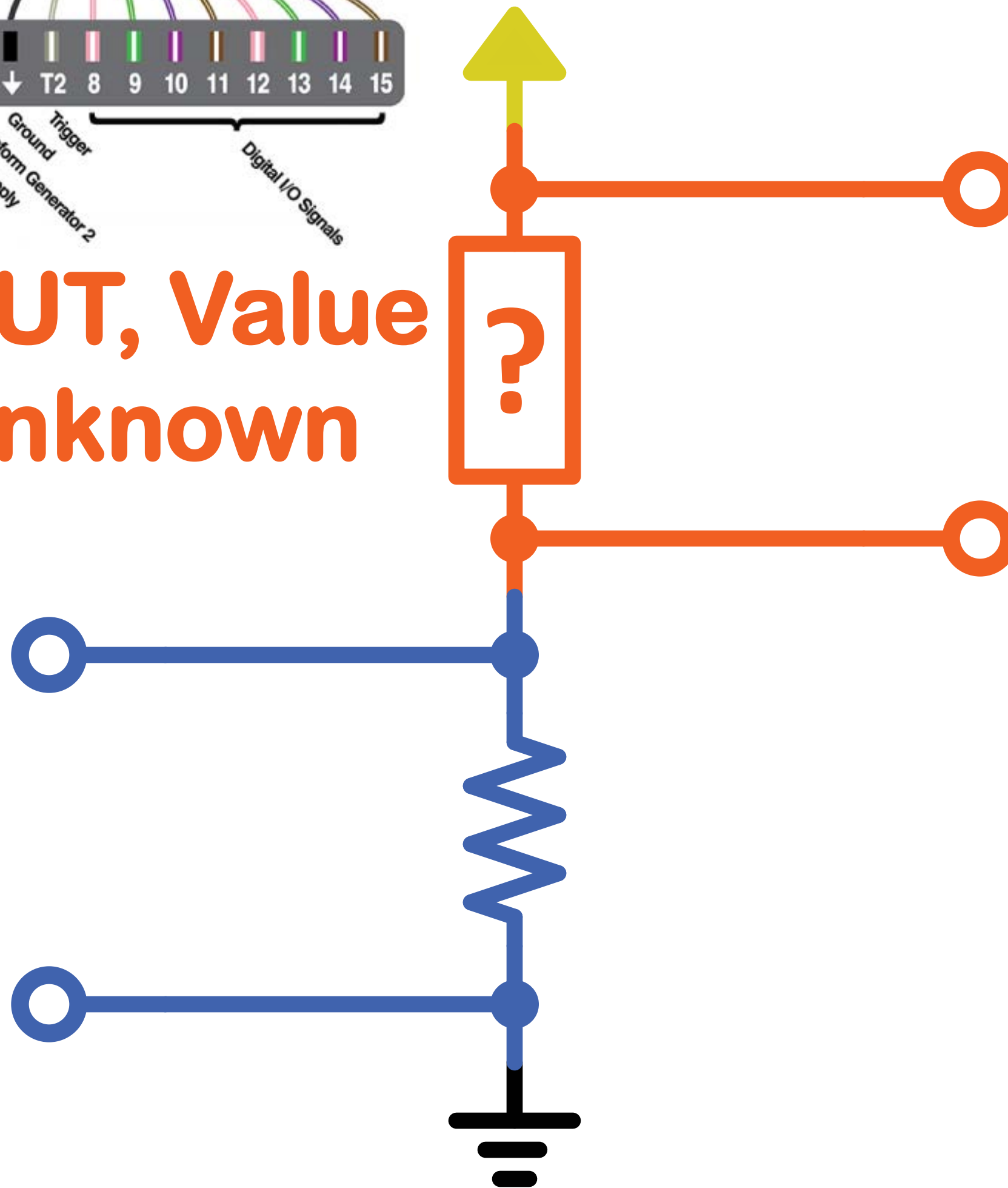

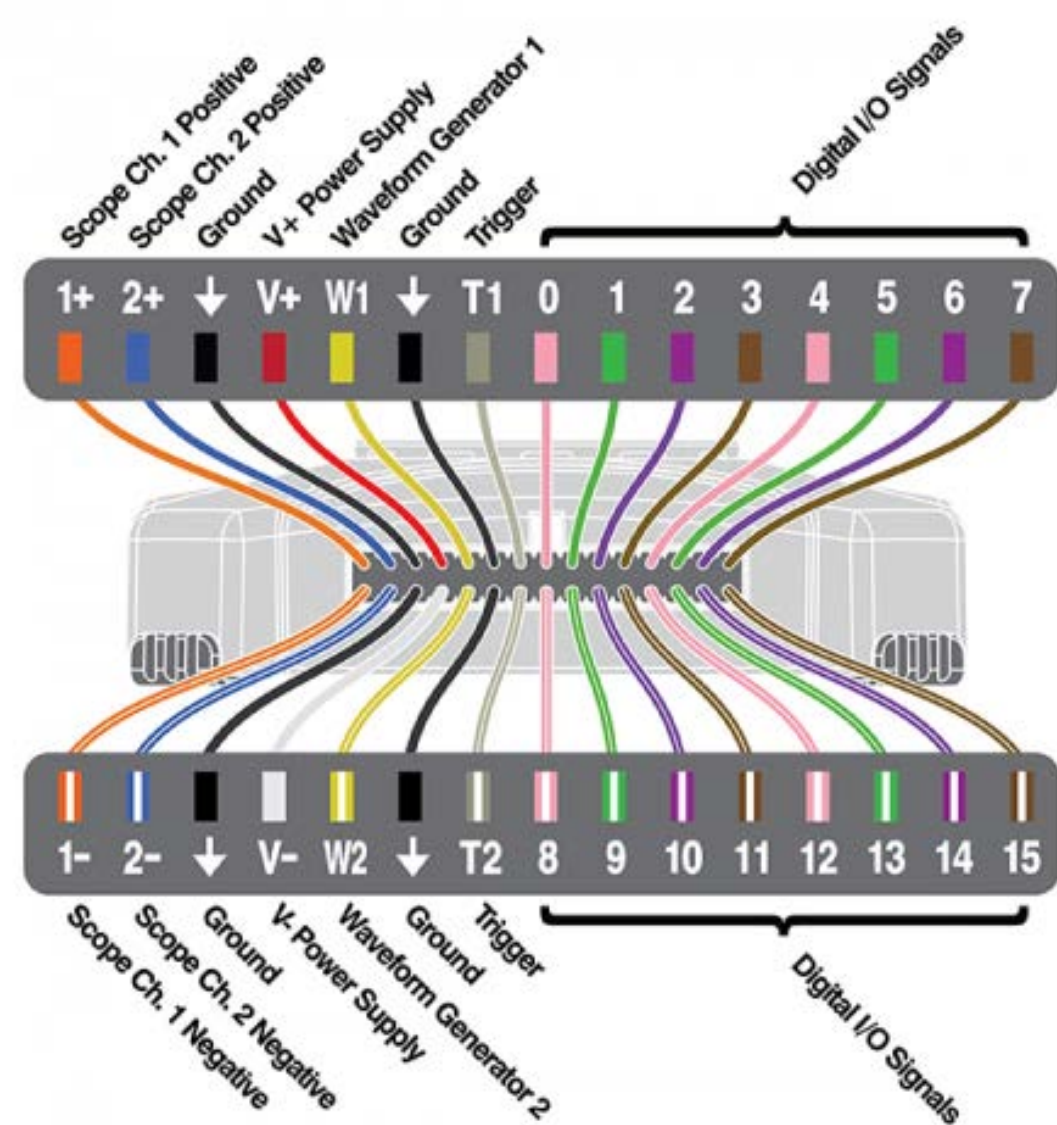

Determine the i-v relationship of an unknown device.

Variable Voltage Source, V_{IN}
Sweep Value from -5V to 5V

DUT, Value Unknown

Measure Device Voltage, V_{DUT}

Measure V_R



$$I_{DUT} = I_R = V_R / 100$$

Known Resistance, 100Ω
(to determine current)


Plot the i-v curve. Determine the DUT value. How does it compare to the actual value?

Save Results to an Excel File.

Example: Set up

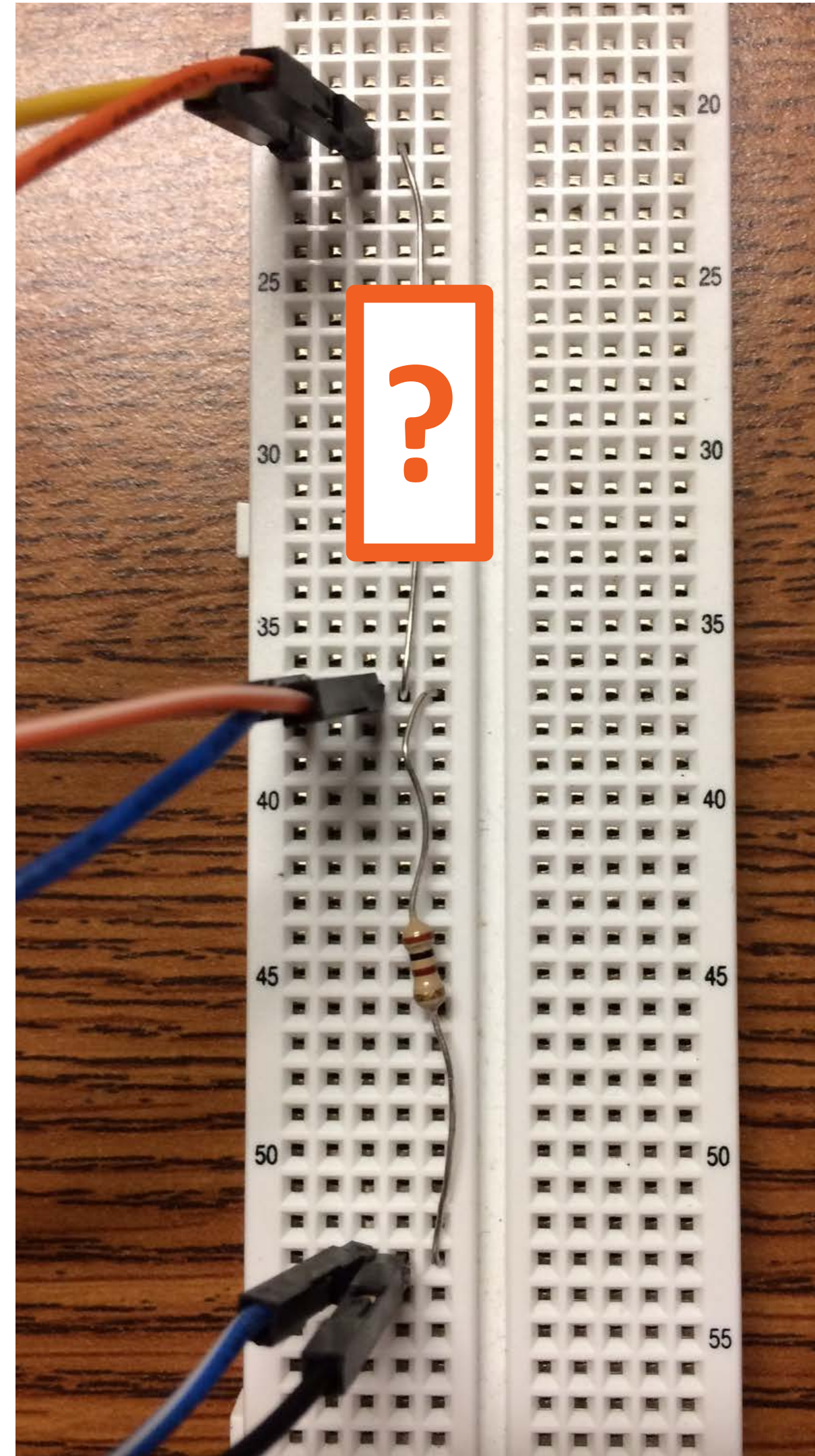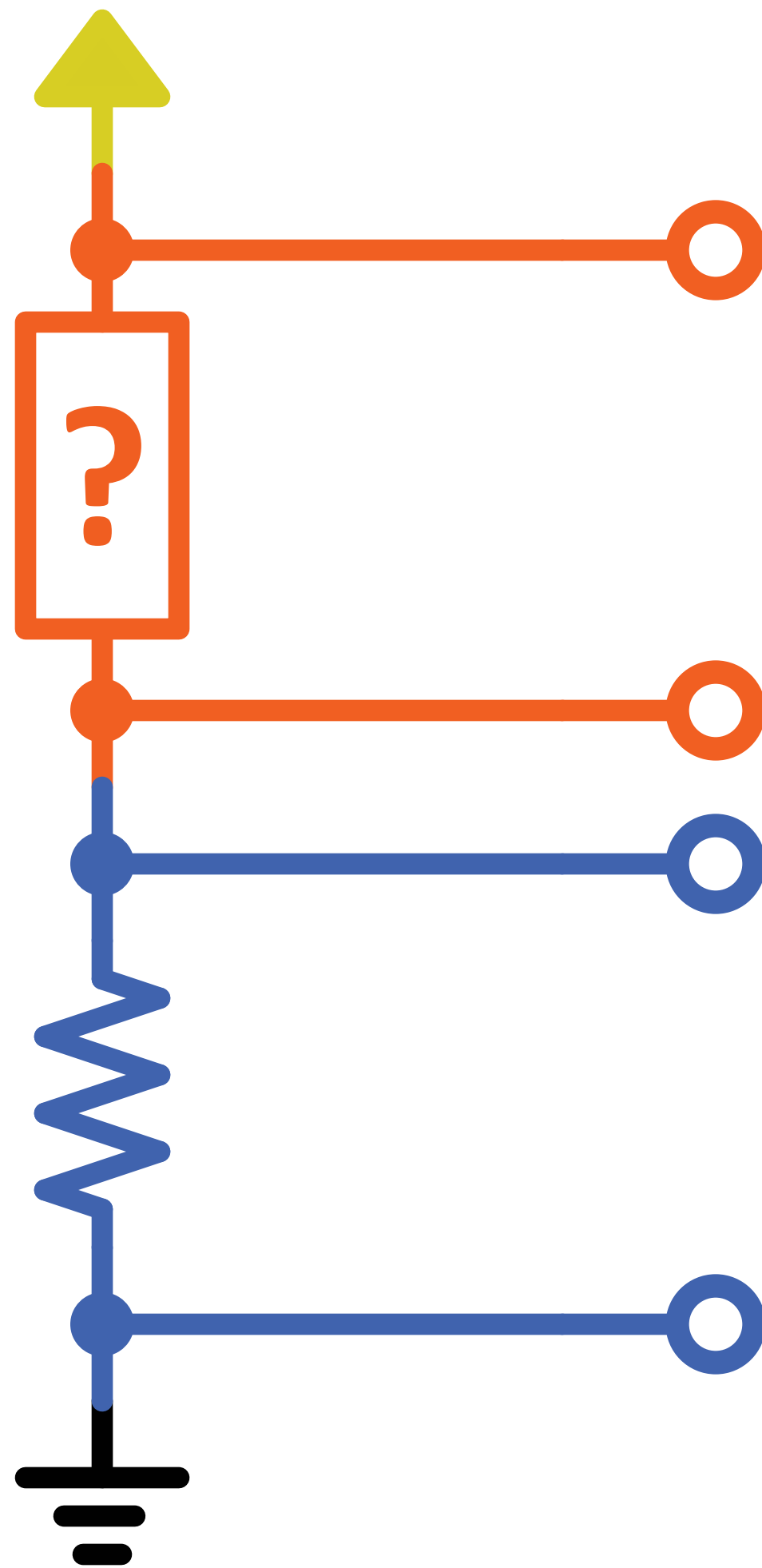

Example: $i_R(v_R)=?$

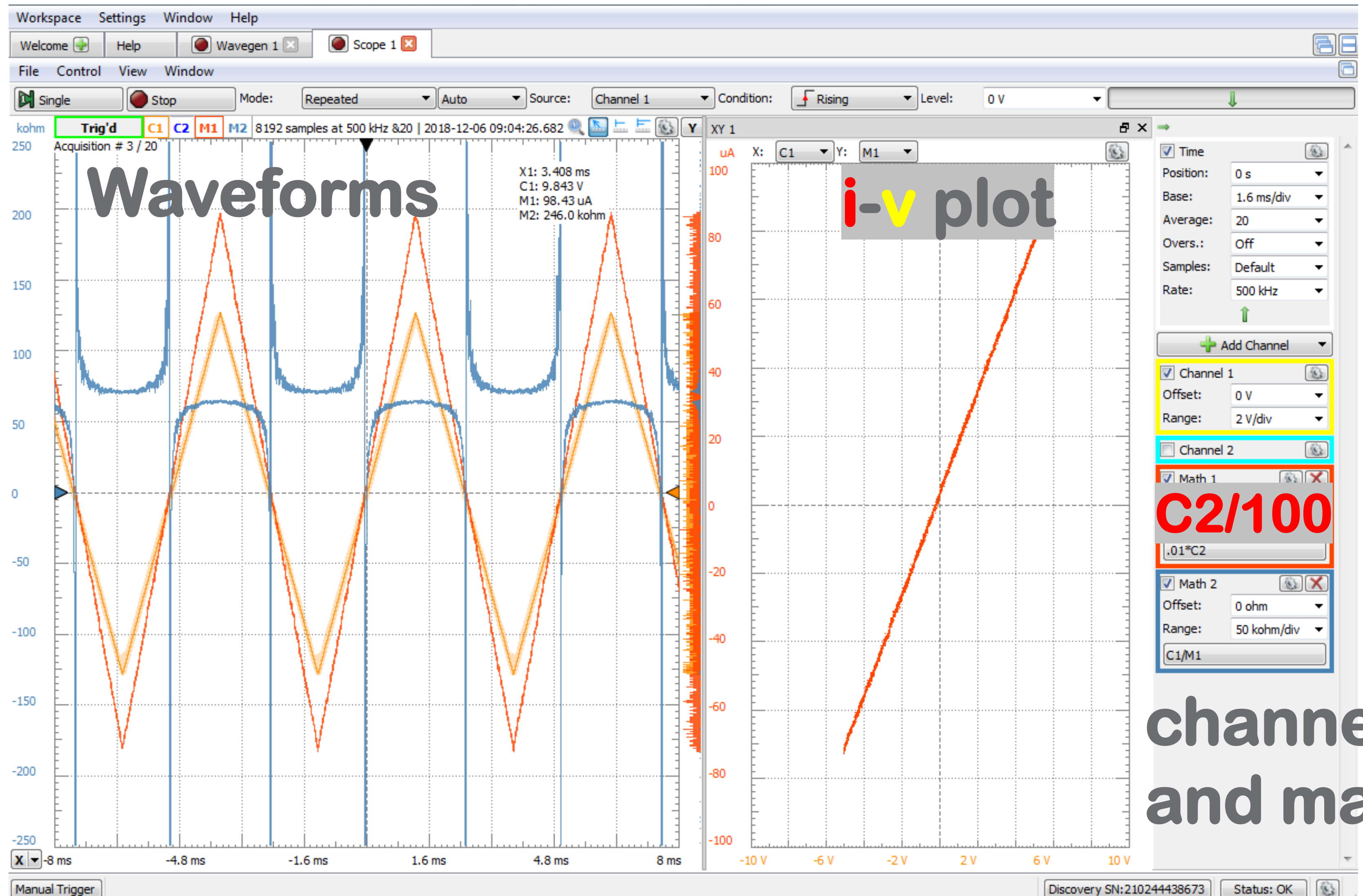


channels
and math

What is this?


Example: $i_R(v_R)=?$

What is this?

~A straight line through the 0,0.

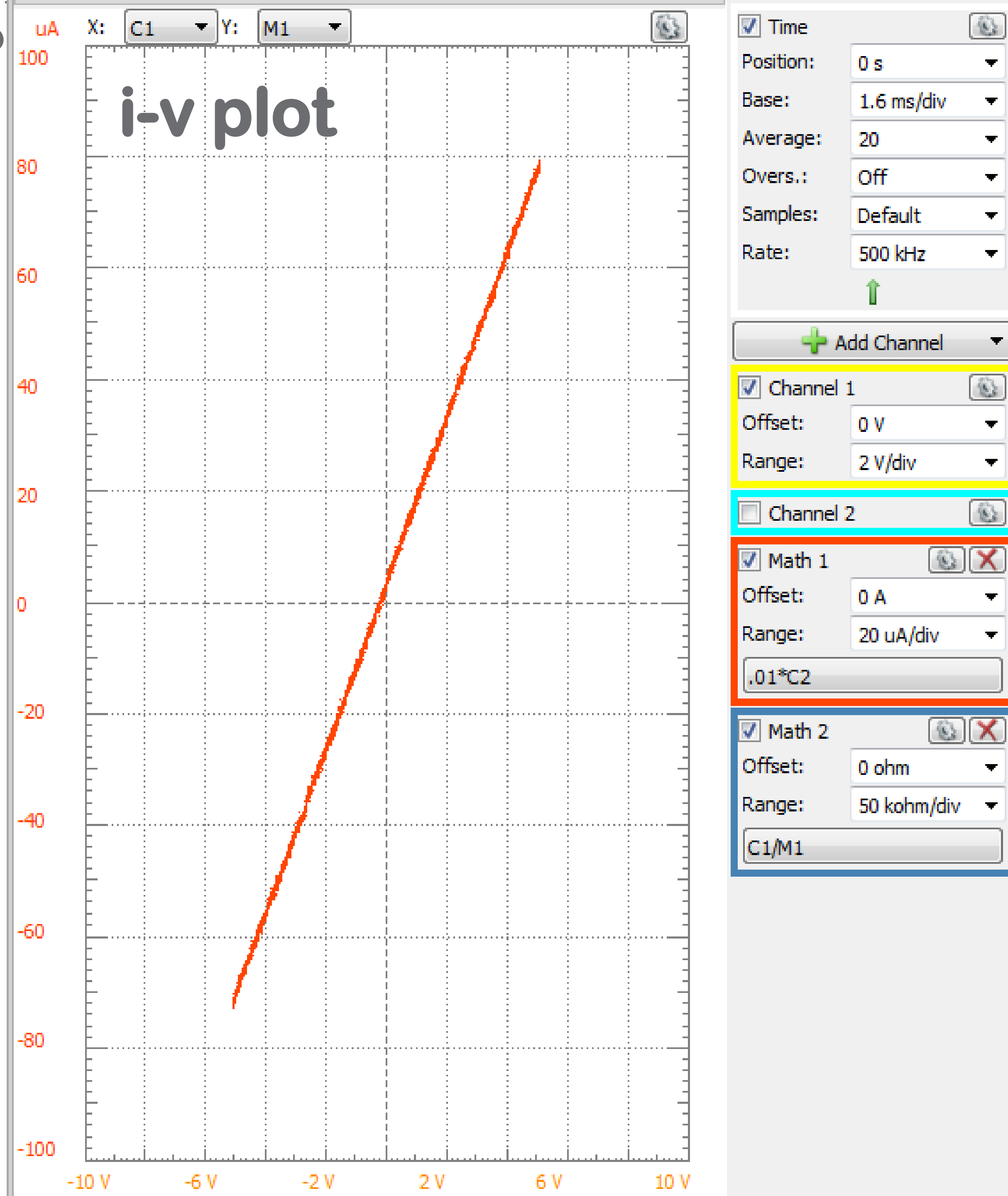



Resistor Example: $i_R = v_R/R$

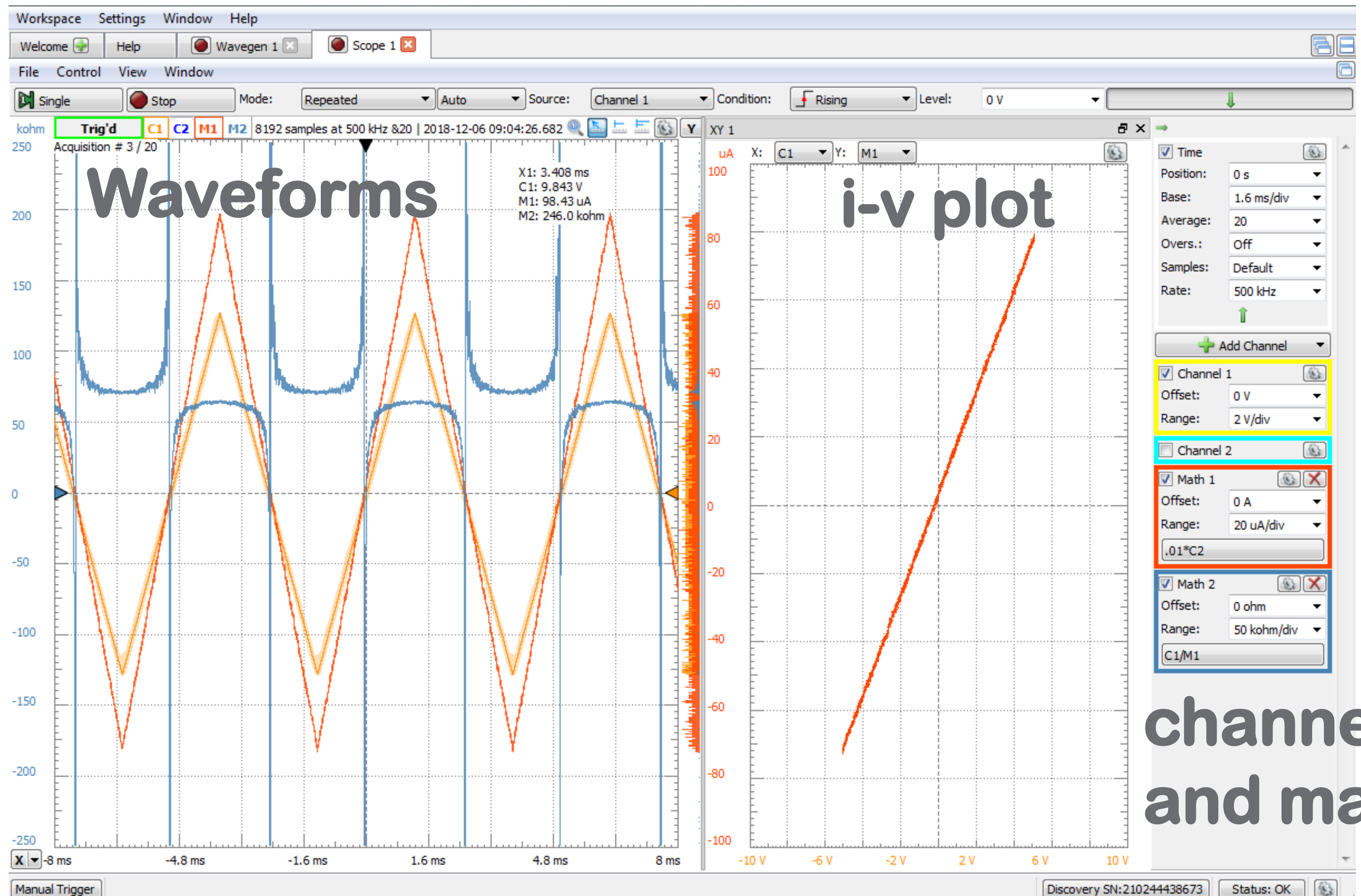

$$R = v_R / i_R = 1 / (\text{i-v slope}) = 100 * (\Delta C1) / (\Delta C2)$$

$$\text{Resistance} = 10V / .00015A = 67 \text{ k}\Omega$$

Resistor Example: Set up

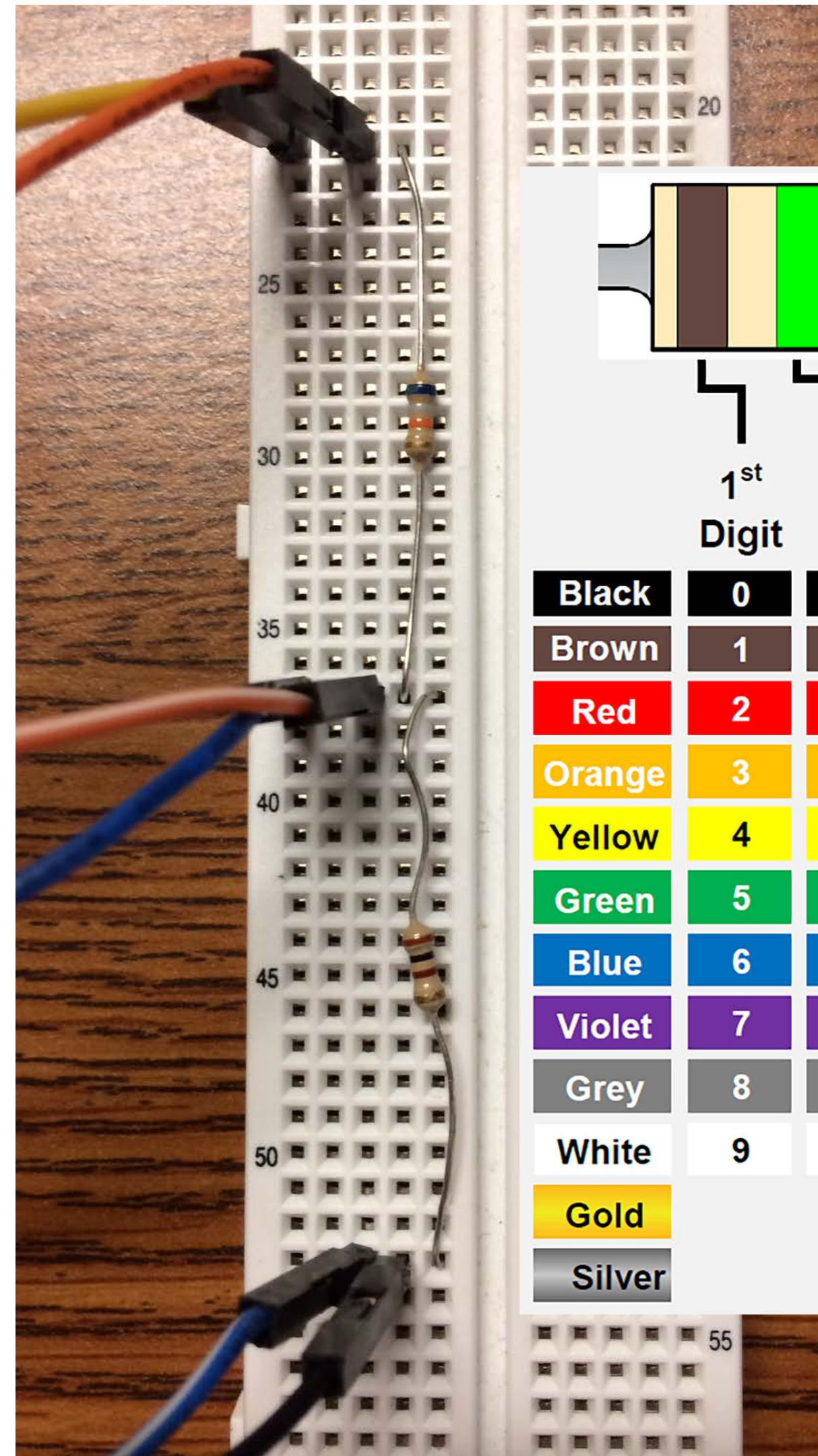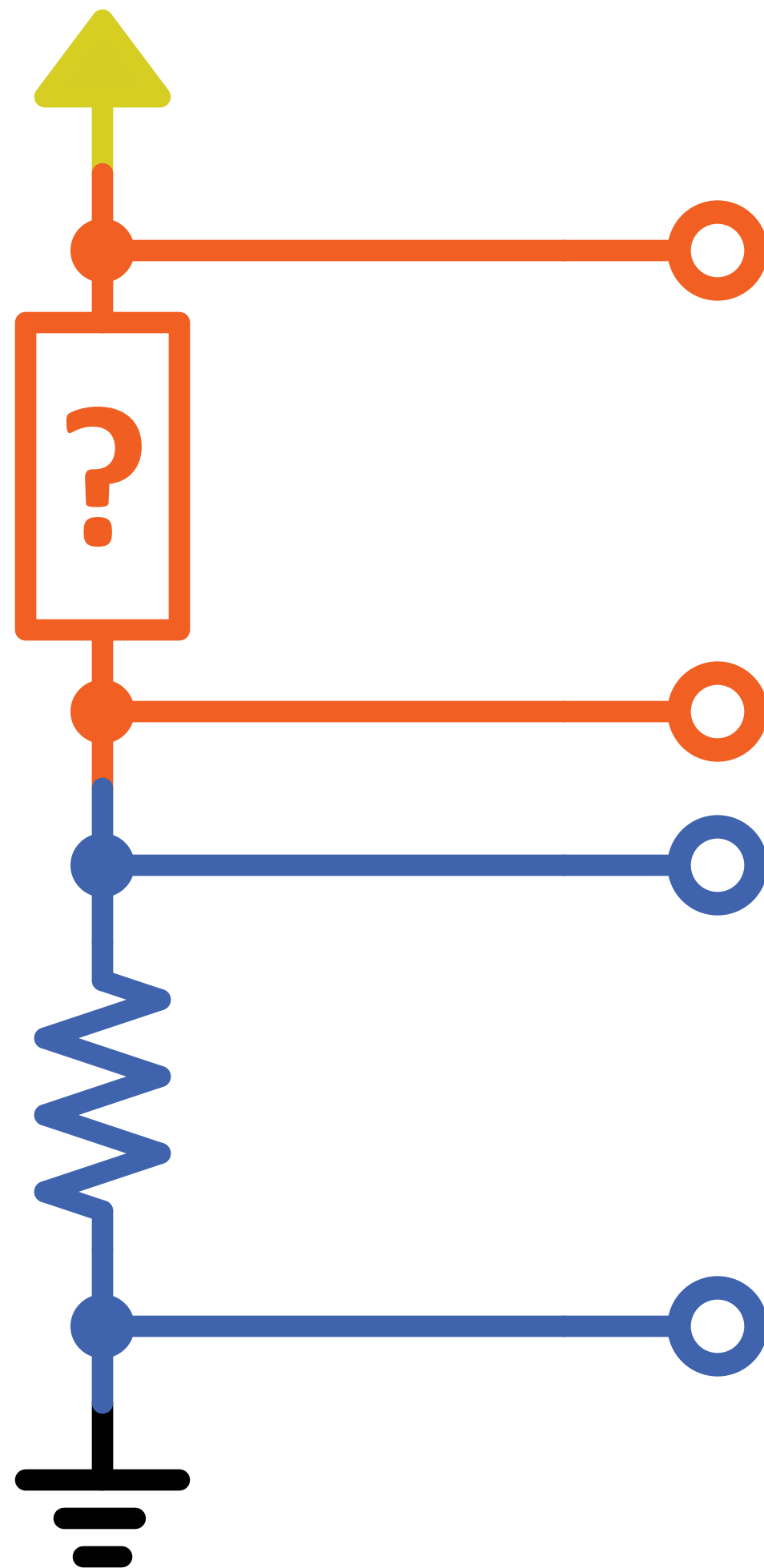

	1 st Digit	2 nd Digit	Multiplier	Tolerance
Black	0	0	x 1	
Brown	1	1	x10	±1%
Red	2	2	x10 ²	±2%
Orange	3	3	x10 ³	±3%
Yellow	4	4	x10 ⁴	±4%
Green	5	5	x10 ⁵	±0.5%
Blue	6	6	x10 ⁶	±0.25%
Violet	7	7	x10 ⁷	±0.1%
Grey	8	8	x10 ⁸	±0.05%
White	9	9	x10 ⁹	
Gold			x10 ⁻¹	±5%
Silver			x10 ⁻²	±10%

Resistance = 68 k Ω