
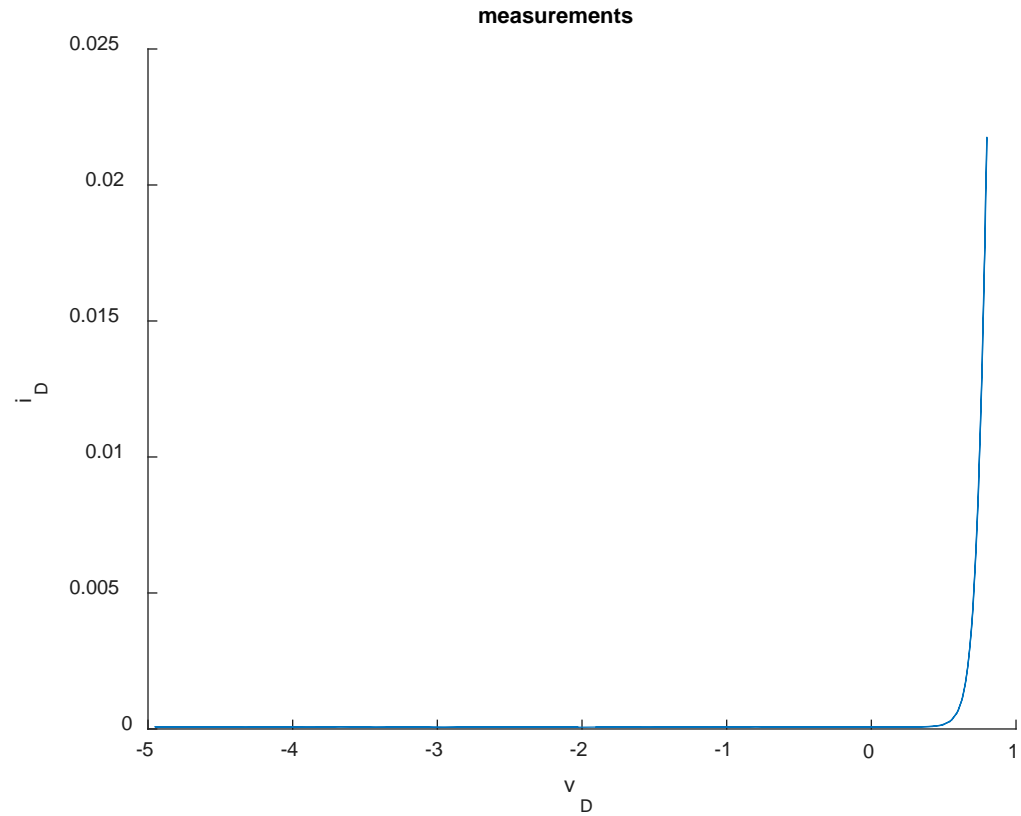


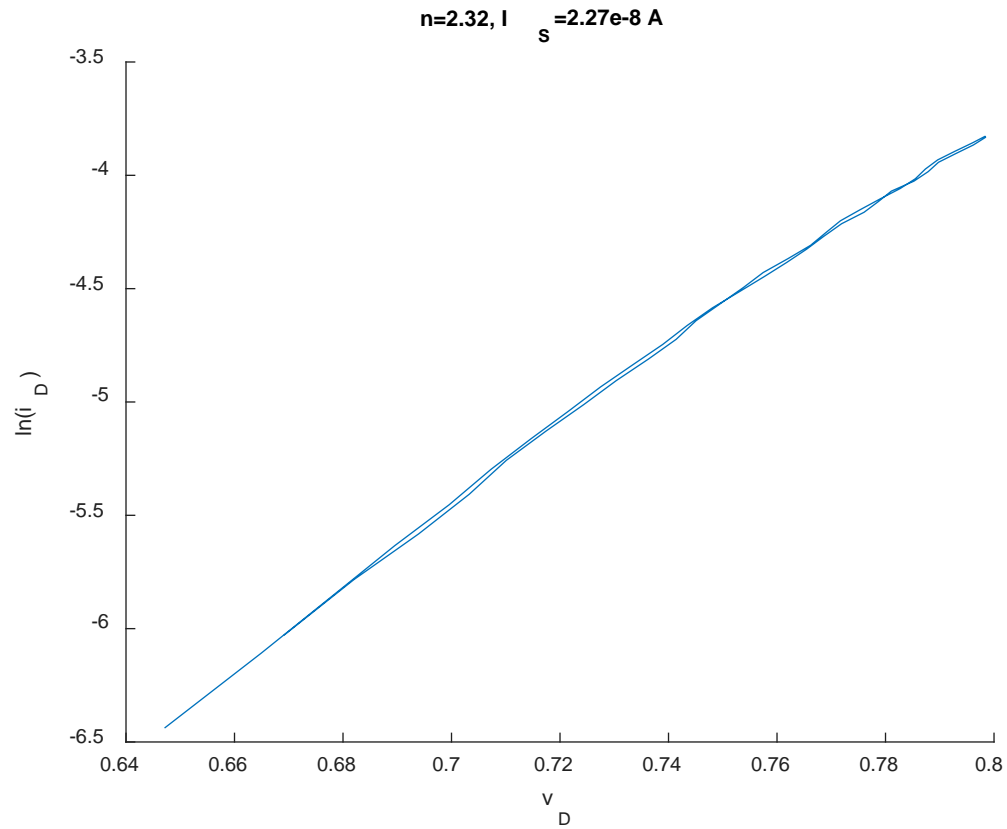
Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic



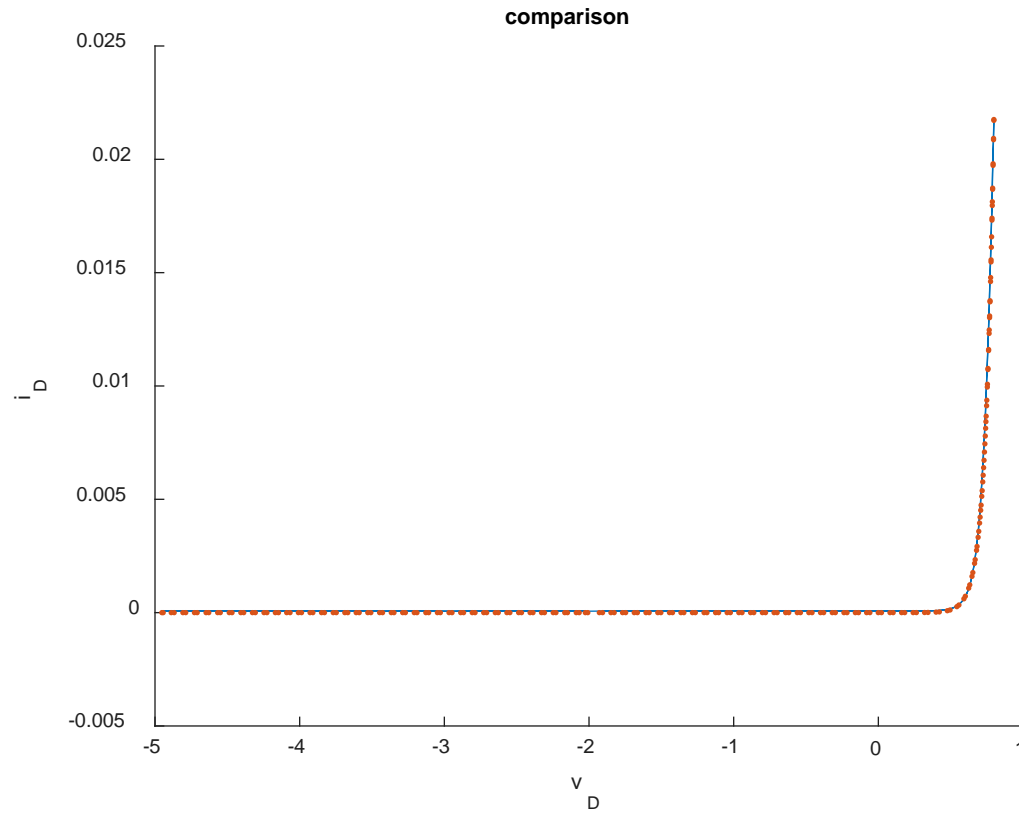Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic

- Simple circuit consisting of a source, a resistor, and a diode.
- For forward bias we have 2 models for the diode.


1) Ideal Diode: Short Circuit

$$V_D = 0$$

$$I_D > 0$$

2) Exponential Model

$$I_D = I_S e^{V_D/nV_T}$$

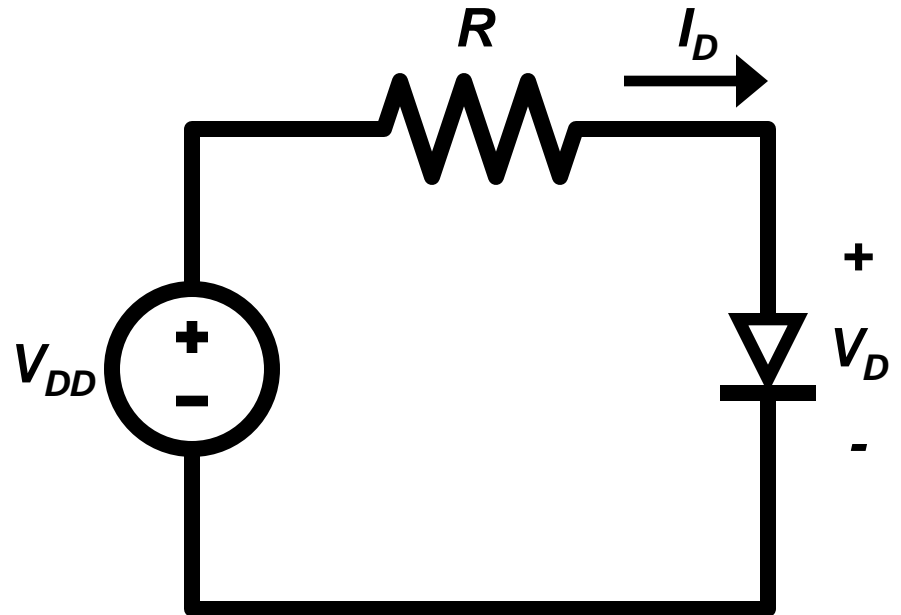

- In this section, we will:
 - 1) Address the suitability of these two models.
 - 2) Develop new models.
- This will help us to:
 - 1) Analyze diode circuits efficiently.
 - 2) Provide a foundation for modeling transistor operation.

Modeling the Diode Forward Characteristic

A) The Exponential Model


- 1) The most accurate model.
- 2) The hardest to analyze.

Let's analyze a circuit using the exponential model.

$$I_D = I_S e^{V_D / nV_T}$$

$$I_D = I_R = \frac{V_{DD} - V_D}{R}$$
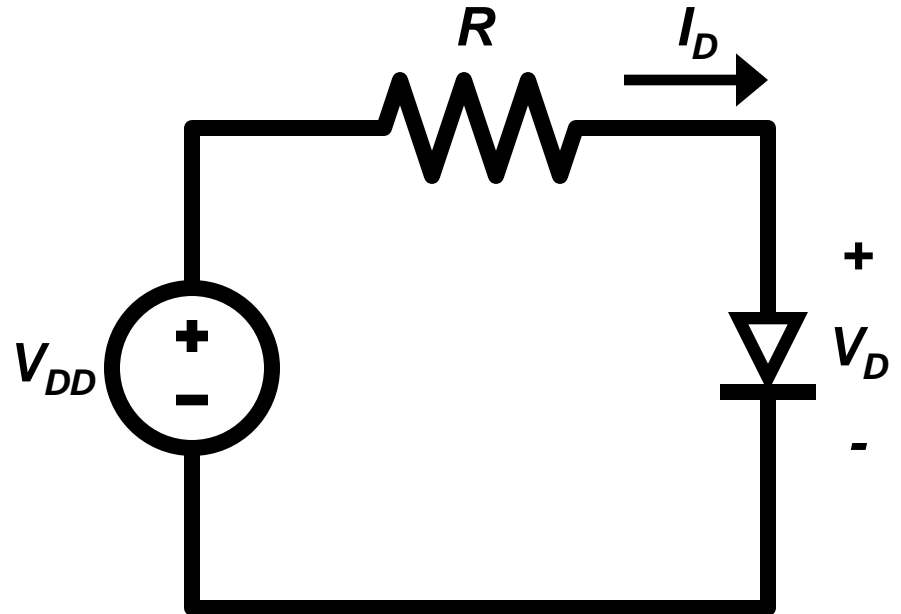
$$I_D = -\frac{1}{R}V_D + \frac{V_{DD}}{R}$$



I_S , n , V_T are known quantities.

We have two equations with two unknowns.

Q. How do we solve for I_D and V_D ?

Modeling the Diode Forward Characteristic

Graphically


a) Plot the two equations on the i - v plane.

Eq. 1: diode characteristic curve.

$$I_D = I_S e^{V_D/nV_T}$$

Eq. 2: load line.
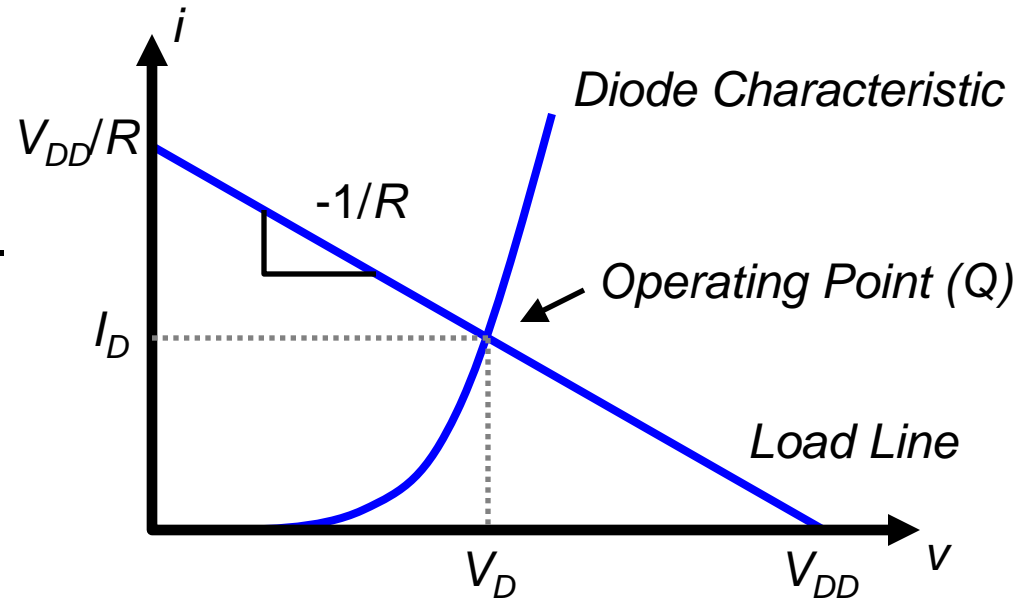
$$I_D = -\frac{1}{R}V_D + \frac{V_{DD}}{R}$$





b) The solution is the intersection, Q , of the two curves and is referred to as the operating point.

- Graphical analysis becomes very difficult for complex circuits.
- Too difficult to be justified for practical use.

Modeling the Diode Forward Characteristic

```
vS = [2 2 2 5 5 5 5 10 10 10];
```
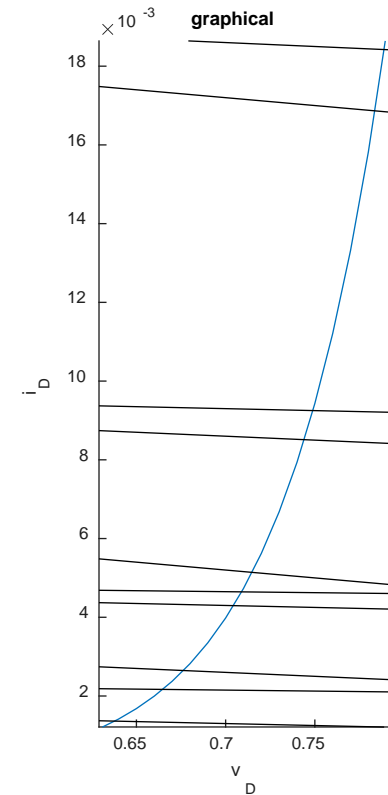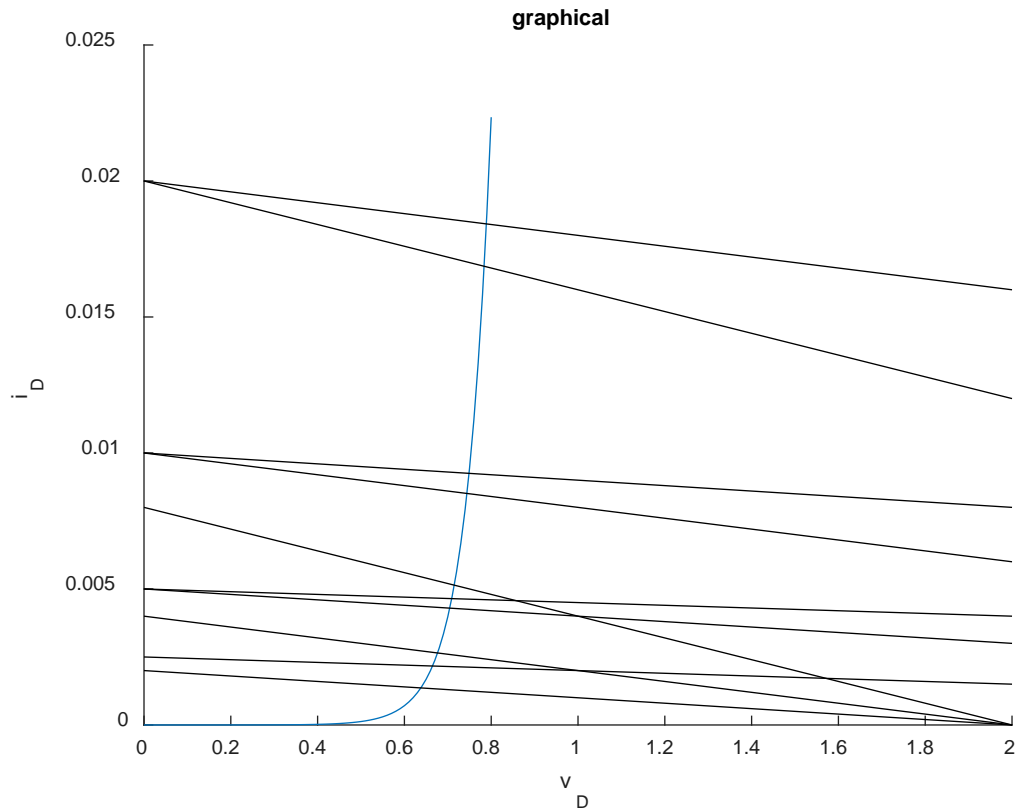
```
R = [1000 500 250 2000 1000 500 250 2000 1000 500];
```




Modeling the Diode Forward Characteristic

```
vS = [2 2 2 5 5 5 5 10 10 10];
```

```
R = [1000 500 250 2000 1000 500 250 2000 1000 500];
```

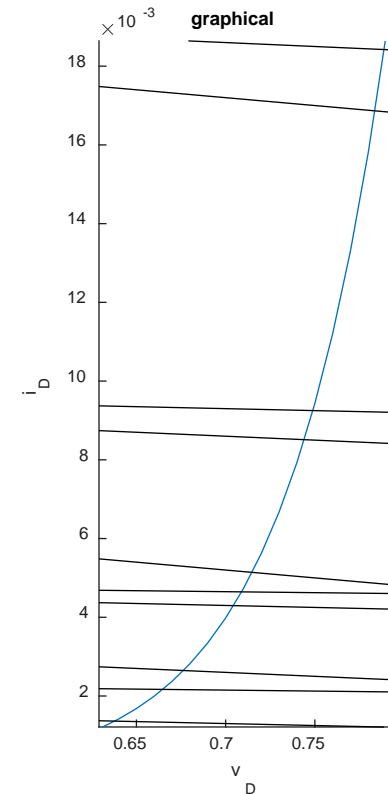- $v_D = 0.7V$ (between 0.6V and 0.8V) is a really good initial guess.
- This is due to the characteristic of the diode.
- i_D can vary significantly within the 0.7V box.
- An approximate value for i_D is determined primarily by the load line.
- Where it intersects 0.7V.



Modeling the Diode Forward Characteristic

Iterative analysis

Remember the two equations: $I_D = I_S e^{V_D/nV_T}$ Diode Characteristic

$$I_D = -\frac{1}{R}V_D + \frac{V_{DD}}{R} \quad \text{Load Line}$$

What do we know about a diode in forward bias?

The voltage across the diode is between 0.6 and 0.8 Volts.

Approach:


- 1) Assume V_D is 0.7 Volts.
- 2) Solve for I_D using circuit equation (load line).
- 3) Calculate new value of V_D or ΔV_D using the Diode Characteristic curve.

$$V_D = nV_T \ln\left(\frac{I_D}{I_S}\right) \quad \text{or} \quad \Delta V_D = nV_T \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$


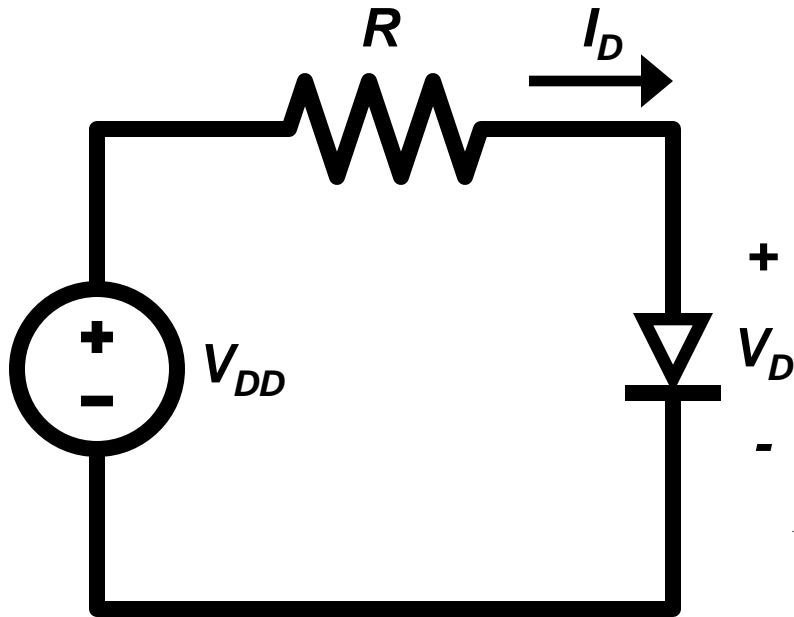
- 4) Go back to step 2 and repeat until the answer converges.

Modeling the Diode Forward Characteristic

From the measurements:
 $nV_T = .058 \text{ V}$, $I_S = 2.27 \times 10^{-8} \text{ A}$
 $V_{DD} = 10 \text{ V}$, and $R = 500 \Omega$.



vD	0.7000	0.7894	0.7888
iD	0.0186	0.0184	0.0184

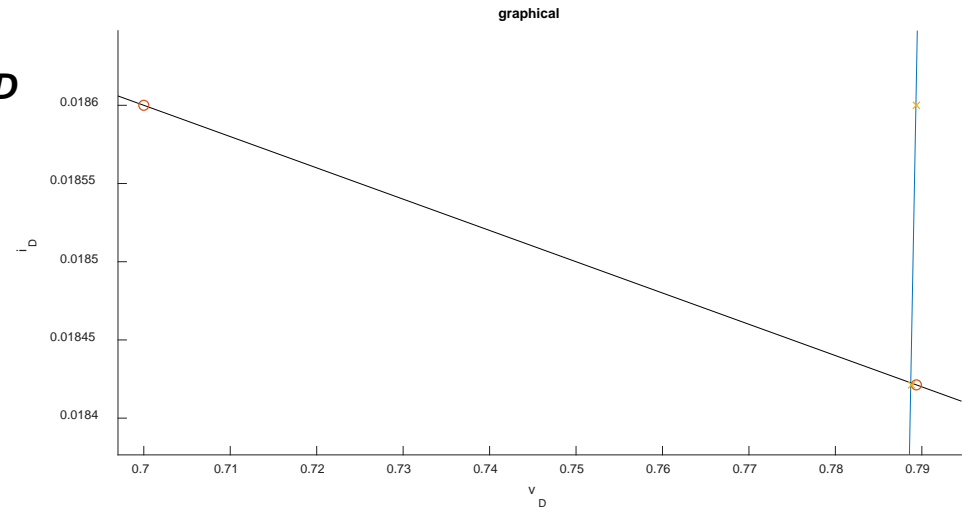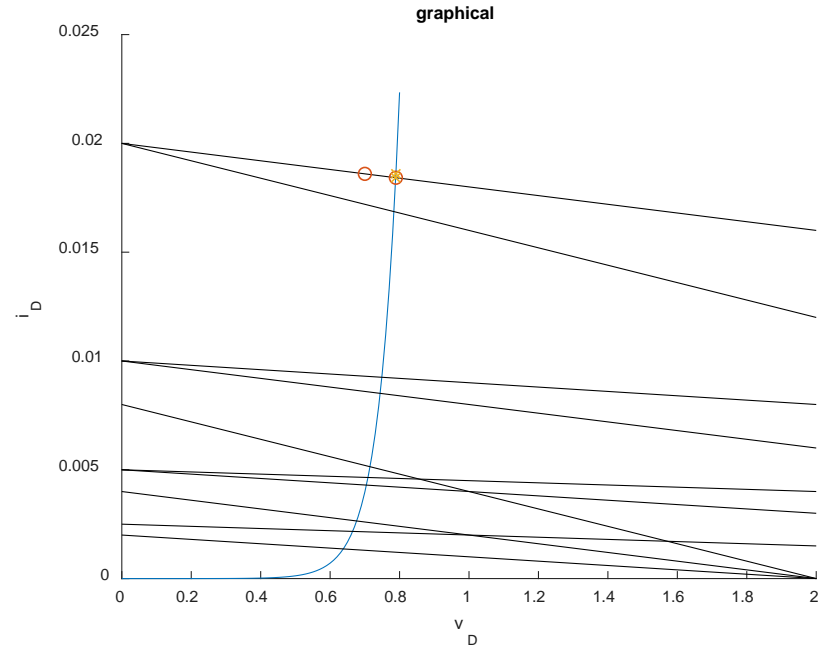

Modeling the Diode Forward Characteristic

- For complex circuits this approach is very time consuming to do by hand, because you must re-analyze the circuit for each iteration.
- However, this approach can be easily iterated using computer analysis.

Conclusions


- the graphical and iterative solution methods using the exponential model are inefficient.
- For effective circuit analysis a simple model for the junction diode is needed.

Modeling the Diode Forward Characteristic

```
vS = [2 2 2 5 5 5 5 10 10 10];
```

```
R = [1000 500 250 2000 1000 500 250 2000 1000 500];
```

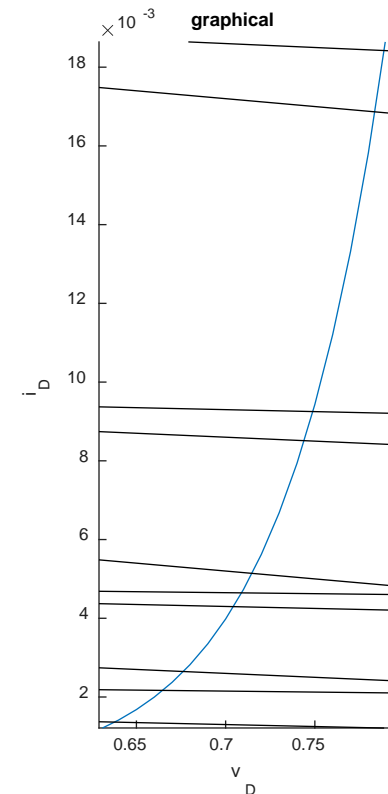
- $v_D = 0.7V$ (between 0.6V and 0.8V) is a really good initial guess.
- This is due to the characteristic of the diode.
- i_D can vary significantly within the 0.7V box.
- An approximate value for i_D is determined primarily by the load line.
- Where it intersects 0.7V.




Modeling the Diode Forward Characteristic

The Constant Voltage Drop Model.

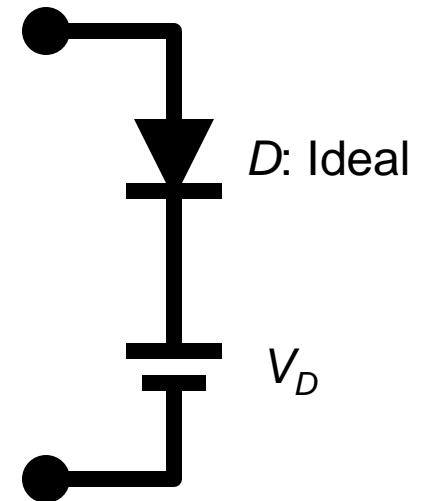- Consider the i-v relationship for the following configuration.
- An ideal diode, a battery.
- V_D uses a value between 0.6V and 0.8V (typically 0.7V).
- The battery models the small amount of potential needed to start conducting.




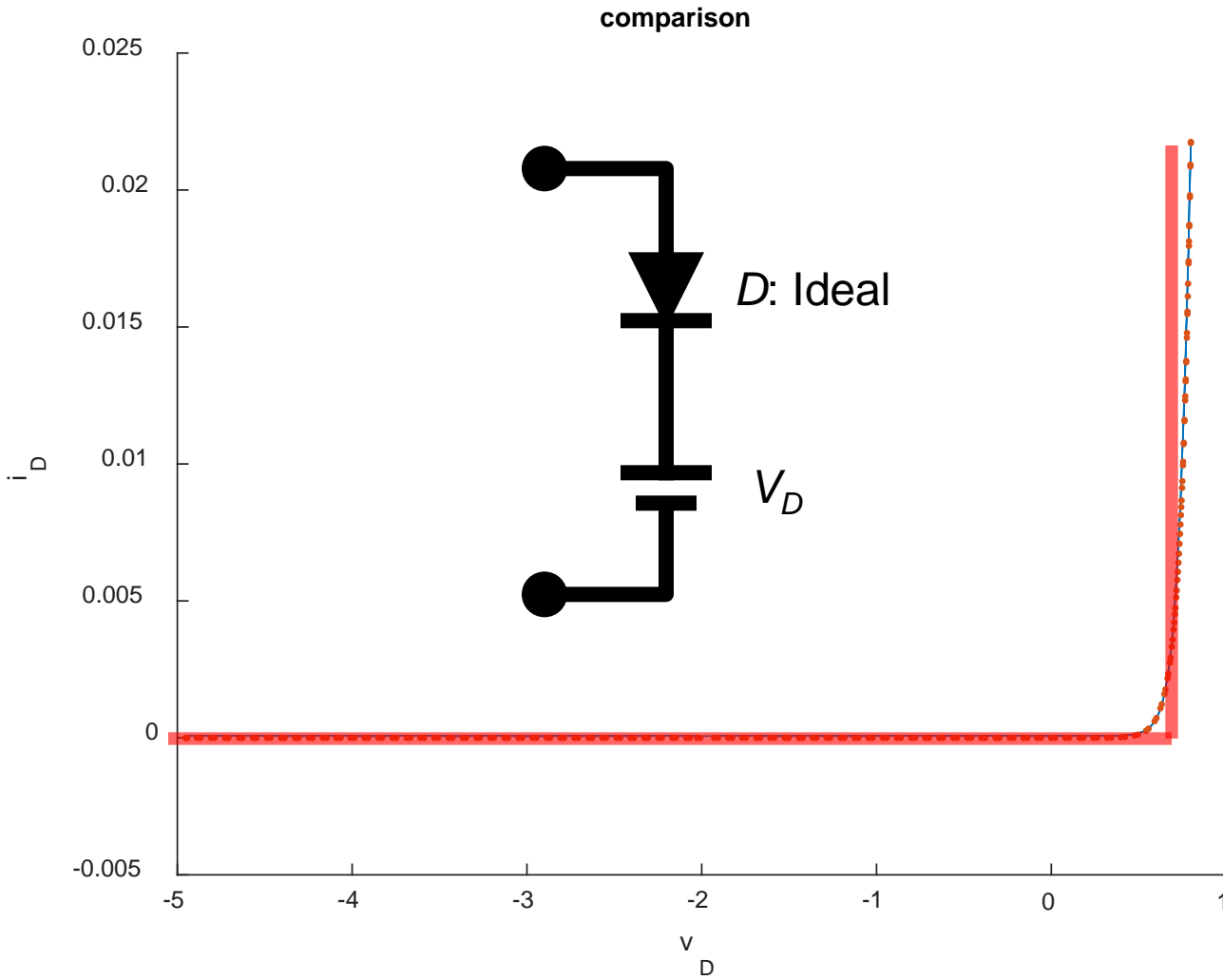Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic


$$V_D = 0.7$$

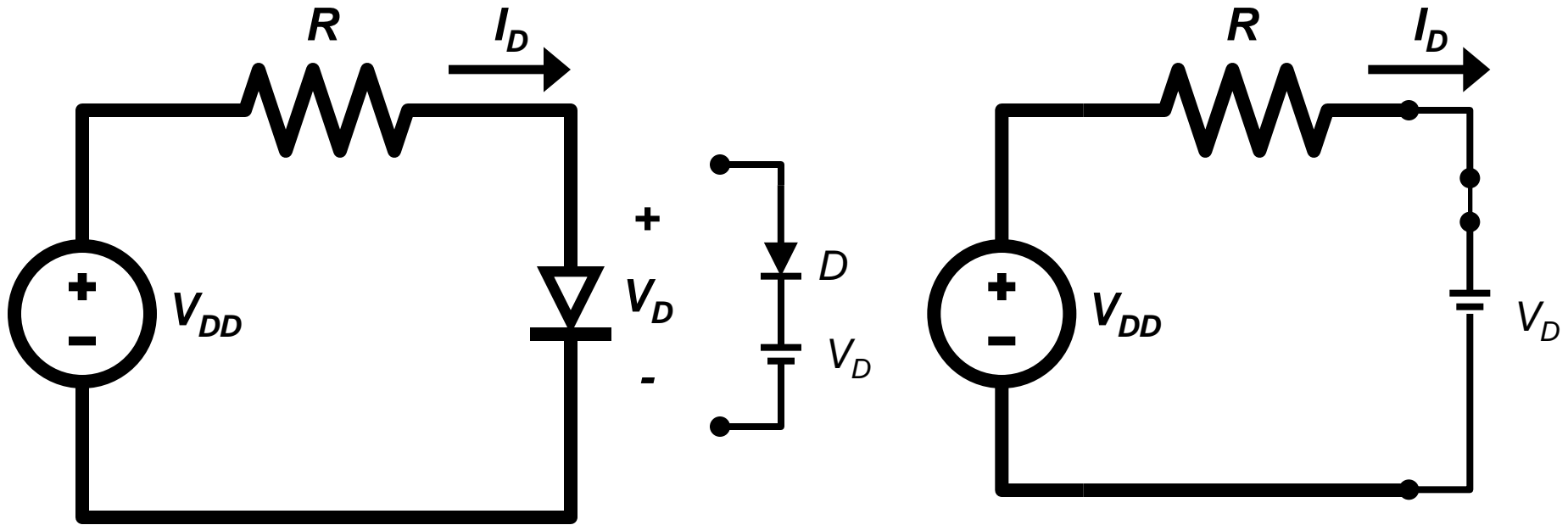

Modeling the Diode Forward Characteristic

$$V_D = 0.7$$

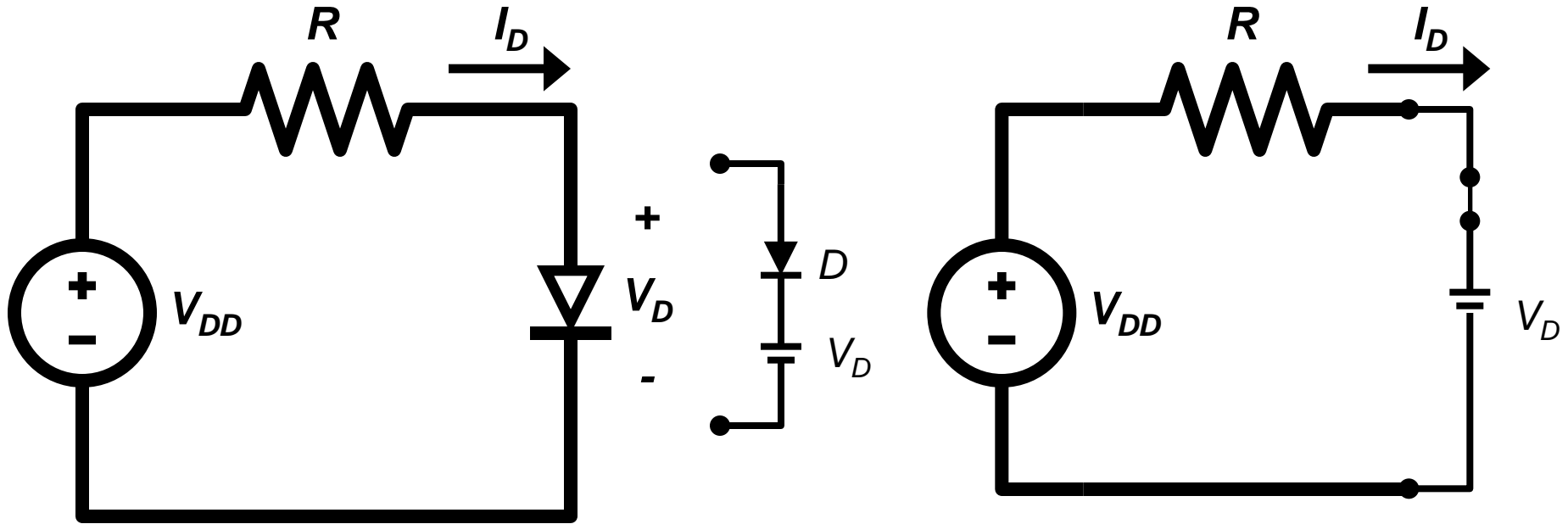
$$i_D = (10 - 0.7) / 500 = 18.6 \text{ mA}$$





Modeling the Diode Forward Characteristic

The Constant Voltage Drop Model.

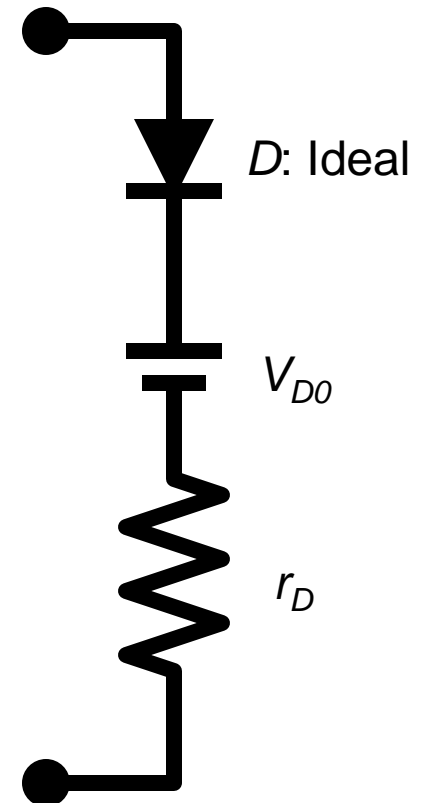- Consider the i-v relationship for the following configuration.
- An ideal diode, a battery, and a resistor.
- V_D uses a value between 0.6V and 0.8V (typically 0.7V).
- The battery models the small amount of potential needed to start conducting.
- The resistor models the slope of the exponential curve.





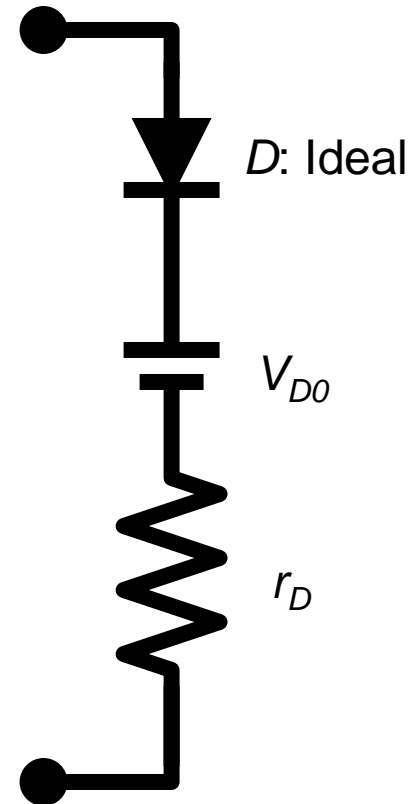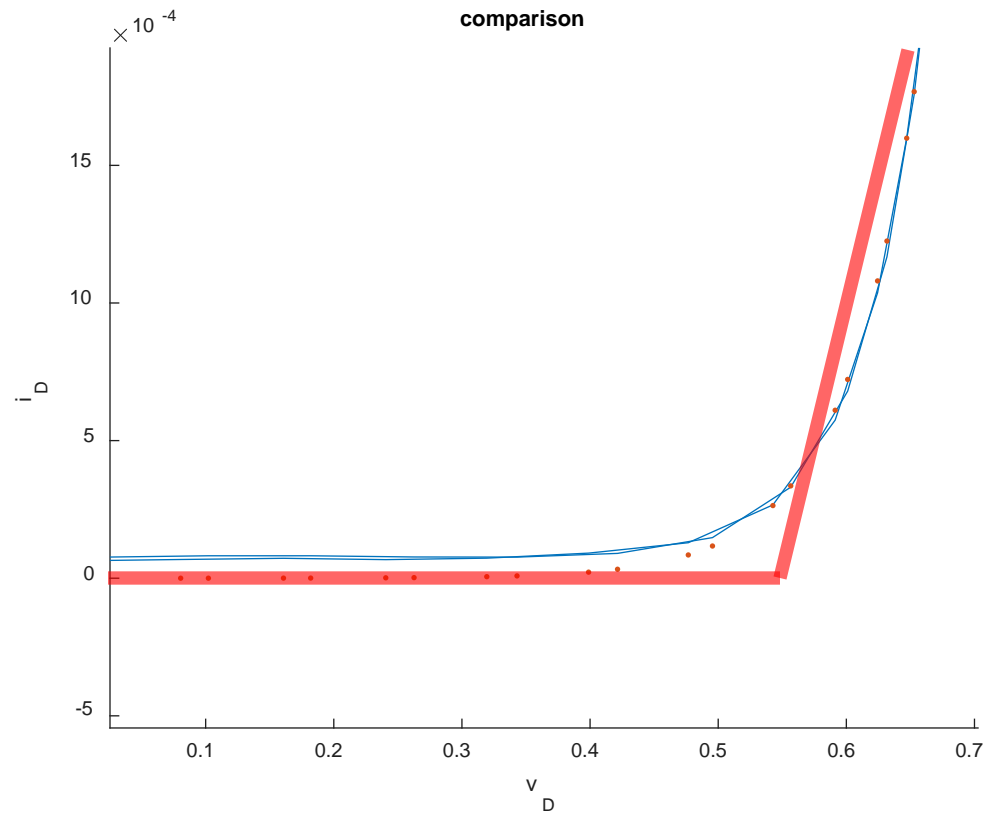Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic

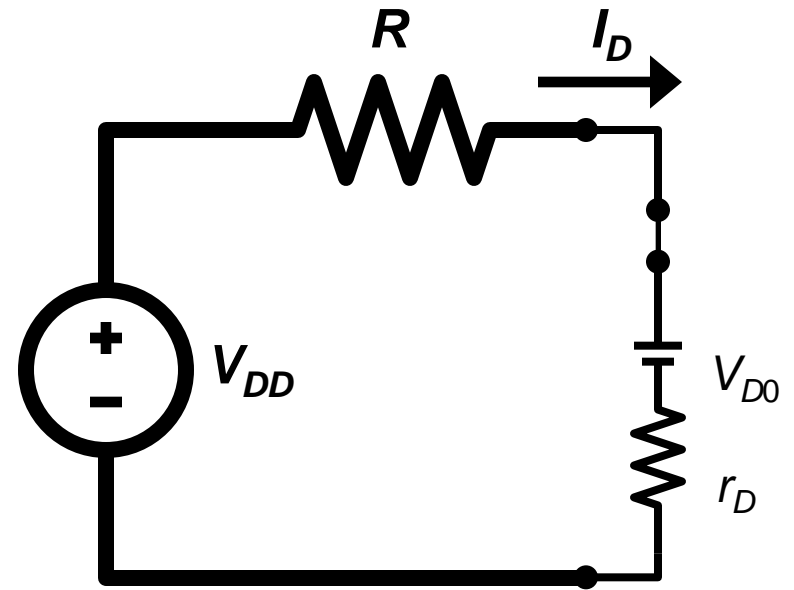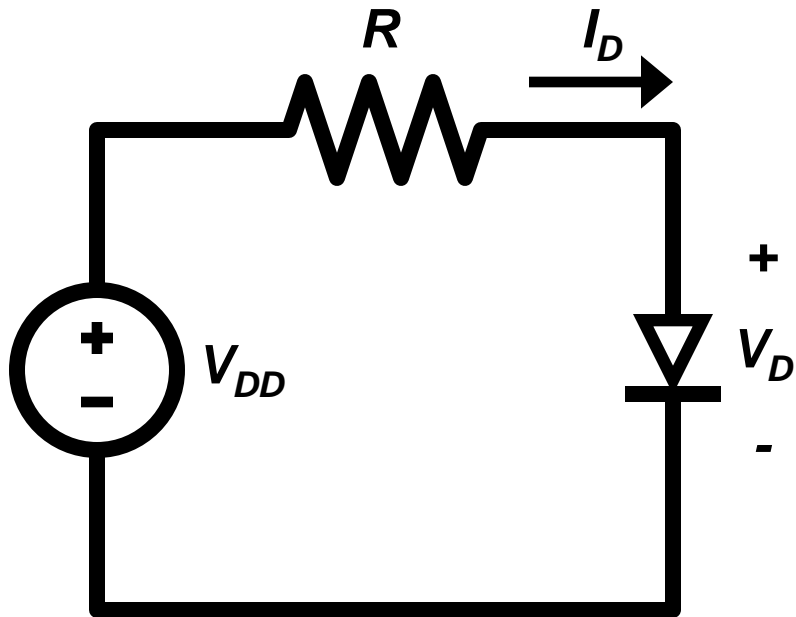$V_{D0}=0.55\text{ V}$ and $r_D=15\ \Omega$.





Modeling the Diode Forward Characteristic

$V_{D0}=0.55\text{ V}$ and $r_D=15\ \Omega$.

$$i_D = (10 - 0.55) / 515 = 18.3\text{ mA}$$

$$V_D = V_{D0} + r_D \cdot i_D = 0.825$$

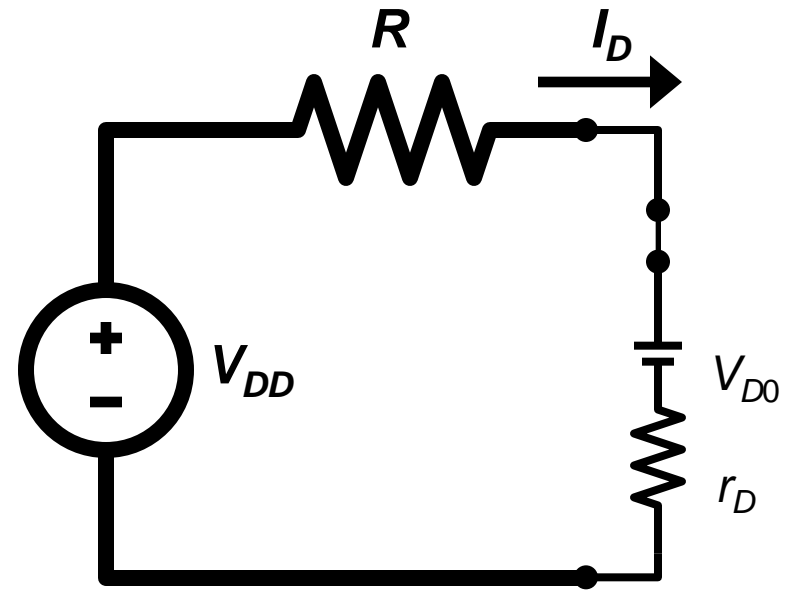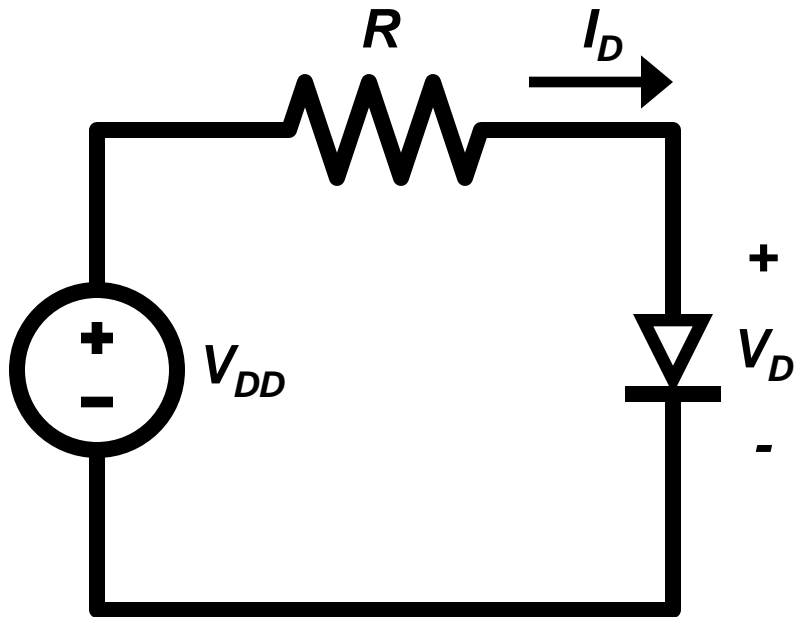

Modeling the Diode Forward Characteristic

Q. How are values for V_{D0} and r_D determined?

A. Minimize error within a certain range of operating conditions.

A. 1 point and a slope.

A. Given 2 points we can find a line.

Modeling the Diode Forward Characteristic

Accurate (*depends on correct model parameters*) Simple

V_D 0.7000 0.78
 I_D 0.0186 0.01

Exponential


Battery Plus Resistance
 Piecewise Linear

Constant Voltage Drop

Ideal



$$i_d = I_S e^{v_d / nV_T}$$

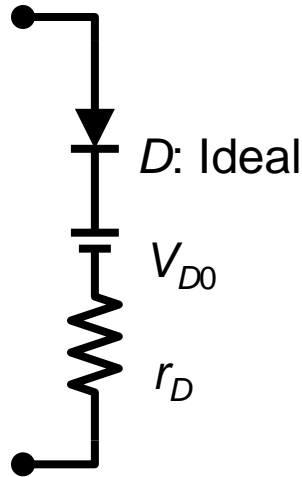


$$i_d = 0, \quad v_d \leq V_{D0}$$

$$i_d = \frac{v_d - V_{D0}}{r_D}, \quad v_d \geq V_{D0}$$

$V_D = 0.7888V$
 $I_D = 18.4mA$

$V_D = 0.825V$
 $I_D = 18.3mA$

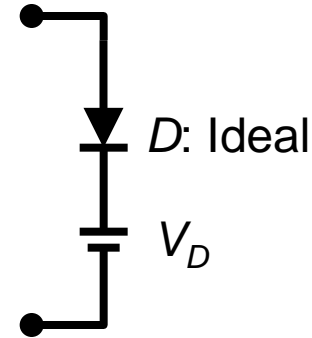

$$i_d = 0, \quad v_d \leq V_D$$

$$i_d = \text{short}, \quad v_d \geq V_D$$

$V_D = 0.7V$
 $I_D = 18.6mA$



$$i_d = 0, \quad v_d \leq 0$$

$$i_d = \text{short}, \quad v_d \geq 0$$

$V_D = 0.0V$
 $I_D = 2mA$