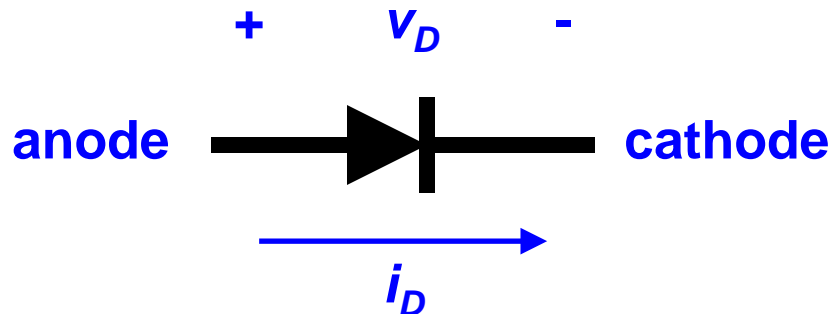


# The Ideal Diode

Diodes: A fundamental non-linear circuit element.

## A) The (Ideal) Diode Symbol



*\* The anode and cathode get their names from way back in the vacuum tube days.*

Notes:

- 1) The device is not symmetrical, we must specify (name) the connections: anode and cathode.
- 2) Positive voltage is defined from the anode to the cathode.
  - Forward Direction
- 3) Positive current is defined from the anode to the cathode.


# The Ideal Diode

Why do we study the “**ideal**” diode rather than a real diode?


- An ideal diode is a close approximation to the real thing, and it is simplified (easy to understand).
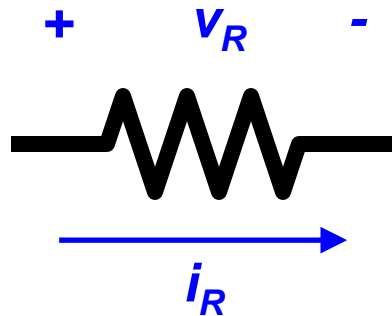
## Resistor Extremes (a quick review)



- We are going to start easy and work our way up; but first let's start really easy and review the resistor, specifically in the extreme cases when  $R=0$  and  $R=\infty$ .



$$i_R = V_R / R$$

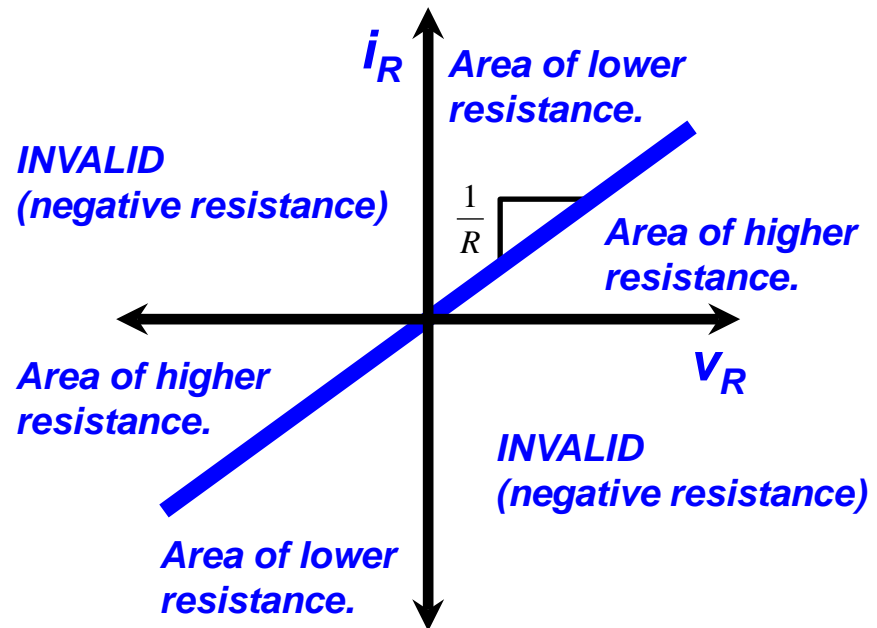

# The Ideal Diode

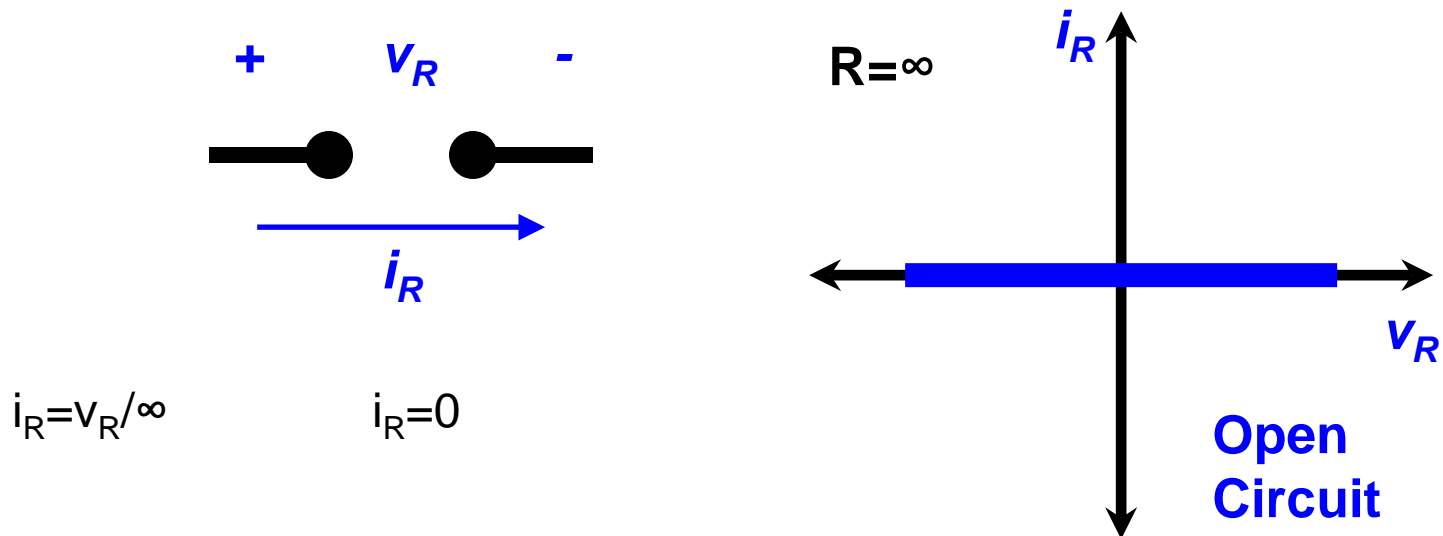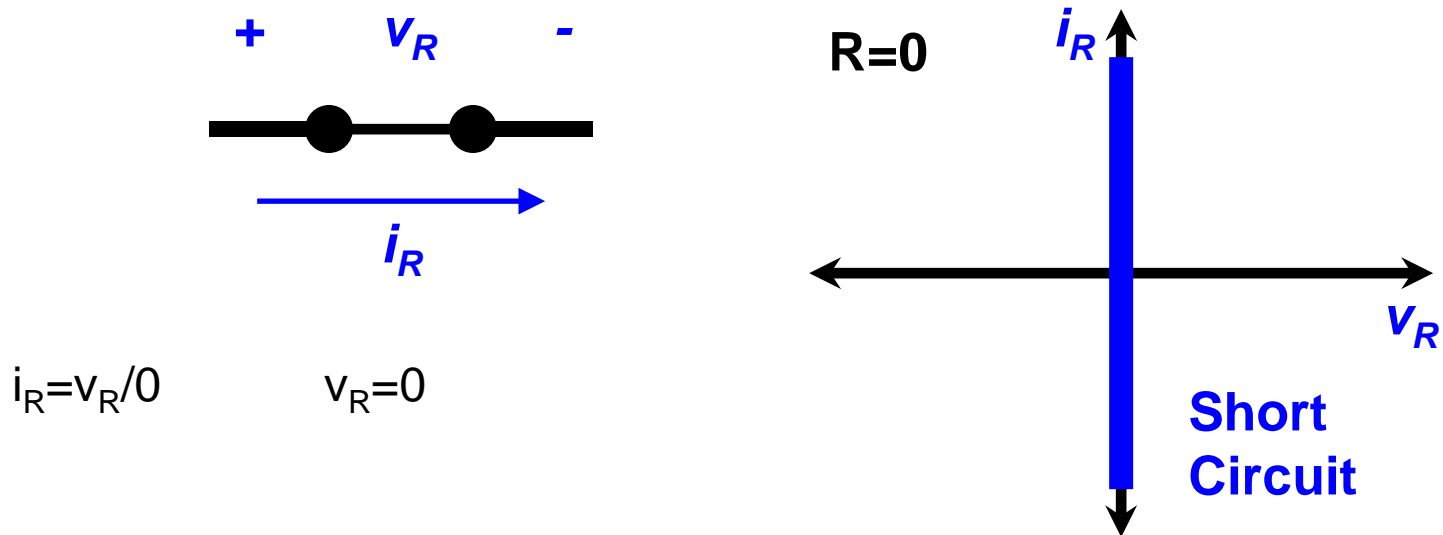


# The Ideal Diode
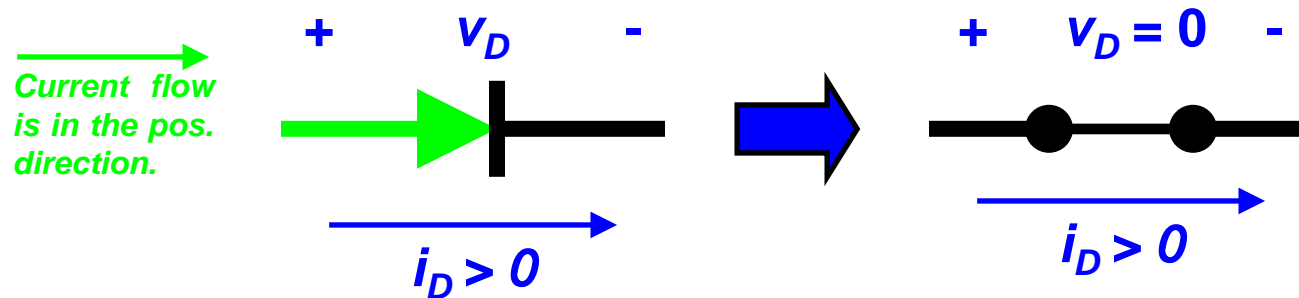
## C) The Ideal Diode Bias Regions

A resistor with  $R=0$  is a short circuit ( $v=0$ ) and a resistor with  $R=\infty$  is an open circuit ( $i=0$ ), but what does this have to do with a diode?

- The ideal diode can act as a short or an open depending on what voltage or current are applied (bias).
- When current flow is in the **positive direction**, the ideal diode is a **short circuit or FORWARD BIASED**.




**Forward Biased:  $i_D > 0$  &  $v_D = 0$   
SHORT CIRCUIT**

# The Ideal Diode
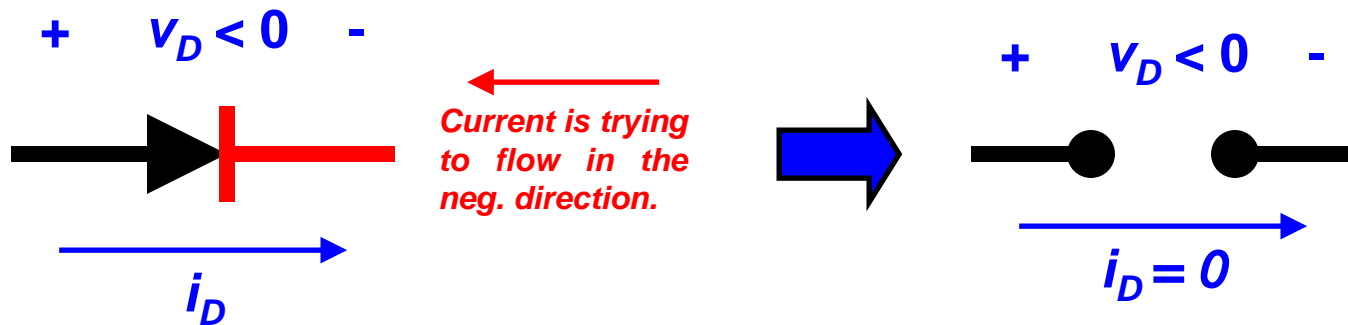
## C) The Ideal Diode Bias Regions (Continued)

- When current **tries** to flow in the **negative direction** (**negative voltage applied**), the ideal diode is an **open circuit or REVERSE BIASED**.




**Reverse Biased:  $v_D < 0$  &  $i_D = 0$**   
**OPEN CIRCUIT**

- The ideal diode only lets current flow in one direction. When current is flowing in the positive direction there is no resistance (**arrow**), and when current tries to flow in the negative direction there is infinite resistance (**wall**).

# The Ideal Diode
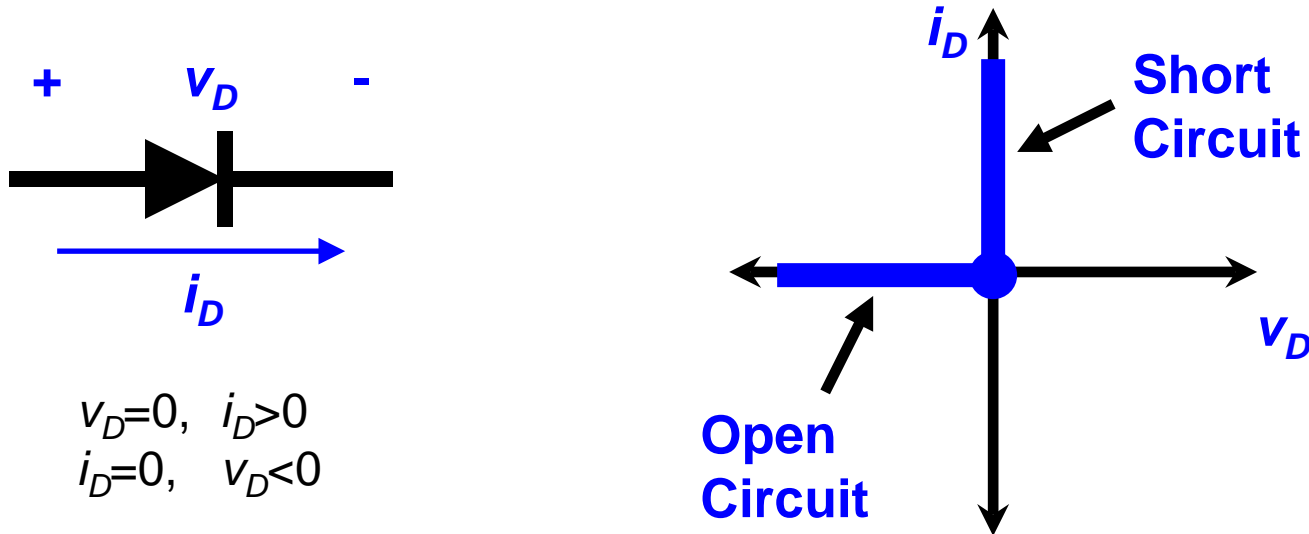
## D) The Ideal Diode $i$ - $v$ Relationship

- Remember the ideal diode acts like a short when it is **forward biased**,  $i_D > 0$  ( $v_D = 0$ ), and like an open when it is **reverse biased**,  $v_D < 0$  ( $i_D = 0$ ).





Is ideal diode is linear?

What is the power dissipated in the ideal diode?

# The Ideal Diode
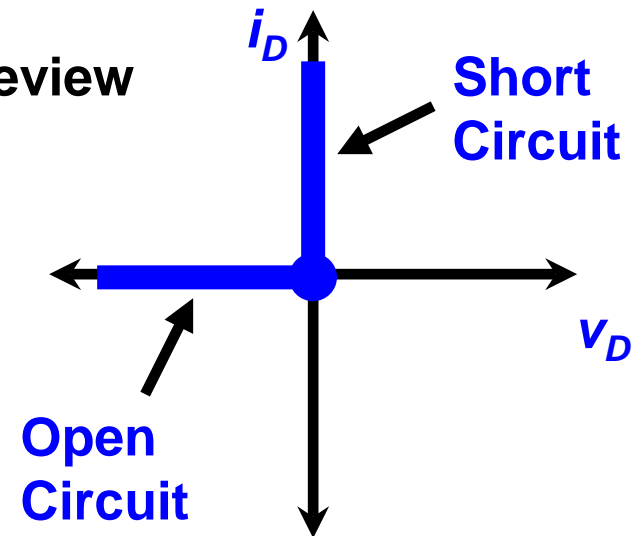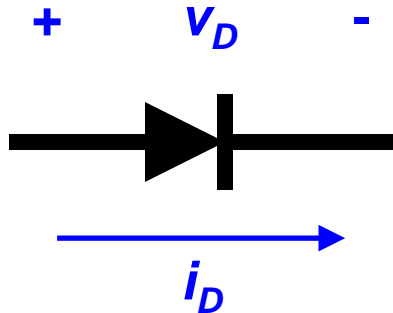
## D) The Ideal Diode $i$ - $v$ Relationship Review



	$v_D < 0$	$v_D = 0$	$v_D > 0$
$i_D > 0$	INVALID	Forward Biased Short Circuit	INVALID
$i_D = 0$	Reverse Biased Open Circuit	No Bias*	INVALID
$i_D < 0$	INVALID	INVALID	INVALID


\*can be included with either Forward Bias or Reverse Bias

# The Ideal Diode

## E) The Ideal Diode Mechanical Analog (Continued)

- An analog for the diode is a mechanical valve to control liquid flow (another could be a ratchet).

### Infinite Source: Water Tower

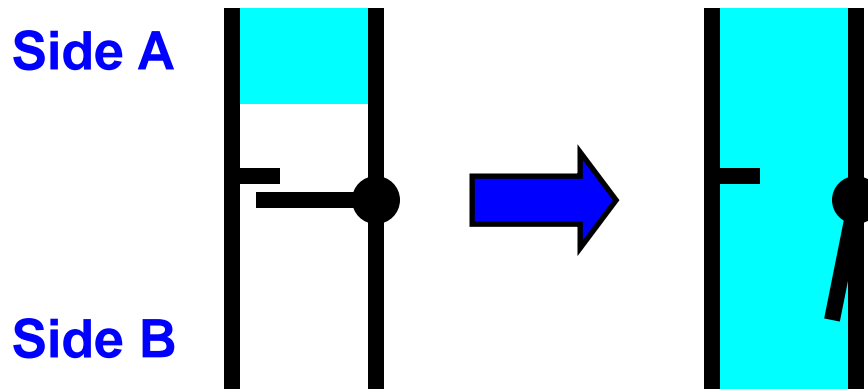


- When liquid flows in the positive direction through the valve there is no pressure difference between the two sides.
- This is the short circuit analog.



# The Ideal Diode

## E) The Ideal Diode Mechanical Analog


**Infinite Source: Water Tower**

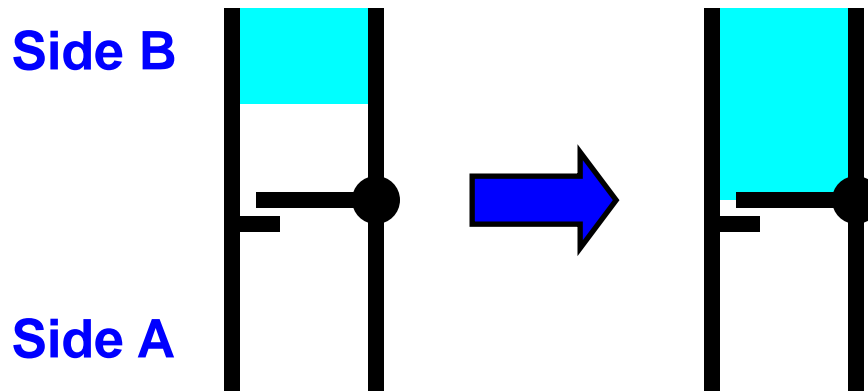

- When the valve is reversed and liquid tries to flow in the negative direction through the valve, there is no flow and a pressure difference exists between the two sides.
- This is the open circuit analog.

# The Ideal Diode
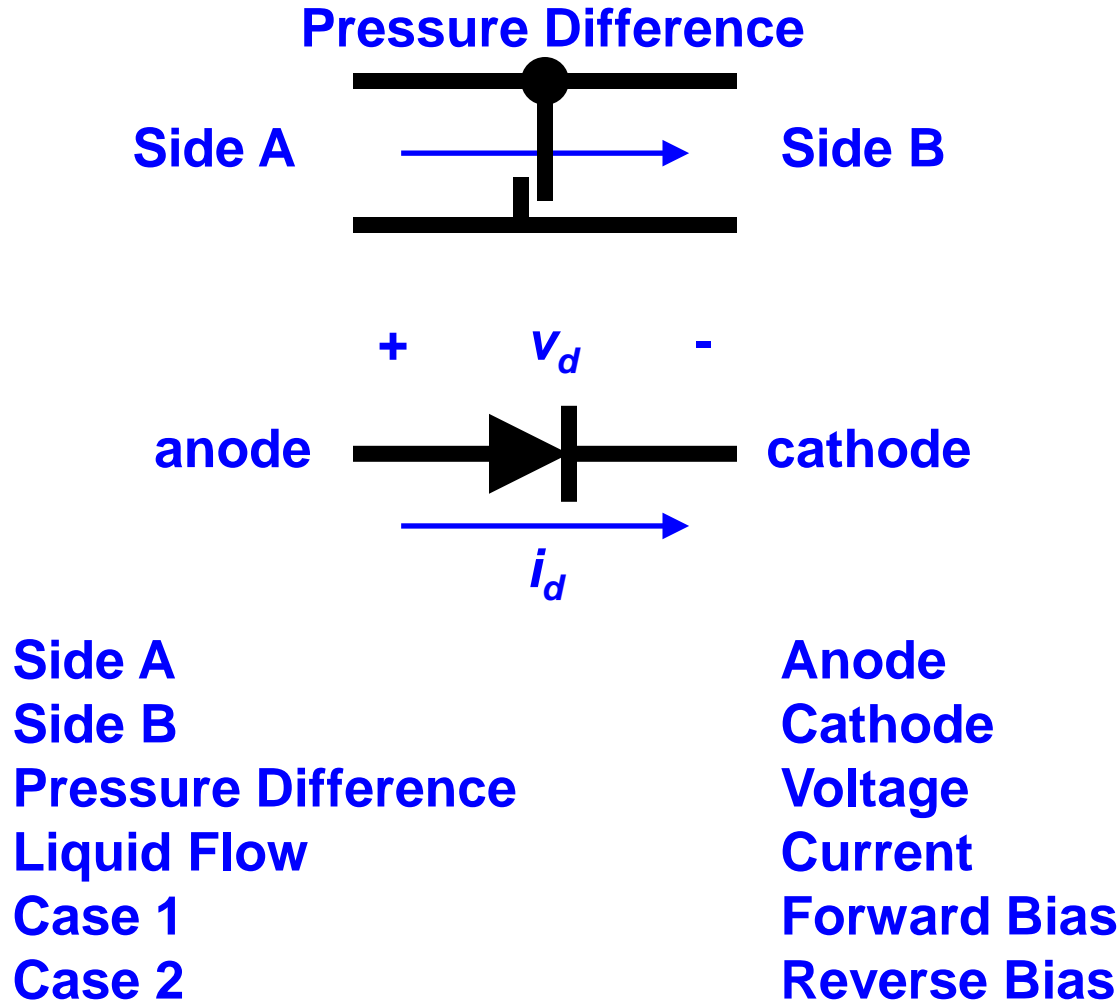
## E) The Ideal Diode Mechanical Analog (Continued)



# The Ideal Diode

## F) Circuit Analysis with the Ideal Diode

- We have shown that the ideal diode can be replaced by either a short circuit when it is forward biased or an open circuit when it is reverse biased.
- We also know that it is easy to analyze a circuit containing an open or a short circuit; so if we know how the diode is biased, we can replace it with an open or short and solve.

But what determines how the diode is biased?

- The circuit attached to it.

### The Chicken and the Egg Dilemma

- We need to solve the circuit to figure out how the ideal diode is biased, but we need to know how it is biased before we can solve the circuit.
- There is a very elegant solution...First an Example.



# The Ideal Diode

## F) Circuit Analysis with the Ideal Diode


### The Five Step Guide to Analyzing Ideal Diode Circuits

- 1) Assume a bias state for each diode (In other words, just GUESS or educated GUESS).
  - a) ASSUME the ideal diode is forward biased (short).
  - b) ASSUME the ideal diode is reverse biased (open).
- Since each ideal diode has two possible states; there will be  $n^2$  possible configurations, where  $n$  is the number of diodes.
- 2) Enforce the EQUALITY condition of your ASSUMPTION.  
(Replace the diode with the equivalent circuit)
  - a) If you assumed forward bias then E.C. is  $v_d=0$ .  
Replace it with a short circuit.
  - b) If you assumed reverse bias then E.C. is  $i_d=0$ .  
Replace it with an open circuit.


# The Ideal Diode
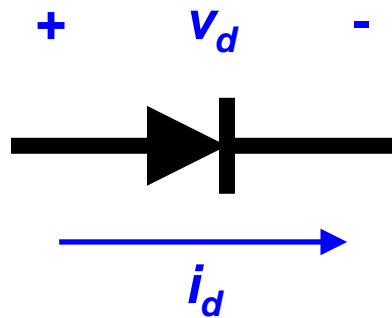
## F) Circuit Analysis with the Ideal Diode


- IMPORTANT!!** RETAIN THE SAME VOLTAGE AND CURRENT DEFINITIONS (DIRECTIONS) WHEN YOU REPLACE THE IDEAL DIODE.




Assume  
Forward Bias  
(Short)

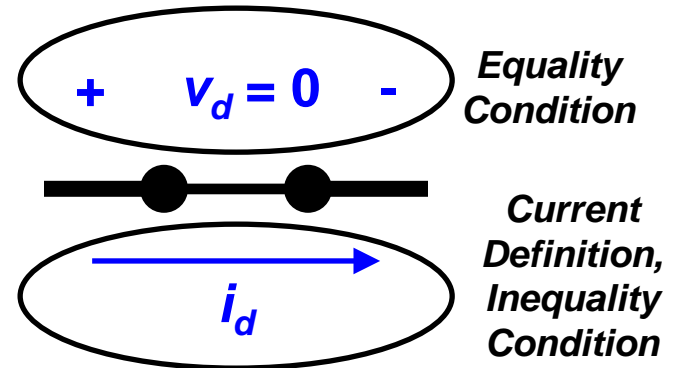

OR

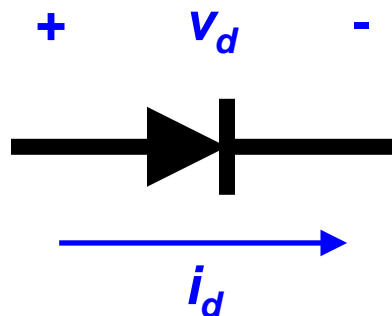

Assume  
Reverse Bias  
(Open)

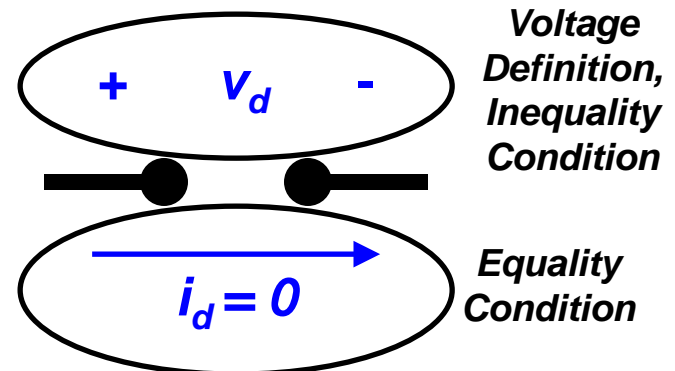

# The Ideal Diode

## F) Circuit Analysis with the Ideal Diode

3) Analyze the circuit.

- Do this after you have replaced all the diodes with either short circuits or open circuits.
  - a) Determine all desired (required) circuit values.
  - b) Determine  $i_d$  across the short circuit, and  
Determine  $v_d$  across the open circuit.
    - You will need these to check your initial assumptions.

# The Ideal Diode

## F) Circuit Analysis with the Ideal Diode

4) Check if the INEQUALITY Condition of your assumption is correct.

- a) An ideal diode cannot have a negative current. If you assumed forward bias then the current must be non-negative (Inequality condition is  $i_d \geq 0$ ).
  - b) An ideal diode cannot have a positive voltage. If you assumed reverse bias then the voltage must be non-positive (Inequality condition is  $v_d \leq 0$ ).
- Bias, Short, Open, Equality Condition, Inequality Condition?

Diode Bias	Equality Condition	Equivalent Circuit	Inequality Condition
Forward	$v_d = 0$	(Short Circuit)	$i_d \geq 0$
Reverse	$i_d = 0$	(Open Circuit)	$v_d \leq 0$

***This chart or something similar is useful to keep track of assumption during analysis.***



# The Ideal Diode

## F) Circuit Analysis with the Ideal Diode

5) If the inequality conditions do not match with the analysis results then change your assumption and go back to step 2.

- **Hints for ideal diode circuit analysis.**

1) you must check all inequality conditions.

$$v_d = 2.2V \leq 0 \quad \text{NO ... start again.}$$

$$i_d = 1.5A \geq 0 \quad \text{YES}$$

2) Do not check the equality conditions, check the inequality conditions.

3) There is only one solution (set of assumptions) that will be correct.

# The Ideal Diode

## F) Circuit Analysis with the Ideal Diode (Summary)

- 1. Guess (Assume) a Bias for each diode. If possible make an educated guess based on your interpretation of the circuit.**
- 2. Enforce the Bias for each Diode.**
  - **FB: Short Circuit,  $v_D=0$**
  - **RB: Open Circuit,  $i_D=0$**
- 3. Solve the circuit.**
  - **The Solution of the Circuit.**
  - **The inequality variable of each diode assumption.**
    - **FB: Solve for  $i_D$ .**
    - **RB: Solve for  $v_D$ .**
- 4. Compare the solutions of the inequality variables with the inequality conditions.**
  - **FB:  $i_D > 0$**
  - **RB:  $v_D < 0$**
- 5. If correct, the problem is finished; if not, go back to step (1) and try another Guess.**

# The Ideal Diode

## G) Transfer Function with the Ideal Diode (Summary)

1. Choose a Bias for each diode.
2. Enforce the Bias for each Diode.
  - FB: Short Circuit,  $v_D=0$
  - RB: Open Circuit,  $i_D=0$
3. Solve the circuit in terms of the independent variable.
  - The Solution of the Circuit.
  - The inequality variable of each diode assumption.
    - FB: Solve for  $i_D$  in terms of the independent variable.
    - RB: Solve for  $v_D$  in terms of the independent variable.
4. Compare the solutions of the inequality variables with the inequality conditions to determine the range of values that the solution is valid.
  - FB:  $i_D > 0$
  - RB:  $v_D < 0$
5. Repeat process for all possible bias combinations.

# The Ideal Diode

- Application: Digital Logic