

Modeling the Diode Forward Characteristic

- Simple circuit consisting of a source, a resistor, and a diode.
- For forward bias we have 2 models for the diode.


1) Ideal Diode: Short Circuit

$$V_D = 0$$

$$I_D > 0$$

2) Exponential Model

$$I_D = I_S e^{V_D / nV_T}$$

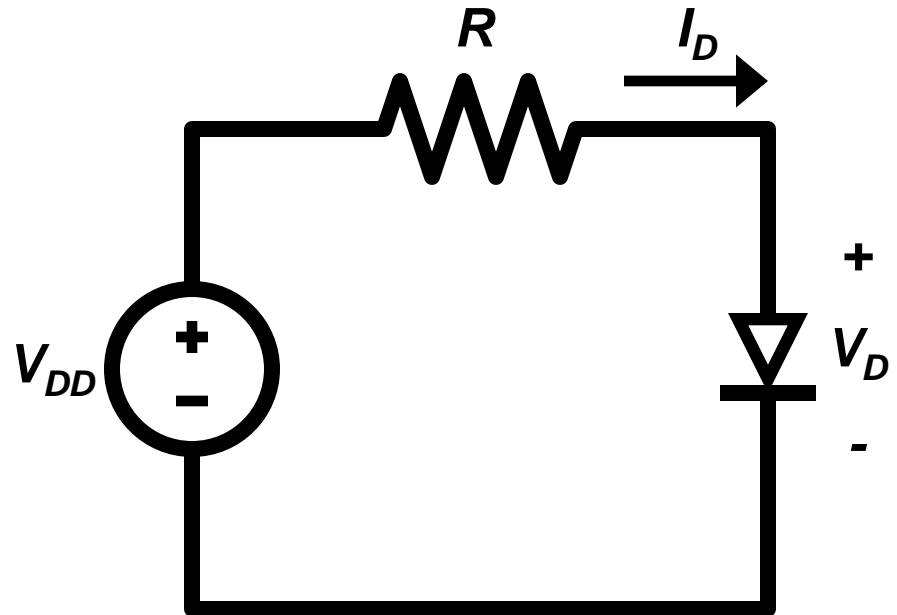

- In this section, we will:
 - 1) Address the suitability of these two models.
 - 2) Develop new models.
- This will help us to:
 - 1) Analyze diode circuits efficiently.
 - 2) Provide a foundation for modeling transistor operation.

Modeling the Diode Forward Characteristic

A) The Exponential Model


- 1) The most accurate model.
- 2) The hardest to analyze.

Let's analyze a circuit using the exponential model.

$$I_D = I_S e^{V_D / nV_T}$$

$$I_D = I_R = \frac{V_{DD} - V_D}{R}$$
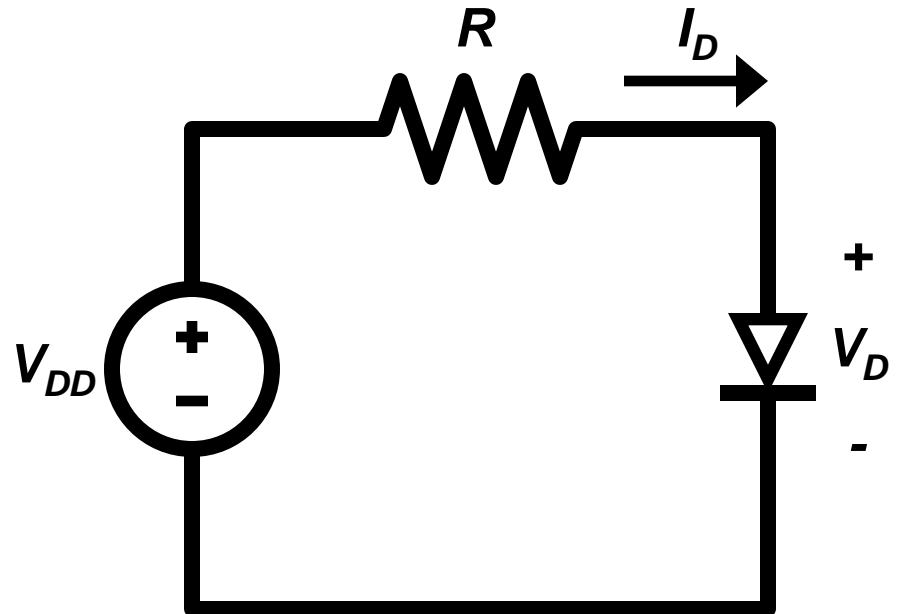
$$I_D = -\frac{1}{R}V_D + \frac{V_{DD}}{R}$$



I_S , n , V_T are known quantities.

We have two equations with two unknowns.

Q. How do we solve for I_D and V_D ?

Modeling the Diode Forward Characteristic

Graphically


a) Plot the two equations on the i - v plane.

Eq. 1: diode characteristic curve.

$$I_D = I_S e^{V_D / nV_T}$$

Eq. 2: load line.

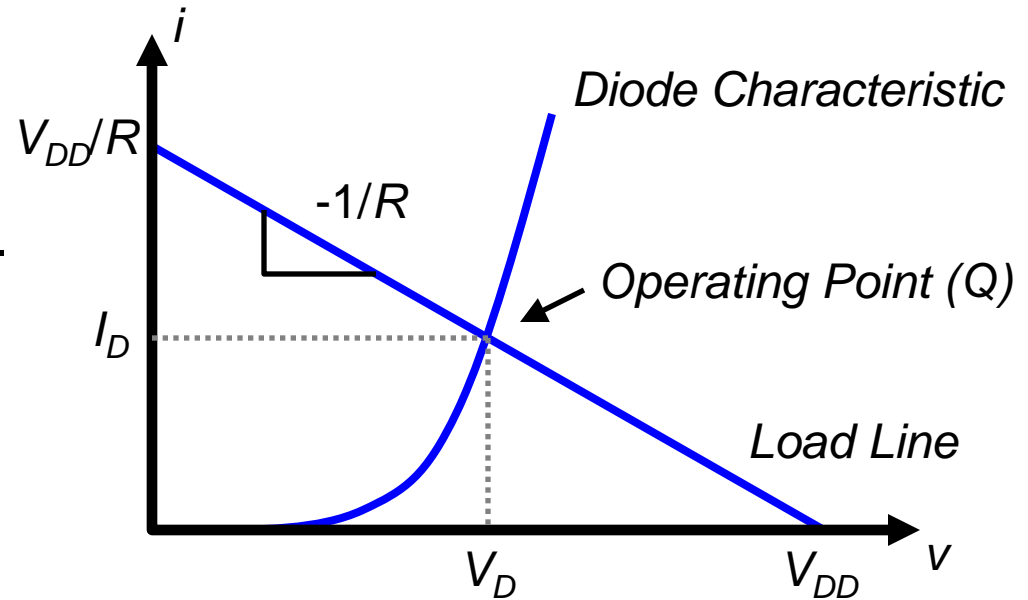
$$I_D = -\frac{1}{R}V_D + \frac{V_{DD}}{R}$$



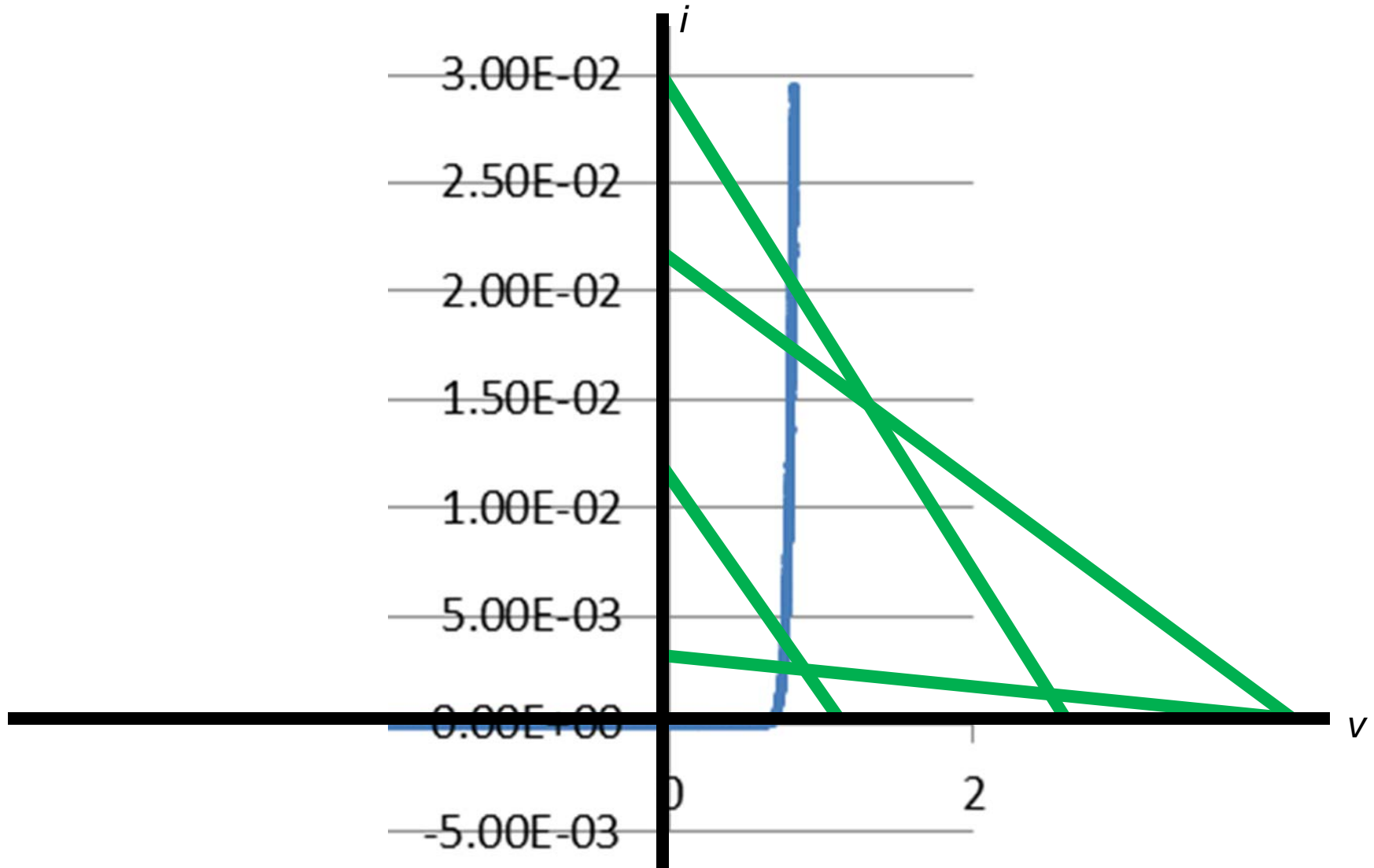
b) The solution is the intersection, Q, of the two curves and is referred to as the operating point.

- Graphical analysis becomes very difficult for complex circuits.
- Too difficult to be justified for practical use.

Modeling the Diode Forward Characteristic




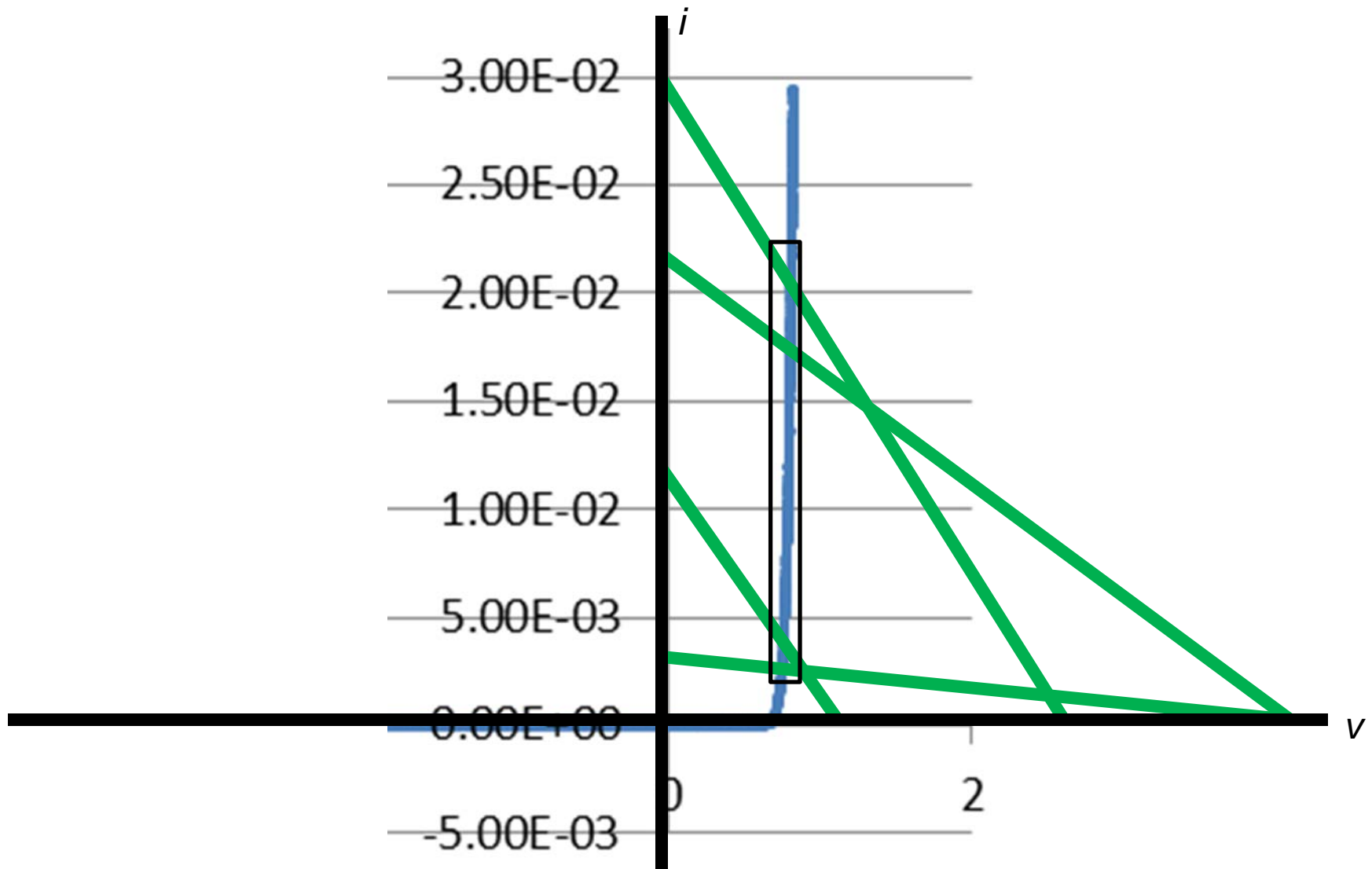Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic

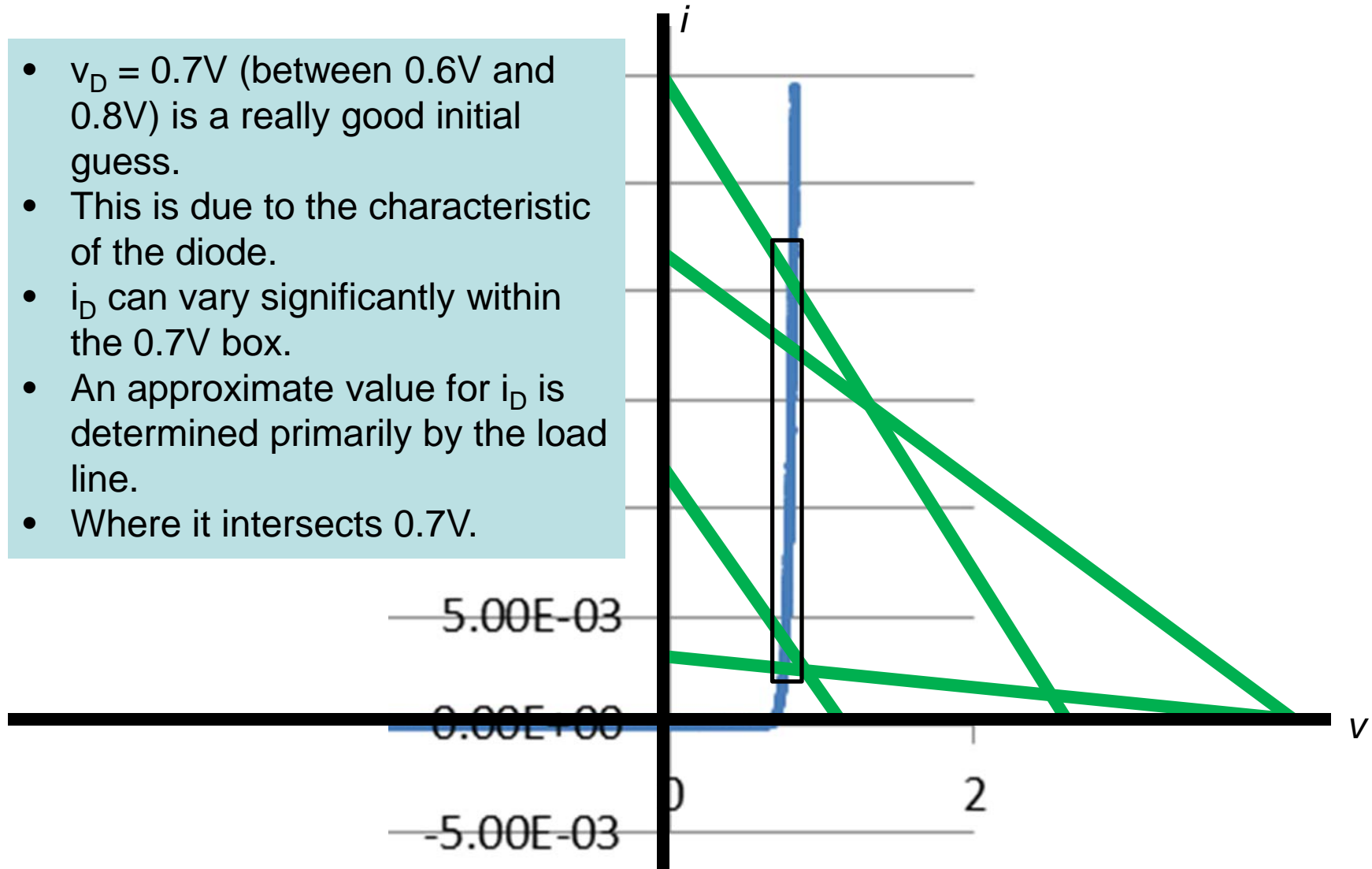- $v_D = 0.7V$ (between 0.6V and 0.8V) is a really good initial guess.
- This is due to the characteristic of the diode.
- i_D can vary significantly within the 0.7V box.
- An approximate value for i_D is determined primarily by the load line.
- Where it intersects 0.7V.



Modeling the Diode Forward Characteristic

Iterative analysis

Remember the two equations: $I_D = I_S e^{V_D / nV_T}$ Diode Characteristic

$$I_D = -\frac{1}{R}V_D + \frac{V_{DD}}{R} \quad \text{Load Line}$$

What do we know about a diode in forward bias?

The voltage across the diode is between 0.6 and 0.8 Volts.

Approach:

- 1) Assume V_D is 0.7 Volts.
- 2) Solve for I_D using circuit equation (load line).
- 3) Calculate new value of V_D or ΔV_D using the Diode Characteristic curve.

$$V_D = nV_T \ln\left(\frac{I_D}{I_S}\right) \quad \text{or} \quad \Delta V_D = nV_T \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$


- 4) Go back to step 2 and repeat until the answer converges.

Modeling the Diode Forward Characteristic

From the measurements:

$$nV_T = .05 \text{ V}, I_S = 1 \times 10^{-8} \text{ A}$$
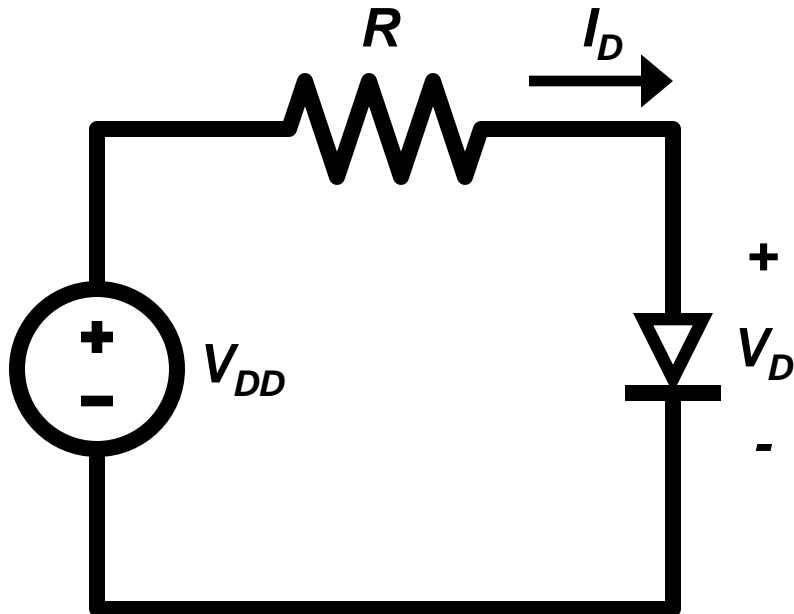
$$V_{DD} = 5 \text{ V}, \text{ and } R = 1 \text{ k}\Omega.$$




Modeling the Diode Forward Characteristic

- For complex circuits this approach is very time consuming to do by hand, because you must re-analyze the circuit for each iteration.
- However, this approach can be easily iterated using computer analysis.

Conclusions

- the graphical and iterative solution methods using the exponential model are inefficient.
- For effective circuit analysis a simple model for the junction diode is needed.

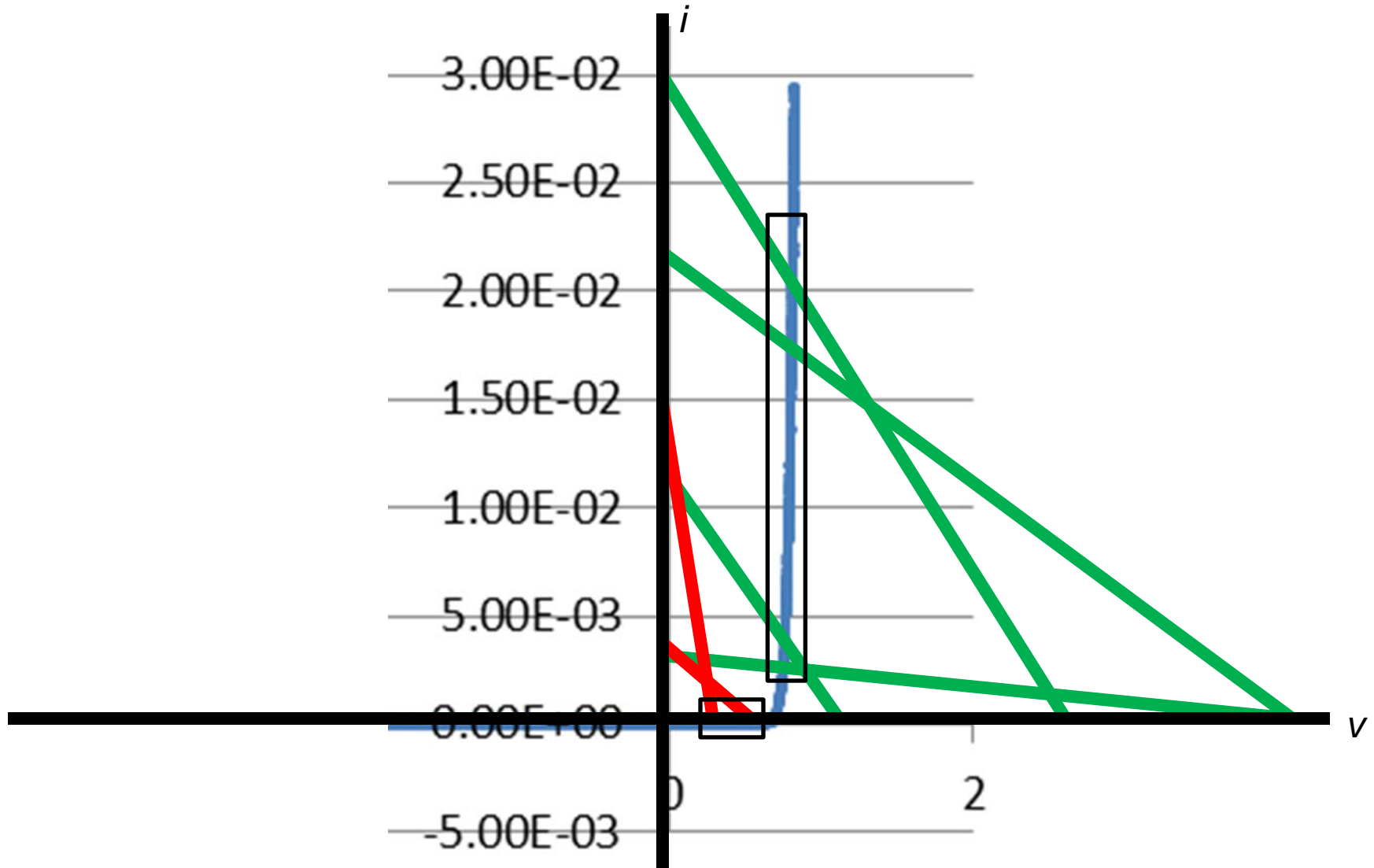
Modeling the Diode Forward Characteristic





Modeling the Diode Forward Characteristic

The Constant Voltage Drop Model.

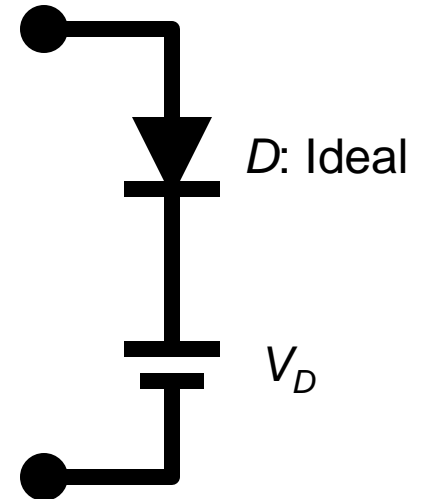- Consider the i-v relationship for the following configuration.
- An ideal diode, a battery.
- V_D uses a value between 0.6V and 0.8V (typically 0.7V).
- The battery models the small amount of potential needed to start conducting.





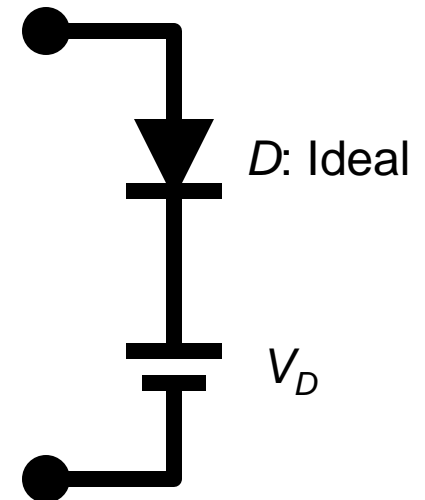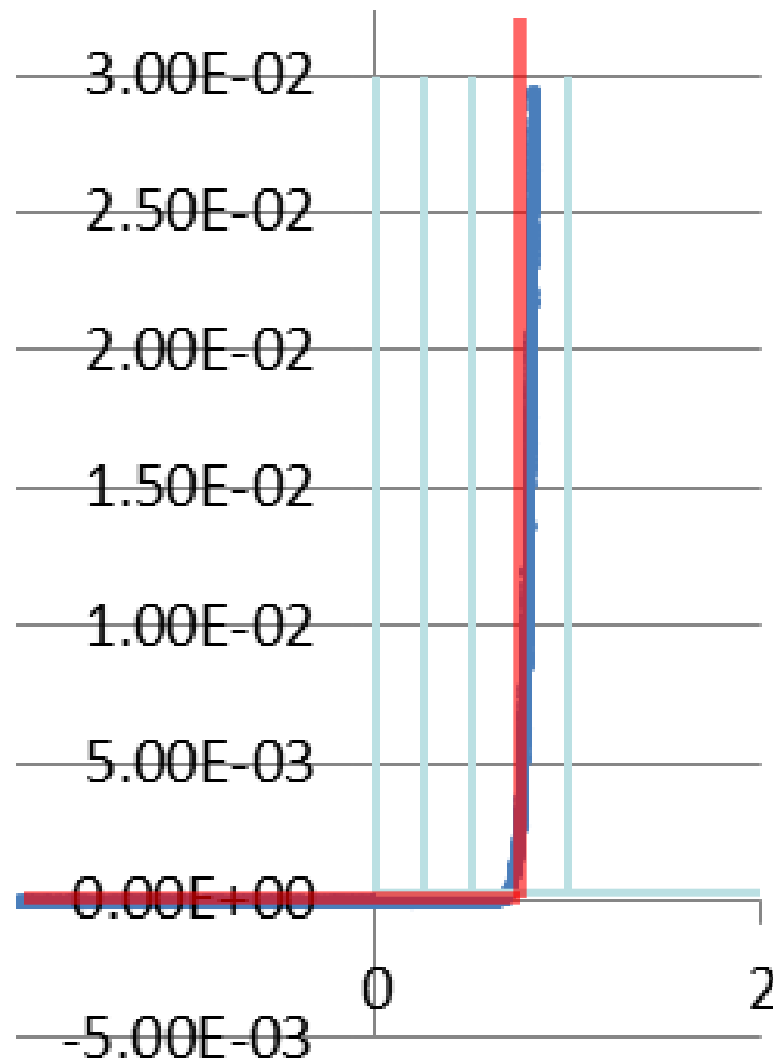Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic


$$V_D = 0.7$$

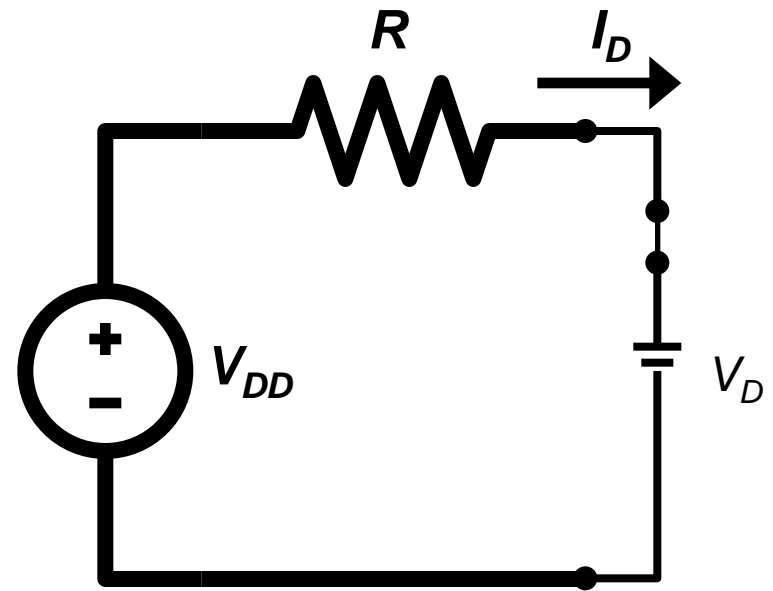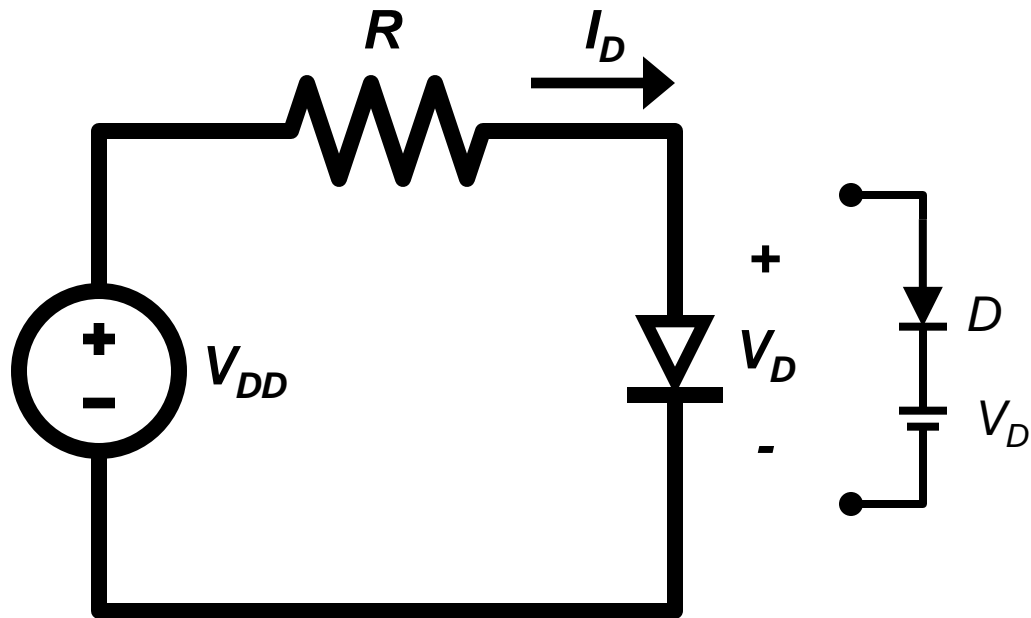


Modeling the Diode Forward Characteristic

The Constant Voltage Drop Model.

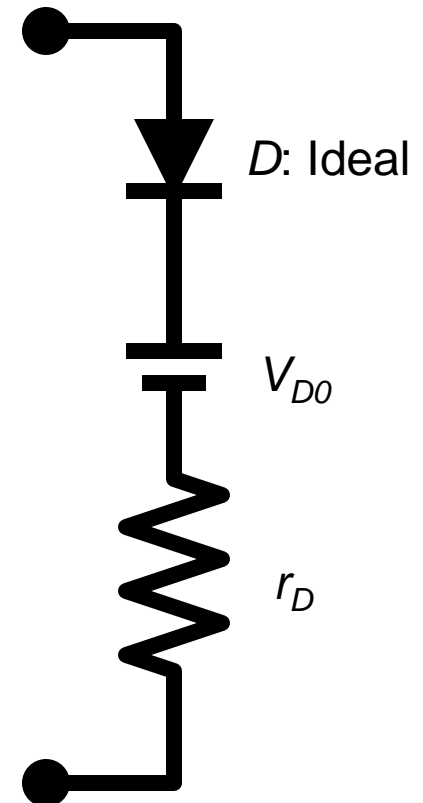- Consider the i-v relationship for the following configuration.
- An ideal diode, a battery, and a resistor.
- V_D uses a value between 0.6V and 0.8V (typically 0.7V).
- The battery models the small amount of potential needed to start conducting.
- The resistor models the slope of the exponential curve.





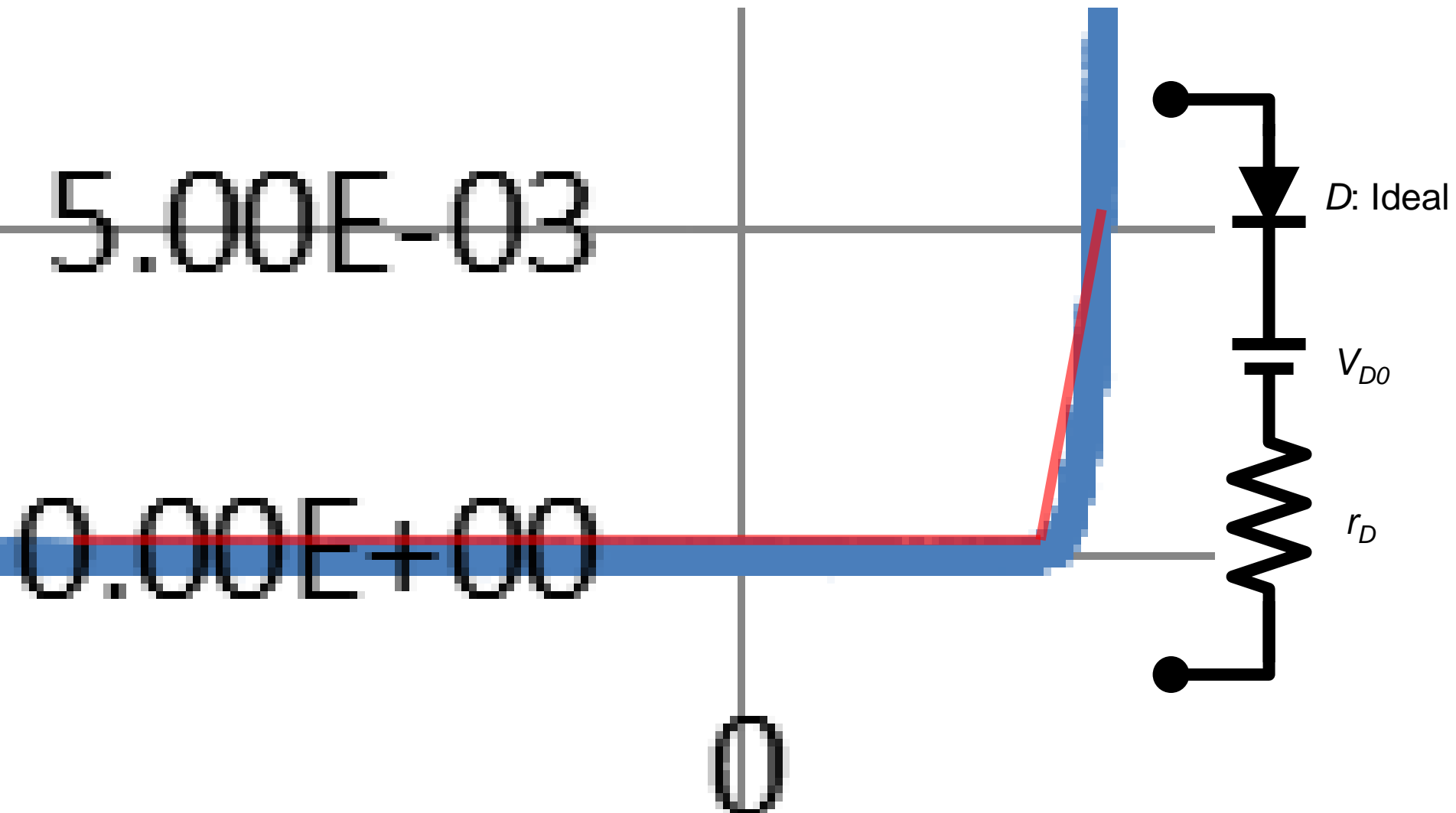Modeling the Diode Forward Characteristic



Modeling the Diode Forward Characteristic

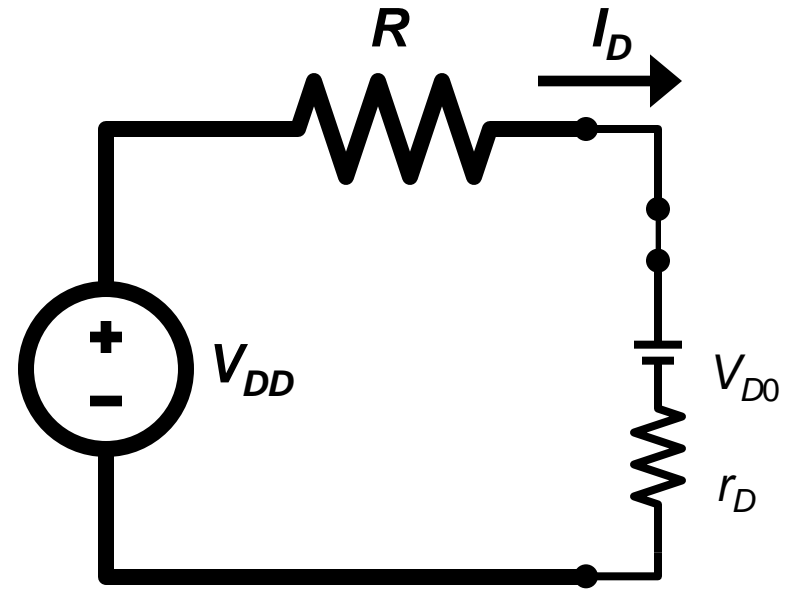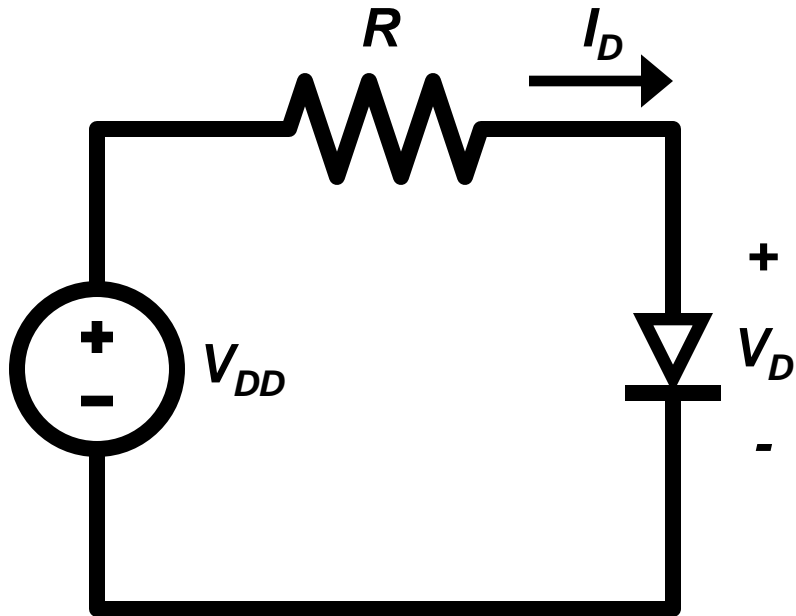$V_{D0}=0.6\text{ V}$ and $r_D=20\ \Omega$.



Modeling the Diode Forward Characteristic

Q. How are values for V_{D0} and r_D determined?

A. Minimize error within a certain range of operating conditions.

A. 1 point and a slope.

A. Given 2 points we can find a line.

Modeling the Diode Forward Characteristic

Accurate (*depends on correct model parameters*) Simple

Exponential




$$i_d = I_S e^{v_d / nV_T}$$

$$V_D = 0.649V$$

$$I_D = 4.351mA$$

Battery Plus Resistance
Piecewise Linear

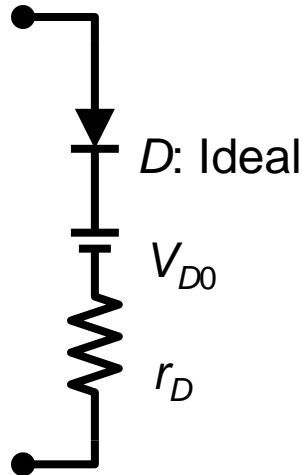


$$i_d = 0, \quad v_d \leq V_{D0}$$

$$i_d = \frac{v_d - V_{D0}}{r_D}, \quad v_d \geq V_{D0}$$

$$V_D = 0.686V$$

$$I_D = 4.314mA$$

Constant Voltage Drop

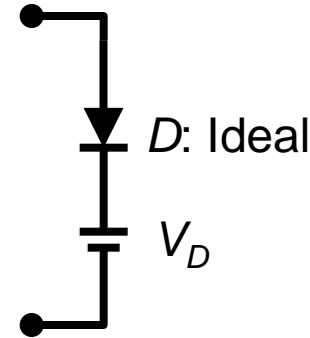


$$i_d = 0, \quad v_d \leq V_D$$

$$i_d = \text{short}, \quad v_d \geq V_D$$

$$V_D = 0.7V$$

$$I_D = 4.3mA$$

Ideal

 

$$i_d = 0, \quad v_d \leq 0$$

$$i_d = \text{short}, \quad v_d \geq 0$$

$$V_D = 0.0V$$

$$I_D = 5mA$$