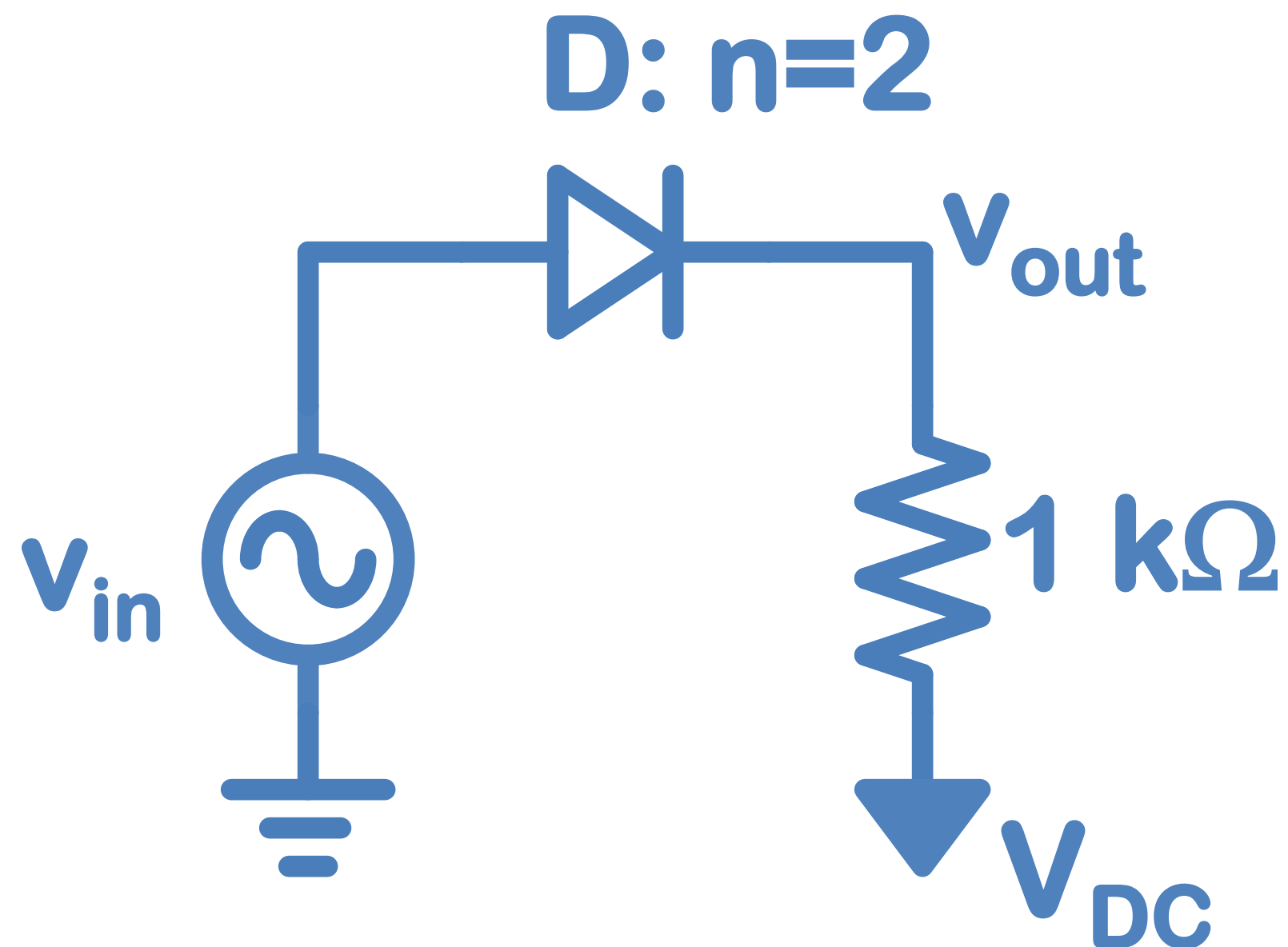


Consider the circuit below to find the small signal relationship: v_{out}/v_{in}



How does v_{out}/v_{in} change for $V_{DC}=-0.8\text{V}$? or $V_{DC}=-.071$?

How is the small signal model related to the PWL model?

Steps:

1. LARGE SIGNAL ANALYSIS

Use 0.7V CVD model to find I_D with $V_{DC}=-5\text{V}$.

Remember $v_{in}=0$ for this part.

2. SMALL SIGNAL MODEL

Calculate the small signal resistance of the diode:

$$r_d = nV_T/I_D$$


and replace the diode with the small signal model, r_d .

3. SMALL SIGNAL ANALYSIS

Use the voltage divider eq. to find the relationship: v_{out}/v_{in}

Remember $V_{DC}=0$ for this part.

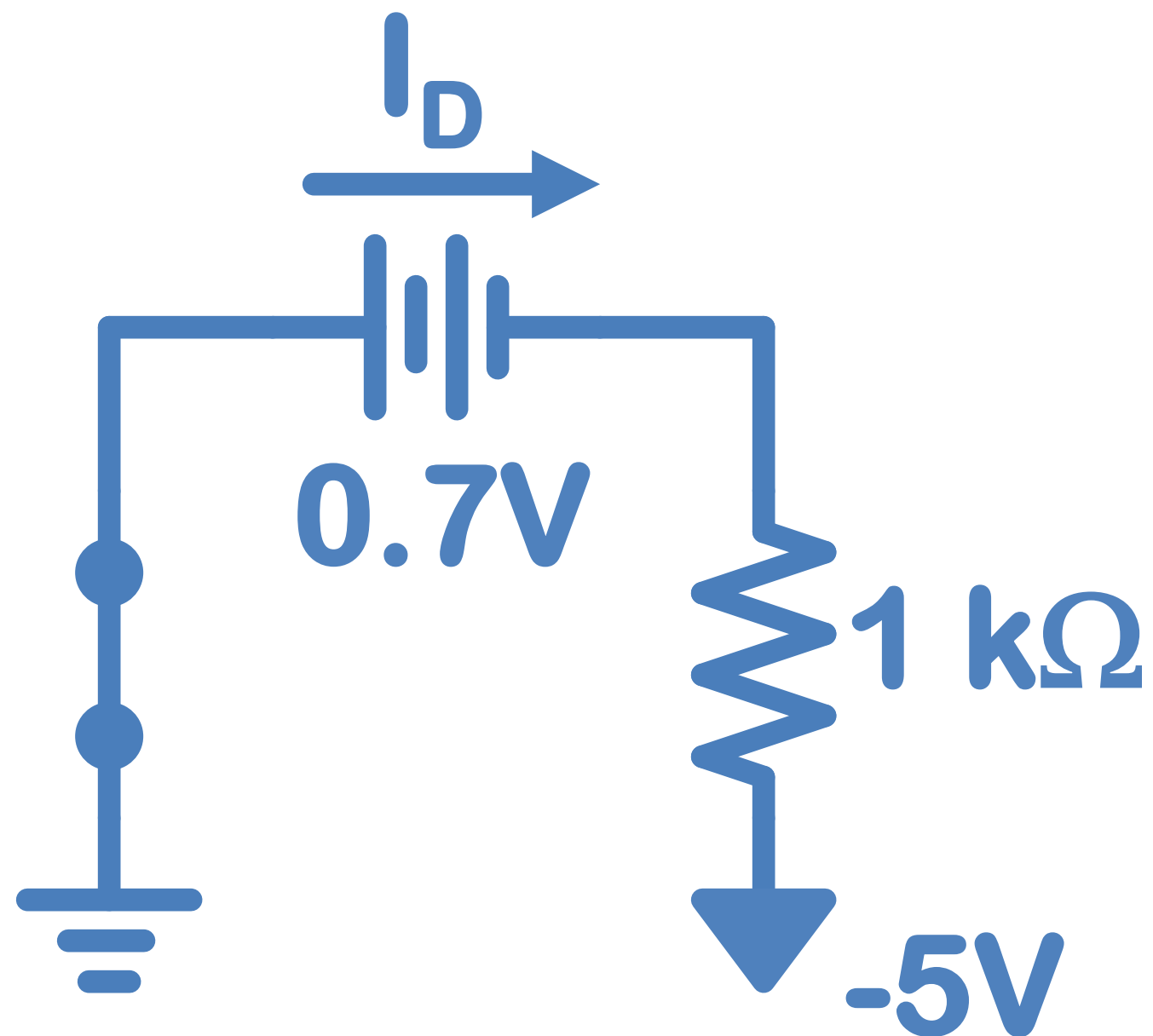Consider the circuit below to find the small signal relationship: v_{out}/v_{in}



Steps:


1. LARGE SIGNAL ANALYSIS

Use 0.7V CVD model to find I_D with $V_{DC} = -5V$.

Remember $v_{in} = 0$ for this part.

$$I_D = (-0.7 - (-5)) / 1000 = 4.3 \text{ mA}$$

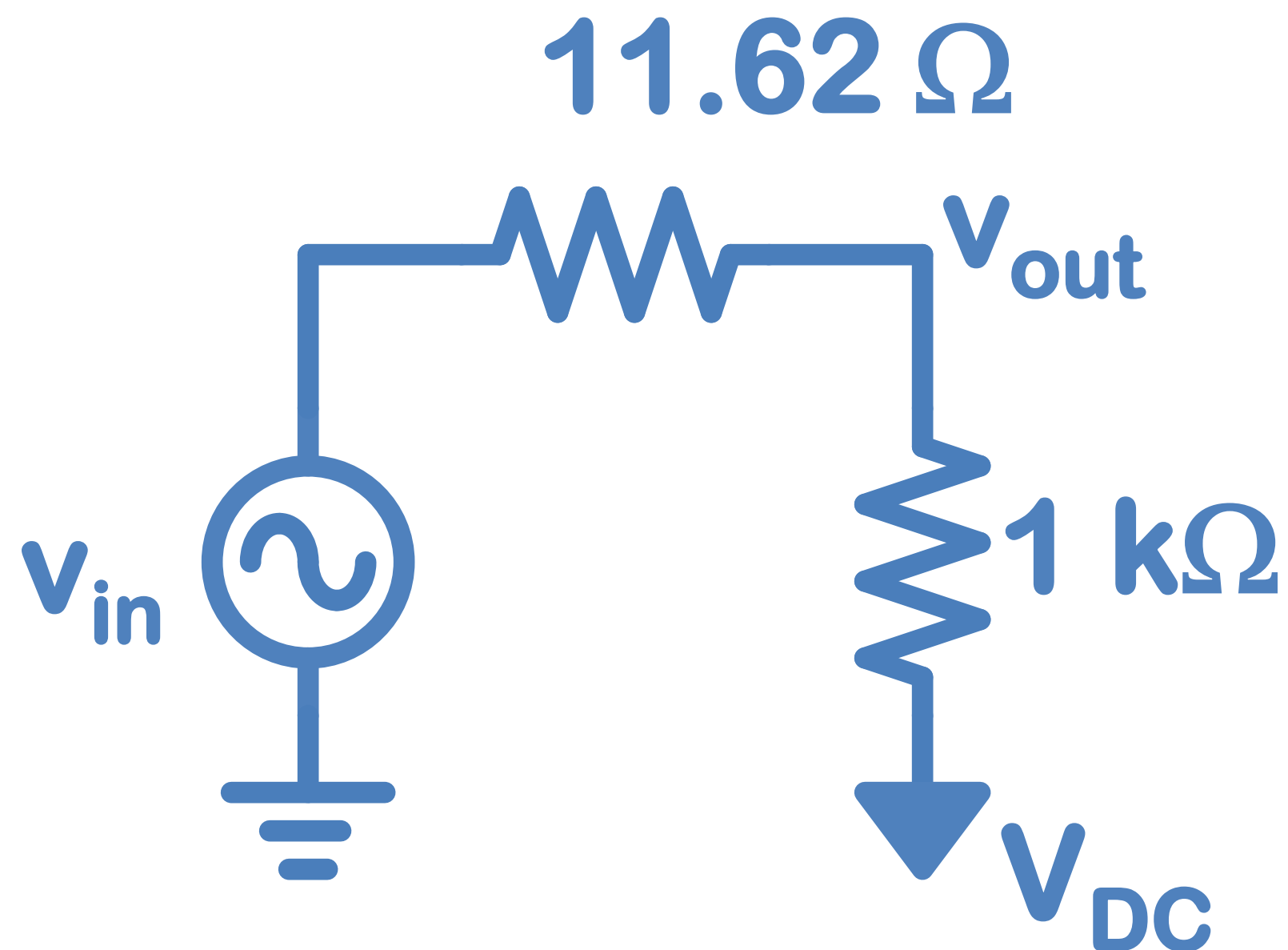Consider the circuit below to find the small signal relationship: v_{out}/v_{in}



Steps:

1. LARGE SIGNAL ANALYSIS

Use 0.7V CVD model to find I_D with $V_{DC} = -5\text{V}$.

Remember $v_{in} = 0$ for this part.

2. SMALL SIGNAL MODEL


Calculate the small signal resistance of the diode:

$$r_d = nV_T / I_D$$

and replace the diode with the small signal model, r_d .

$$r_d = 2 * 25\text{mV} / 4.3\text{mA} = 11.62\ \Omega$$

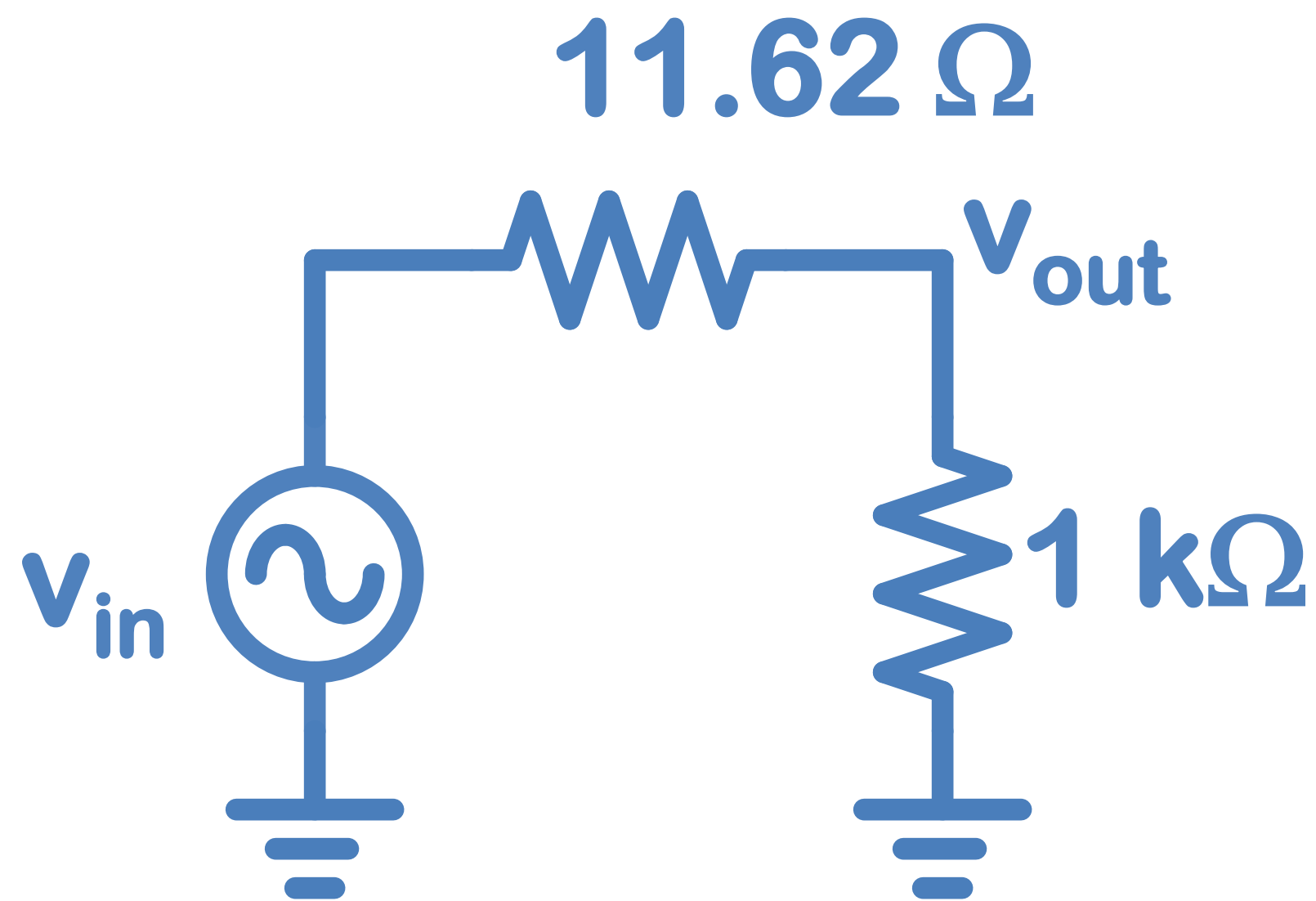Consider the circuit below to find the small signal relationship: v_{out}/v_{in}



$$v_{out}/v_{in} = 1000/1011.62$$

$$v_{out}/v_{in} = 0.99$$

Steps:

1. LARGE SIGNAL ANALYSIS

Use 0.7V CVD model to find I_D with $V_{DC} = -5V$.

Remember $v_{in} = 0$ for this part.

2. SMALL SIGNAL MODEL

Calculate the small signal resistance of the diode:

$$r_d = nV_T/I_D$$


and replace the diode with the small signal model, r_d .

3. SMALL SIGNAL ANALYSIS

Use the voltage divider eq. to find the relationship: v_{out}/v_{in}

Remember $V_{DC} = 0$ for this part.

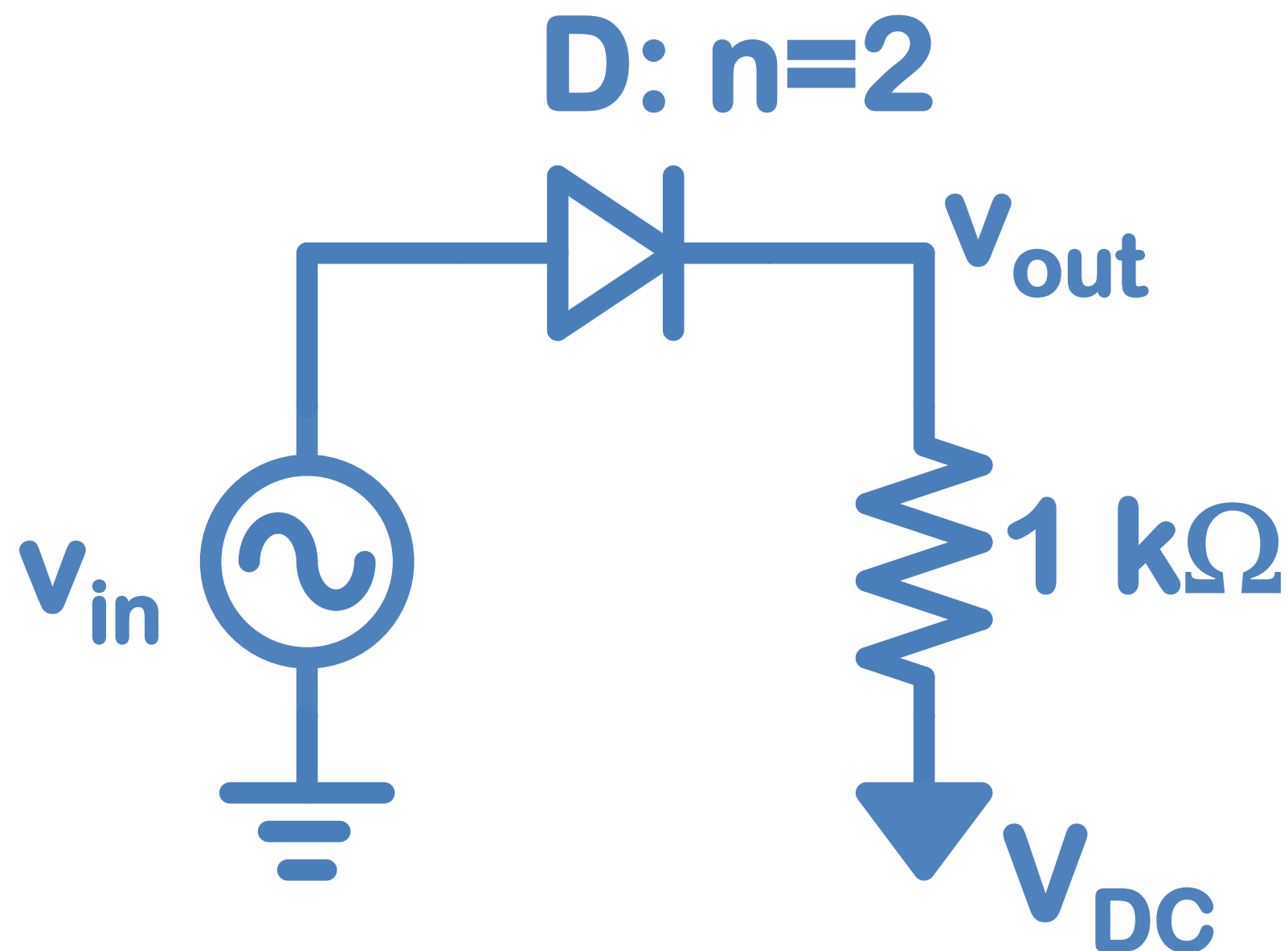Consider the circuit below to find the small signal relationship: v_{out}/v_{in}



How does v_{out}/v_{in} change for $V_{DC}=-0.8\text{V}$? or $V_{DC}=-.071$?

-0.8V: .1mA, 500Ω , .66

-0.71V: .01mA, $5\text{ k}\Omega$, .16

Steps:

1. LARGE SIGNAL ANALYSIS

Use 0.7V CVD model to find I_D with $V_{DC}=-5\text{V}$.

Remember $v_{in}=0$ for this part.

2. SMALL SIGNAL MODEL

Calculate the small signal resistance of the diode:

$$r_d = nV_T/I_D$$


and replace the diode with the small signal model, r_d .

3. SMALL SIGNAL ANALYSIS

Use the voltage divider eq. to find the relationship: v_{out}/v_{in}

Remember $V_{DC}=0$ for this part.

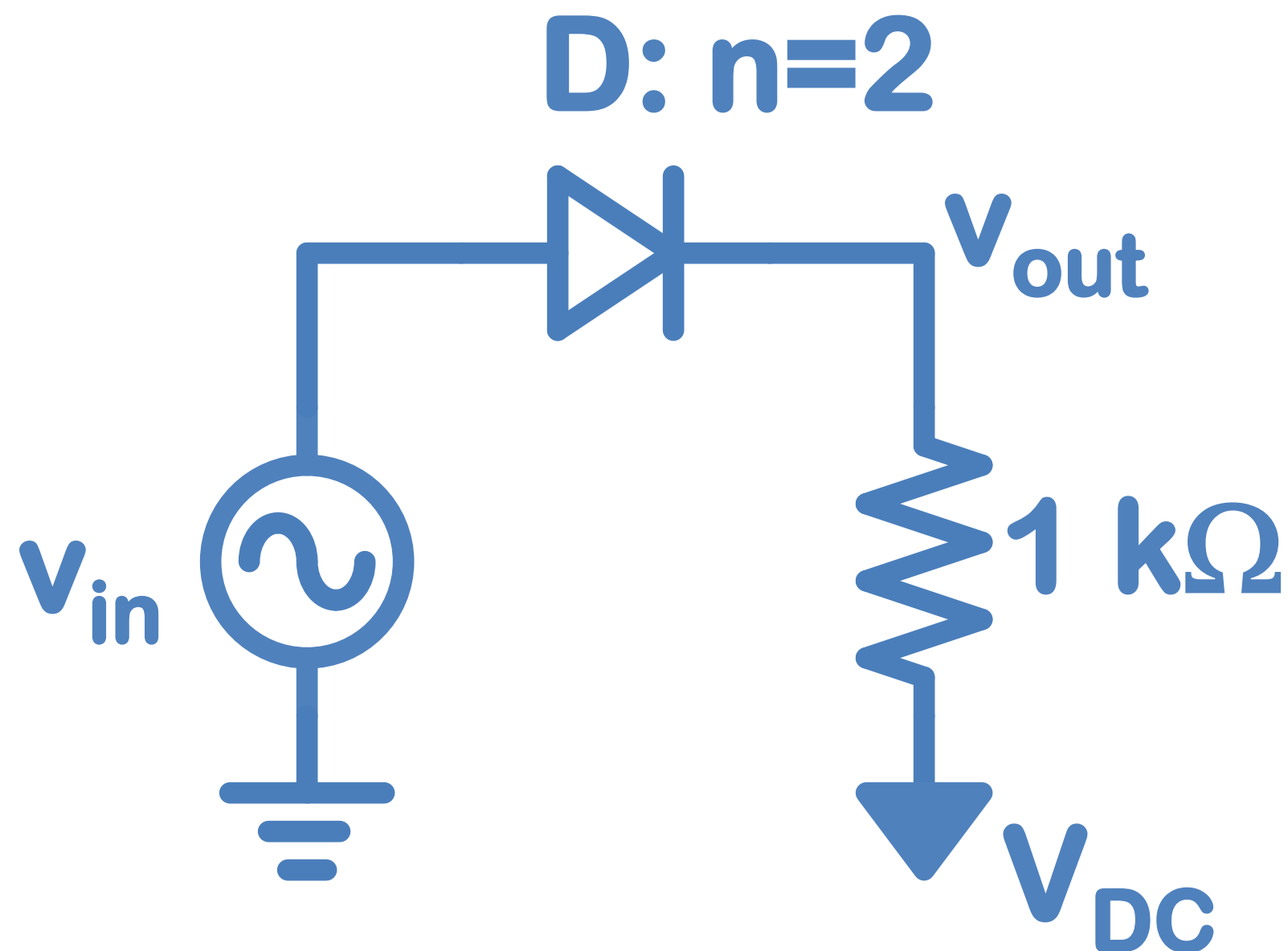Consider the circuit below to find the small signal relationship: v_{out}/v_{in}



How does v_{out}/v_{in} change for $V_{DC}=-0.8\text{V}$? or $V_{DC}=-.071$?

How is the small signal model related to the PWL model?
Iterative Technique?

Steps:

1. LARGE SIGNAL ANALYSIS

Use 0.7V CVD model to find I_D with $V_{DC}=-5\text{V}$.

Remember $v_{in}=0$ for this part.

2. SMALL SIGNAL MODEL

Calculate the small signal resistance of the diode:

$$r_d = nV_T/I_D$$


and replace the diode with the small signal model, r_d .

3. SMALL SIGNAL ANALYSIS

Use the voltage divider eq. to find the relationship: v_{out}/v_{in}

Remember $V_{DC}=0$ for this part.

Biasing the Diode

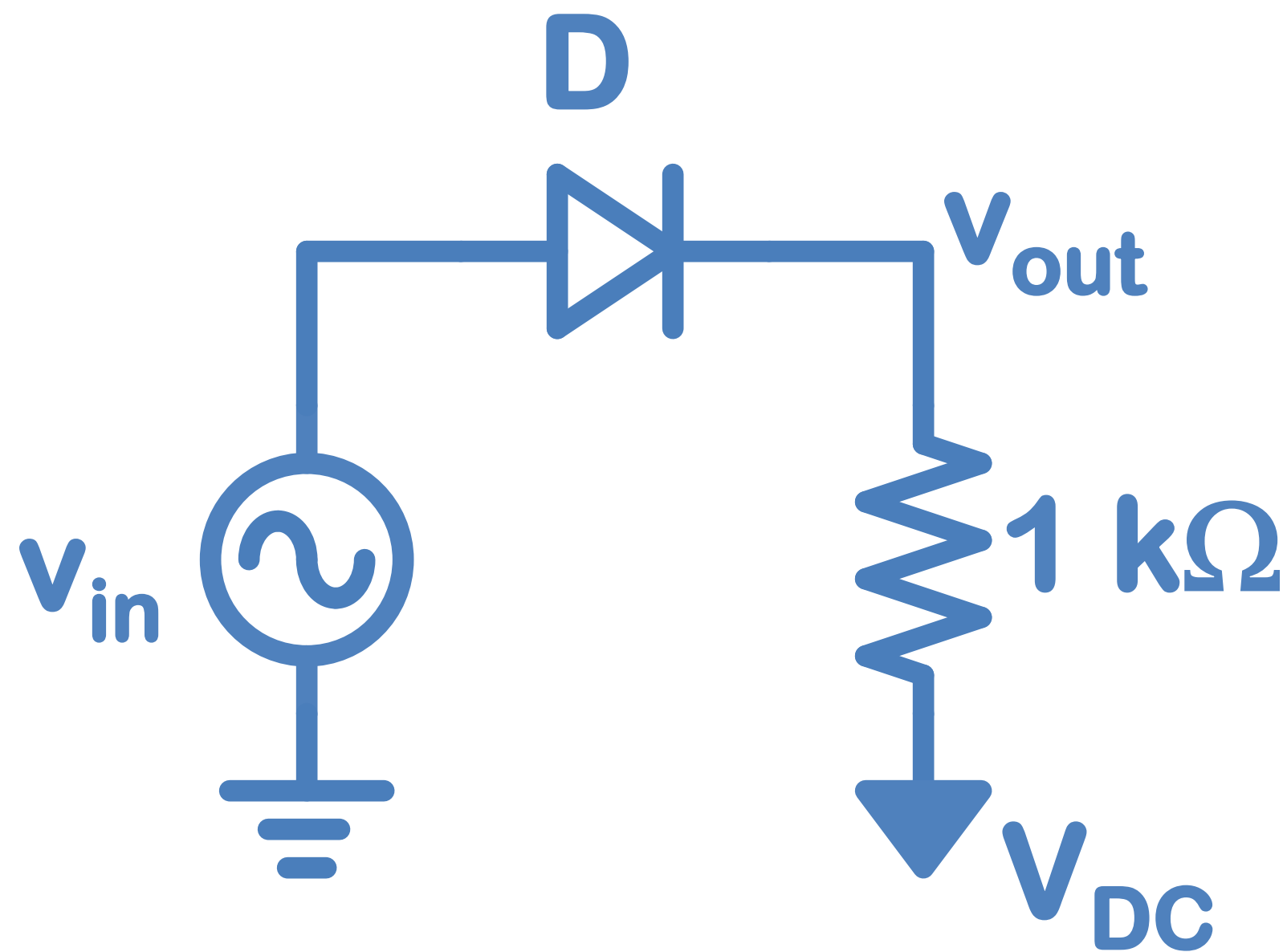

A large signal current is generated through the diode to set the small signal resistance.

- In this example, I_D is set by V_{DC} and the $1\text{ k}\Omega$ resistor.


What do we not like about this set-up?

- The small signal source and load are integrated with the large signal source and biasing resistor.

How can we fix this?


- Capacitors and Inductors

Consider this circuit with Capacitors

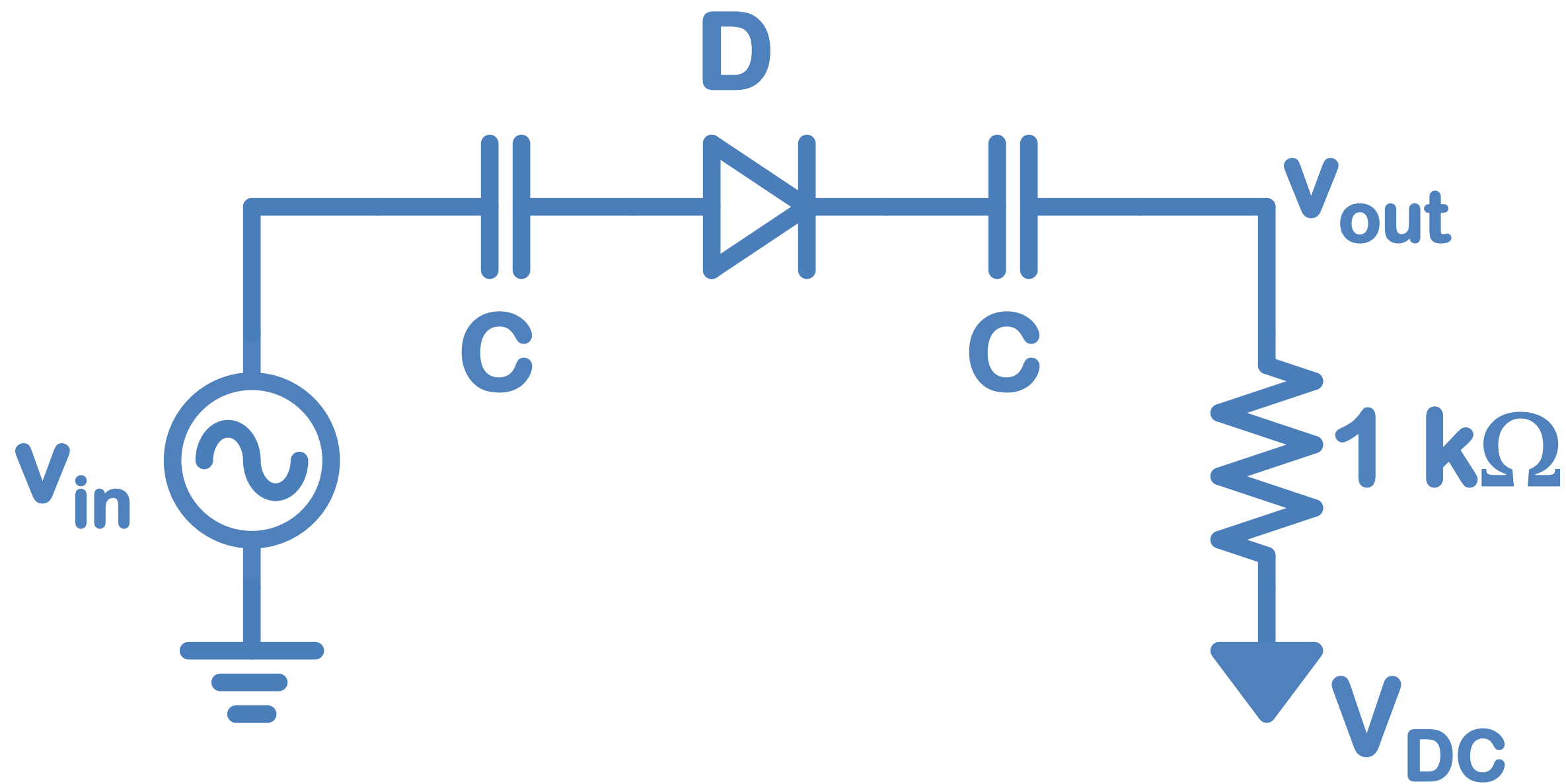

What do the capacitors do (C is Large)?
 $Z=1/(j\omega C)$:

Consider this circuit with Capacitors

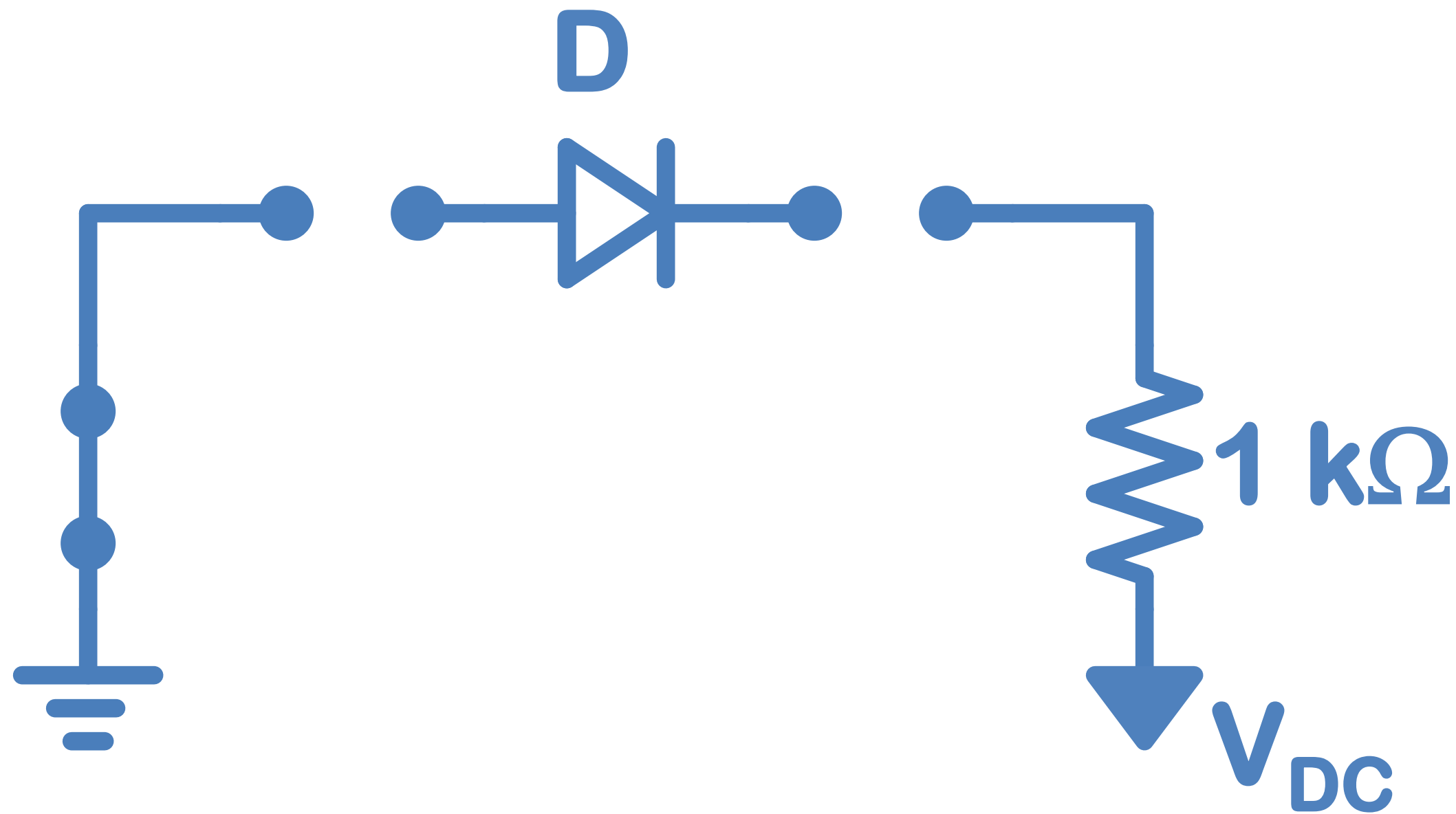


What do the capacitors do (C is Large)?

$Z=1/(j\omega C)$: For Large Signal Model at DC

$Z=\infty$ or an open

Consider this circuit with Capacitors

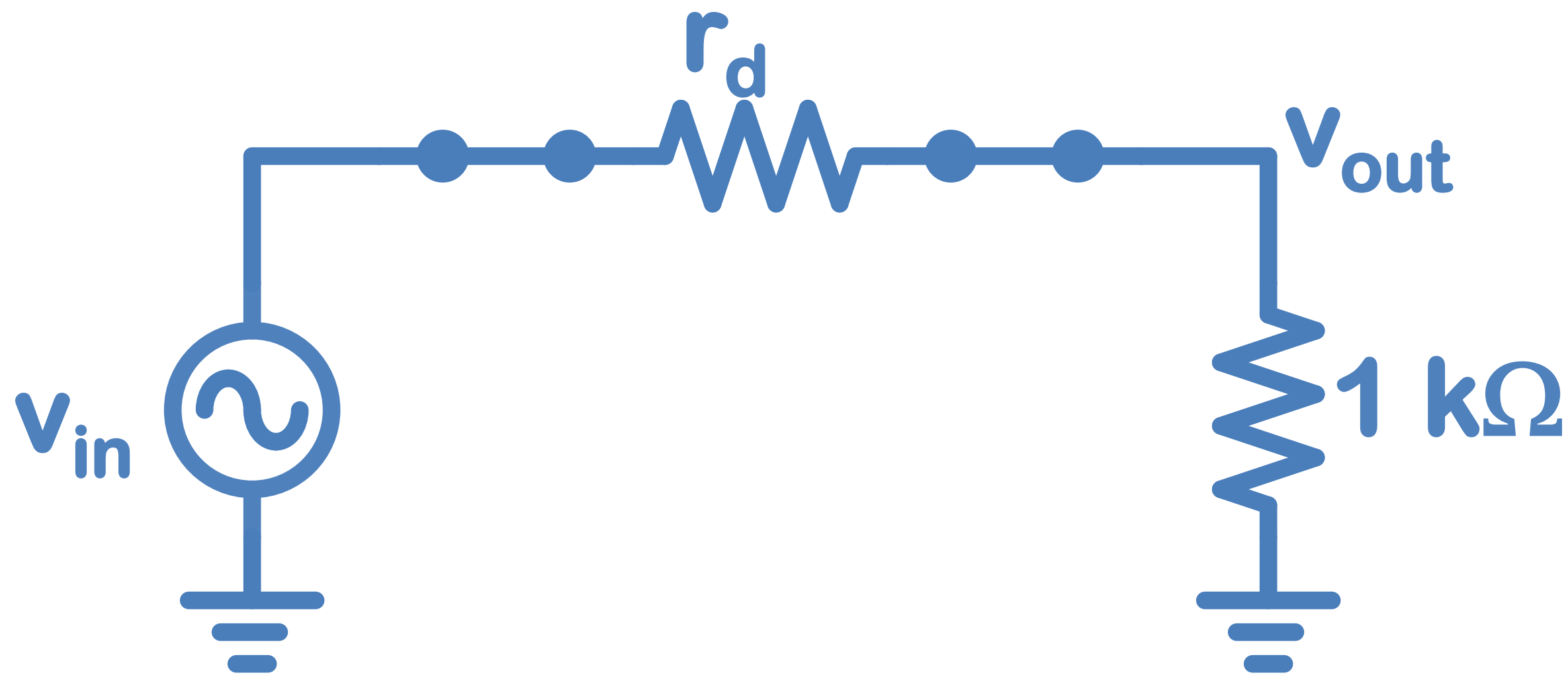

What do the capacitors do (C is Large)?


$Z=1/(j\omega C)$: For Large Signal Model at DC

$Z=\infty$ or an open

For Small Signal Model, Time Varying


$Z=0$ or a short

Consider this circuit with Inductors

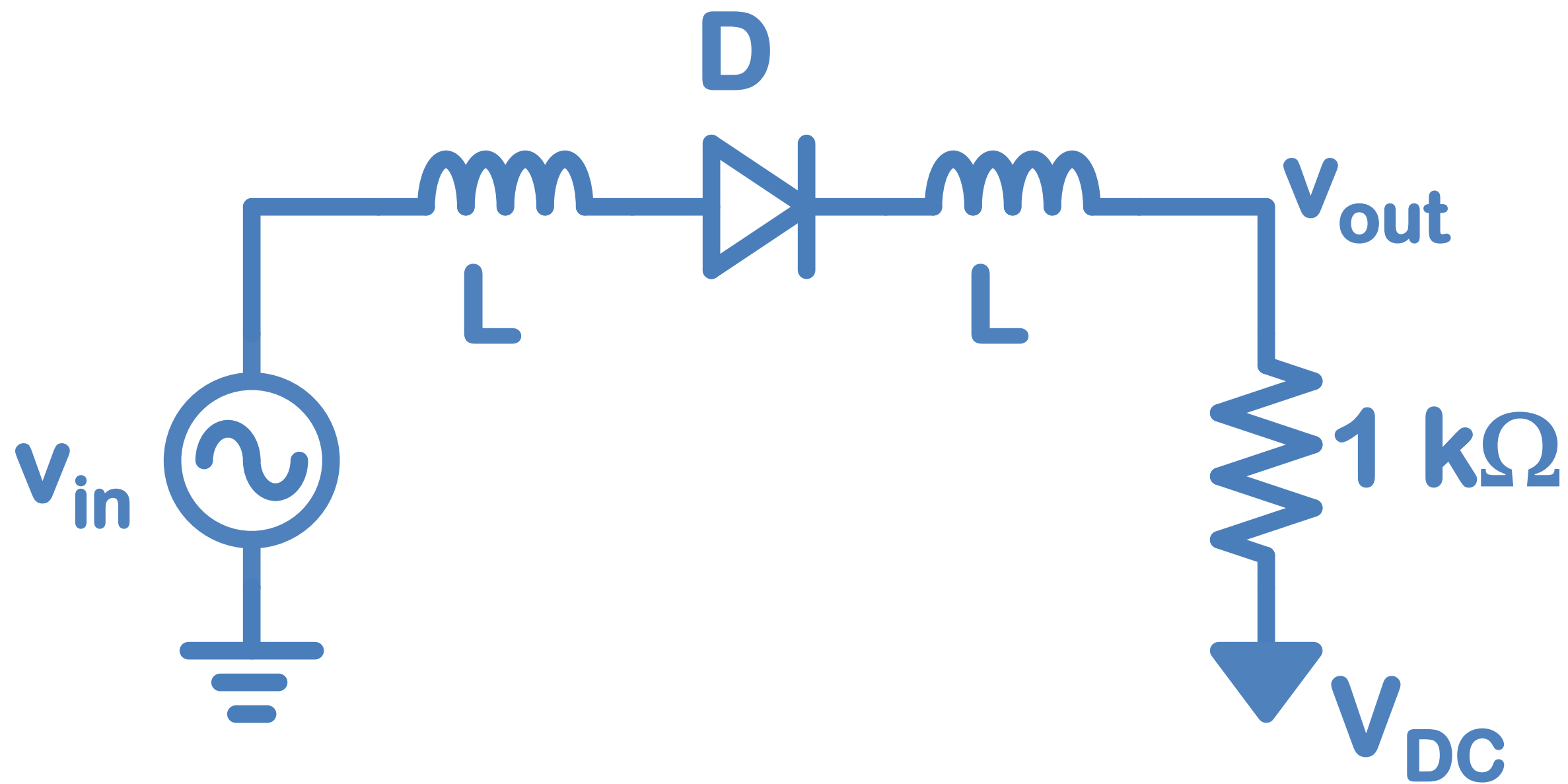

What do the inductors do (L is Large)?
 $Z=j\omega L$:

Consider this circuit with Inductors

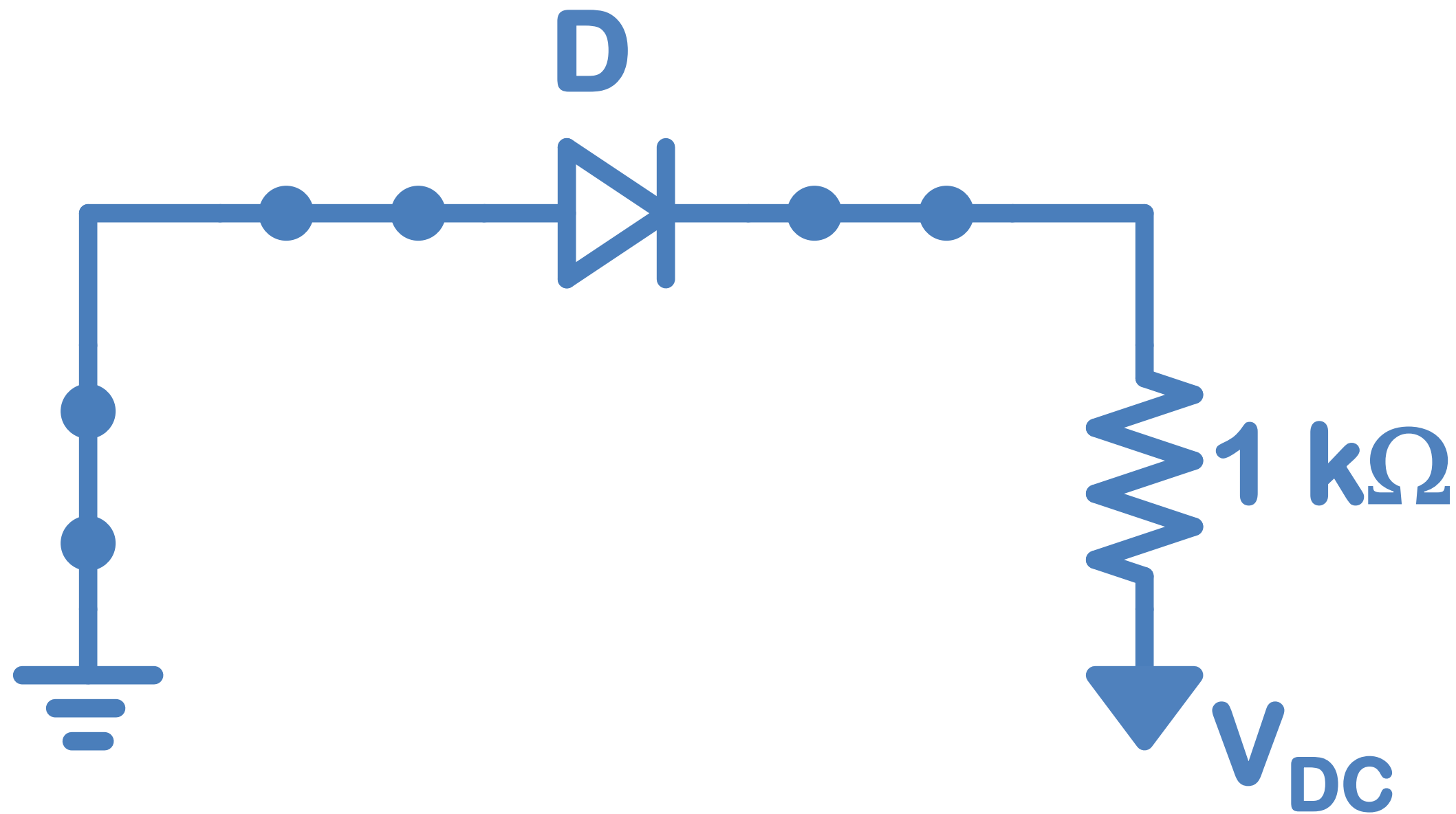


What do the inductors do (L is Large)?

$Z=j\omega L$:

For Large Signal Model at DC

$Z=0$ or a short

Consider this circuit with Inductors

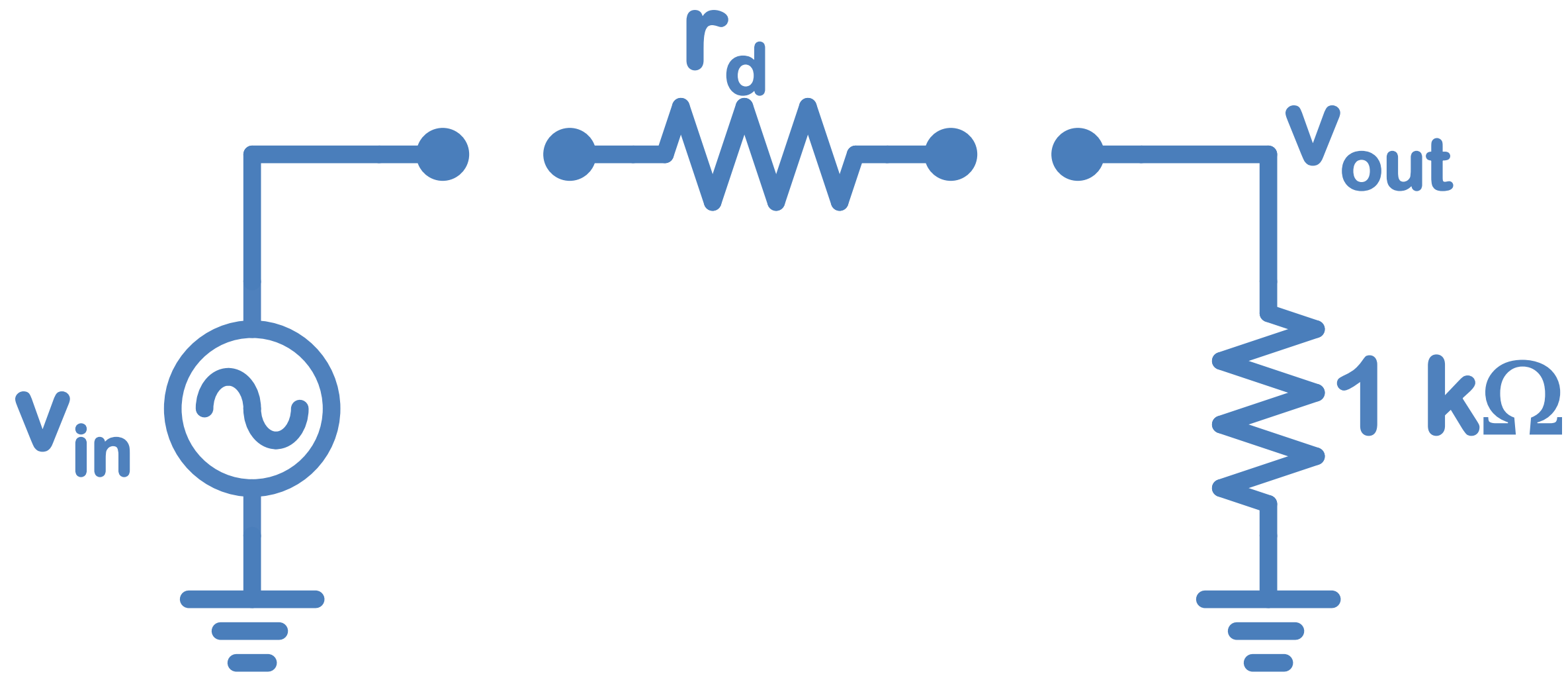

What do the inductors do (L is Large)?

$Z=j\omega L$:

For Large Signal Model at DC

$Z=0$ or a short

For Small Signal Model, Time Varying

$Z=\infty$ or an open

Capacitors and Inductors in Small Signal Analysis

Isolates or Connects sections of the circuit for exclusion or inclusion in small signal analysis or large signal analysis.


Capacitors: connects components for small signal analysis.

Inductors: connects components for large signal analysis.


Components in Large Signal and Small Signal Circuits.

Component	Large Signal Circuit Model	Small Signal Circuit Model
Large Signal Voltage (V_s)	V_s	Short
Small Signal Voltage (v_s)	Short	v_s
Large Signal Current (I_s)	I_s	Open
Small Signal Current (i_s)	Open	i_s
Resistor (R)	R	R
Capacitor (C)	Open	Short
Inductor (L)	Short	Open
Diode (D)	D	$r_d = nV_T / I_D$


Biased Circuit Small Signal Analysis.

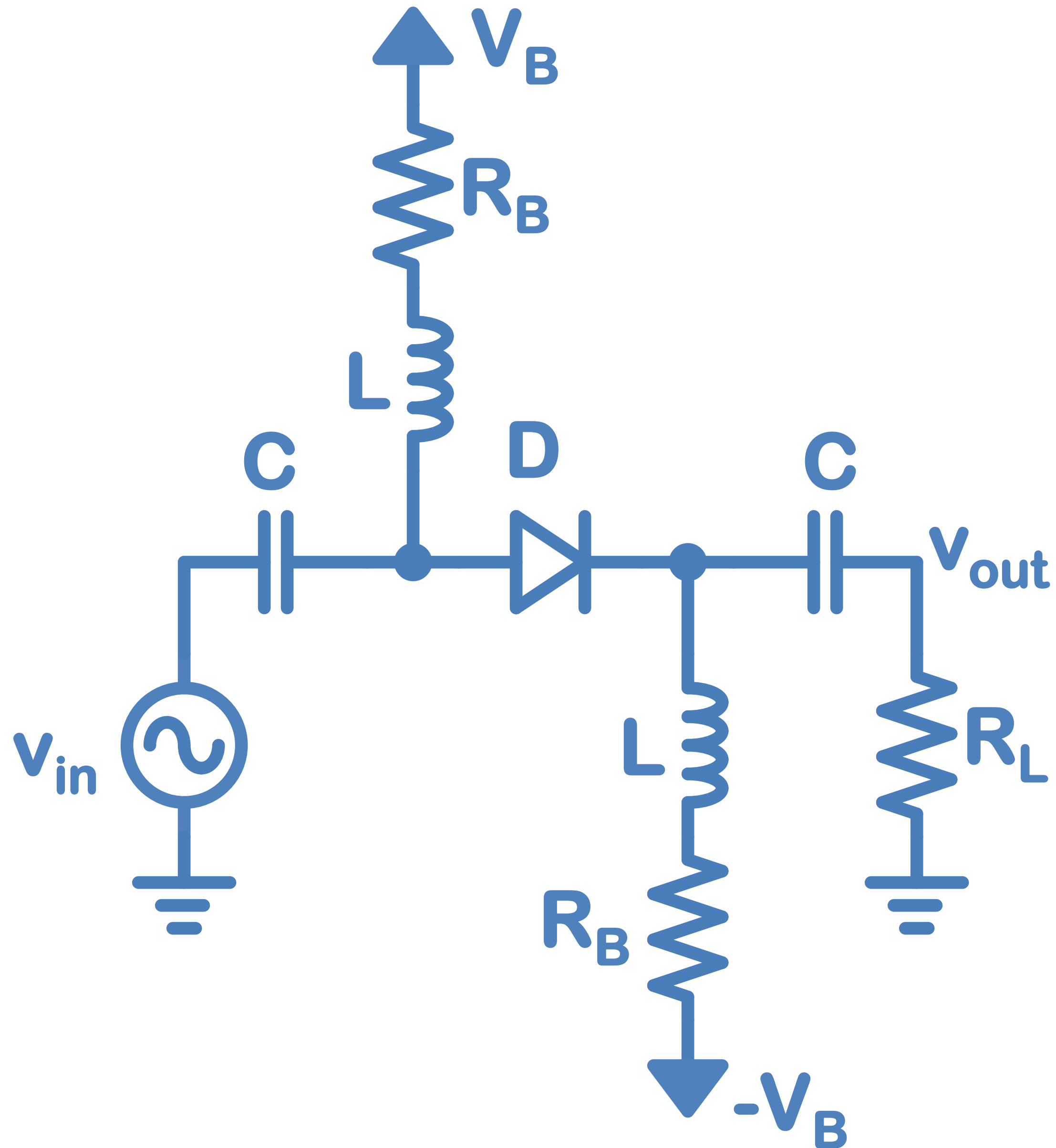

Large Signal Circuit.

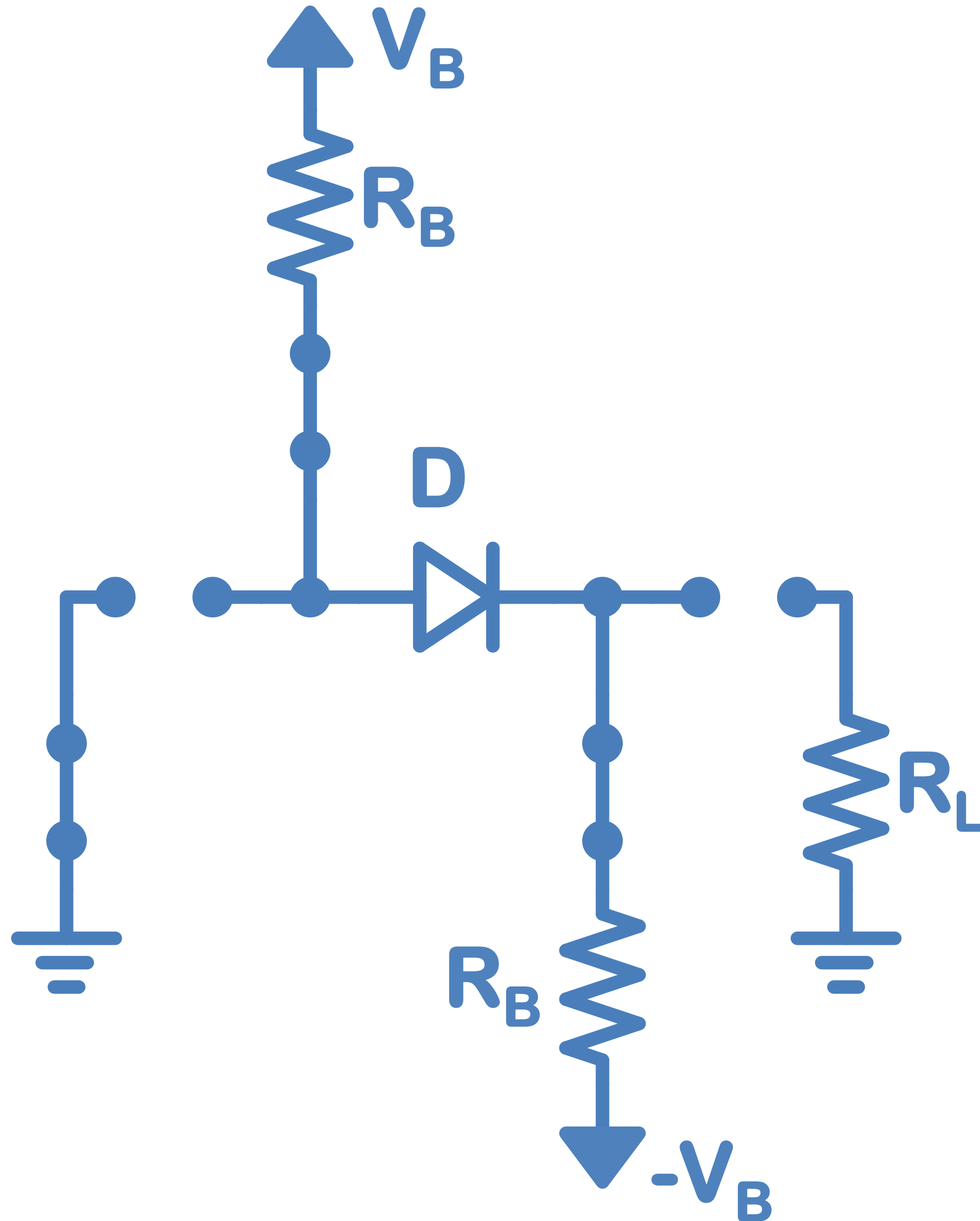

Large Signal Circuit Analysis.

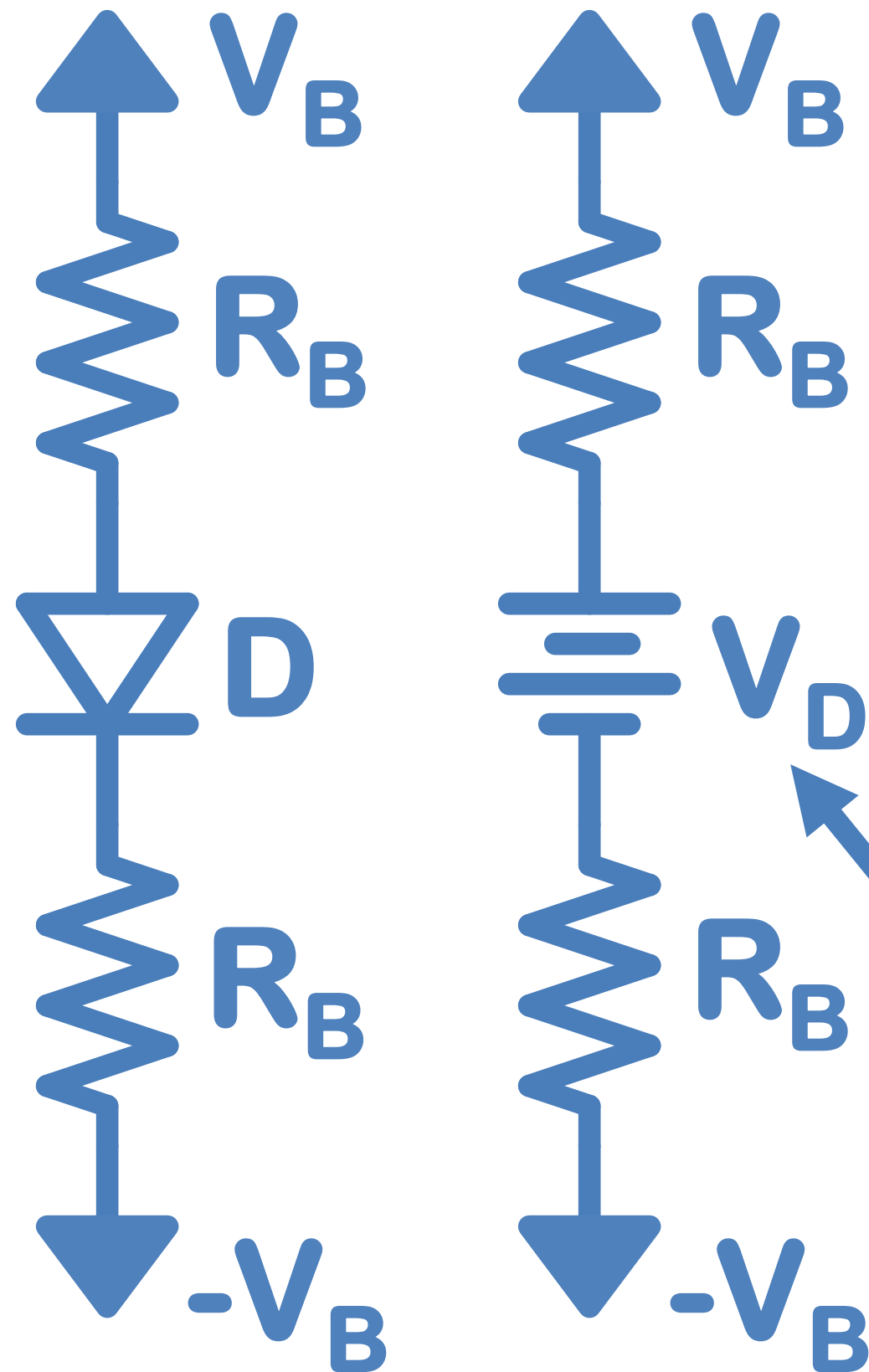

Find I_D :

$$I_D = (2V_B - V_D) / (2R_B)$$


Calculate r_d :

$$r_d = nV_T / I_D$$

$$r_d = (2nR_B V_T) / (2V_B - V_D)$$

Why do we start with a voltage for D rather than a current?


Large Signal Circuit Analysis.

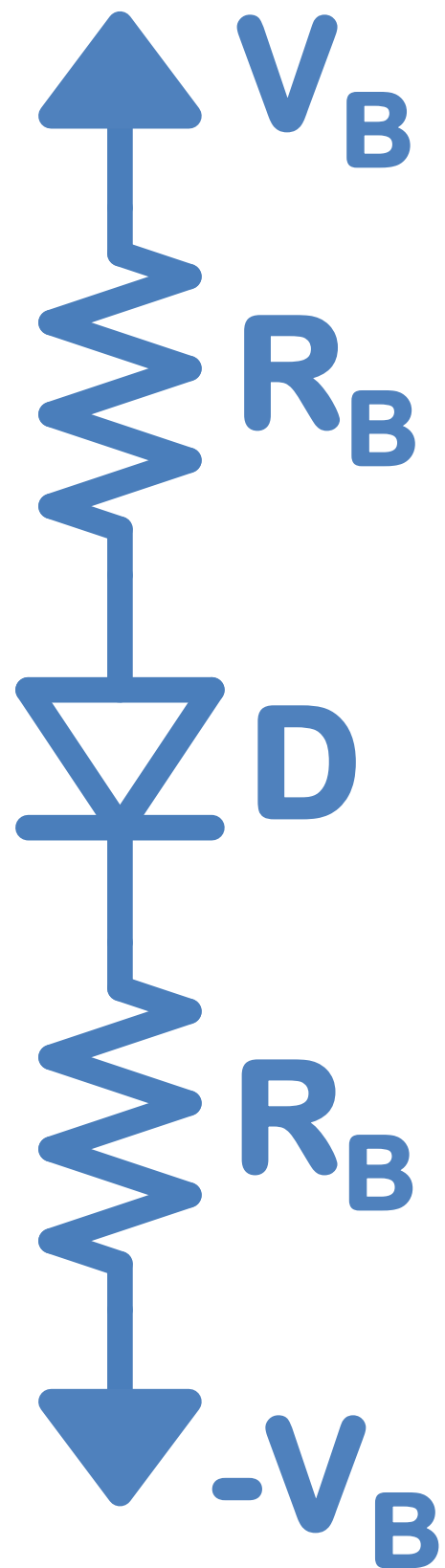

$$I_D = (2V_B - V_D) / (2R_B)$$


$$V_D = 2V_B - 2R_B I_D$$

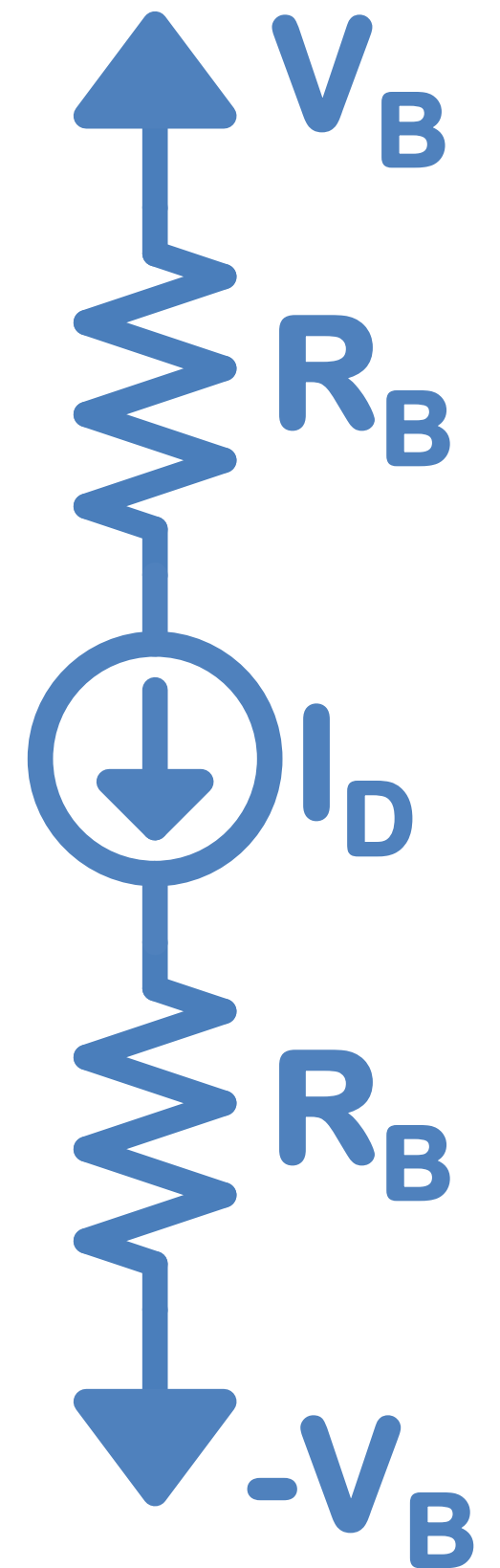For a typical junction diode, I_D can span several orders of magnitude (0.1mA to 100mA) for small changes (deltas) in V_D (+/-100mV) around 0.7V.



Large Signal Circuit Analysis.


Calculating I_D from a guess of V_D .

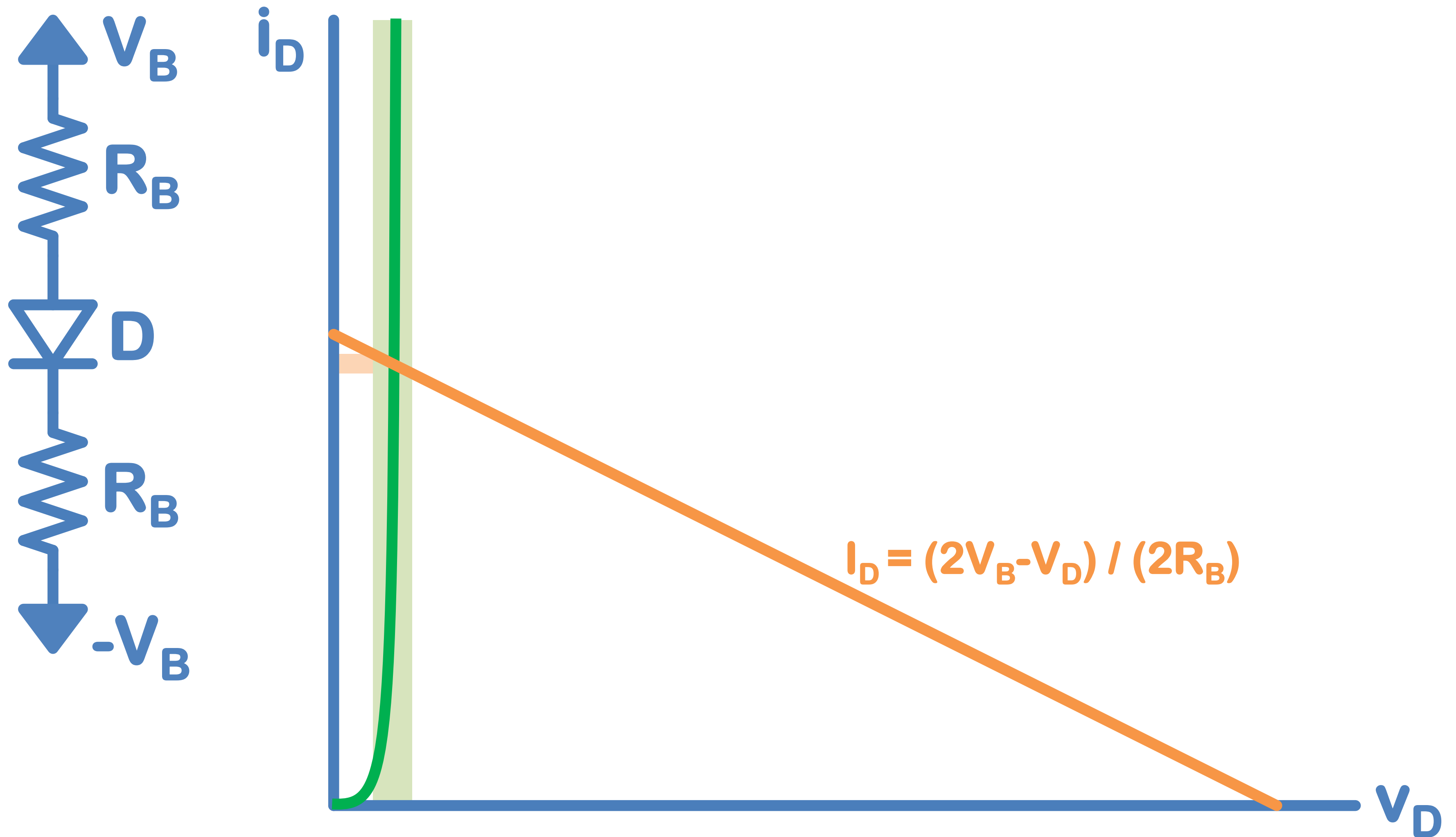


Large Signal Circuit Analysis.

Calculating V_D from a guess of I_D .

could yield results that are not usable

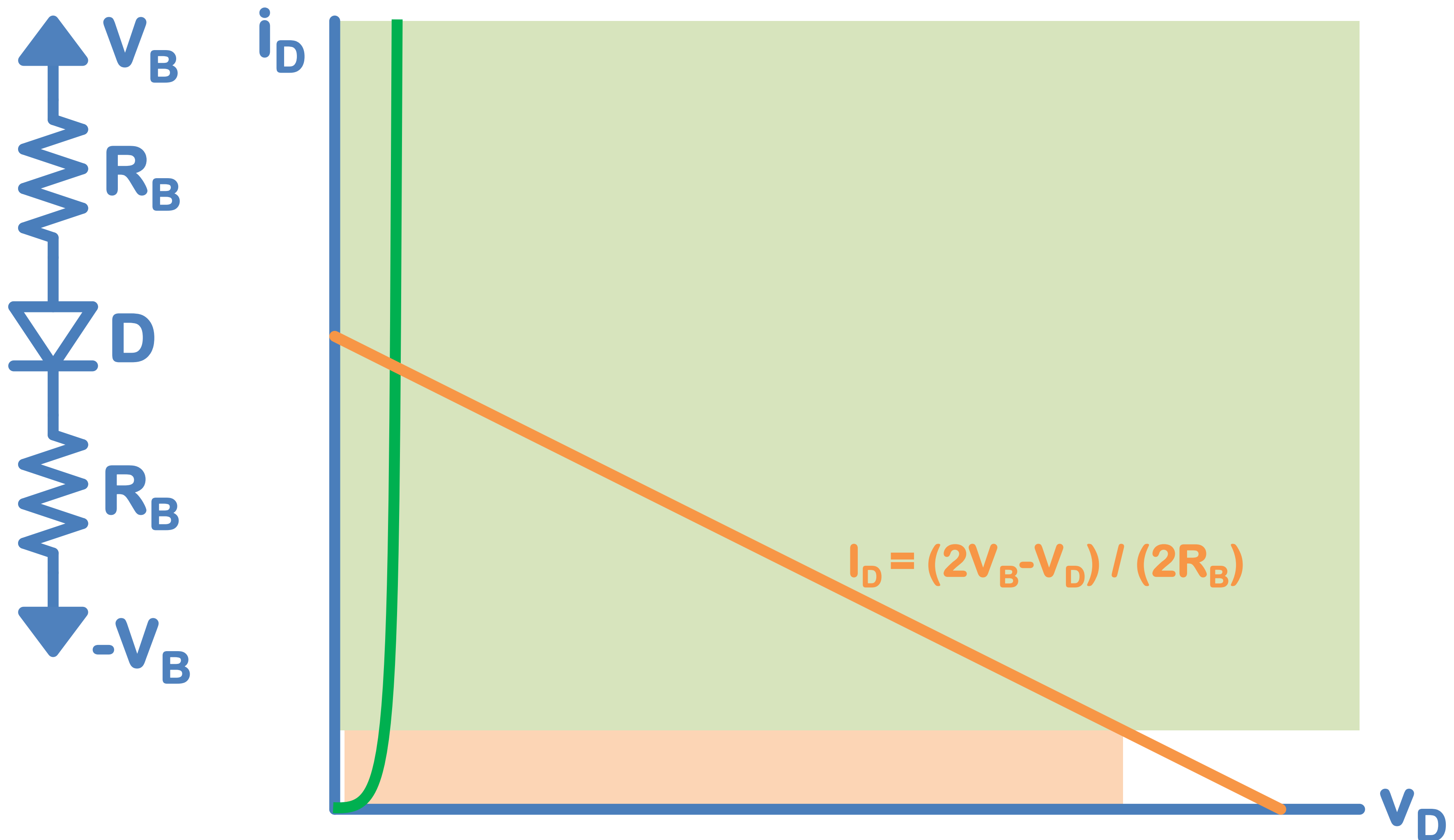

Small Signal Circuit.

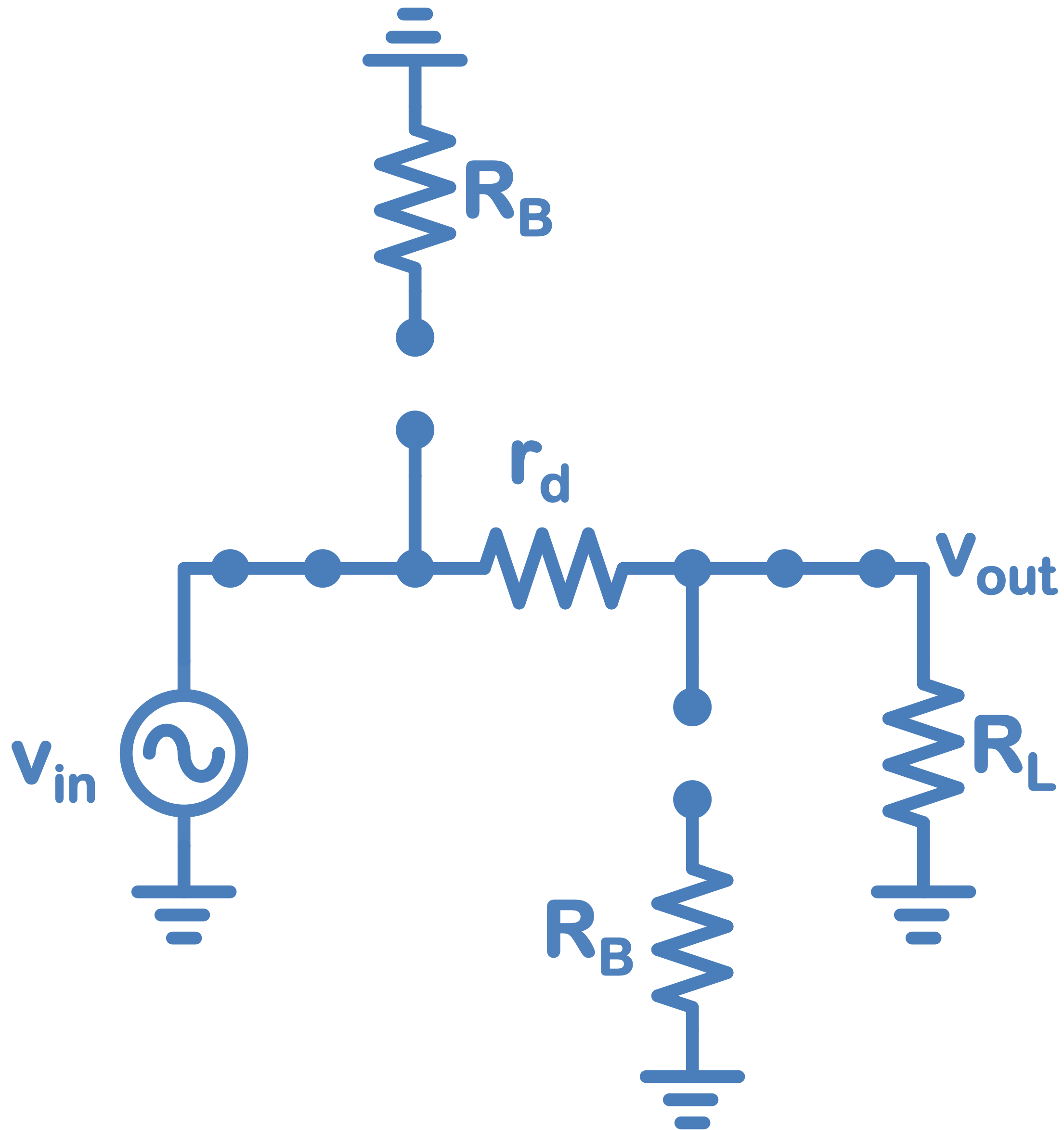

Small Signal Circuit and Analysis.

Calculate v_{out}/v_{in} :

$$v_{out}/v_{in} = R_L / (R_L + r_d)$$

where

$$r_d = (2nR_B V_T) / (2V_B - V_D)$$

