 


# Combinational Logic Design




## Two Complementary Networks

### Pull Up Network (PUN):

- **Conducting** (ties the output Y high) when the Function (F) result in logic True (1).
- **Open** when the Function (F) result in logic False (0).
- **Constructed with PMOS devices.**
- **PMOS are conducting** when the input (gate voltage) is Low or False (0).
- **Prefer the Function (F) to be expressed as:**

$$Y = F_{\text{PUN}}(\overline{A}, \overline{B}, \dots)$$

# Combinational Logic Design

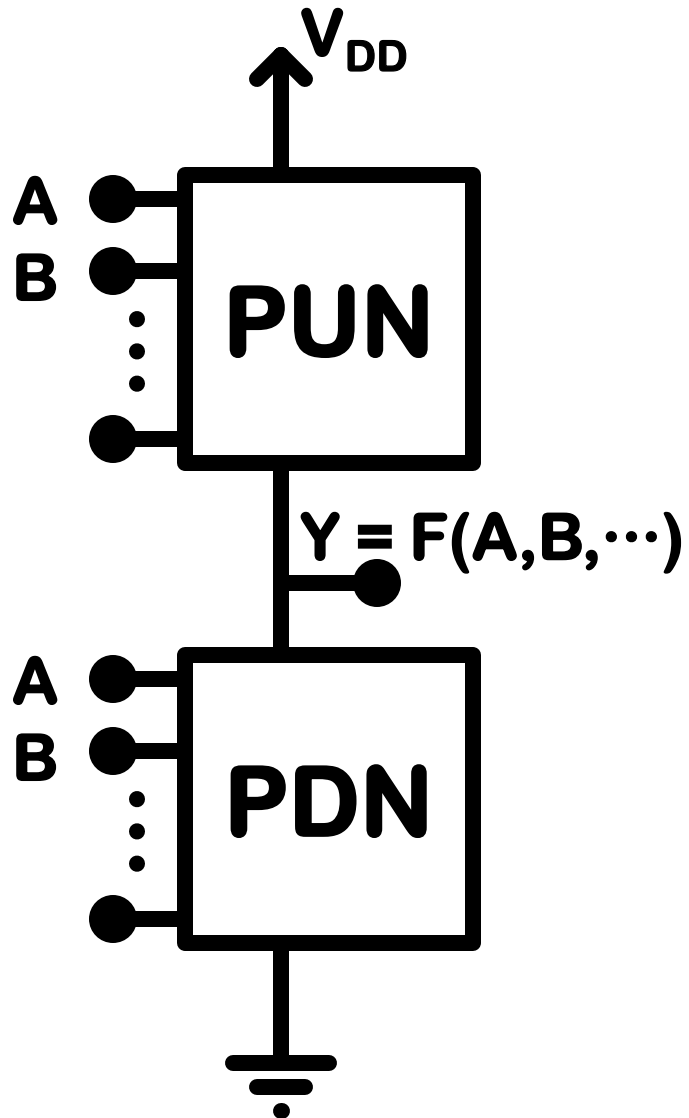


## Two Complementary Networks

### Pull Down Network (PDN):

- Conducting (ties the output Y low) when the Function (F) result in logic False (0).
- Open when the Function (F) result in logic True (1).
- Constructed with NMOS devices.
- NMOS are conducting when the input (gate voltage) is High or True (1).
- Prefer the Function (F) to be expressed as:

$$Y = \overline{F_{PDN}(A, B, \dots)}$$

# Combinational Logic Design

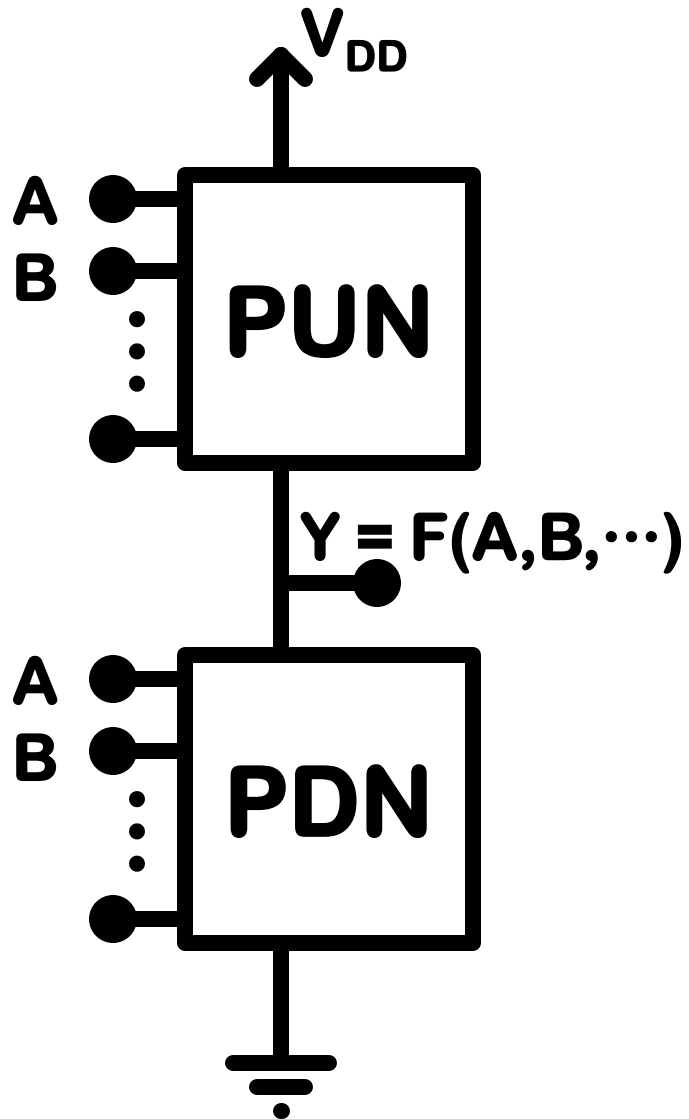


## Two Complementary Networks

### Other Notes:

- Networks must be complementary:  
When PUN is conducting, PDN is open.  
When PDN is conducting, PUN is open.
- Both open would leave  $Y$  floating.
- Both conducting would dissipate more power and leave  $Y$  in transition region.
- $\overline{F_{PDN}(A, B, \dots)} = F_{PUN}(\overline{A}, \overline{B}, \dots) = F(A, B, \dots)$

# Combinational Logic Design

 


## Two Complementary Networks

### CMOS Inverter:


- Networks must be complementary:  
When PUN is conducting, PDN is open.  
When PDN is conducting, PUN is open.
- Both open would leave  $Y$  floating.
- Both conducting would dissipate more power and leave  $Y$  in transition region.
 
# Combinational Logic Design: Parallel PMOS PUN




<u>A</u>	<u>B</u>	<u><math>r_{SDA}</math></u>	<u><math>r_{SDB}</math></u>	<u><math>r_{PUN}</math></u>	<u><math>r_{PDN}</math></u>	<u>Y</u>
0	0					
0	1					
1	0					
1	1					
 
# Combinational Logic Design: Parallel PMOS PUN



<u>A</u>	<u>B</u>	<u><math>r_{SDA}</math></u>	<u><math>r_{SDB}</math></u>	<u><math>r_{PUN}</math></u>	<u><math>r_{PDN}</math></u>	<u>Y</u>
0	0	$r_{SD}$	$r_{SD}$	$r_{SD}/2$	O.C.	1
0	1	$r_{SD}$	O.C.	$r_{SD}$	O.C.	1
1	0	O.C.	$r_{SD}$	$r_{SD}$	O.C.	1
1	1	O.C.	O.C.	O.C.	$r_{PDN}$	0
 
# Combinational Logic Design: Parallel PMOS PUN



<u>A</u>	<u>B</u>	<u><math>r_{SDA}</math></u>	<u><math>r_{SDB}</math></u>	<u><math>r_{PUN}</math></u>	<u><math>r_{PDN}</math></u>	<u>Y</u>
0	0	$r_{SD}$	$r_{SD}$	$r_{SD}/2$	O.C.	1
0	1	$r_{SD}$	O.C.	$r_{SD}$	O.C.	1
1	0	O.C.	$r_{SD}$	$r_{SD}$	O.C.	1
1	1	O.C.	O.C.	O.C.	$r_{PDN}$	0


This is a NAND Gate

$$Y = \overline{A \cdot B}$$

But we like to use


$$Y = \overline{A} + \overline{B}$$
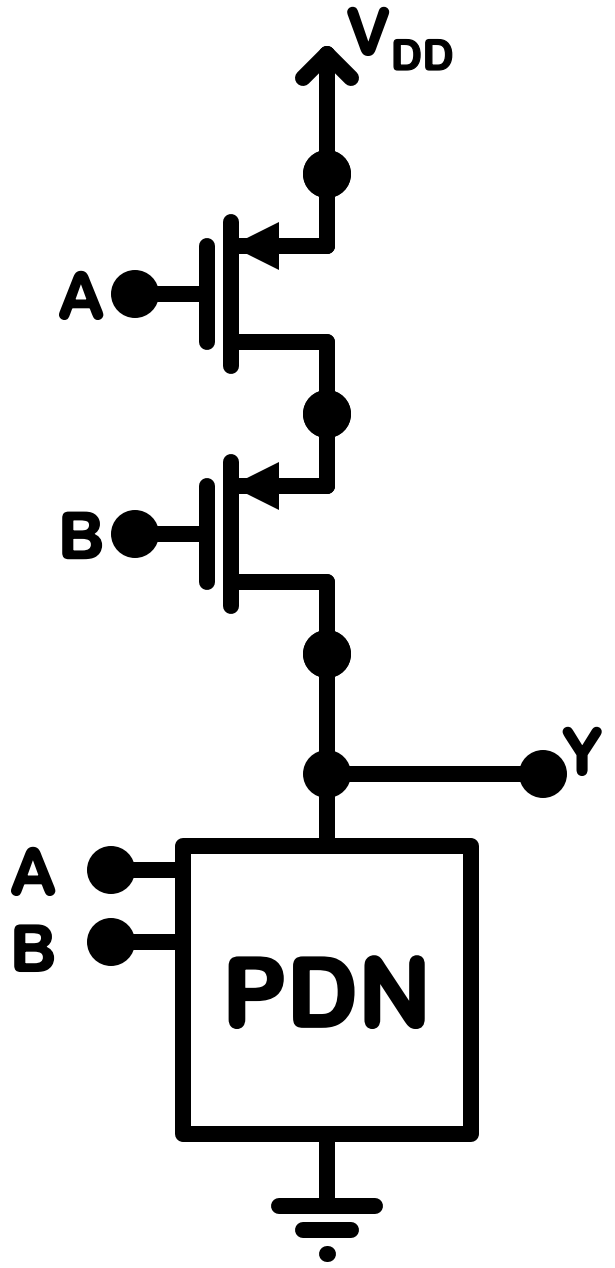
# Combinational Logic Design: Series PMOS PUN




<u>A</u>	<u>B</u>	<u><math>r_{SDA}</math></u>	<u><math>r_{SDB}</math></u>	<u><math>r_{PUN}</math></u>	<u><math>r_{PDN}</math></u>	<u>Y</u>
0	0					
0	1					
1	0					
1	1					
 
# Combinational Logic Design: Series PMOS PUN



<u>A</u>	<u>B</u>	<u><math>r_{SDA}</math></u>	<u><math>r_{SDB}</math></u>	<u><math>r_{PUN}</math></u>	<u><math>r_{PDN}</math></u>	<u>Y</u>
0	0	$r_{SD}$	$r_{SD}$	$2r_{SD}$	<b>O.C.</b>	<b>1</b>
0	1	$r_{SD}$	<b>O.C.</b>	<b>O.C.</b>	$r_{PDN}$	<b>0</b>
1	0	<b>O.C.</b>	$r_{SD}$	<b>O.C.</b>	$r_{PDN}$	<b>0</b>
1	1	<b>O.C.</b>	<b>O.C.</b>	<b>O.C.</b>	$r_{PDN}$	<b>0</b>
 
# Combinational Logic Design: Series PMOS PUN



<u>A</u>	<u>B</u>	<u><math>r_{SDA}</math></u>	<u><math>r_{SDB}</math></u>	<u><math>r_{PUN}</math></u>	<u><math>r_{PDN}</math></u>	<u>Y</u>
0	0	$r_{SD}$	$r_{SD}$	$2r_{SD}$	O.C.	1
0	1	$r_{SD}$	O.C.	O.C.	$r_{PDN}$	0
1	0	O.C.	$r_{SD}$	O.C.	$r_{PDN}$	0
1	1	O.C.	O.C.	O.C.	$r_{PDN}$	0


This is a NOR Gate

$$Y = \overline{A + B}$$

But we like to use


$$Y = \overline{A} \cdot \overline{B}$$
 
# Combinational Logic Design: Parallel NMOS PDN




<u>A</u>	<u>B</u>	<u><math>r_{DSA}</math></u>	<u><math>r_{DSB}</math></u>	<u><math>r_{PDN}</math></u>	<u><math>r_{PUN}</math></u>	<u>Y</u>
0	0					
0	1					
1	0					
1	1					
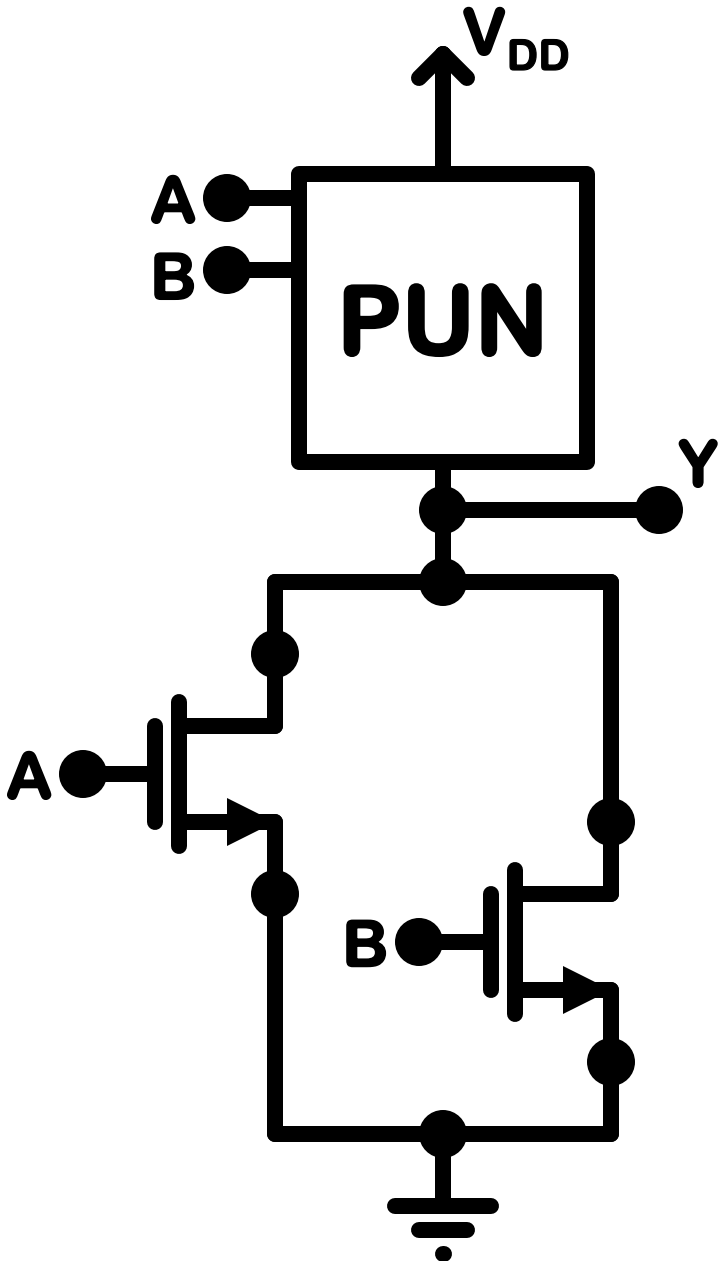
# Combinational Logic Design: Parallel NMOS PDN



<u>A</u>	<u>B</u>	<u><math>r_{DSA}</math></u>	<u><math>r_{DSB}</math></u>	<u><math>r_{PDN}</math></u>	<u><math>r_{PUN}</math></u>	<u>Y</u>
0	0	o.c.	o.c.	o.c.	$r_{PUN}$	1
0	1	o.c.	$r_{DS}$	$r_{DS}$	o.c.	0
1	0	$r_{DS}$	o.c.	$r_{DS}$	o.c.	0
1	1	$r_{DS}$	$r_{DS}$	$r_{DS}/2$	o.c.	0
 
# Combinational Logic Design: Parallel NMOS PDN



<u>A</u>	<u>B</u>	<u><math>r_{DSA}</math></u>	<u><math>r_{DSB}</math></u>	<u><math>r_{PDN}</math></u>	<u><math>r_{PUN}</math></u>	<u>Y</u>
0	0	o.c.	o.c.	o.c.	$r_{PUN}$	1
0	1	o.c.	$r_{DS}$	$r_{DS}$	o.c.	0
1	0	$r_{DS}$	o.c.	$r_{DS}$	o.c.	0
1	1	$r_{DS}$	$r_{DS}$	$r_{DS}/2$	o.c.	0


This is a NOR Gate

$$Y = \overline{A + B}$$

But we like to use


$$\overline{Y} = A + B$$
 
# Combinational Logic Design: Series NMOS PDN




<u>A</u>	<u>B</u>	<u><math>r_{DSA}</math></u>	<u><math>r_{DSB}</math></u>	<u><math>r_{PDN}</math></u>	<u><math>r_{PUN}</math></u>	<u>Y</u>
0	0					
0	1					
1	0					
1	1					
 
# Combinational Logic Design: Series NMOS PDN



<u>A</u>	<u>B</u>	<u><math>r_{DSA}</math></u>	<u><math>r_{DSB}</math></u>	<u><math>r_{PDN}</math></u>	<u><math>r_{PUN}</math></u>	<u>Y</u>
0	0	O.C.	O.C.	O.C.	$r_{PUN}$	1
0	1	O.C.	$r_{DS}$	O.C.	$r_{PUN}$	1
1	0	$r_{DS}$	O.C.	O.C.	$r_{PUN}$	1
1	1	$r_{DS}$	$r_{DS}$	$2r_{DS}$	O.C.	0
 
# Combinational Logic Design: Series NMOS PDN



<u>A</u>	<u>B</u>	<u><math>r_{DSA}</math></u>	<u><math>r_{DSB}</math></u>	<u><math>r_{PDN}</math></u>	<u><math>r_{PUN}</math></u>	<u>Y</u>
0	0	o.c.	o.c.	o.c.	$r_{PUN}$	1
0	1	o.c.	$r_{DS}$	o.c.	$r_{PUN}$	1
1	0	$r_{DS}$	o.c.	o.c.	$r_{PUN}$	1
1	1	$r_{DS}$	$r_{DS}$	$2r_{DS}$	o.c.	0

This is a NAND Gate


$$Y = \overline{A \cdot B}$$

But we like to use

$$\overline{Y} = A \cdot B$$


# NAND

$$Y = \overline{A \cdot B}$$

 


# NOR

$$Y = \overline{A + B}$$

 


# NAND

$$Y = \overline{A \cdot B}$$

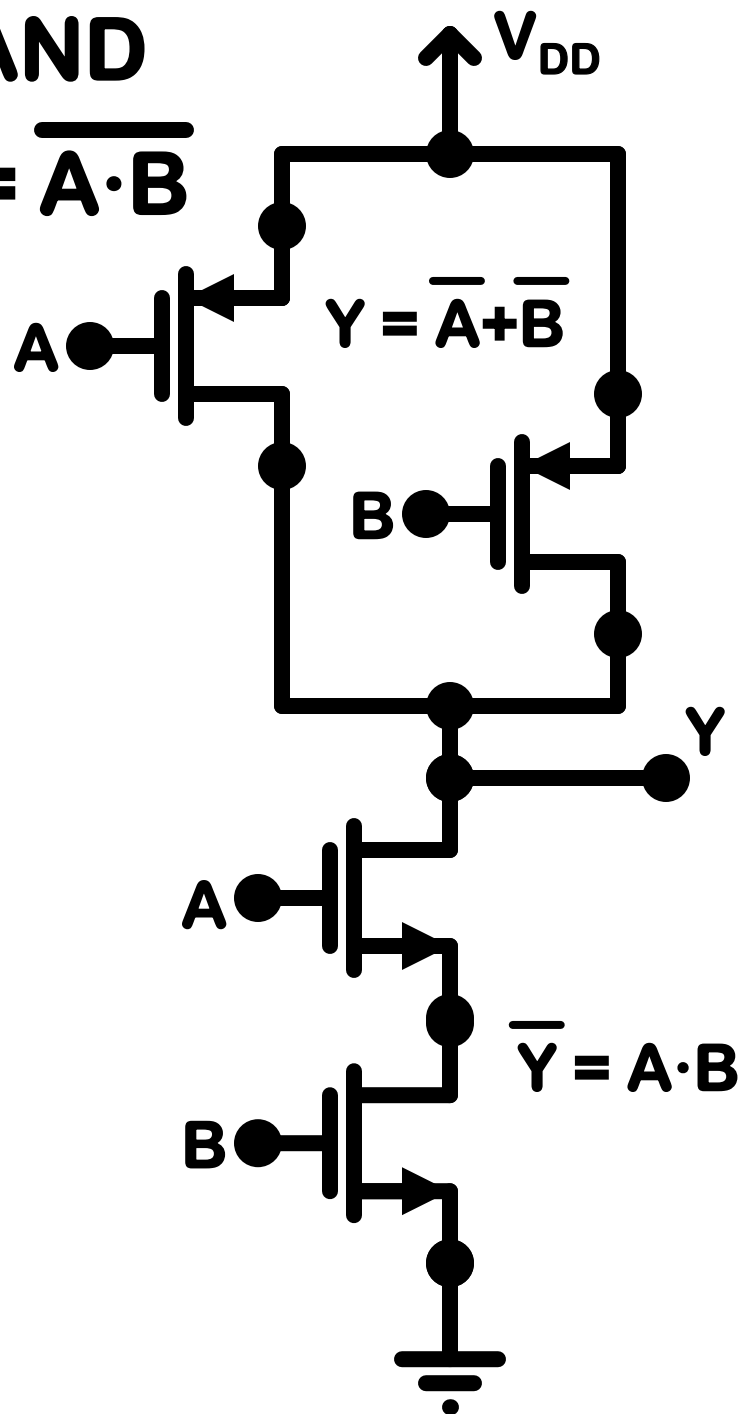


# NOR

$$Y = \overline{A + B}$$

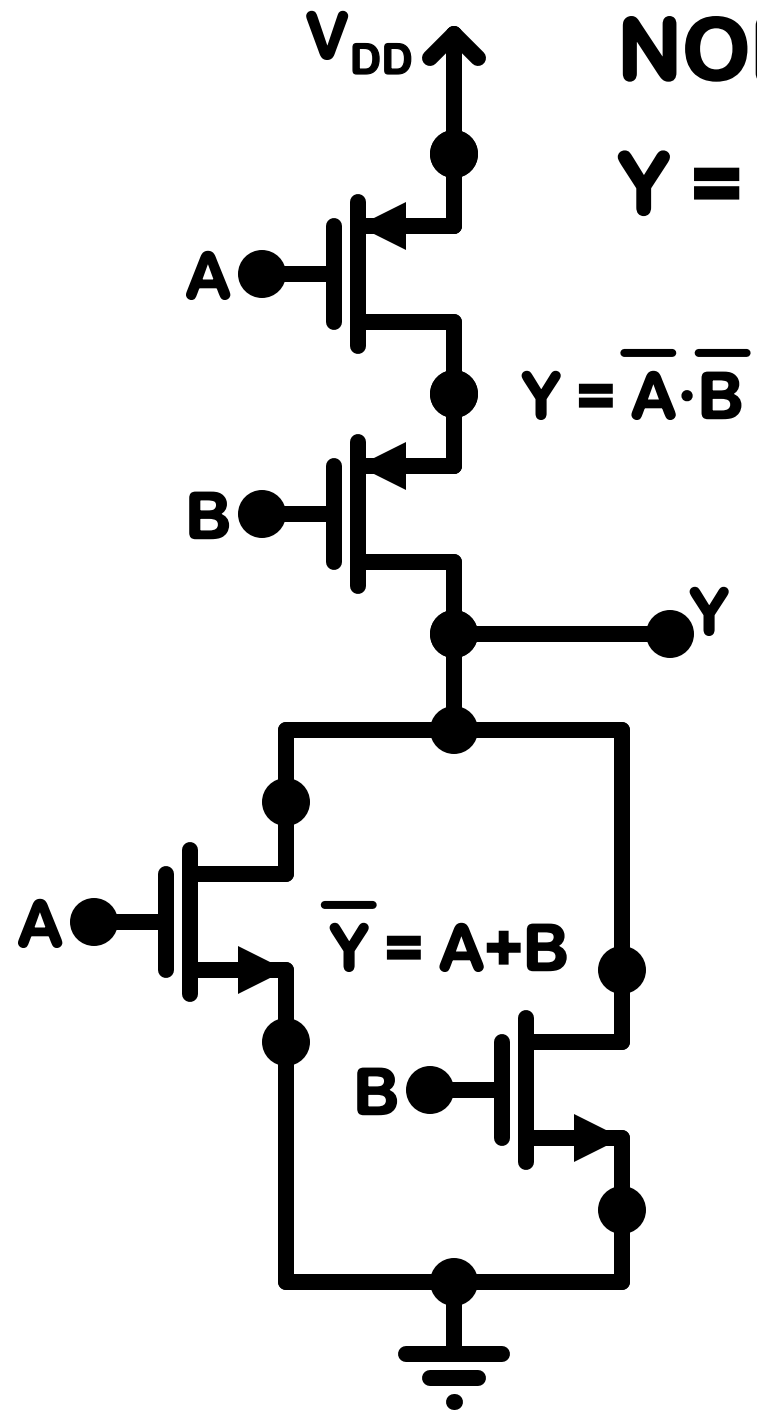

# Combinational Logic Design

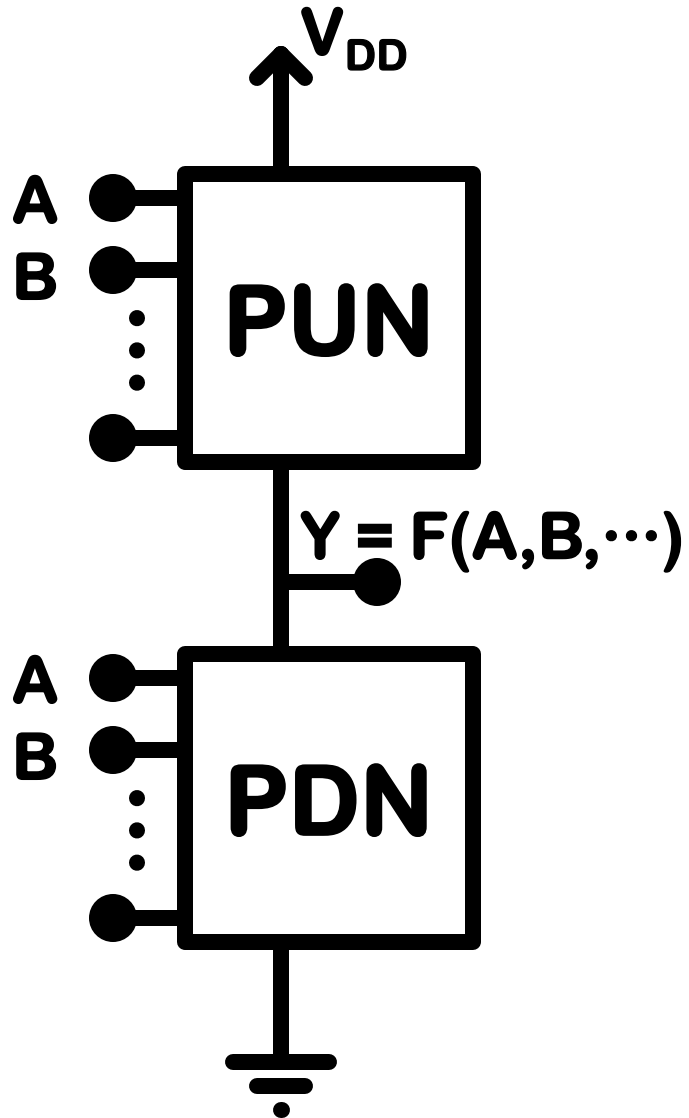

## Two Complementary Networks

### Pull Up Network (PUN):

- Express Y in terms of inverted inputs.
- Constructed with PMOS devices.
- “ANDs” are serial connections.
- “ORs” are parallel connections.

### Pull Down Network (PDN):

- Express inverted Y in terms inputs.
- Constructed with NMOS devices.
- “ANDs” are serial connections.
- “ORs” are parallel connections.

# Combinational Logic Design: Examples

$$Y = \overline{A} \cdot (\overline{B} + \overline{C})$$

$$Y = \overline{A} \cdot \overline{B \cdot C + D}$$

# Combinational Logic Design: Examples, find the function and PDN

