

Digital Logic ... EECS140

Two Categories

Combinational

Sequential

Digital Logic ... EECS140

Two Categories

Combinational

and, or, xor, ...

*Output transitions with inputs.

Sequential

latch, FF, Memory



*Output Transitions with a clock or S/R.

*Holds its value.

Logic Design

Performance (speed, power, size)



The Ideal Inverter

  

$V_{OUT} = V_{DD}$ at $V_{IN} = 0$
 $V_{OUT} = 0$ at $V_{IN} = V_{DD}$

But what about between 0 and V_{DD} ?



The Ideal Inverter

  

$$\begin{array}{ll} v_{OUT} = V_{DD} & \text{for } v_{IN} < V_{DD}/2 \\ v_{OUT} = 0 & \text{for } v_{IN} > V_{DD}/2 \end{array}$$

At $V_{DD}/2$ it is either V_{DD} , 0, or undefined.



A General Inverter

  

Observations:

- v_{OUT} doesn't necessarily equal V_{DD} at $v_{IN}=0$.
- v_{OUT} doesn't necessarily equal 0 at $v_{IN}=V_{DD}$.
- There is a transition region in between.
- The slope, $v_{OUT}'(v_{IN})$, is always negative.



A General Inverter

  

Regions:

- i. V_{IN} is LOW and V_{OUT} is HIGH.
 $|v_{OUT}'(v_{IN})| < 1$, magnitude of slope is less than one.
- ii. Transition Region (Stay out for Logic Applications).
 $|v_{OUT}'(v_{IN})| > 1$, magnitude of slope is greater than one.
- iii. V_{IN} is HIGH and V_{OUT} is LOW.
 $|v_{OUT}'(v_{IN})| < 1$, magnitude of slope is less than one.

A General Inverter

  

Parameters

V_{OH} : Output High Voltage:

V_{OL} : Output Low Voltage:

V_{IL} : Input Low Voltage:

V_{IH} : Input High Voltage:

$$V_{OH} = v_{OUT}(0)$$

$$V_{OL} = v_{OUT}(V_{DD})$$

1st point where $v_{OUT}'(v_{IN}) = -1$

2nd point where $v_{OUT}'(v_{IN}) = -1$

V_{IL} and V_{IH} are interpreted as values of v_{IN} that define the edges of the transition region, $v_{OUT}'(v_{IN})$ crosses -1.

logic diagram (positive logic)

recommended operating conditions (see Note 3)

		SN5404			SN7404			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V _{CC}	Supply voltage	2	5	5.5	2	5	5.5	V
V _{IH}	High-level input voltage	2			2			V
V _{IL}	Low-level input voltage			0.8			0.8	V
I _{OH}	High-level output current			-0.4			-0.4	mA
I _{OL}	Low-level output current			16			16	mA
T _A	Operating free-air temperature	-55		125	0		70	°C

NOTE 3: All unused inputs of the device must be held at V_{CC} or GND to ensure proper device operation. Refer to the TI application report, *Implications of Slow or Floating CMOS Inputs*, literature number SCBA004.


electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS‡			SN5404			SN7404			UNIT
				MIN	TYP§	MAX	MIN	TYP§	MAX	
V _{CC}	V _{CC} = MIN	I _I = 12 mA				1.5			1.5	V
V _{OH}	V _{CC} = MIN, V _{IL} = 0.8 V, I _{OH} = -0.4 mA			2.4	3.4		2.4	3.4		V
V _{OL}	V _{CC} = MIN, V _{IH} = 2 V, I _{OL} = 16 mA				0.2	0.4		0.2	0.4	V
I _{IH}	V _{CC} = MAX, V _I = 2.4 V					40			40	μA
I _{IL}	V _{CC} = MAX, V _I = 0.4 V					-1.6			-1.6	mA
I _{OS} ¶	V _{CC} = MAX			-20		-55	-18		-55	mA
I _{CCH}	V _{CC} = MAX, V _I = 0 V				6	12		6	12	mA
I _{CCL}	V _{CC} = MAX, V _I = 4.5 V				18	33		18	33	mA

‡ For conditions shown as MIN or MAX, use the appropriate value specified under recommended operating conditions.

§ All typical values are at V_{CC} = 5 V, T_A = 25°C.

 ¶ Not more than one output should be shorted at a time.




$$Y = \overline{A}$$

<https://www.ti.com/lit/ds/symlink/sn74ahcu04-ep.pdf?ts=1679658099795>

As long as the input is at least 2.0V, the input is registered high and the output will be low with a voltage that is at most 0.4V. ($v_{IN} > 2.0$, $v_{OUT} < 0.4$)

As long as the input is at most 0.8V, the input is registered low and the output will be high with a voltage that is at least 2.4V. ($v_{IN} < 0.8$, $v_{OUT} > 2.4$)

Why are these values important?

 


As long as the input is at least 2.0V, the input is registered high and the output will be low with a voltage that is at most 0.4V. ($v_{IN} > 2.0$, $v_{OUT} < 0.4$)

As long as the input is at most 0.8V, the input is registered low and the output will be high with a voltage that is at least 2.4V. ($v_{IN} < 0.8$, $v_{OUT} > 2.4$)

Why are these values important?

What if V_{OH} was actually 1.8V?

A General Inverter

 


As long as the input is at least 2.0V, the input is registered high and the output will be low with a voltage that is at most 0.4V. ($v_{IN} > 2.0$, $v_{OUT} < 0.4$)

As long as the input is at most 0.8V, the input is registered low and the output will be high with a voltage that is at least 2.4V. ($v_{IN} < 0.8$, $v_{OUT} > 2.4$)

Why are these values important?

What if V_{OH} was actually 1.8V?

A General Inverter

 


NOISE MARGIN: The maximum magnitude of noise that the circuit can tolerate to ensure v_{IN2} stays out of the transition region.

NM_L : when v_{IN1} is the ideal high input, V_{DD} .

NM_H : when v_{IN1} is the ideal low input, 0.

NM : The minimum value of NM_L or NM_H .

A General Inverter

 


NM_L :

$$V_{IN1} = V_{DD}$$


$$V_{OUT1} = V_{OL}$$

$$V_{IN2} = V_{OL} + |v_N| < V_{IL}$$

$$v_N < V_{IL} - V_{OL} = NM_L$$

 

A General Inverter

 


NM_H :

$$V_{IN1} = 0$$




$$V_{OUT1} = V_{OH}$$

$$V_{IN2} = V_{OH} - |v_N| > V_{IH}$$

$$v_N < V_{OH} - V_{IH} = NM_H$$

 

A General Inverter

   

The Ideal Inverter achieves the maximum NM.

Parameters

V_{OH} : Output High Voltage:

V_{OL} : Output Low Voltage:

V_{IL} : Input Low Voltage:

V_{IH} : Input High Voltage:

NM_L : Noise Margin Low:

NM_H : Noise Margin High:

NM : Noise Margin:

$$V_{OH} = v_{OUT}(0)$$

$$V_{OL} = v_{OUT}(V_{DD})$$

1st point where $v_{OUT}'(v_{IN}) = -1$

2nd point where $v_{OUT}'(v_{IN}) = -1$



$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$




$$NM = \min(NM_L, NM_H)$$

Implementation



NMOS Inverter

  


NMOS Inverter

   


NMOS Inverter (models)

  

 At $v_{IN} = V_{DD}$
 $r_{DS} = 1/(k_n(V_{DD} - V_{tn}))$




 V_{IN} is LOW,
Switch is OPEN,
Not Conducting,
 V_{OUT} is HIGH.




$$P_D = 0$$

Basic Inverter
NMOS Inspired

 

 V_{IN} is HIGH,
Switch is CLOSED.
Conducting,
 V_{OUT} is LOW.



$$r_{PDN} = r_{DS} = 1/(k_n(V_{DD} - V_{tn}))$$

$$P_D = V_{DD}^2 / (R_D + r_{PDN})$$

PMOS Inverter



Notes:

$$V_{IN} = V_{DD} - V_{SG}$$

$$V_{OUT} = V_{DD} - V_{SD} = R_D i_D$$

As v_{IN} (or $V_{DD} - v_{SG}$) increases from zero to V_{DD} .

Modes: triode, saturation, cutoff

  

Triode

$$V_{SD} < V_{SG} - |V_{tp}|$$

$$V_{DD} - V_{OUT} < V_{DD} - V_{IN} - |V_{tp}|$$

$$V_{OUT} > V_{IN} + |V_{tp}|$$

Saturation

$$V_{OUT} < V_{IN} + |V_{tp}|$$

Cutoff

$$V_{SG} < |V_{tp}|$$

$$V_{DD} - V_{IN} < |V_{tp}|$$

$$V_{IN} > V_{DD} - |V_{tp}|$$



PMOS Inverter

Notes:

$$v_{IN} = V_{DD} - v_{SG}$$

$$v_{OUT} = V_{DD} - v_{SD} = R_D i_D$$

  As v_{IN} (or $V_{DD} - v_{SG}$) increases from zero to V_{DD} .
Modes: triode, saturation, cutoff



Triode (small v_{SD})

$$v_{OUT} > v_{IN} + |V_{tp}|$$

$$v_{OUT} = R_D k_p (V_{DD} - v_{IN} - |V_{tp}|)(V_{DD} - v_{OUT})$$

$$v_{OUT} = V_{DD} / (1 + 1 / (R_D k_p (V_{DD} - v_{IN} - |V_{tp}|)))$$

Saturation

$$v_{OUT} < v_{IN} + |V_{tp}|$$

$$v_{OUT} = 0.5 R_D k_p ((V_{DD} - |V_{tp}|) - v_{IN})^2$$

$$v_{OUT} = 0.5 R_D k_p (v_{IN} - (V_{DD} - |V_{tp}|))^2$$

Cutoff




$$v_{IN} > V_{DD} - |V_{tp}|$$

$$v_{OUT} = 0$$


PMOS Inverter (models)

At $v_{IN}=0$

$$r_{SD} = 1/(k_p(V_{DD}-|V_{tp}|))$$

   

 
v_{IN} is LOW,
Switch is CLOSED,
Conducting,
 v_{OUT} is HIGH.




$$r_{PUN} = r_{SD} = 1/(k_p(v_{DD} - |V_{tp}|))$$

$$P_D = V_{DD}^2 / (R_D + r_{PUN})$$

Basic Inverter
PMOS Inspired



 


 v_{IN} is HIGH,
Switch is OPEN.
Not Conducting,
 v_{OUT} is LOW.



$$P_D = 0$$




CMOS Inverter

   

CMOS Inverter (models)

At $v_{IN}=0$


$$r_{SD} = 1/(k_p(v_{DD}-|V_{tp}|))$$

   

At $v_{IN}=V_{DD}$


$$r_{DS} = 1/(k_n(v_{DD}-V_{tn}))$$

 v_{IN} is LOW,
PMOS is conducting,
 v_{OUT} is HIGH.




$$P_D=0$$

Basic Inverter
CMOS Inspired

 

 v_{IN} is HIGH,
NMOS is conducting,
 v_{OUT} is LOW.



$$P_D=0$$