
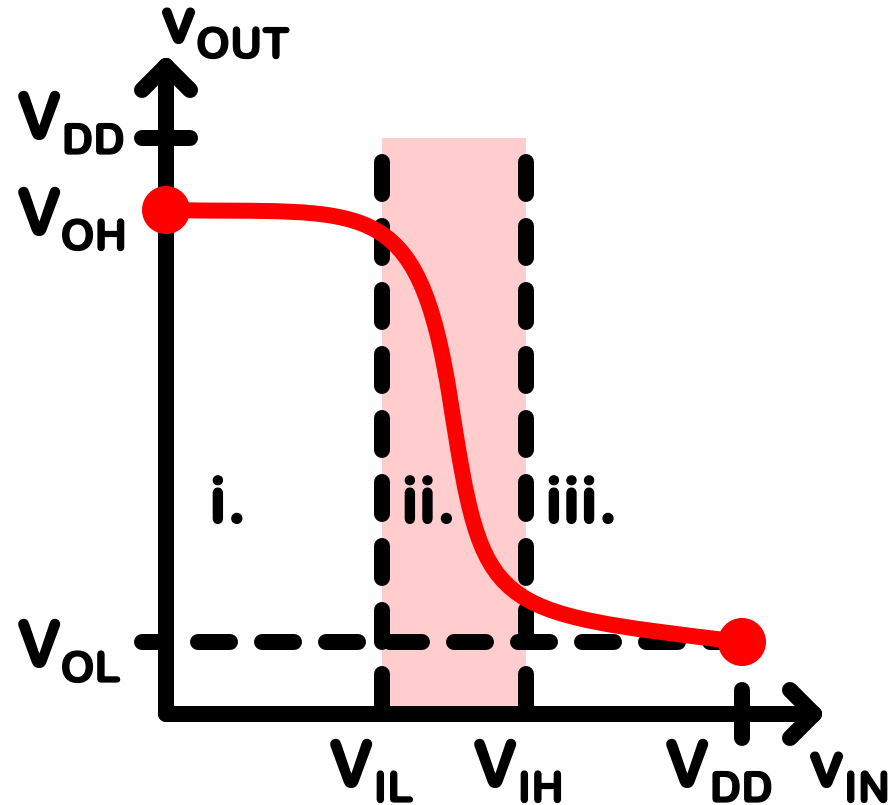


A General Inverter

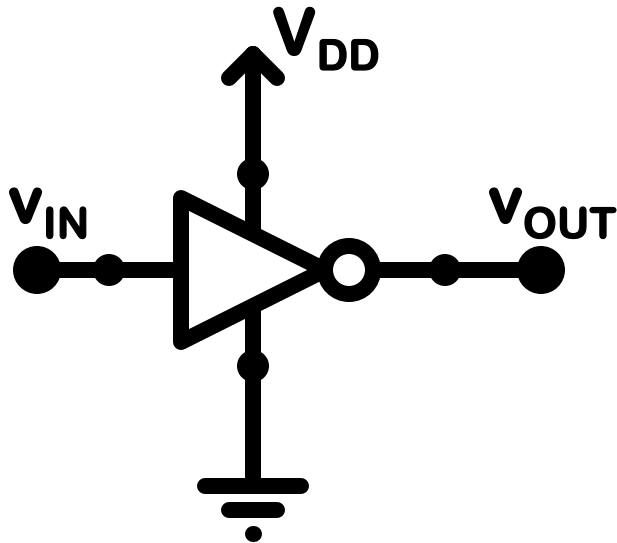

Parameters

V_{OH} : Output High Voltage:

V_{OL} : Output Low Voltage:

V_{IL} : Input Low Voltage:

V_{IH} : Input High Voltage:

$$V_{OH} = v_{OUT}(0)$$

$$V_{OL} = v_{OUT}(V_{DD})$$

1st point where $v_{OUT}'(v_{IN}) = -1$

2nd point where $v_{OUT}'(v_{IN}) = -1$

V_{IL} and V_{IH} can also be interpreted as values of v_{IN} that define the edges of the transition region, $v_{OUT}'(v_{IN})$ crosses -1.

Implementation

NMOS Inverter



Parameters

$$V_{OH} = v_{OUT}(0) = V_{DD}$$

$$V_{OL} = v_{OUT}(V_{DD})$$

$$v_{OUT}'(V_{IL}) = -1$$

$$v_{OUT}'(V_{IH}) = -1$$

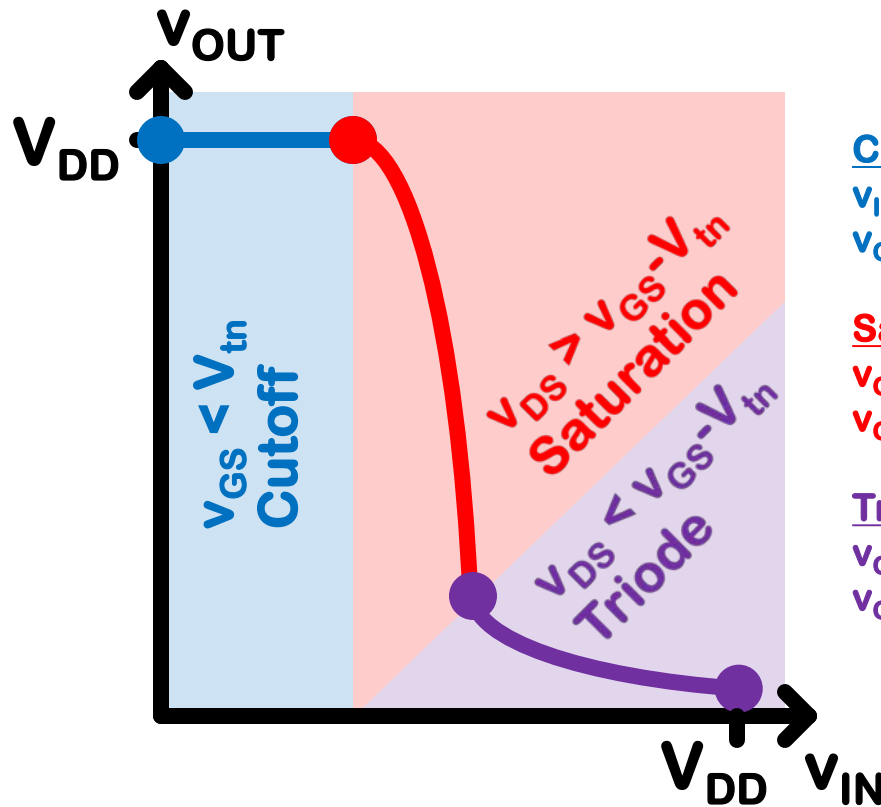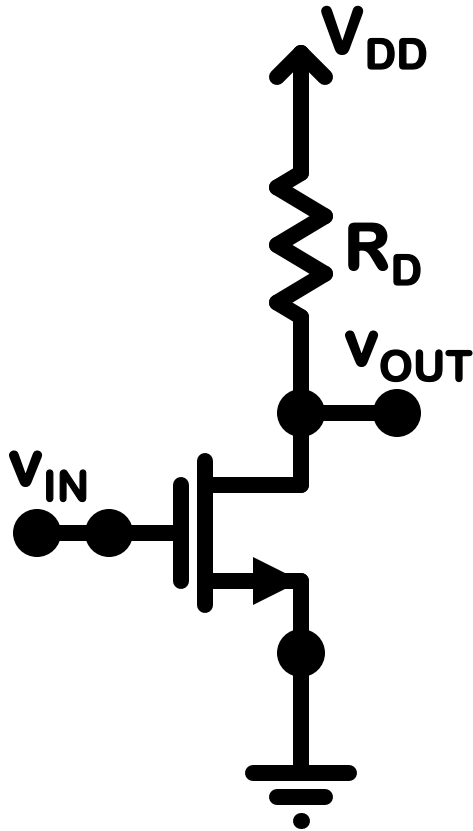

Cutoff

$$V_{IN} < V_{tn}$$

$$V_{OUT} = V_{DD}$$

Saturation

$$V_{OUT} > V_{IN} - V_{tn}$$

$$V_{OUT} = V_{DD} - 0.5R_Dk_n(V_{IN} - V_{tn})^2$$

Triode (small v_{SD})

$$V_{OUT} < V_{IN} - V_{tn}$$

$$V_{OUT} = V_{DD} / (1 + R_Dk_n(V_{IN} - V_{tn}))$$

Implementation

NMOS Inverter



Parameters

$$V_{OH} = v_{OUT}(0) = V_{DD}$$

$$V_{OL} = v_{OUT}(V_{DD}) = V_{DD} / (1 + R_D k_n (V_{DD} - V_{tn}))$$

$$v_{OUT}'(V_{IL}) = -R_D k_n (V_{IL} - V_{tn}) = -1; V_{IL} = (1 / R_D k_n) + V_{tn}$$
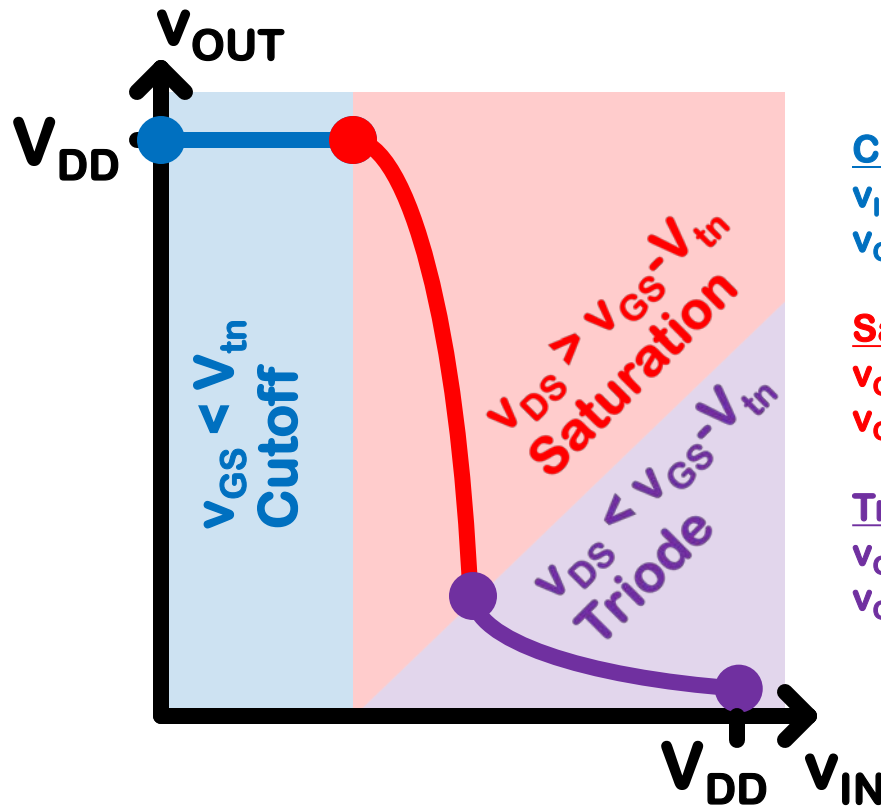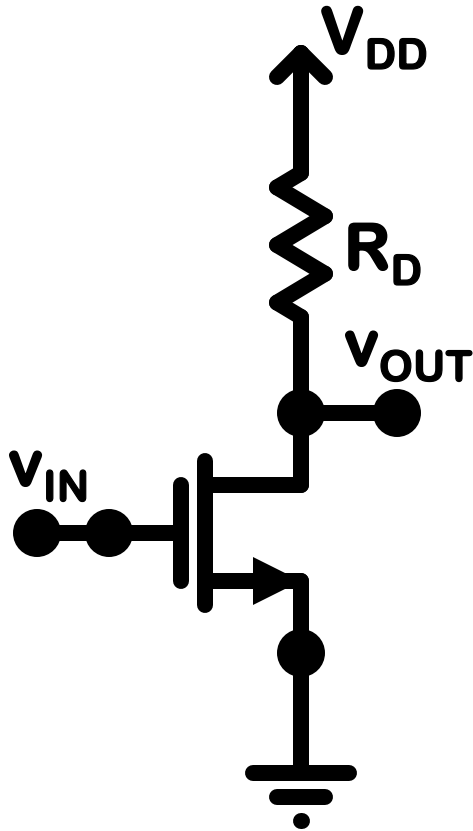
$$v_{OUT}'(V_{IH}) = -1; \text{Triode (small } v_{DS}) \text{ is not applicable}$$



Cutoff

$$V_{IN} < V_{tn}$$

$$V_{OUT} = V_{DD}$$

Saturation

$$V_{OUT} > V_{IN} - V_{tn}$$



$$V_{OUT} = V_{DD} - 0.5 R_D k_n (V_{IN} - V_{tn})^2$$

Triode (small v_{SD})

$$V_{OUT} < V_{IN} - V_{tn}$$

$$V_{OUT} = V_{DD} / (1 + R_D k_n (V_{IN} - V_{tn}))$$

PMOS Inverter

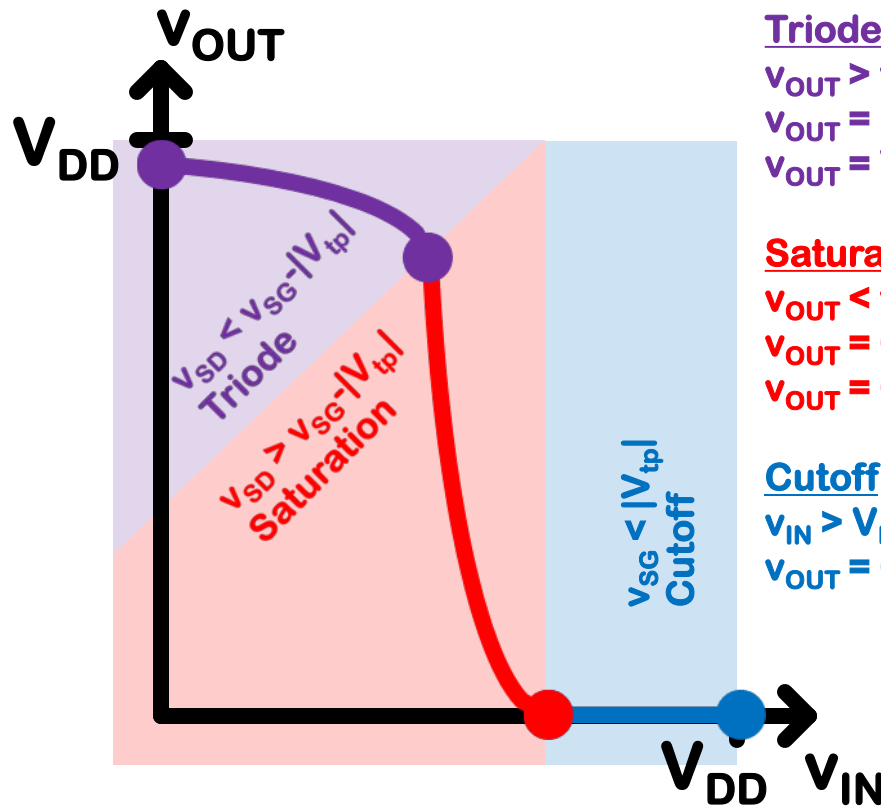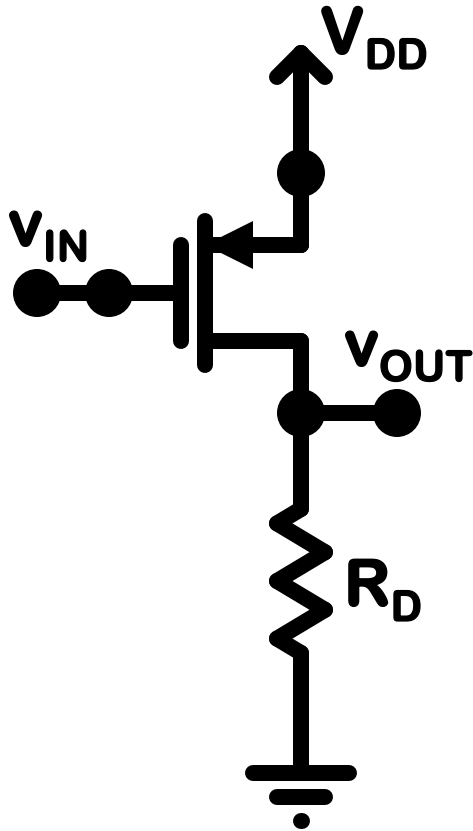

Triode (small v_{SD})

$$v_{OUT} > v_{IN} + |V_{tp}|$$

$$v_{OUT} = R_D k_p (V_{DD} - v_{IN} - |V_{tp}|)(V_{DD} - v_{OUT})$$

$$v_{OUT} = V_{DD} / (1 + 1 / (R_D k_p (V_{DD} - v_{IN} - |V_{tp}|)))$$

Saturation

$$v_{OUT} < v_{IN} + |V_{tp}|$$

$$v_{OUT} = 0.5 R_D k_p ((V_{DD} - |V_{tp}|) - v_{IN})^2$$




$$v_{OUT} = 0.5 R_D k_p (v_{IN} - (V_{DD} - |V_{tp}|))^2$$

Cutoff

$$v_{IN} > V_{DD} - |V_{tp}|$$

$$v_{OUT} = 0$$

CMOS Inverter

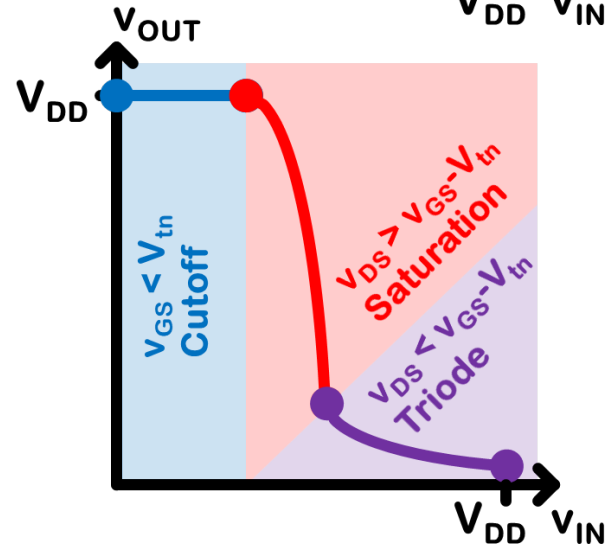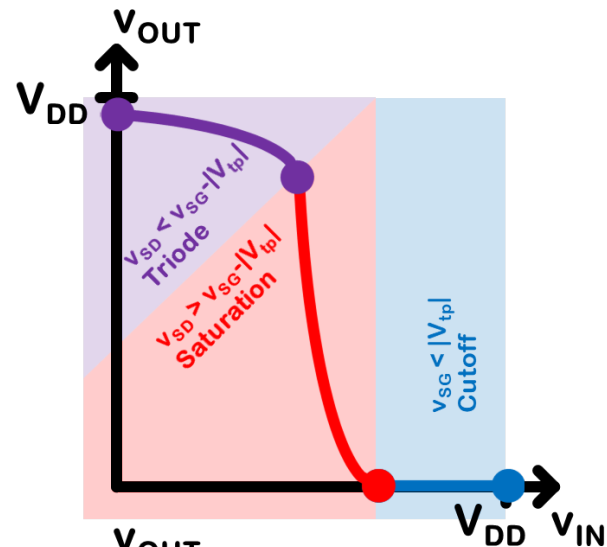
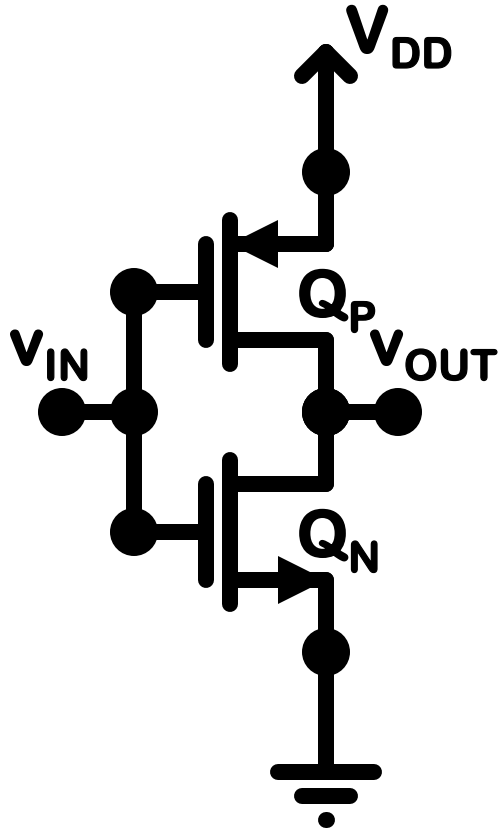


*devices are matched.

* $V_{DD} > 2V_t$


V_{IN} :	0						V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff		
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode		

CMOS Inverter

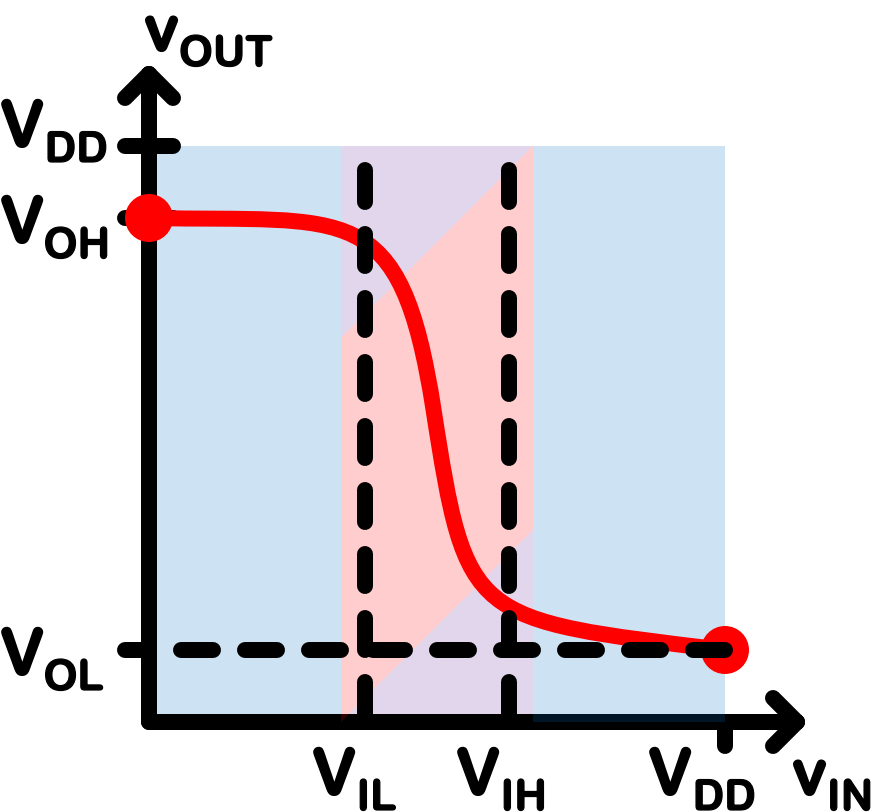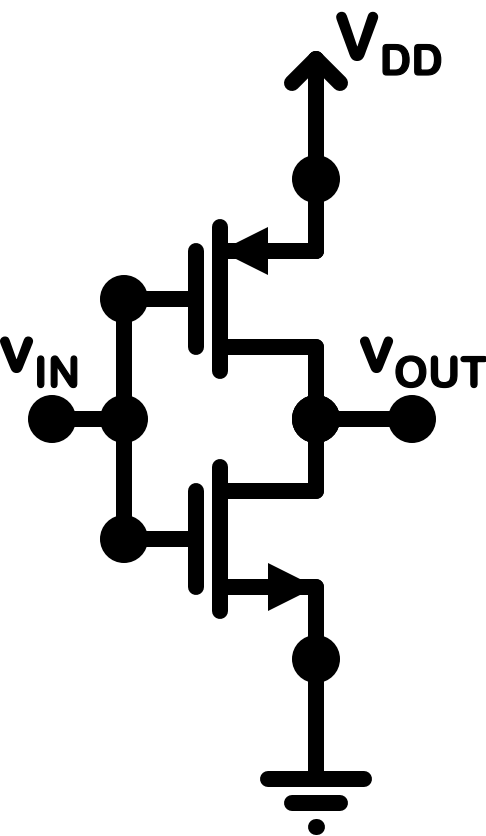


V_{IN} :	0						V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff		
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode		

CMOS Inverter

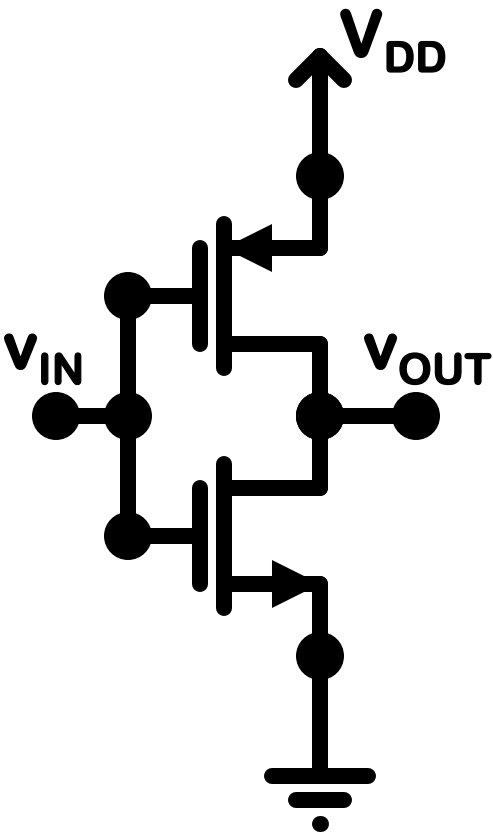

V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

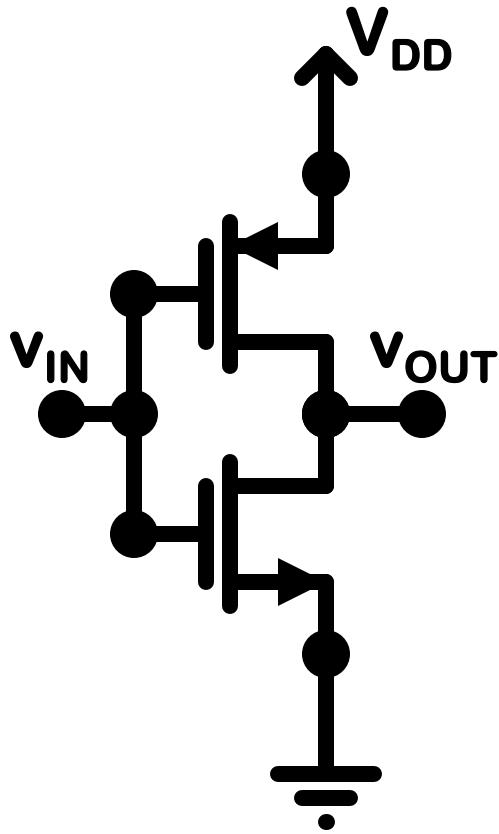

Cutoff

$$i_D = 0$$

Triode

$$i_D = k_n(v_{GS} - V_{tn} - 0.5v_{DS})v_{DS}$$

$$v_{GS} = v_{IN}$$

$$v_{DS} = v_{OUT} = 0$$

$$v_{SG} < |V_{tp}|$$

$$V_{DD} - v_{IN} < |V_{tp}|$$

$$v_{IN} > V_{DD} - |V_{tp}|$$

$$v_{GS} > V_{tn}$$

$$v_{IN} > V_{tn}$$

$$v_{DS} < v_{GS} - V_{tn}$$

$$v_{OUT} < v_{IN} - V_{tn}$$

$$0 < v_{IN} - V_{tn}$$

$$v_{IN} > V_{tn}$$

V_{IN} : 0



PMOS: Triode Triode

NMOS: Cutoff Saturation Saturation Triode

Saturation Saturation


V_{DD}
Cutoff
Triode

CMOS Inverter

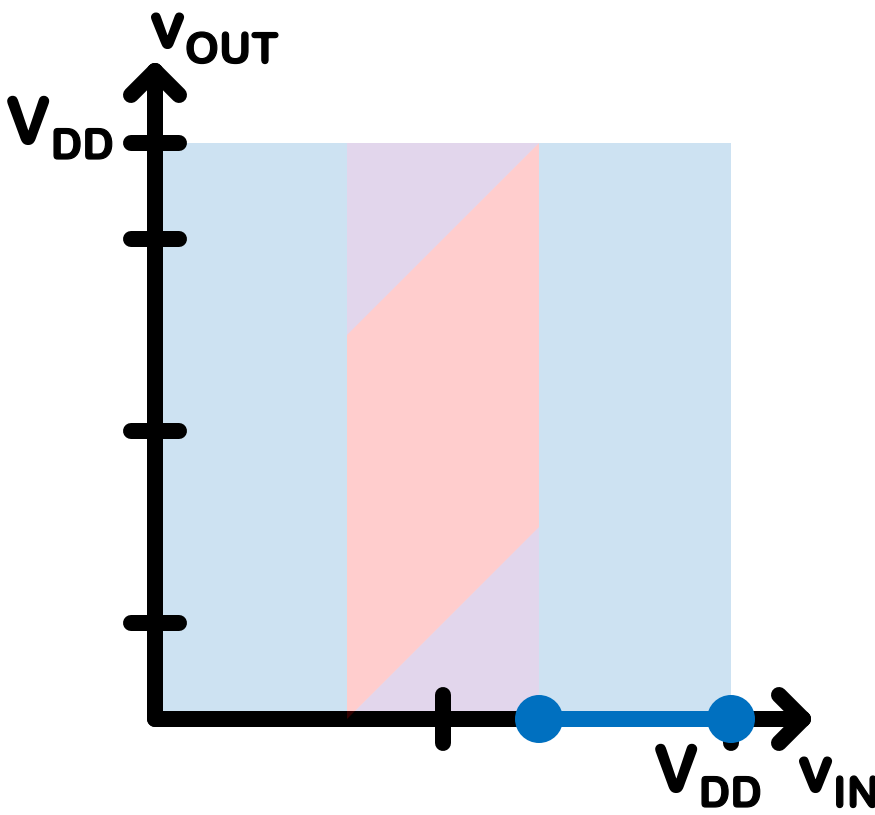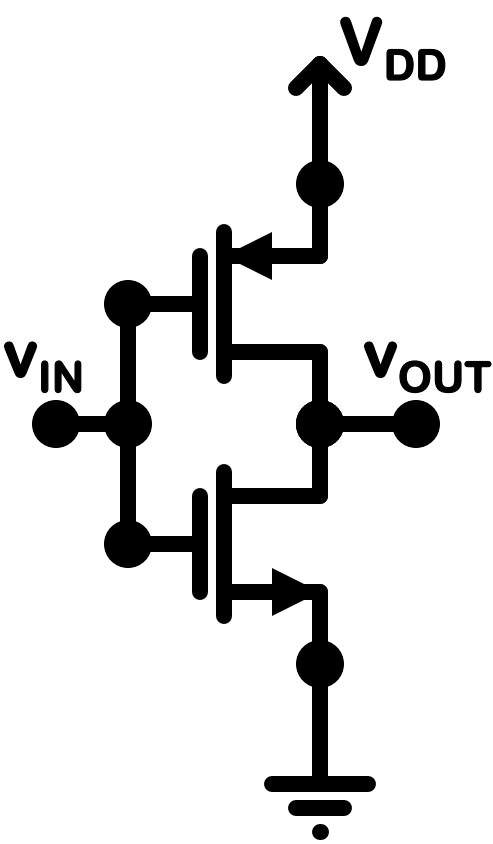

V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

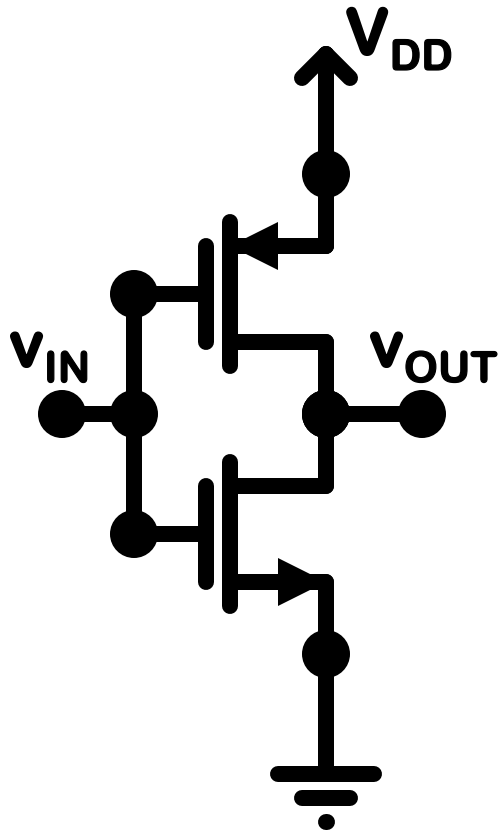

Cutoff

$$i_D = 0$$

Triode

$$i_D = k_p(v_{SG} - |V_{tp}| - 0.5v_{SD})v_{SD}$$

$$v_{SG} = V_{DD} - v_{IN}$$

$$v_{SD} = V_{DD} - v_{OUT} = 0$$

$$v_{OUT} = V_{DD}$$

$$v_{GS} < V_{tn}$$

$$v_{IN} < V_{tn}$$

$$v_{SG} > V_{tn}$$

$$V_{DD} - v_{IN} > |V_{tp}|$$

$$v_{IN} < V_{DD} - |V_{tp}|$$

$$v_{SD} < v_{SG} - |V_{tp}|$$

$$V_{DD} - v_{OUT} < V_{DD} - v_{IN} - |V_{tp}|$$

$$0 < V_{DD} - v_{IN} - |V_{tp}|$$

$$v_{IN} < V_{DD} - |V_{tp}|$$

V_{IN} : 0

PMOS: Triode

NMOS: Cutoff

Triode

Saturation

Saturation

Saturation

Saturation



Triode

Cutoff

Triode


V_{DD}

CMOS Inverter

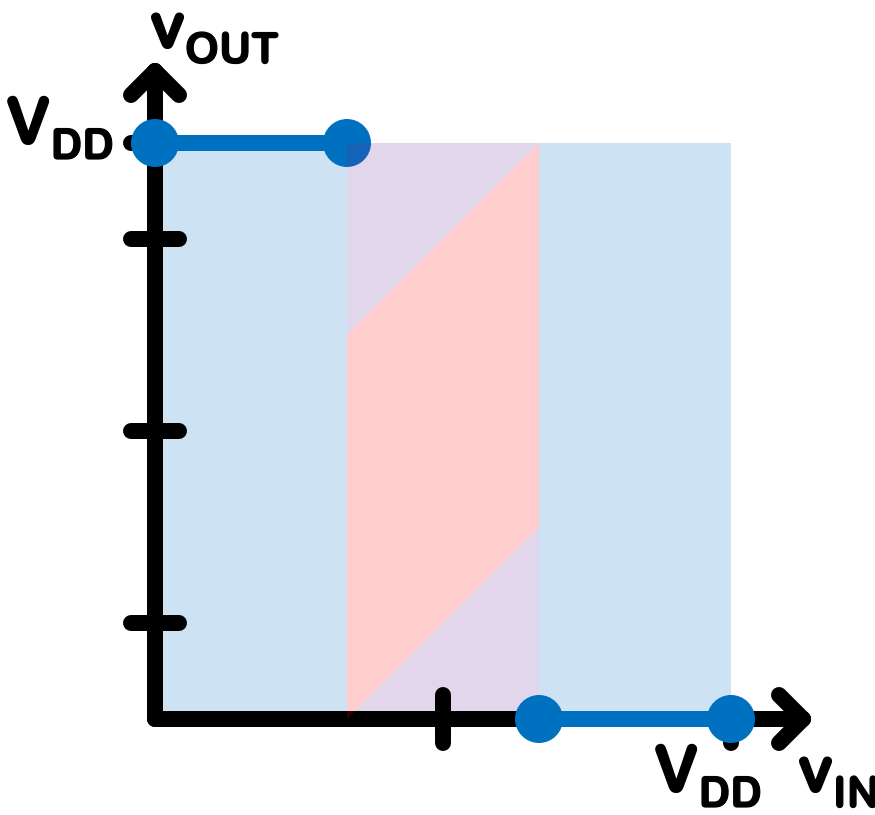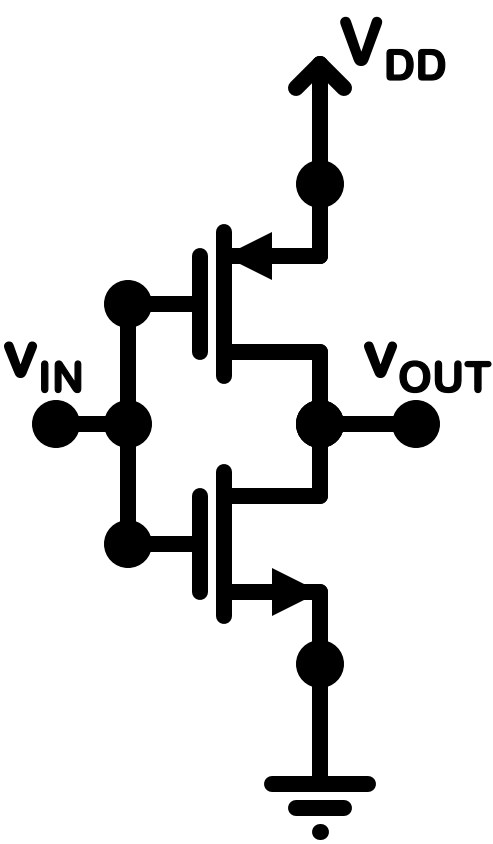


V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

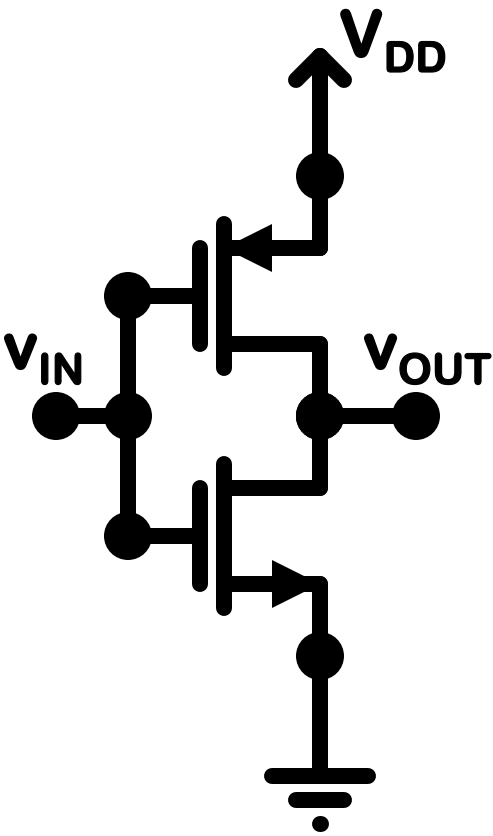

V_{IN} :	0				V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode

CMOS Inverter

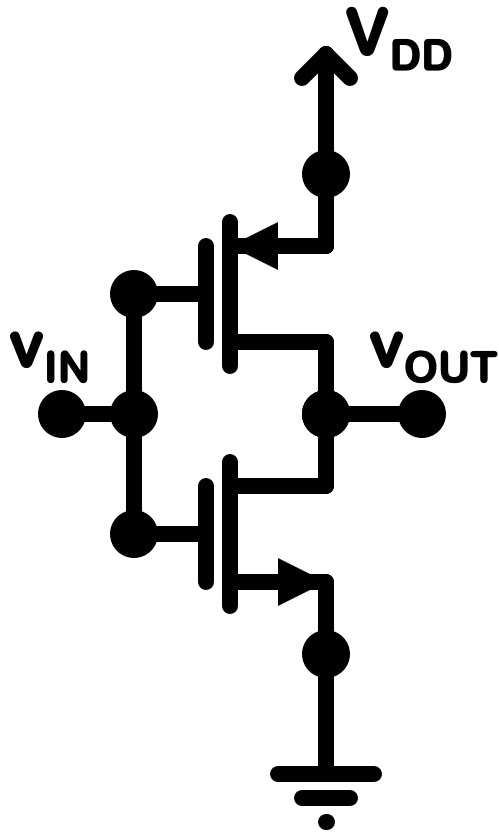

Saturation

$$V_{OUT} > V_{IN} - V_{tn}$$

$$i_D = 0.5k_n(V_{GS} - V_{tn})^2$$

$$i_D = 0.5k_p(V_{SG} - |V_{tp}|)^2$$

$$0.5k_n(V_{GS} - V_{tn})^2 = 0.5k_p(V_{SG} - |V_{tp}|)^2$$

$$(V_{GS}) = (V_{SG})$$

$$V_{IN} = V_{DD} - V_{IN}$$

$$V_{IN} = V_{DD}/2$$

$$V_{GS} > V_{tn} \quad V_{IN} > V_{tn}$$

$$V_{SG} > |V_{tp}| \quad V_{IN} < V_{DD} - |V_{tp}|$$

$$V_{DS} > V_{GS} - V_{tn}$$

$$V_{OUT} > V_{IN} - V_{tn}$$

$$V_{OUT} > V_{DD}/2 - V_{tn}$$

$$V_{OUT} < V_{DD}/2 + V_{tn}$$

V_{IN} : 0

PMOS: Triode Triode

NMOS: Cutoff Saturation

Saturation

Saturation



Saturation Triode

Cutoff

Triode


V_{DD}

CMOS Inverter

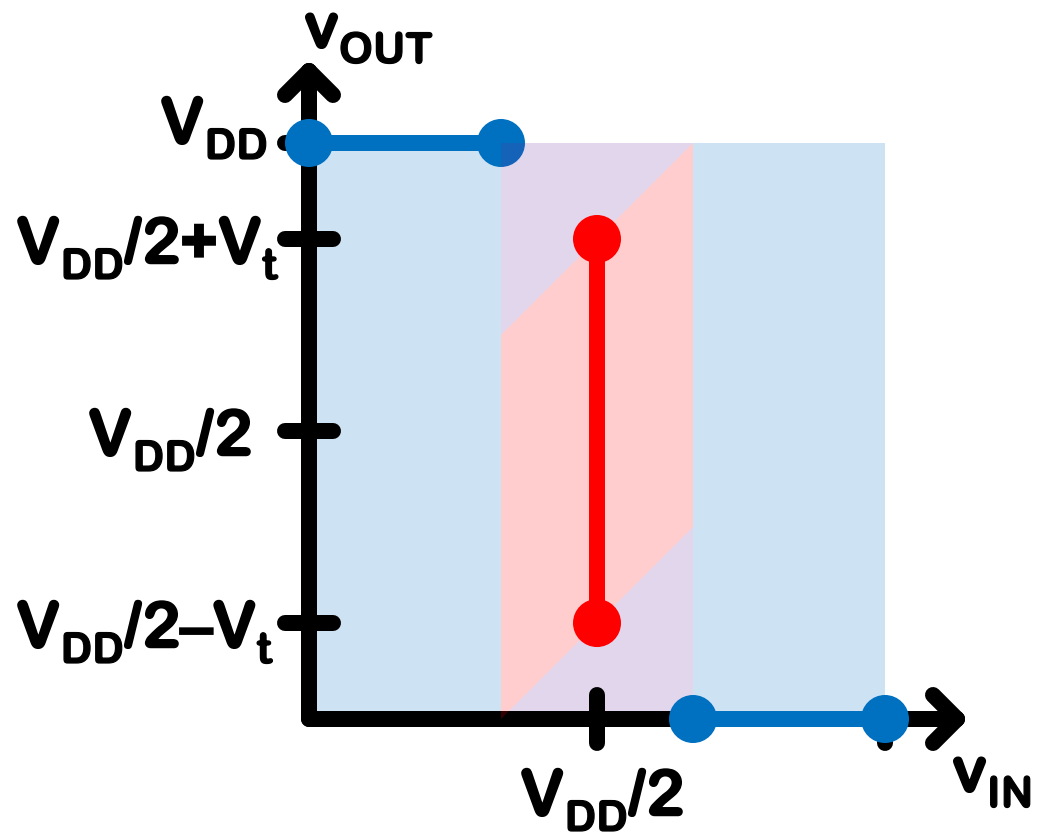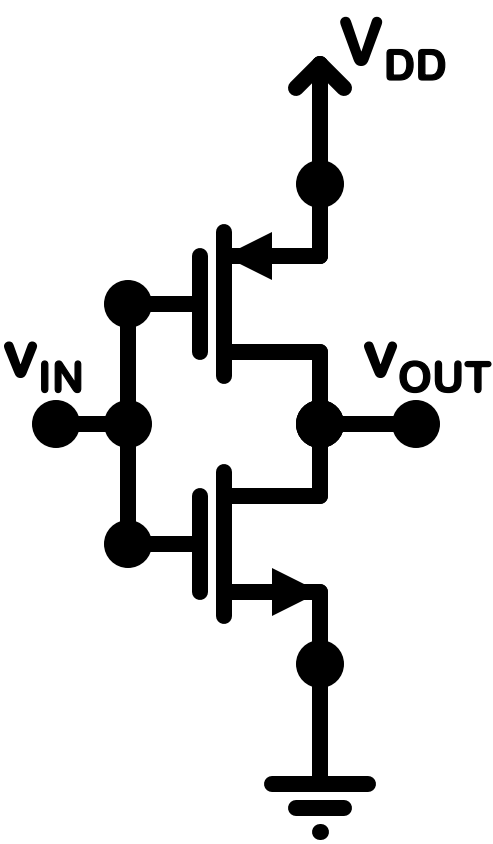


V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

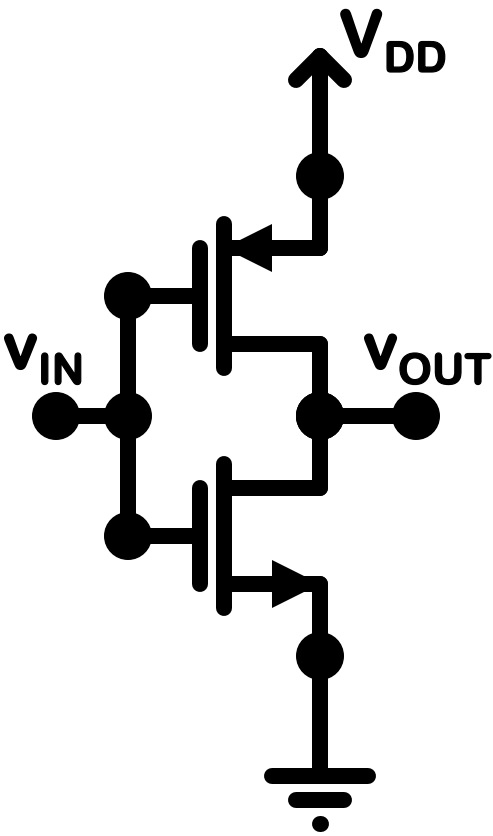

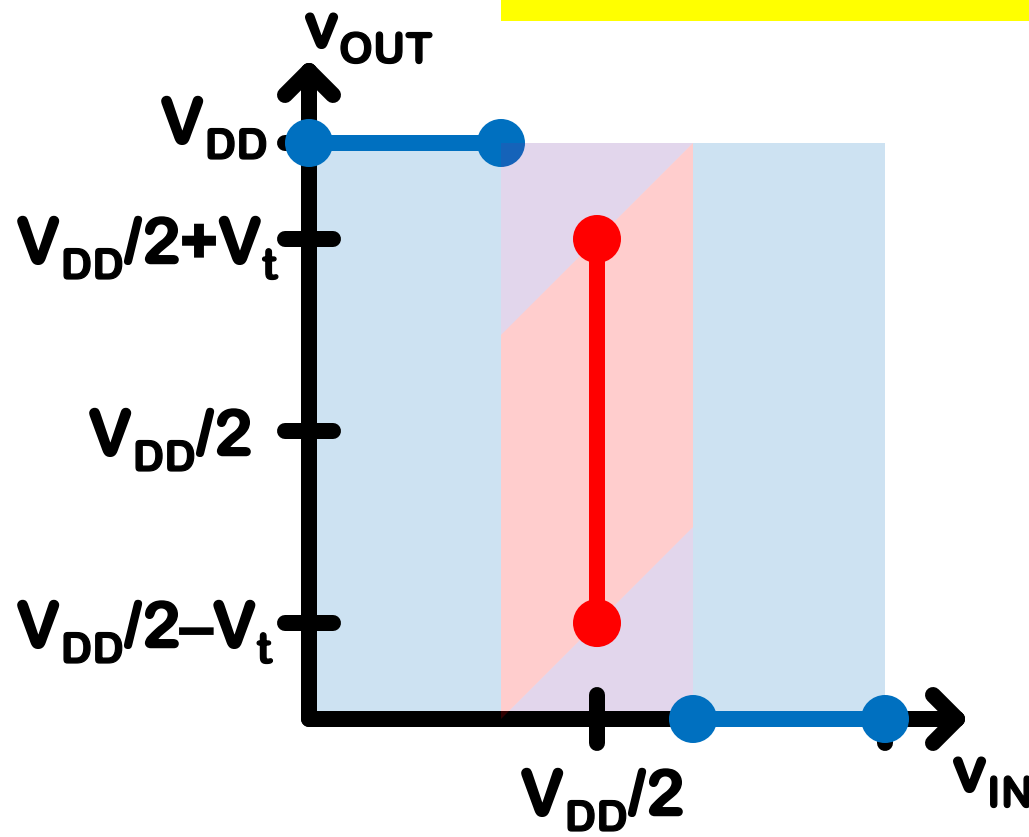
As V_t approaches $V_{DD}/2$ the transfer function resembles an ideal inverter.



Not really vertical, we did not include λ, V_A, r_o .



V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

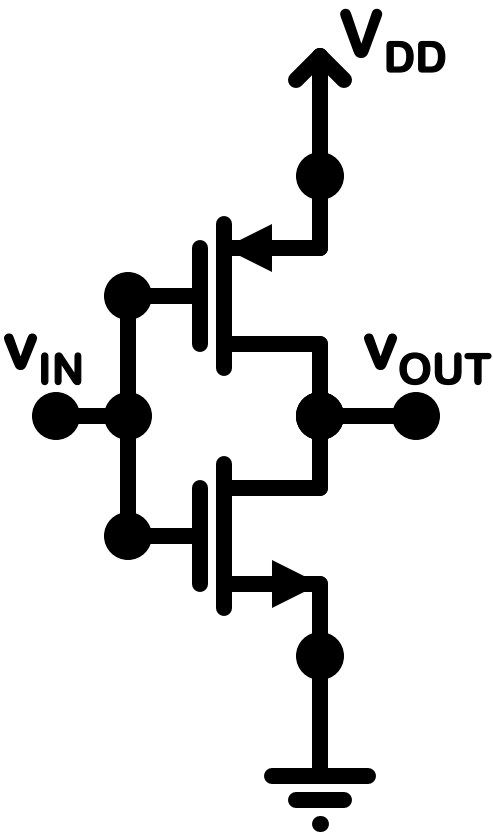



V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

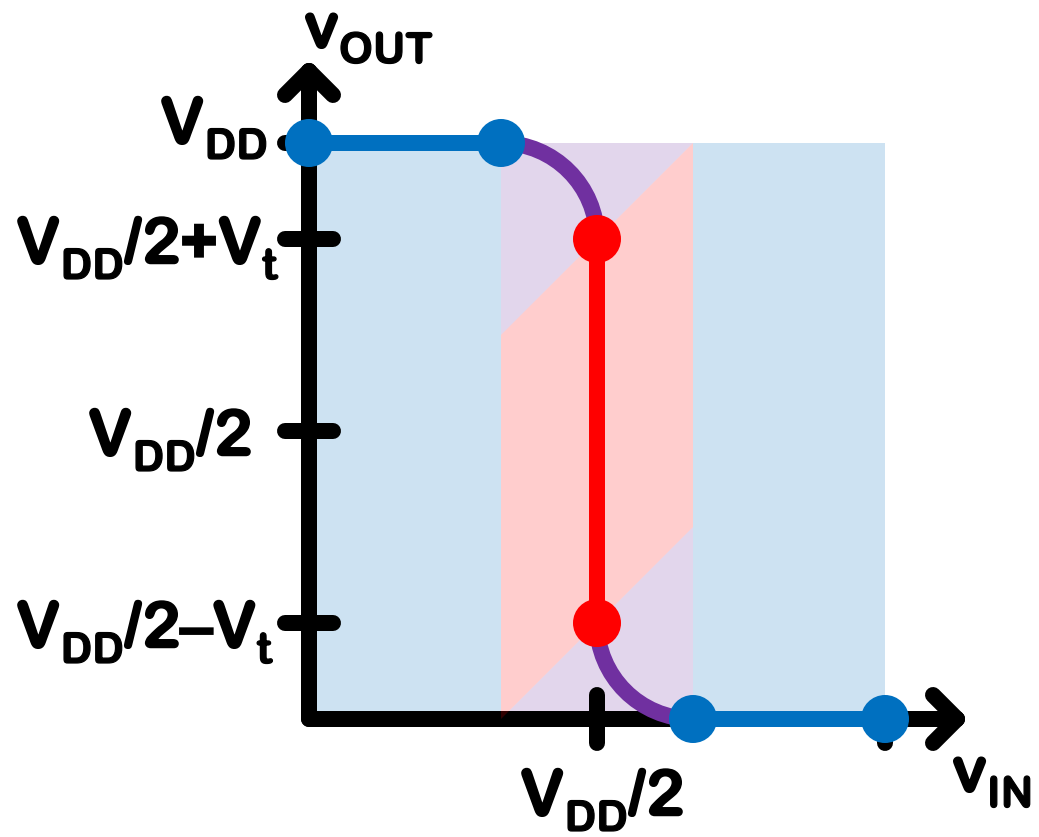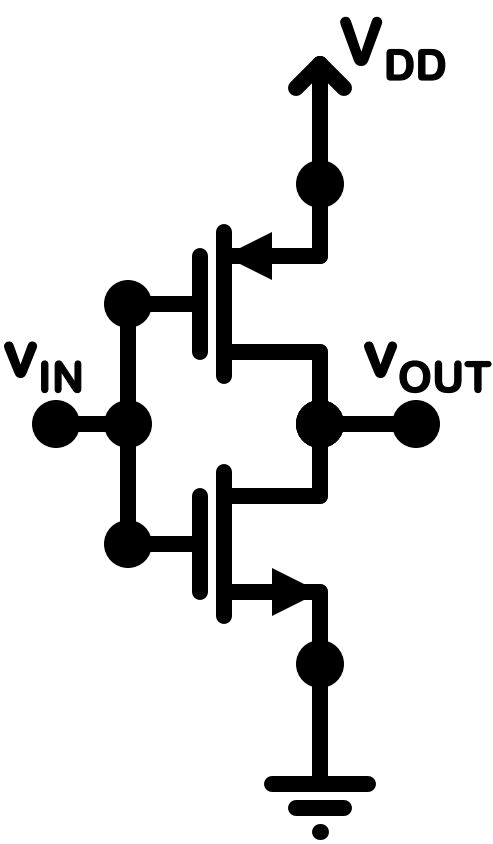

V_{IN} :	0					V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff	
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode	

CMOS Inverter

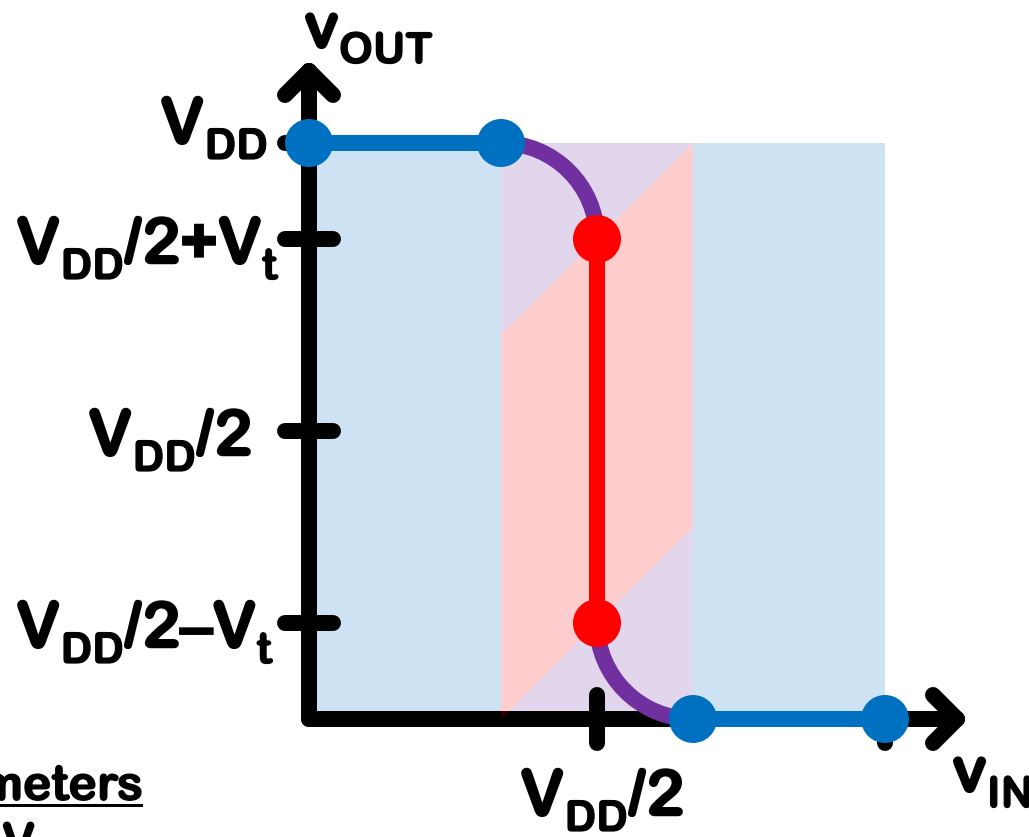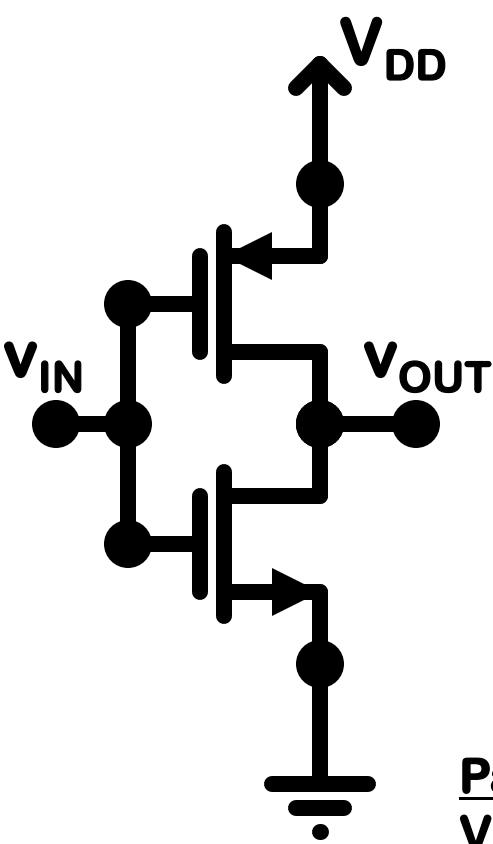


Parameters

- $V_{OH} = V_{DD}$
- $V_{OL} = 0$
- $V_{IH} = ?$
- $V_{IL} = ?$

V_{IN} :	0						V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff		
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode		

CMOS Inverter


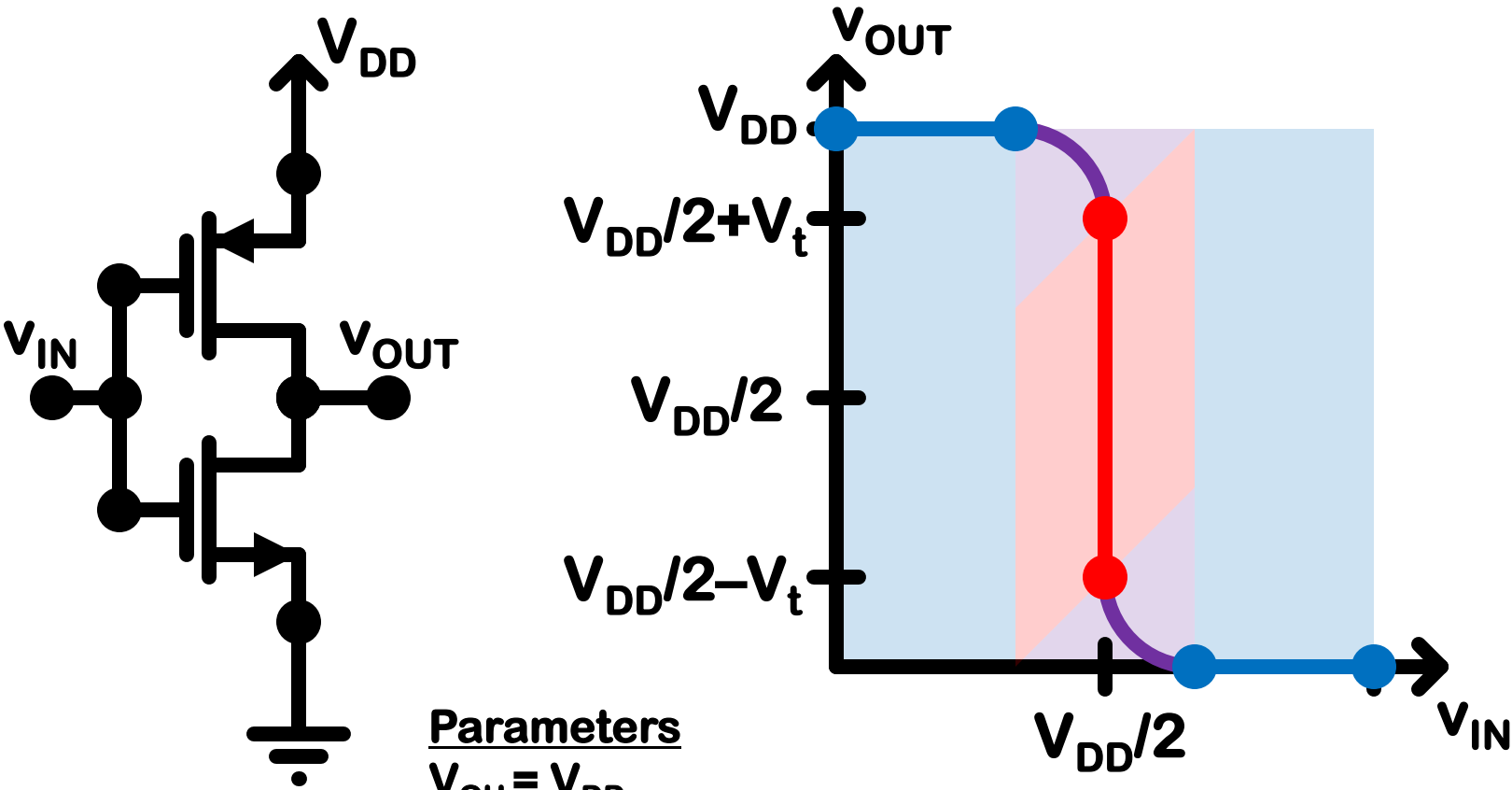


Parameters

$V_{OH} = V_{DD}$
 $V_{OL} = 0$
 $V_{IH} = (5V_{DD} - 2V_t)/8$
 $V_{IL} = (3V_{DD} + 2V_t)/8$

V_{IN} :	0						V_{DD}
PMOS:	Triode	Triode	Saturation	Saturation	Cutoff		
NMOS:	Cutoff	Saturation	Saturation	Triode	Triode		

CMOS Inverter

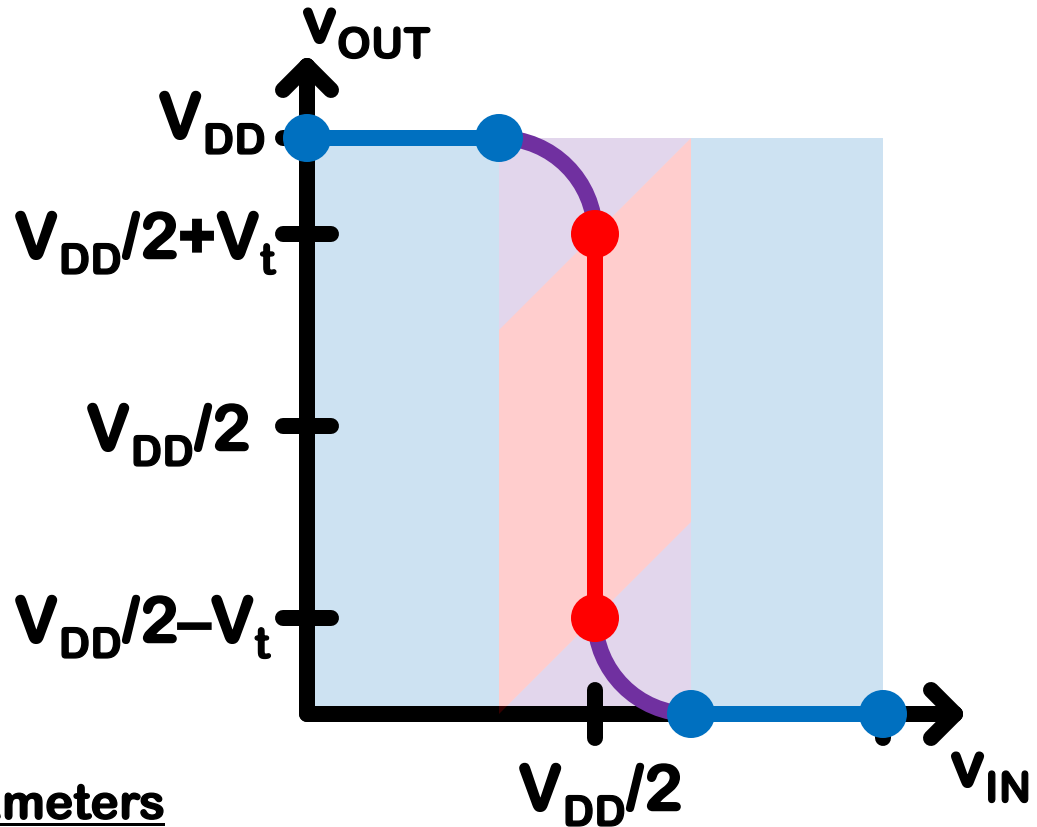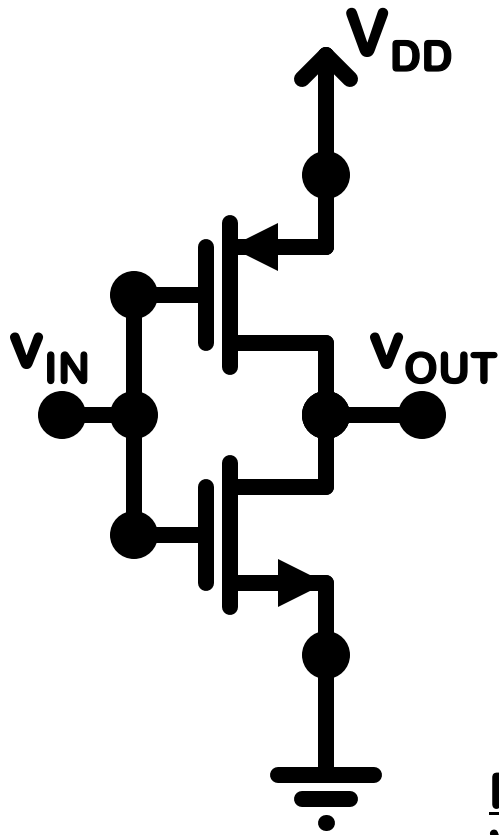

Parameters

$$V_{OH} = V_{DD}$$

$$V_{OL} = 0$$

$$V_{IH} = (5V_{DD} - 2V_t)/8$$

$$V_{IL} = (3V_{DD} + 2V_t)/8$$

$$NM_H = NM_L = NM = (3V_{DD} + 2V_t)/8$$

V_{IN} : 0

PMOS: Triode Triode Saturation Saturation Cutoff

NMOS: Cutoff Saturation Saturation Triode Triode

V_{DD}