

Semiconductor Memories

Semiconductor Memory:

- Semiconductor memory is a fundamental component of digital systems from large computers to embedded microprocessors.

Types of Memories:

- In any given system, there are typically various types of memory that are used to perform different functions such as:
 - Storing instructions
 - Storing data
- Memory can be divide into two broad categories depending on **access time**.
 - The time needed to retrieve data from a particular memory location.

Memory	Cost	Speed
SRAM	High	Fast
DRAM	Moderate	Moderate
Serial	Low	Slow

Semiconductor Memories

- **Main Memory:**
 - Usually referred to as random access memory (RAM).
 - The time required to access a given part of memory is independent of the memory location.
 - Typical volatile – loses contents when power is cut.
- **Mass-Storage Memory:**
 - Usually referred to as serial or sequential memory (disks or tapes), although flash storage is becoming more the norm for personal computers.
 - Typically non-volatile, retains contents.
 - Data are available only in the sequence that the data were stored.
 - The time required to access a given part of memory is dependent on the memory location.
 - Average access time is typically much longer than that of random access memory.

Semiconductor Memories

Memory can also be classified by whether it is read/write or read-only memory.

Read/Write Memory (RAM):

- data can be stored and retrieved with relatively the same access time.
- RAM can be classified even more by Static RAM (SRAM) and Dynamic RAM (DRAM).


Read-Only Memory (ROM):

- has similarly fast retrieve times but restricted writing operations.
- employed in function that require table look-ups.
- employed in video game cartridges.
- low-level computer input/output or Basic Input/Output System (BIOS).

Semiconductor Memories

- Review and comparison of different types of memories.

Volatile	versus	Non-Volatile
Main Memory	versus	Mass Storage
Read/Write	versus	Read Only
Random Access	versus	Serial
Dynamic RAM	versus	Static RAM

 

Semiconductor Memories

Semiconductor Memories

Memory-Chip Organization:

- Random-access memory is typically organized into a two-dimensional grid (2^N by M) of cells that each store a single bit.
 - 2^N refers to the number of address lines (number of rows).
 - M refers to the number of bits per address line (number of columns).
 - a single address line is referred to as a **word line**.
- The bits are addressable (accessed) either individually ($M = 1$) or more generally in groups of powers of 2 ($M = 1, 2, 4, 8, 16, 32, 64$).

Semiconductor Memories

Example:

Consider **128 kbit block** of memory that is **byte addressable**.

We all know that **byte** refers to a group of **8 bits (M=8)**.

The total number of address lines is $128 \text{ kbit} / 8 = 128 \times 1024 / 8 = 16384 = 2^{14}$.

The memory requires a 14-bit address to retrieve a word line (N=14).

What if it is addressable in groups of 64 bits (M=64).

The total number of address lines is $128 \text{ kbit} / 64 = 2048 = 2^{11}$.

This memory would require an 11-bit address.

For both of these cases $N + \log_2(M) = 17$.

Semiconductor Memories

Let's look at this organization as a figure:

- **Memory Cell** – a single bit of the memory block.
- **N** – the number of address bits required by the **row decoder**.
- **M** – Width of the output word.
- **Word Line** – a single row of the memory block addressed by the row decoder.
 - each word line contains M bits.
 - there are a total of 2^N word lines.
- **Bit Lines (Digit Line)** – a single column of the memory block.
 - Input and output data lines

Random Access Memory (RAM) Cells

The RAM Memory Cell (bit):

- **Connections** – Each memory cell has 3 to 4 connections:
 - 1. The **word line** is attached to the output of **row decoder** and is used to **select** (activate or connect) **a row of cells**.
 - » This is an **input only** to the memory cell.
 - » when **high connects** the **row** of cells to the **bit lines & write enable**.

Random Access Memory (RAM) Cells

The RAM Memory Cell (bit):

- ***Basic Operation*** – the word line selects a memory row and activates the **access transistor(s)** providing an active connection to the bit lines.
- ***Structure*** – the structure of the memory cell depends on the type of RAM, which can be either **static (SRAM)** or **dynamic (DRAM)**.

Random Access Memory (RAM) Cells

Static Random Access Memory (SRAM):

- Utilize static latches as the storage mechanism.
- A basic configuration for this static memory bit is:
 - the **memory component**: the **simple CMOS clocked Latch (~16 Transistors)**
 - the **input/output component**: 2 access transistors.
 - **And gate for write enable**: 8 transistors.
 - Total of **26 Transistors** per bit.

The SRAM Read Operation:

- the read operation is non-destructive and the data is retained.

The SRAM Write Operation:

- The bit lines are charge to VDD or 0 depending on what is written.

Random Access Memory (RAM) Cells

Dynamic Random Access Memory (DRAM):

- Utilize capacitors as the storage mechanism.
- A basic configuration is a capacitor attached to the bit lines via an **access transistor**.
 - the **memory component**: a capacitor.
 - the **input/output component**: an access transistor.
- Capacitors discharge (there is no getting around this) so the DRAM memory cell must be periodically recharged by performing a read operation and then writing this data back into the memory.

The DRAM Read Operation

- the read operation is destructive and the data is lost from the cell. This cell is refreshed by what was read.
- the read operation must also include a write operation.

The DRAM Write Operation

- The bit lines are charge to VDD or 0 depending on what is written.

Random Access Memory (RAM) Cells

Comparisons between SRAM and DRAM.

Advantages of DRAM

- Less Complex
- Less Space
- Less Cost

Advantages of SRAM

- Faster
- Lower Power
- No refresh is required
- Non-destructive read operation

Random Access Memory (RAM) Cells

Address Decoder

Operation

- For N address bits, there will be 2^N possible word lines.
- Each word line is a combinational logic function of the N inputs:
 - For N=3 (pull down n equations)
 - $\text{not}(y_0) = A_2 + A_1 + A_0$
 - $\text{not}(y_1) = A_2 + A_1 + \text{not}(A_0)$
 - $\text{not}(y_2) = A_2 + \text{not}(A_1) + A_0$
 - $\text{not}(y_3) = A_2 + \text{not}(A_1) + \text{not}(A_0)$
 - ...
- there will be 2^3 equation each requiring 3 Transistors for the PDN and 3 for the PUN, plus 3 inverters (6 Transistors)
- In General, the Address Decoder will have a Total of $(2^N)(2N) + 2N$ Transistor.