

Diode Content and Equations

Diode Symbol, Terminal Names, Voltage and Current Orientations

Ideal Diode:

FB: $v_D = 0$, for $i_D > 0$

RB: $i_D = 0$, for $v_D < 0$

Model

Short

Open

Junction Diode:

$i_D = I_S(\exp(v_D/nV_T) - 1)$, for both FB and RB

Range of values for I_S (1×10^{-8} to 1×10^{-15} [Amps]) and n (1 to 2).

V_T is dependent on temperature (Typically 0.025V)

FB approximation ($v_D \gg nV_T$):

$i_D = I_S \exp(v_D/nV_T)$

RB approximation ($v_D \ll -nV_T$):

$i_D = -I_S$

0.7V CVD Model:

FB: $v_D = 0.7V$, for $i_D > 0$

RB: $i_D = 0$, for $v_D < 0.7V$

RB: Open or FB: 0.7V Battery

Short in series with 0.7V Battery (ideal diode is FB)

Open in series with 0.7V Battery (ideal diode is RB, $v_{DI} < 0$)

PWL Model:

FB: $i_D = (v_D - V_{D0})/r_D$, for $v_D > V_{D0}$

RB: $i_D = 0$, for $v_D < V_{D0}$

RB: Open or FB: Resistor and Battery

Short in series with Resistor and Battery

Open in series with Resistor and Battery

Small Signal Diode Model:

$r_d = nV_T/I_D$

always assume the diode is FB for small signal analysis problems

Small Signal resistance given $i(v)$ $r = 1/i'_D(v_D)$ evaluated at (V_D, I_D)

Know the table of devices and their Large Signal Model and Small Signal Model

Zener Diode (CVD Model):BD: $v_Z = V_Z$, for $i_Z > 0$ RB: $i_Z = 0$, for $v_Z < V_Z$ **Ideal Diode in series with a Battery**

Short in series with a Battery (ideal diode is FB)

Open in series with a Battery (ideal diode is RB, $v_{DI} < 0$)**Zener Diode (PWL Model):**BD: $i_Z = (v_Z - V_{Z0})/r_Z$, for $v_Z > V_{Z0}$ RB: $i_Z = 0$, for $v_Z < V_{Z0}$ **Ideal Diode in series with Resistor and Battery**

Short in series with Resistor & Battery (ideal diode is FB)

Open in series w/ Res. & Battery (ideal diode is RB, $v_{DI} < 0$)

Zener Symbol and Voltage & Current Orientations

Difference and Similarities between Zener and Junction Diodes

Diode Applications (what is the purpose, basic circuit and basic operation)

Current Protection

Simple Digital Logic

Limiters (Circuit Protection) – Transfer Functions**Rectifier Circuits (v_{OUT}/v_{IN} , PIV)****Regulator (line regulation, load regulation)****AC/DC Supply (approximation for ripple voltage)****Voltage Controlled Attenuator**

Frequency Mixer

Semiconductors

Silicon lattice (intrinsic, covalent bonds).

Current (two types)

Drift – charge moving due to electric field.

Diffusion – charge moving due to heat and concentration gradient.

Doped Silicon

N-Type: use Phosphorus to add extra electrons.

P-Type: use Boron to add extra holes.

Majority carriers

Minority carriers

Depleted

PN Junction and Bias States (FB, RB, Breakdown)

Exam I Organization

Around 4-5 Problem Sections

- Diode analysis at DC:** Given a circuit, assume a bias, find the answer, & verify bias.
- Diode Transfer Function:** Given a circuit, assume a bias, find the transfer function, and find the range of the independent variable.
- Diode Small Signal Analysis:** Large Signal Circuit, Small Signal Resistance, Small Signal Relationship.
- Short Answer Section:** True or False, Calculations (maybe using exponential model), General Application Questions (line regulation, Peak Inverse Voltage, Ripple Voltage, ...), AC/DC Supplies, Quick Analysis, Concept Understanding.

Semiconductor Examples:

HW8. (Concepts, not specific equations)

What are majority carriers in N-type silicon?

What direction does positive drift current flow in the PN junction?

When a P-Type silicon becomes depleted it will be positively charged. True or False.