

$V_{S1} = 3V$

$R_1 = 370\Omega$

$R_3 = 420\Omega$

V_1

$R_2 = 450\Omega$

$\underline{\underline{}}$

I_1

$V_1 = -0.846,$


$I_1 = -1.88mA,$

$I_2 = 12.271mA$


I_2

$V_{S2} = -6V$


(b)

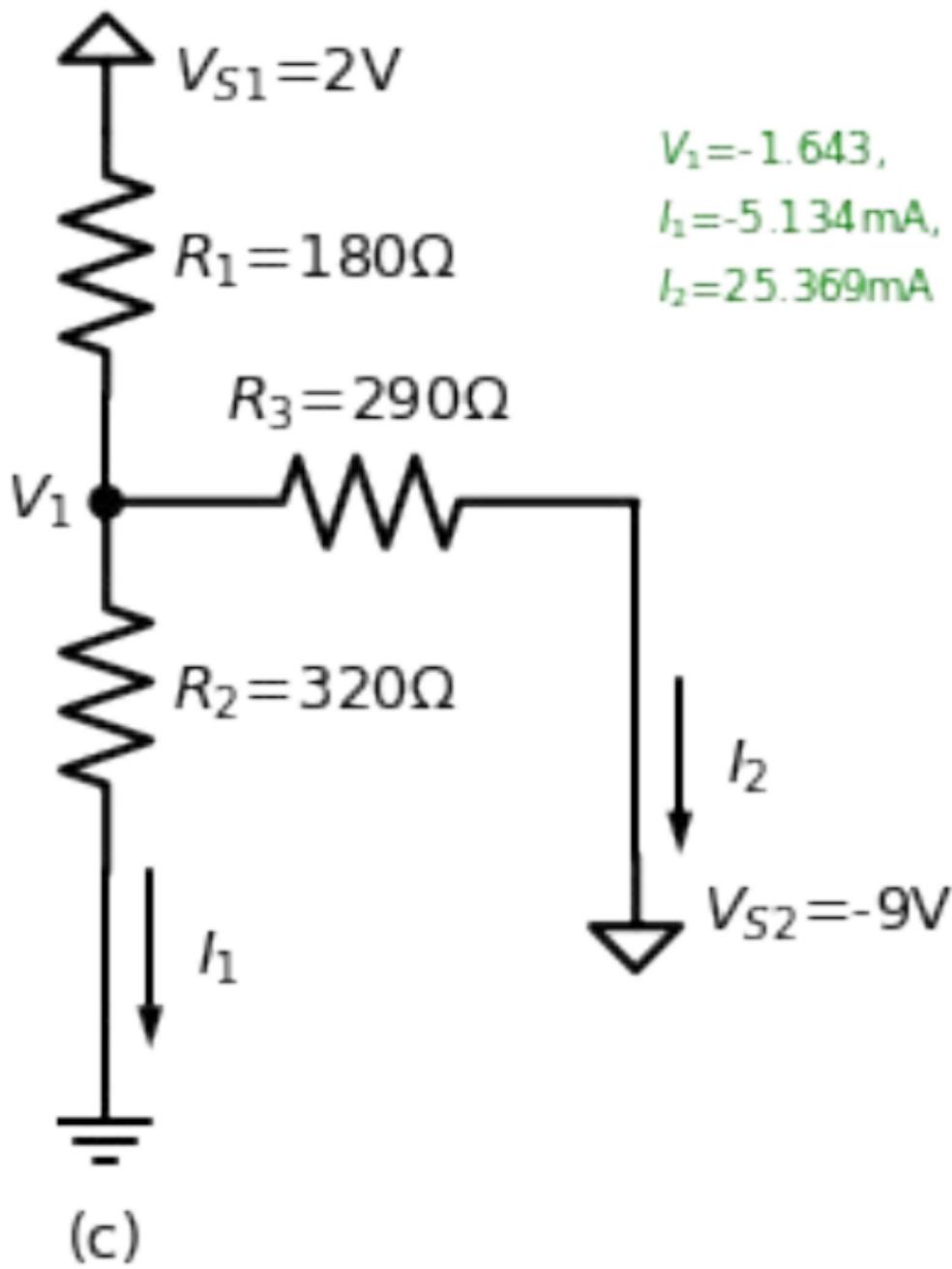


(c)

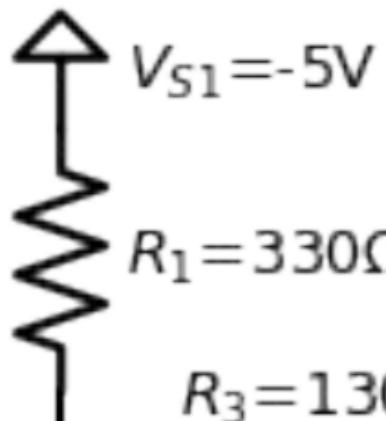
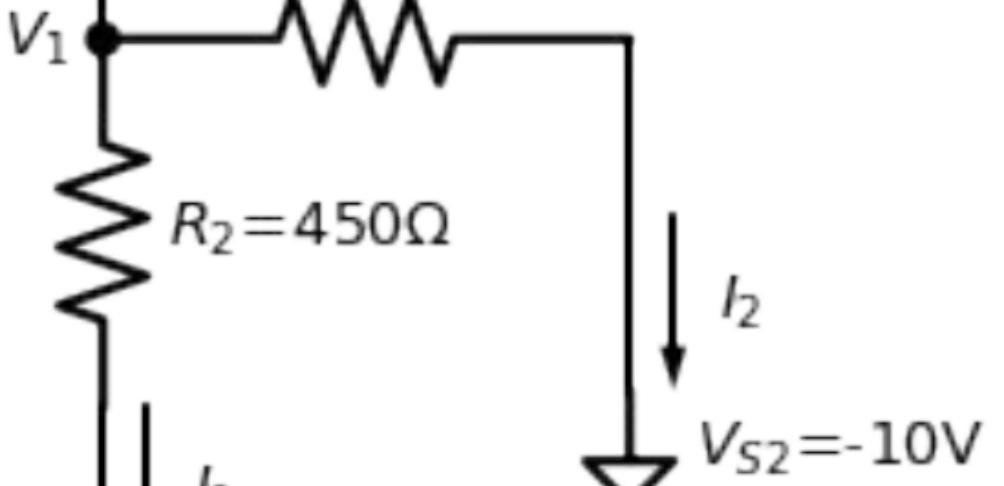
$$V_1 = -7.113,$$
$$I_1 = -15.807\text{mA},$$
$$I_2 = 22.208\text{mA}$$



(d)

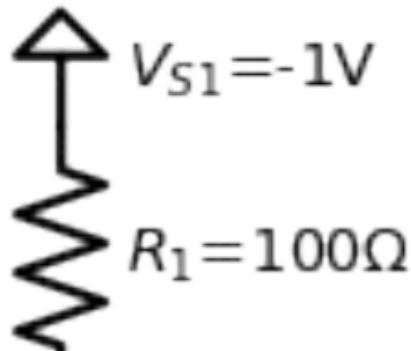

$$R_1 = 100\Omega$$


$$R_3 = 330\Omega$$

$$R_2 = 200\Omega$$


$$I_1$$

$$\begin{aligned}V_1 &= -2.235, \\I_1 &= -11.175\text{mA}, \\I_2 &= 23.53\text{mA}\end{aligned}$$

(e)

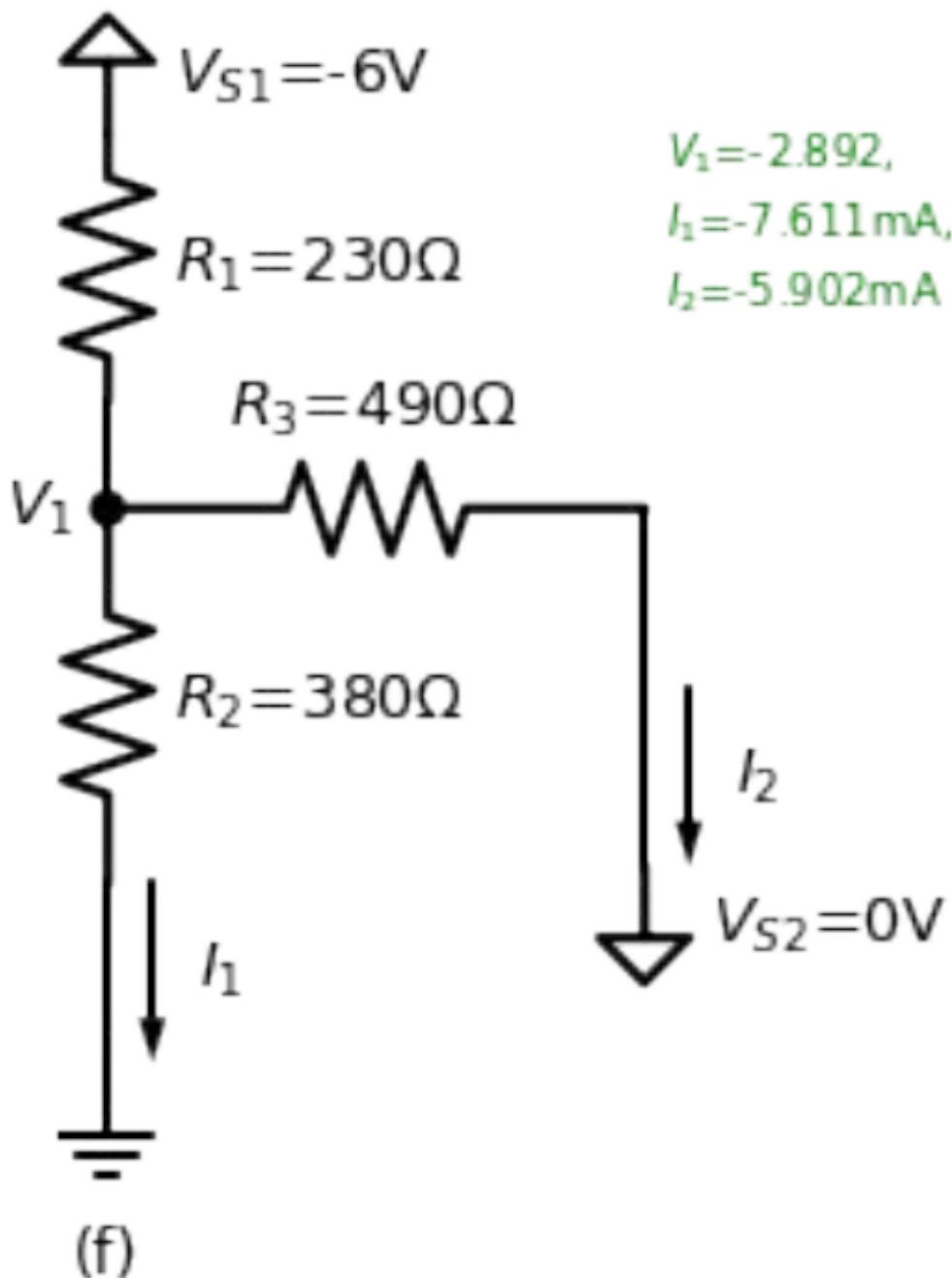

(f)

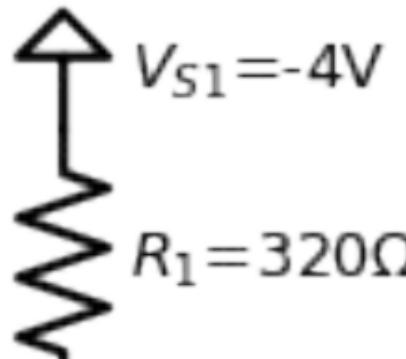


$$R_3 = 300\Omega$$

V_1


$$\begin{aligned}V_1 &= 2.451, \\I_1 &= 5.002\text{mA}, \\I_2 &= -25.163\text{mA}\end{aligned}$$



$$R_2 = 490\Omega$$

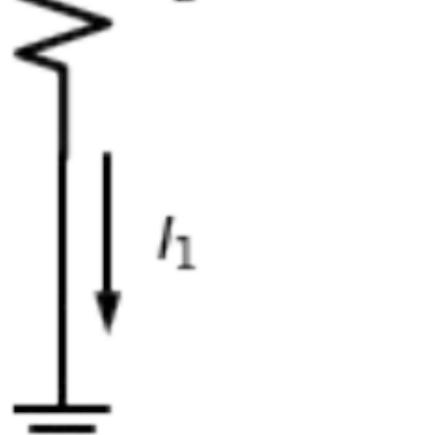


I_1

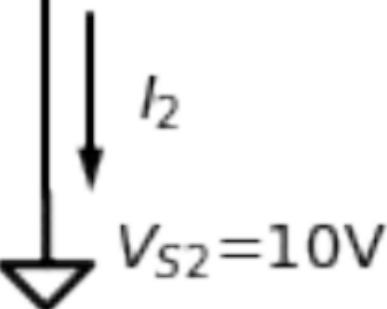

$$V_{S2} = 10V$$

(g)

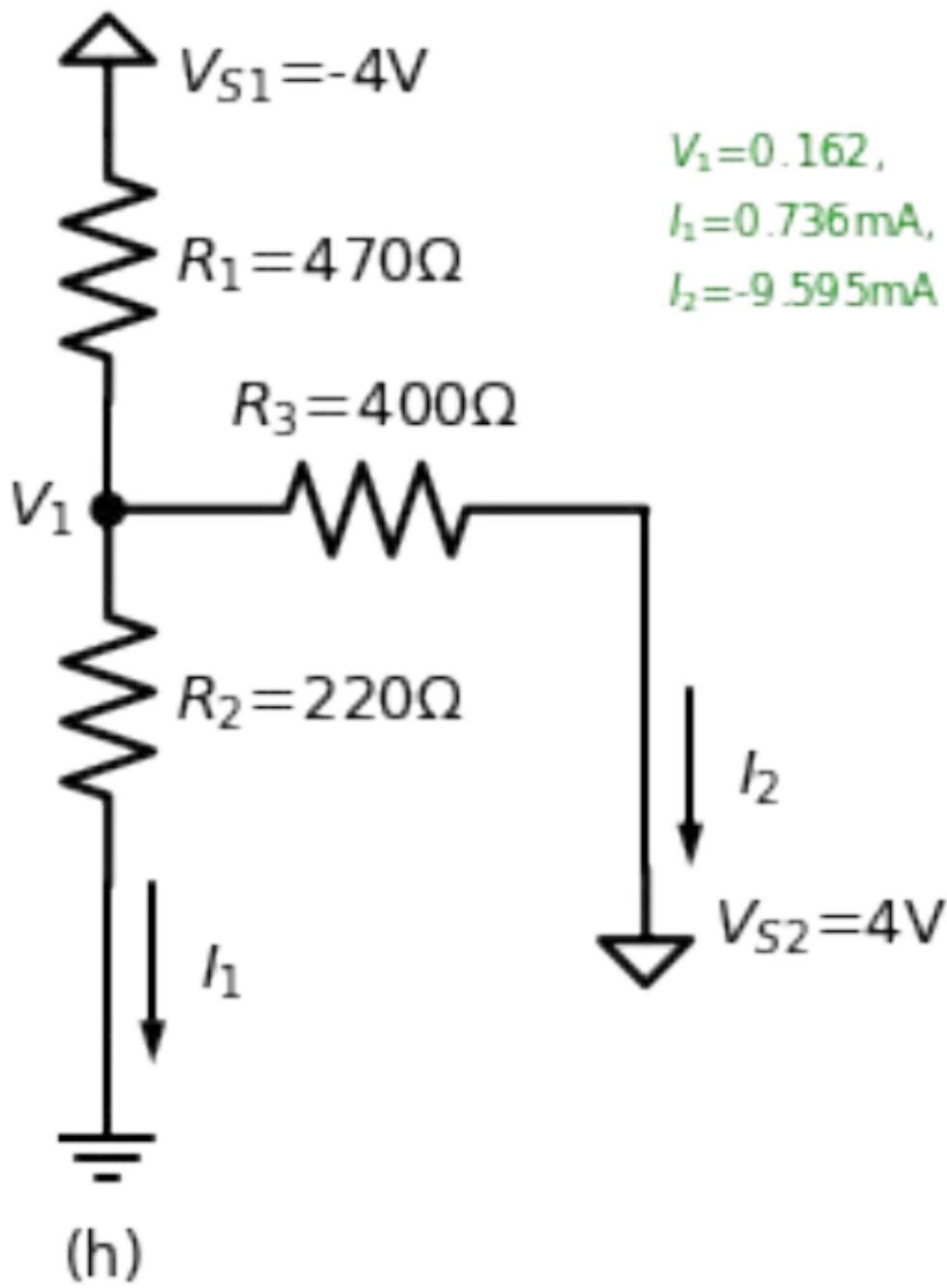

(h)