

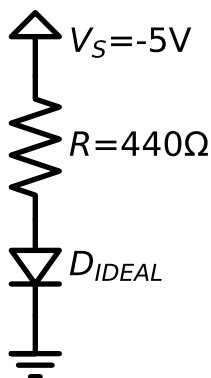
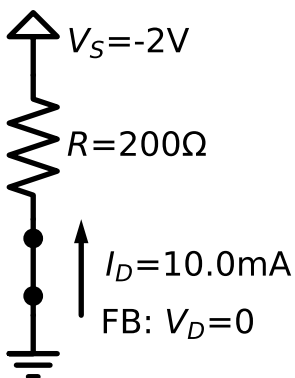




(a)

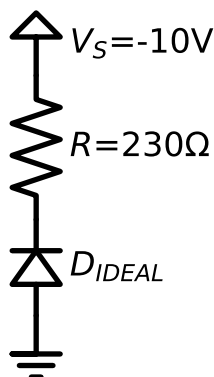



(b)

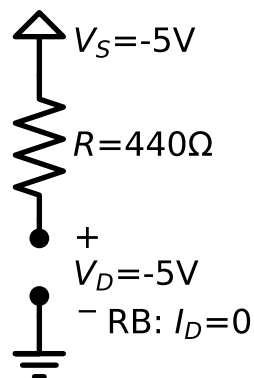



(c)

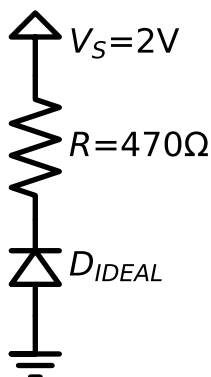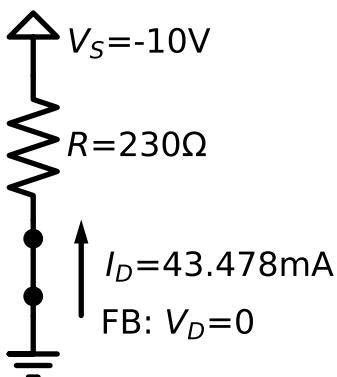


(d)

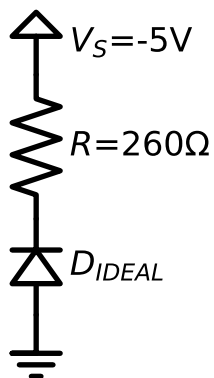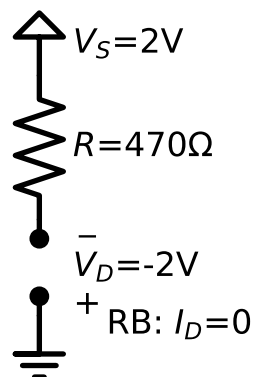


(e)

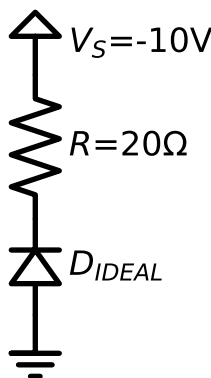
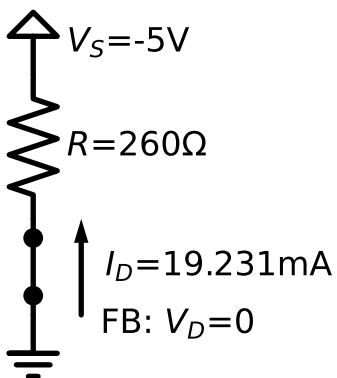


(f)


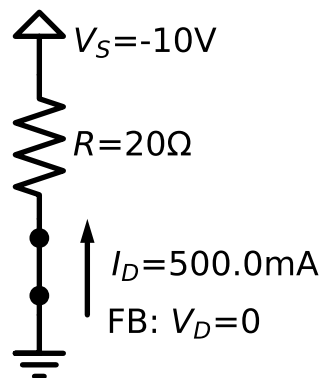


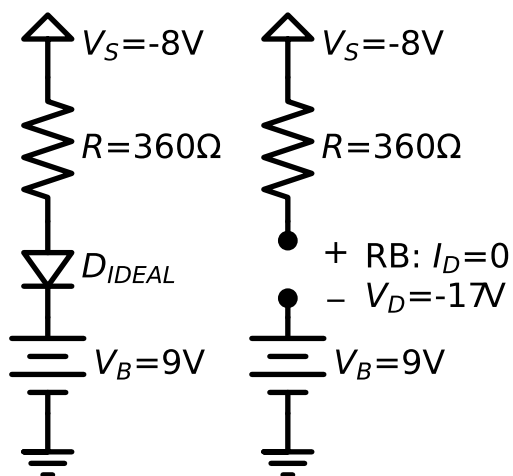



(a)

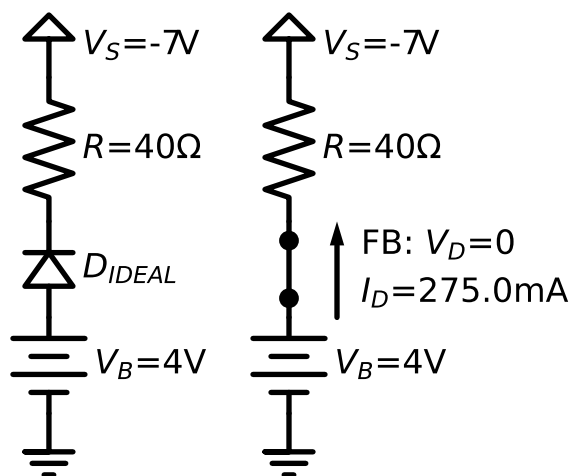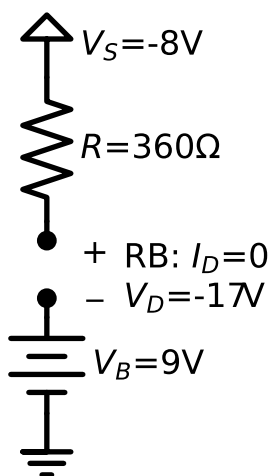



(b)

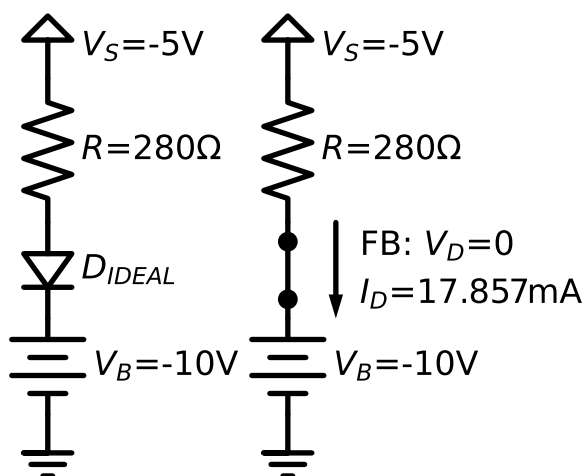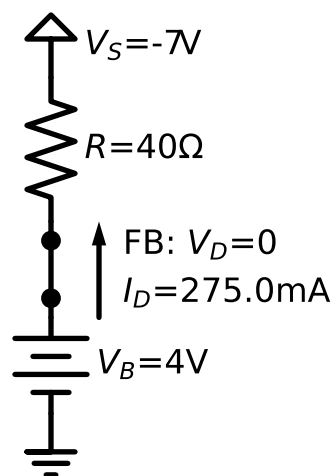



(c)

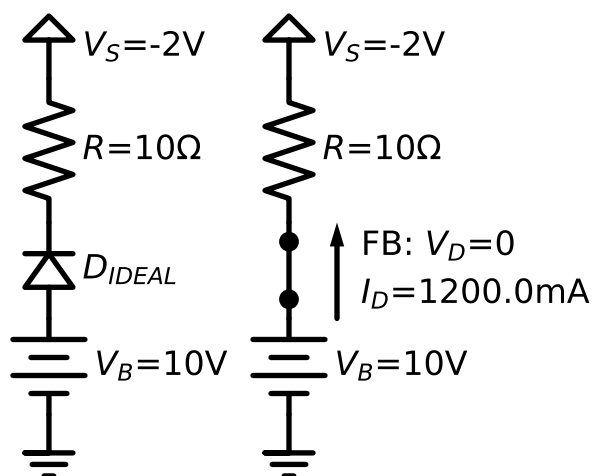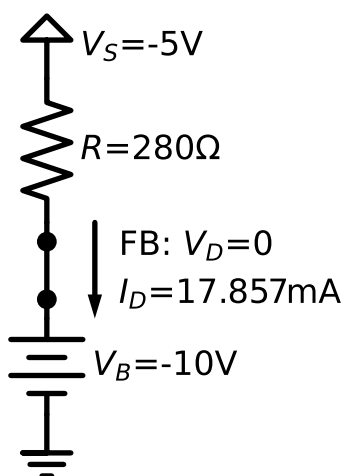


(d)

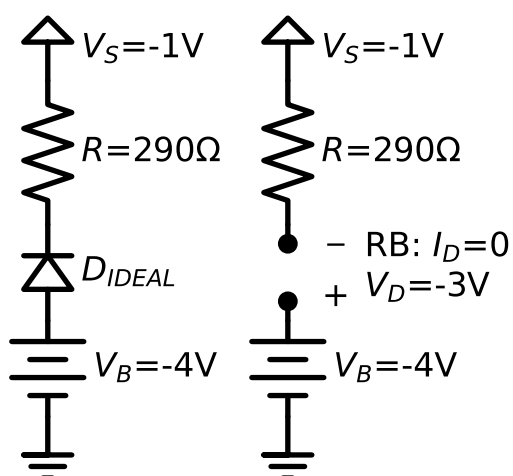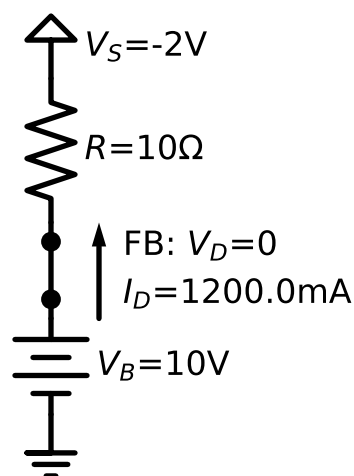


(e)

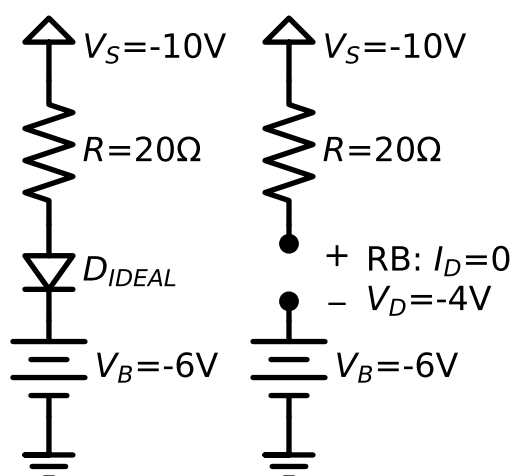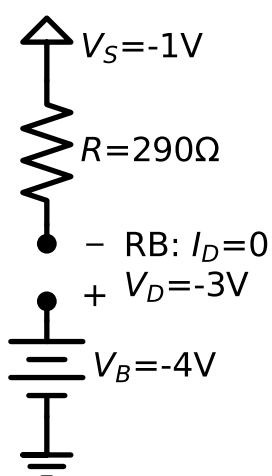

(f)

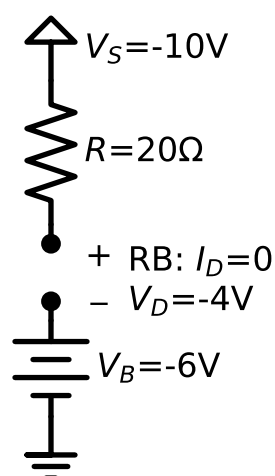

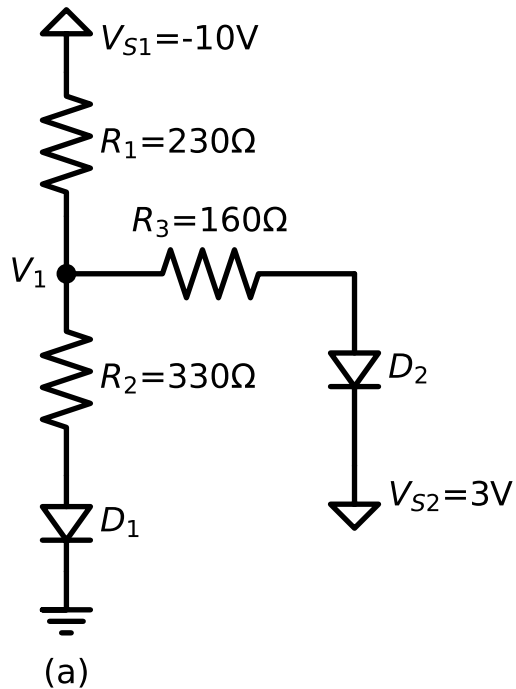

case1: FB, FB: $V_1 = -1.815$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = -5.5mA > 0$, False

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = -30.094mA > 0$, False

case2: FB, RB: $V_1 = -5.893$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = -17.858mA > 0$, False

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = -8.893V \leq 0$, True

case3: RB, FB: $V_1 = -2.333$


D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = -2.333V \leq 0$, True

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = -33.331mA > 0$, False

case4: RB, RB: $V_1 = -10.0$

D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = -10.0V \leq 0$, True

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = -13.0V \leq 0$, True

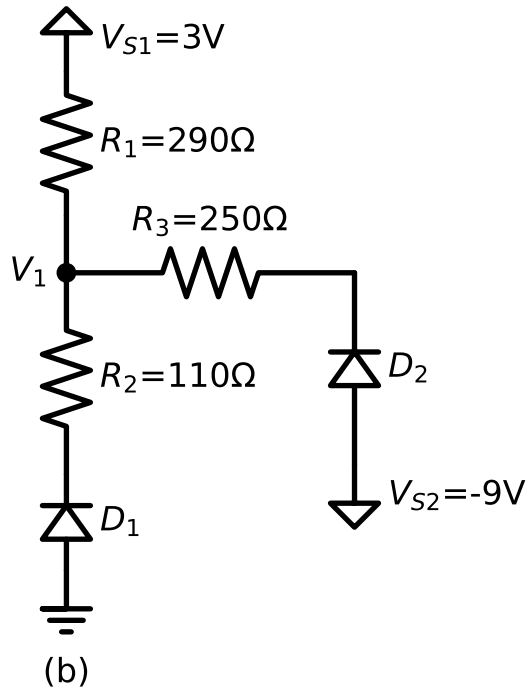

case1: FB, FB: $V_1 = -1.551$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = 14.1mA > 0$, True

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = -29.796mA > 0$, False

case2: FB, RB: $V_1 = 0.825$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = -7.5mA > 0$, False

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = -9.825V \leq 0$, True

case3: RB, FB: $V_1 = -3.444$


D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = 3.444V \leq 0$, False

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = -22.224mA > 0$, False

case4: RB, RB: $V_1 = 3.0$

D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = -3.0V \leq 0$, True

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = -12.0V \leq 0$, True

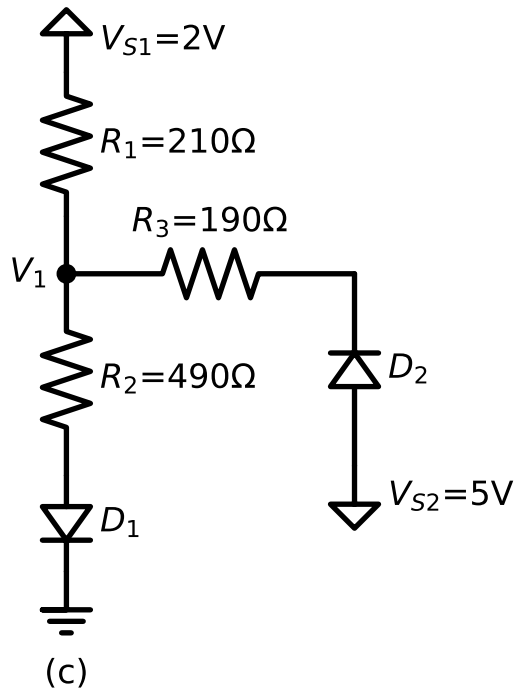

case1: FB, FB: $V_1 = 2.97$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = 6.061mA > 0$, True

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = 10.684mA > 0$, True

case2: FB, RB: $V_1 = 1.4$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = 2.857mA > 0$, True

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = 3.6V \leq 0$, False

case3: RB, FB: $V_1 = 3.575$


D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = 3.575V \leq 0$, False

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = 7.5mA > 0$, True

case4: RB, RB: $V_1 = 2.0$

D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = 2.0V \leq 0$, False

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = 3.0V \leq 0$, False

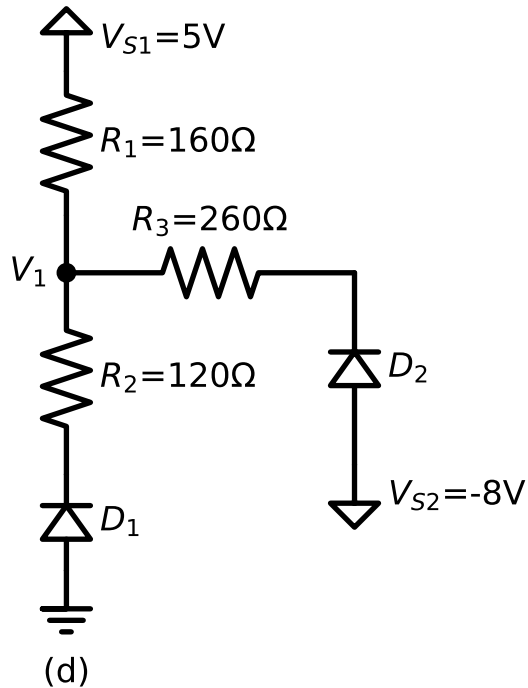

case1: FB, FB: $V_1 = 0.026$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = -0.217mA > 0$, False

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = -30.869mA > 0$, False

case2: FB, RB: $V_1 = 2.143$

D_1 :FB, $V_{D1} = 0V$ (short), $I_{D1} = -17.858mA > 0$, False

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = -10.143V \leq 0$, True

case3: RB, FB: $V_1 = 0.048$

D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = -0.048V \leq 0$, True

D_2 :FB, $V_{D2} = 0V$ (short), $I_{D2} = -30.954mA > 0$, False

case4: RB, RB: $V_1 = 5.0$

D_1 :RB, $I_{D1} = 0V$ (open), $V_{D1} = -5.0V \leq 0$, True

D_2 :RB, $I_{D2} = 0V$ (open), $V_{D2} = -13.0V \leq 0$, True