

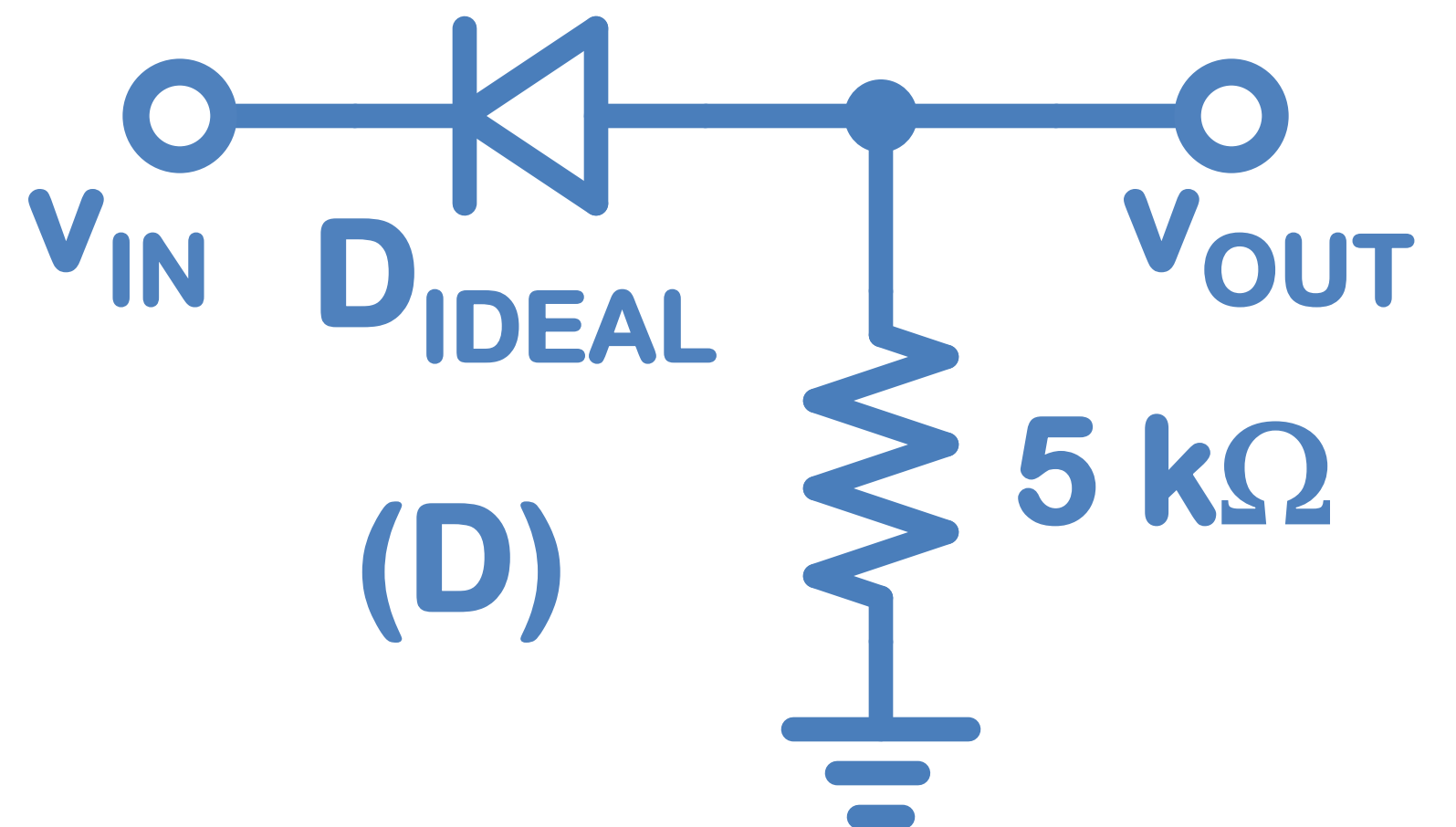
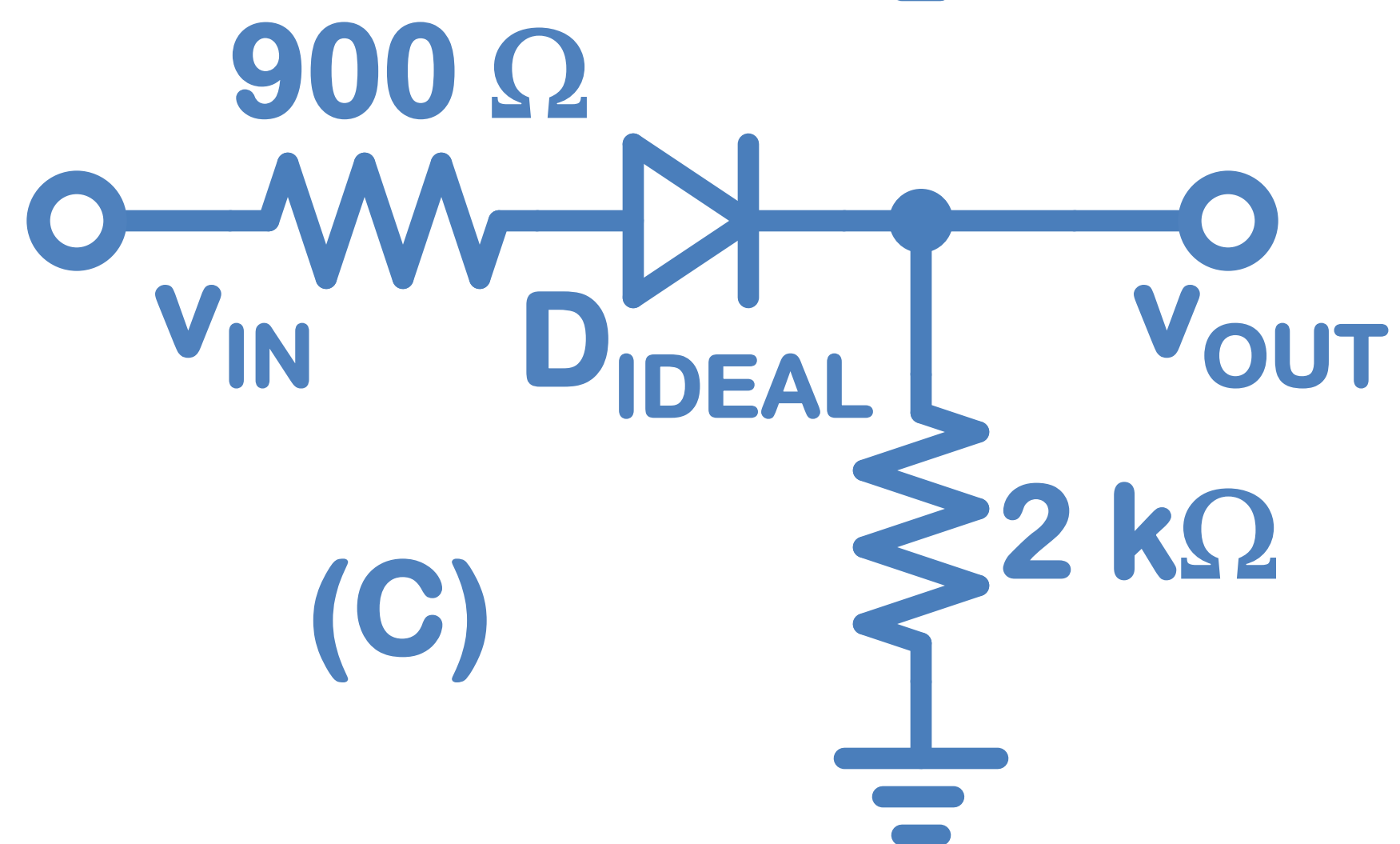
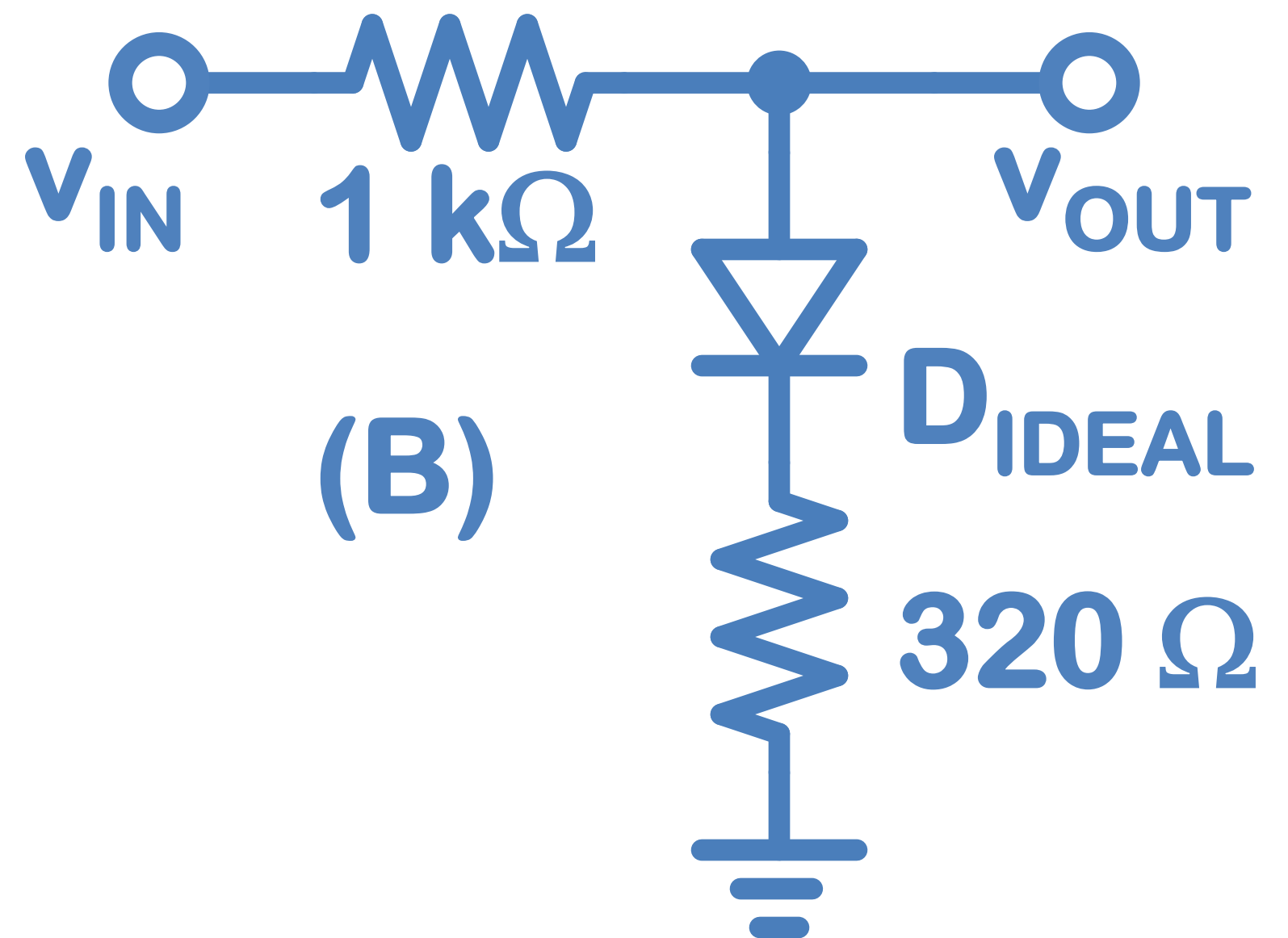
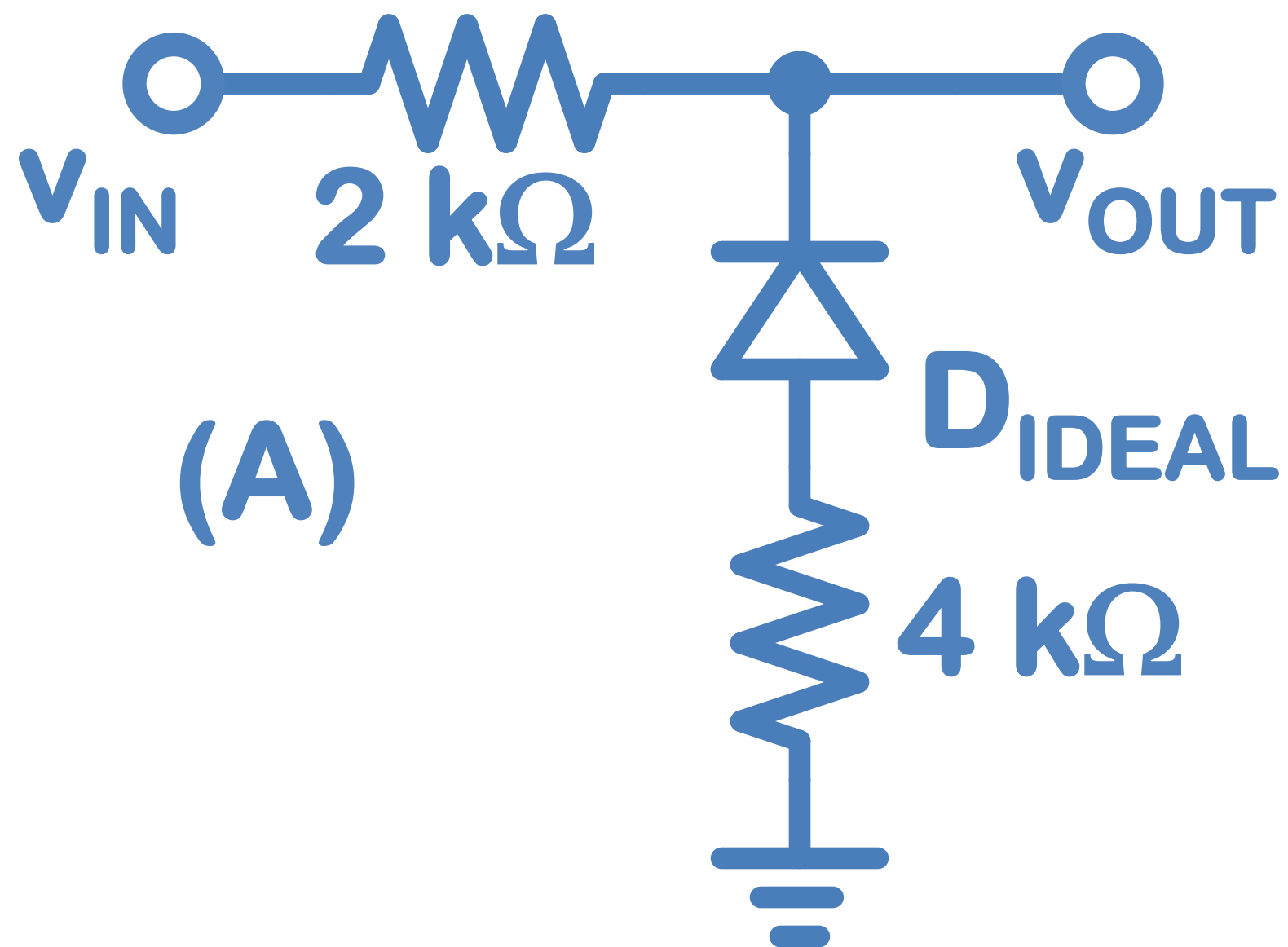


Problem 1. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.

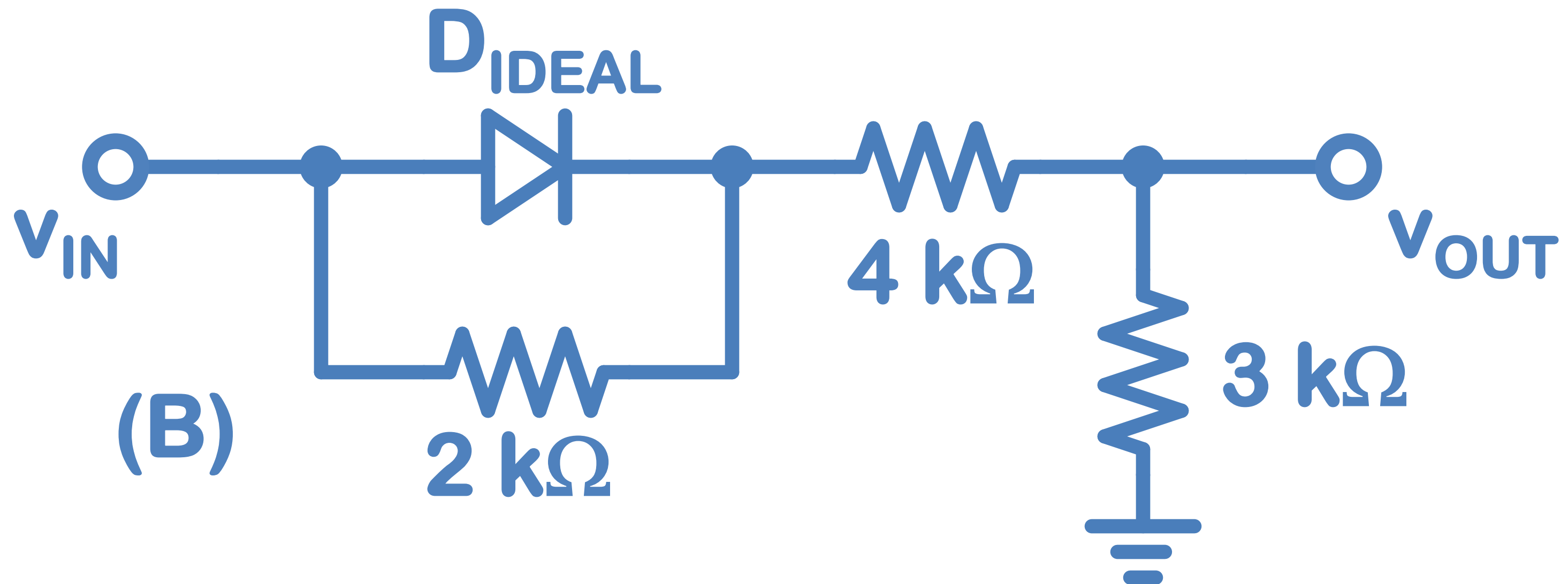

Problem 2.

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.

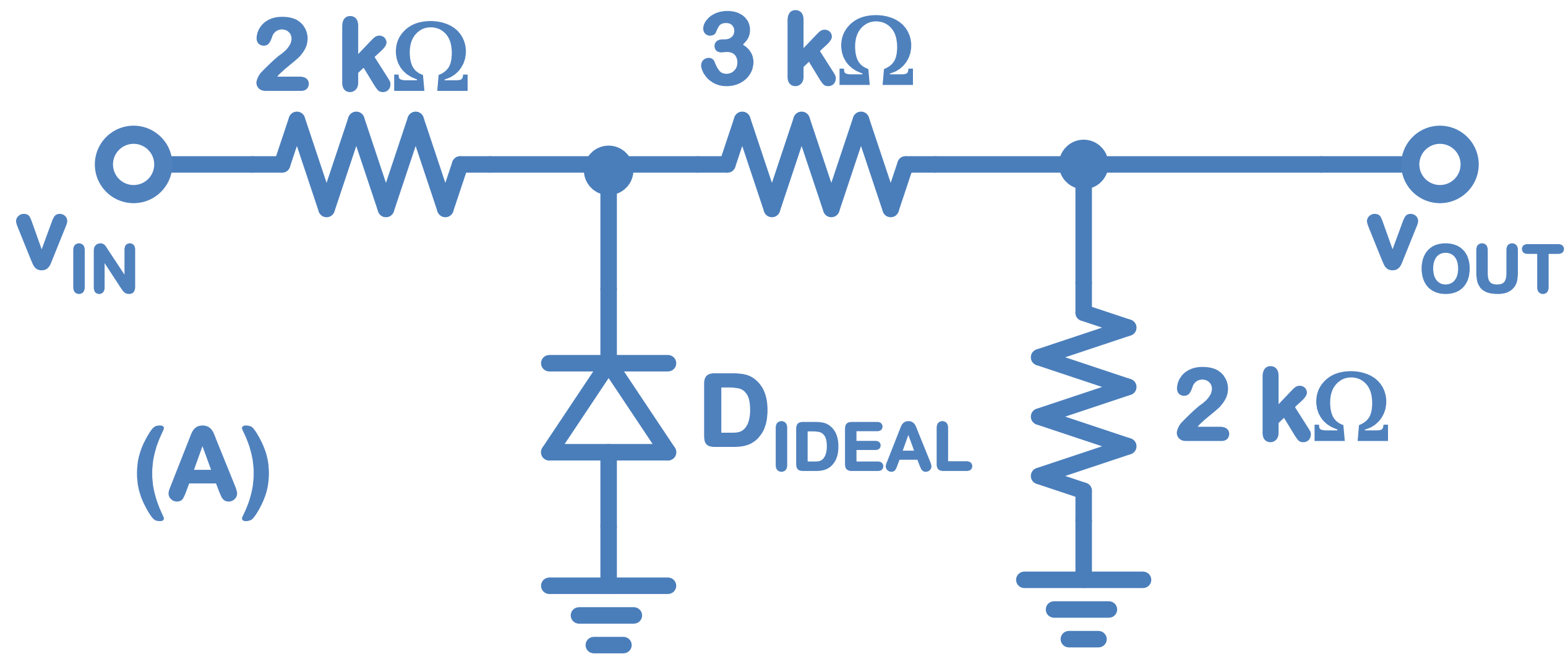

Problem 3.

Find the equation and plot $v_{\text{OUT}}(v_{\text{IN}})$ for the circuit.

