

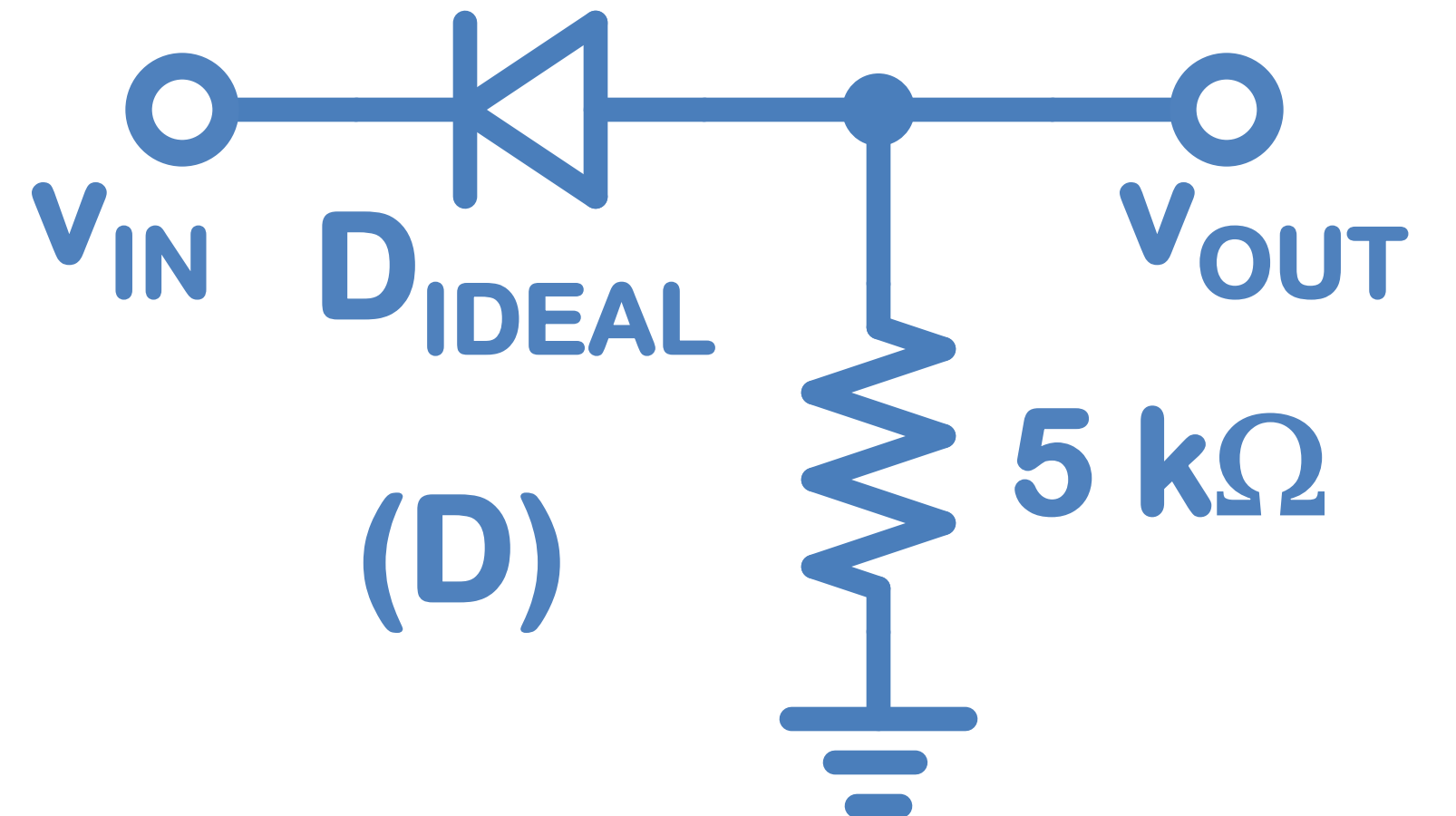
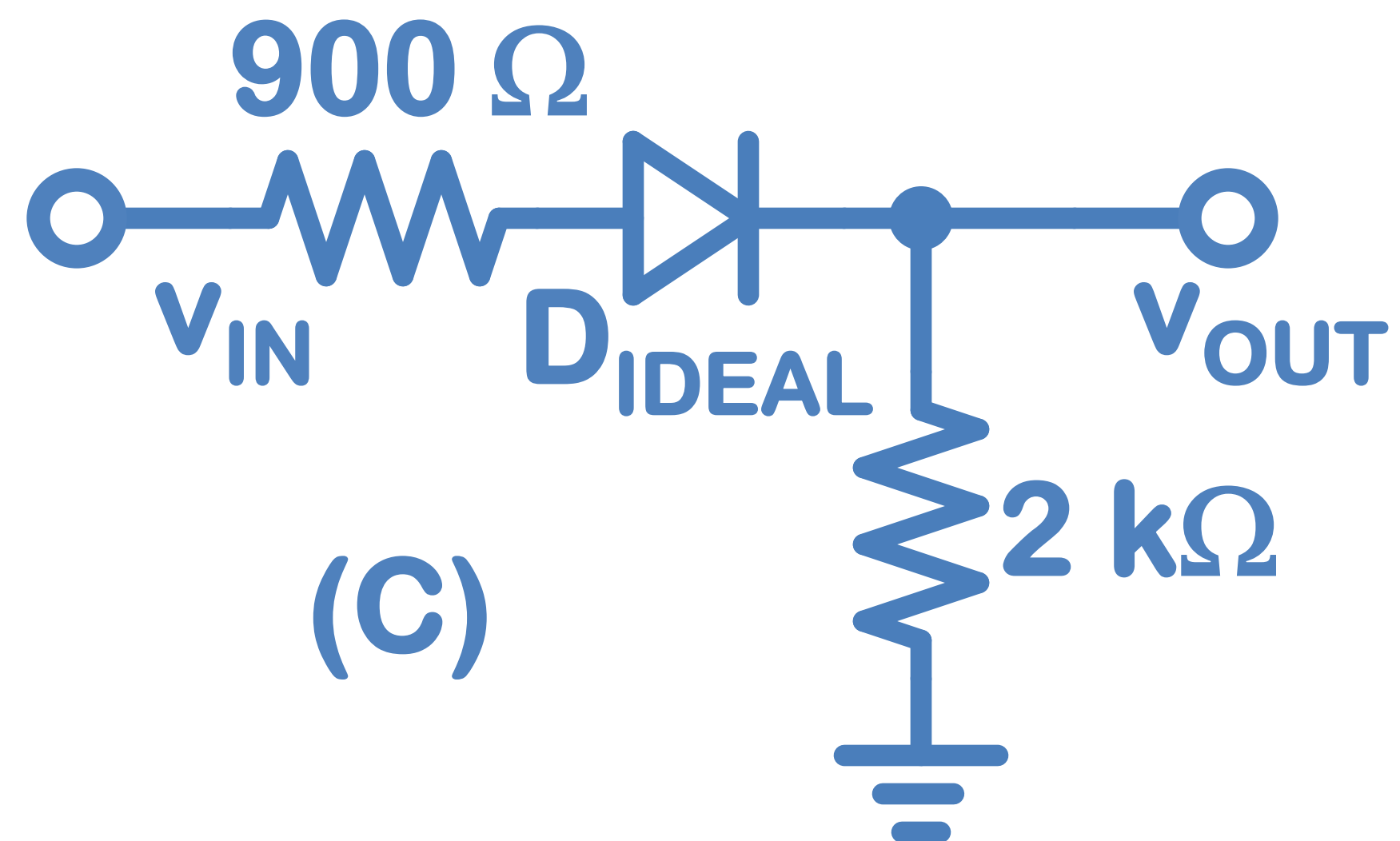
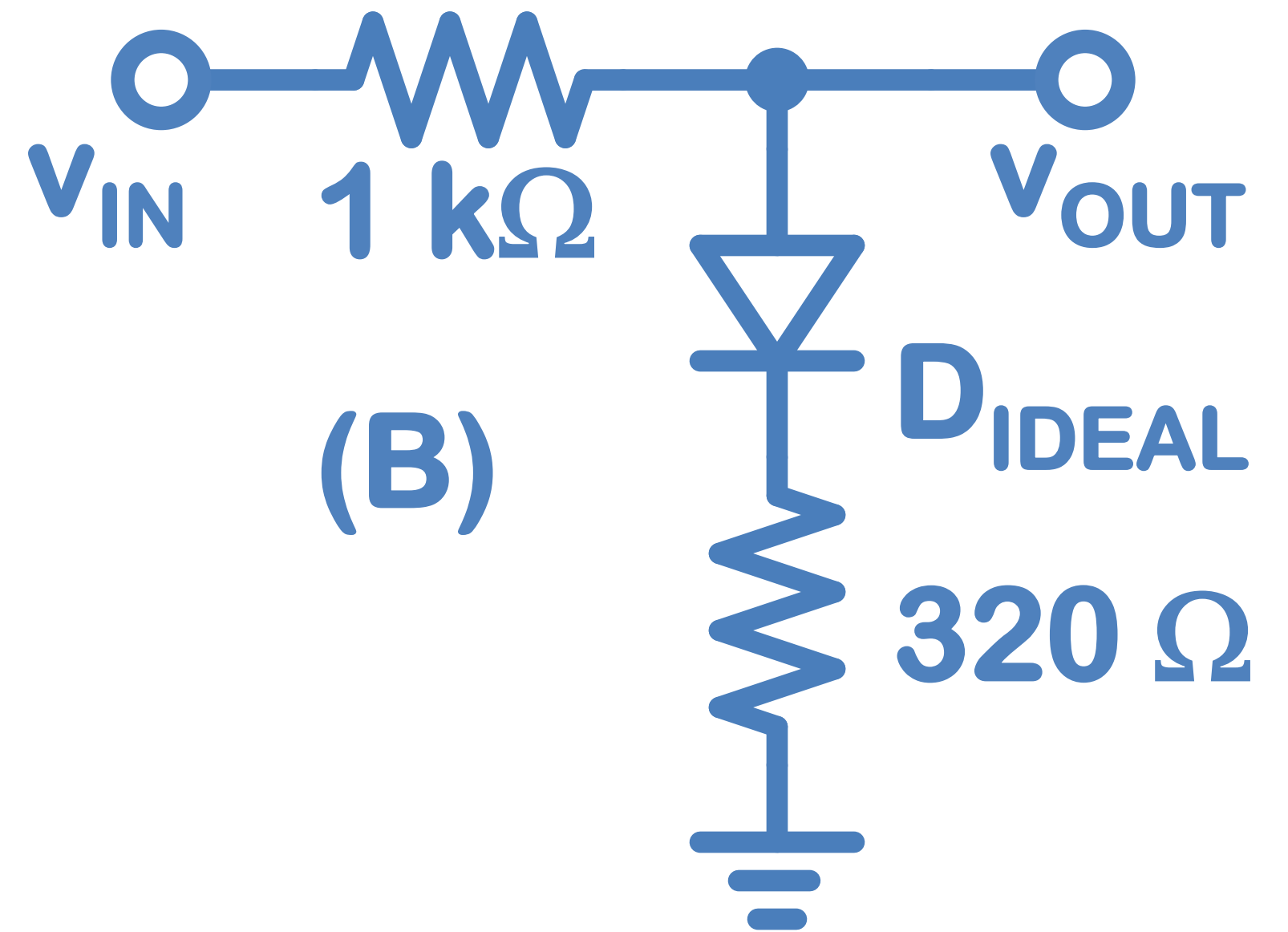


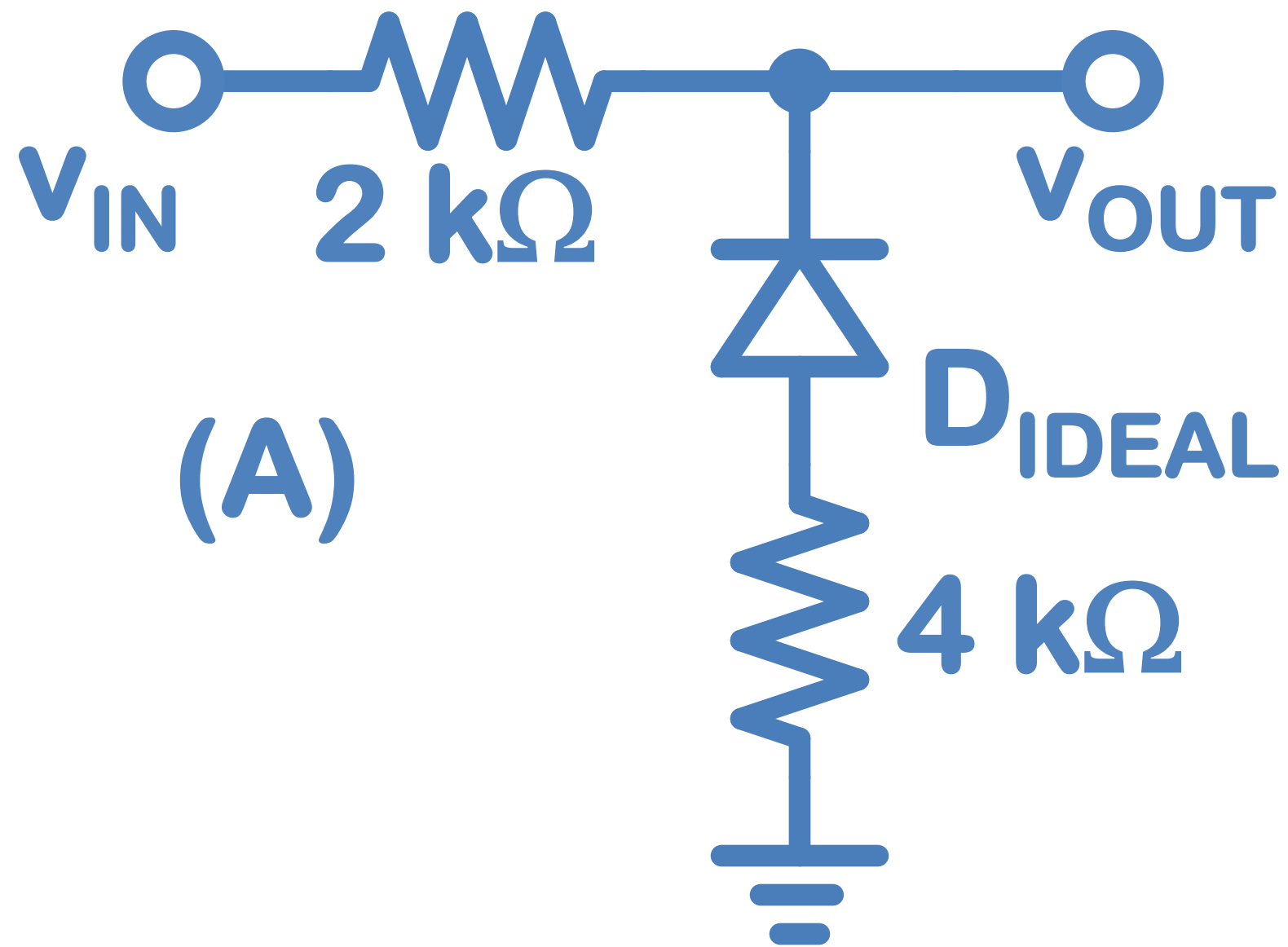Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(A)

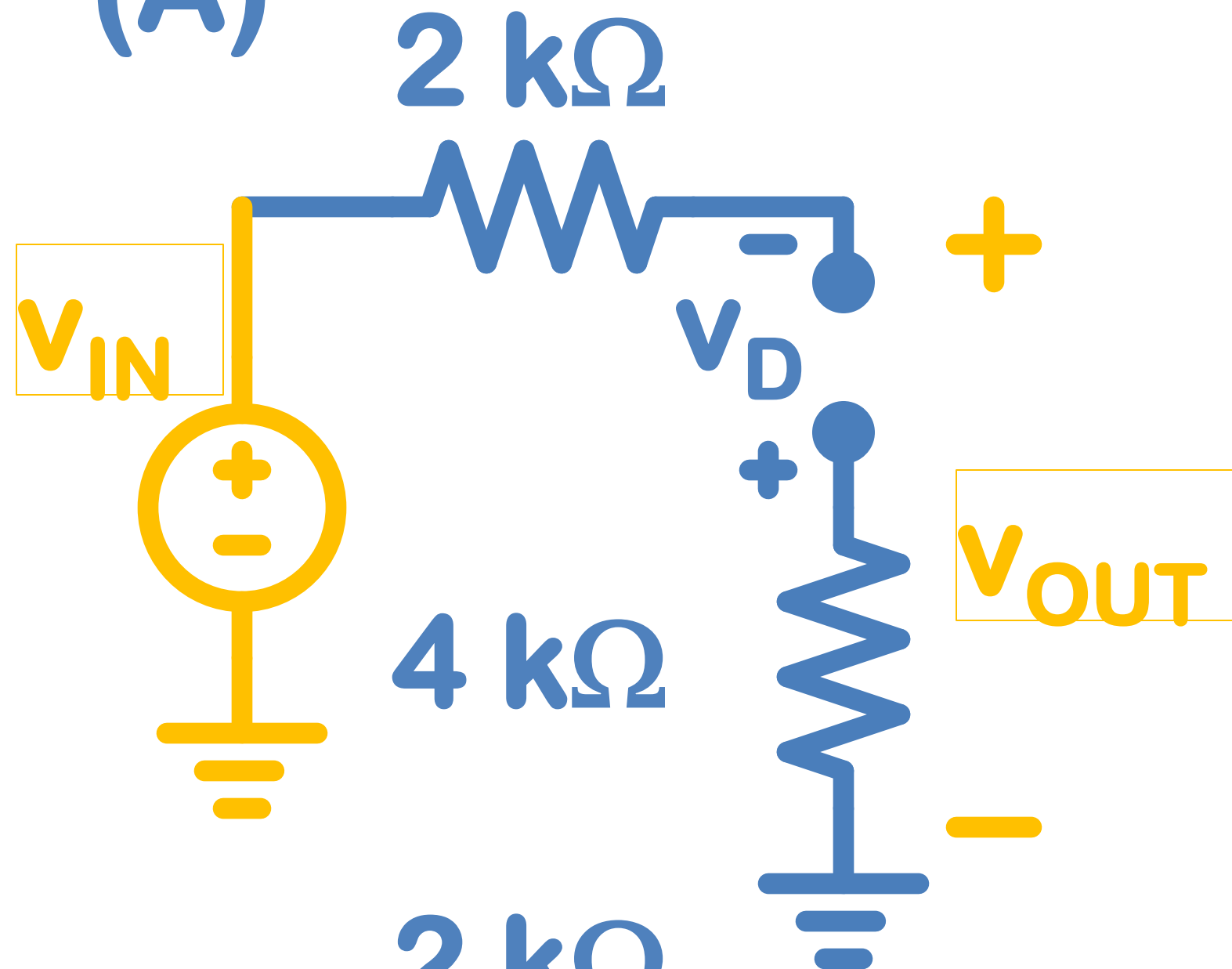

$$v_{OUT} = v_{IN}$$

$$v_D = -v_{IN}$$

$$v_D < 0, \text{ when } v_{IN} > 0$$

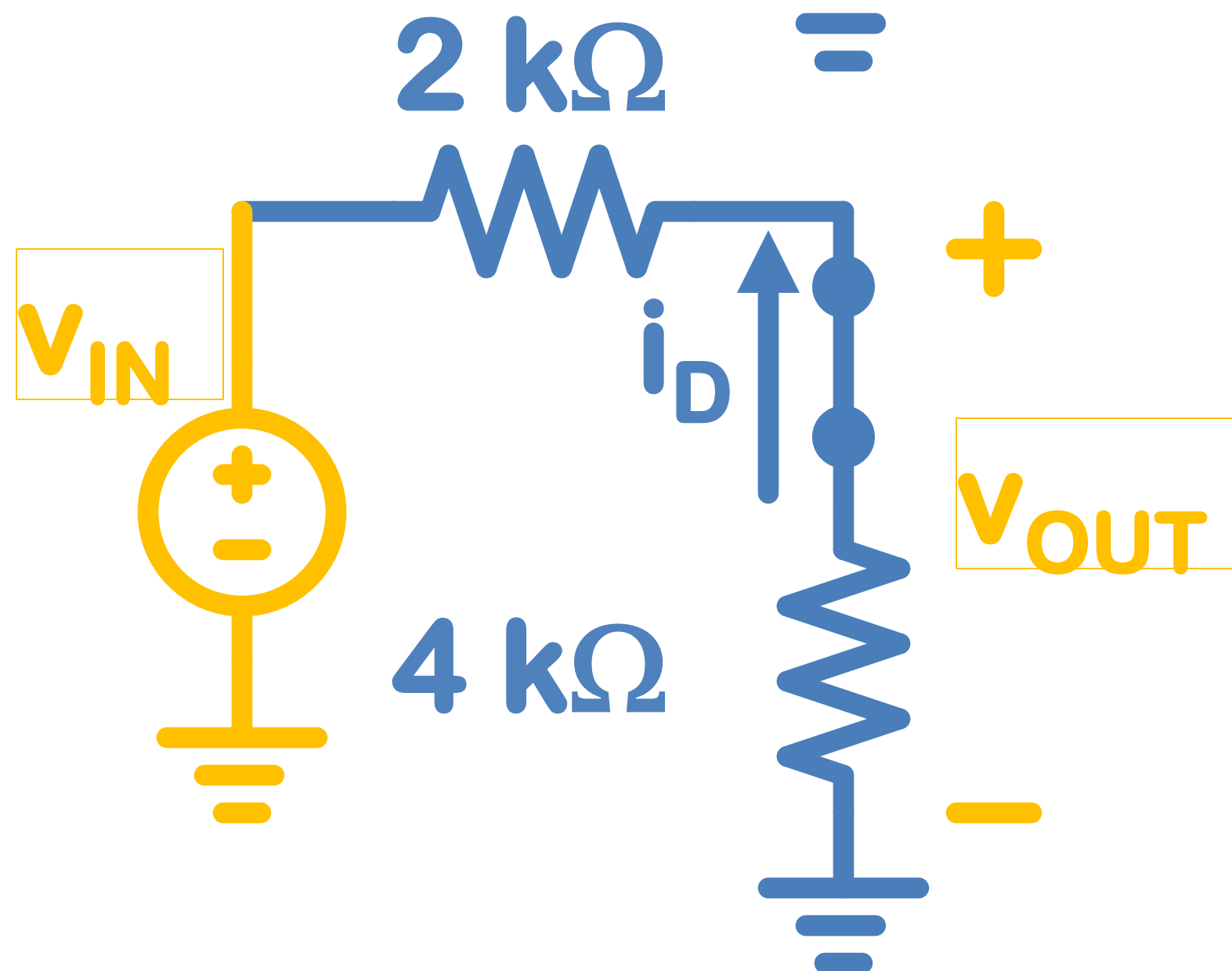


$$v_{OUT} = 0.67 v_{IN}$$

$$i_D = -v_{IN} / 6000$$

$$i_D > 0, \text{ when } v_{IN} < 0$$

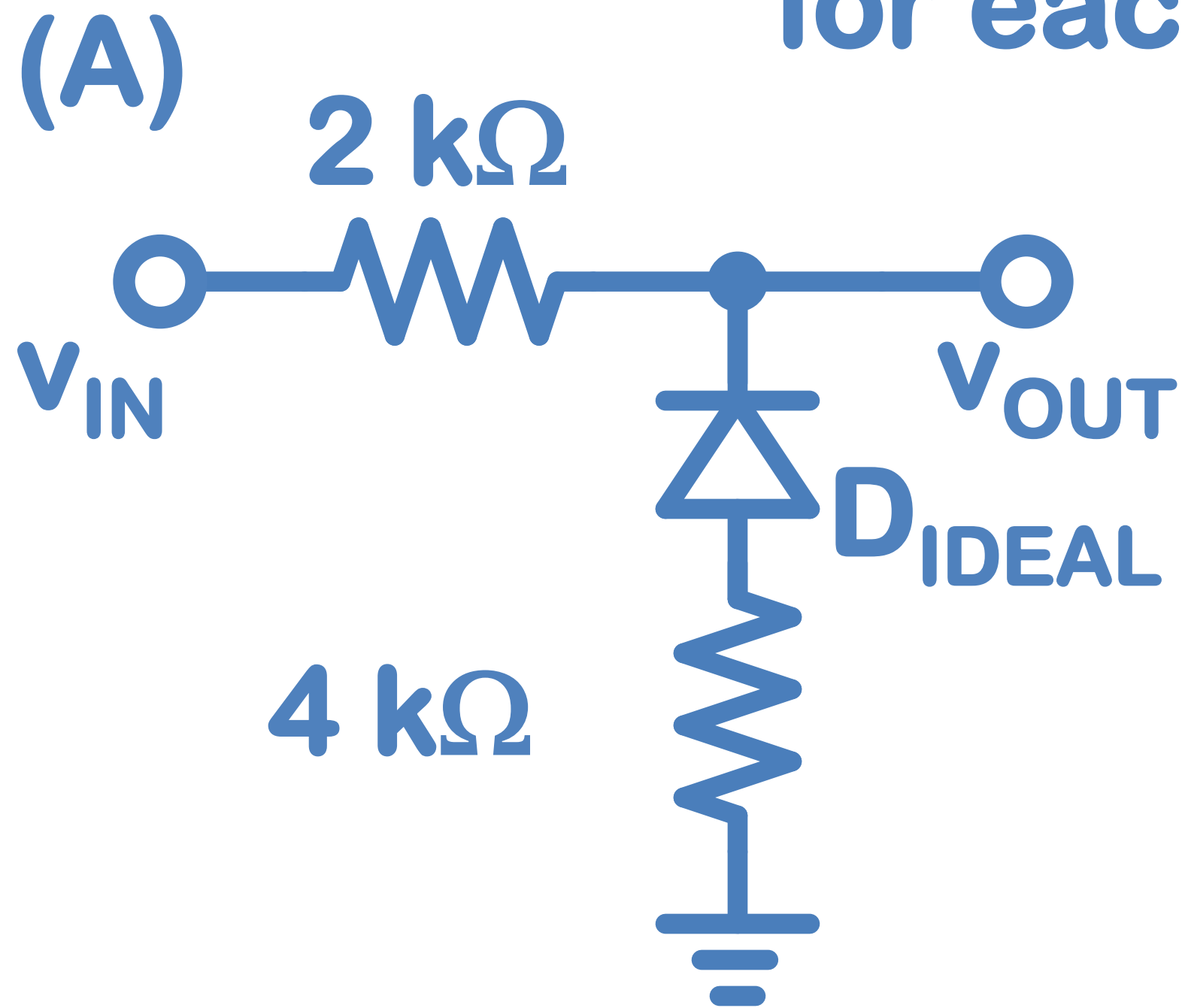
Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



$$v_{OUT} = .67v_{IN}, \text{ when } v_{IN} < 0$$


$$v_{OUT} = v_{IN}, \text{ when } v_{IN} > 0$$

**the equal can go with either case*

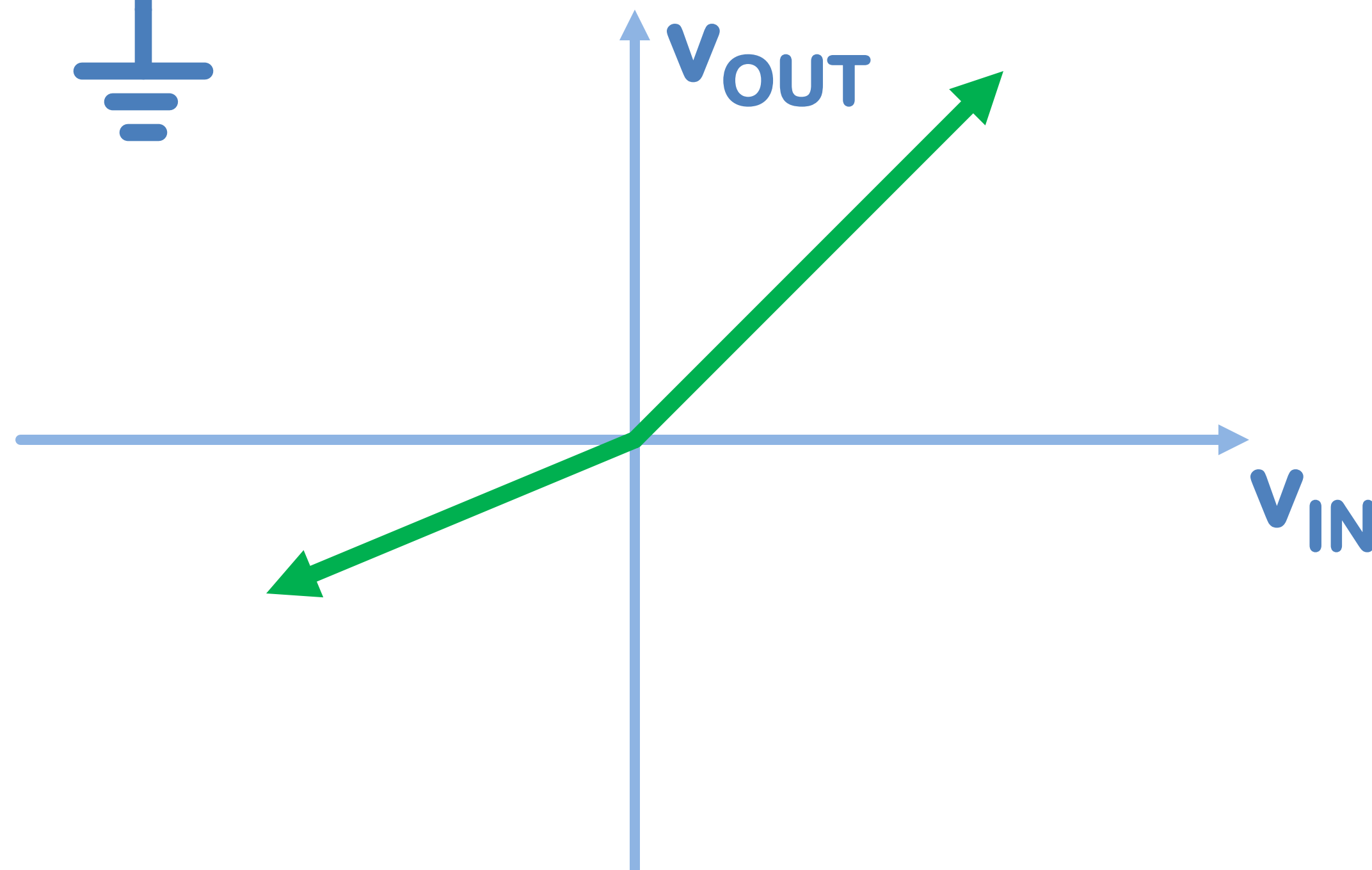

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(B)

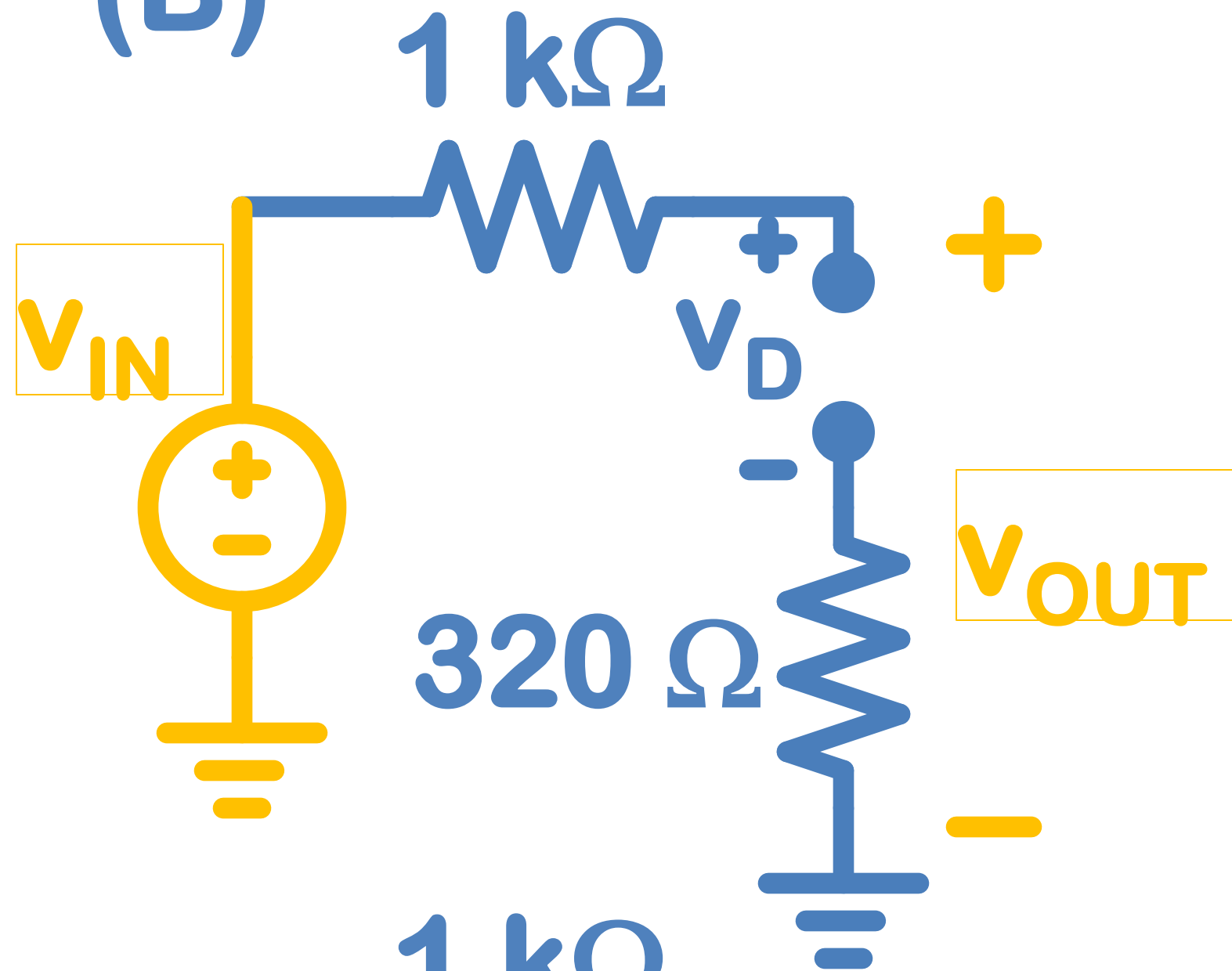

$$v_{OUT} = v_{IN}$$

$$v_D = v_{IN}$$

$$v_D < 0, \text{ when } v_{IN} < 0$$

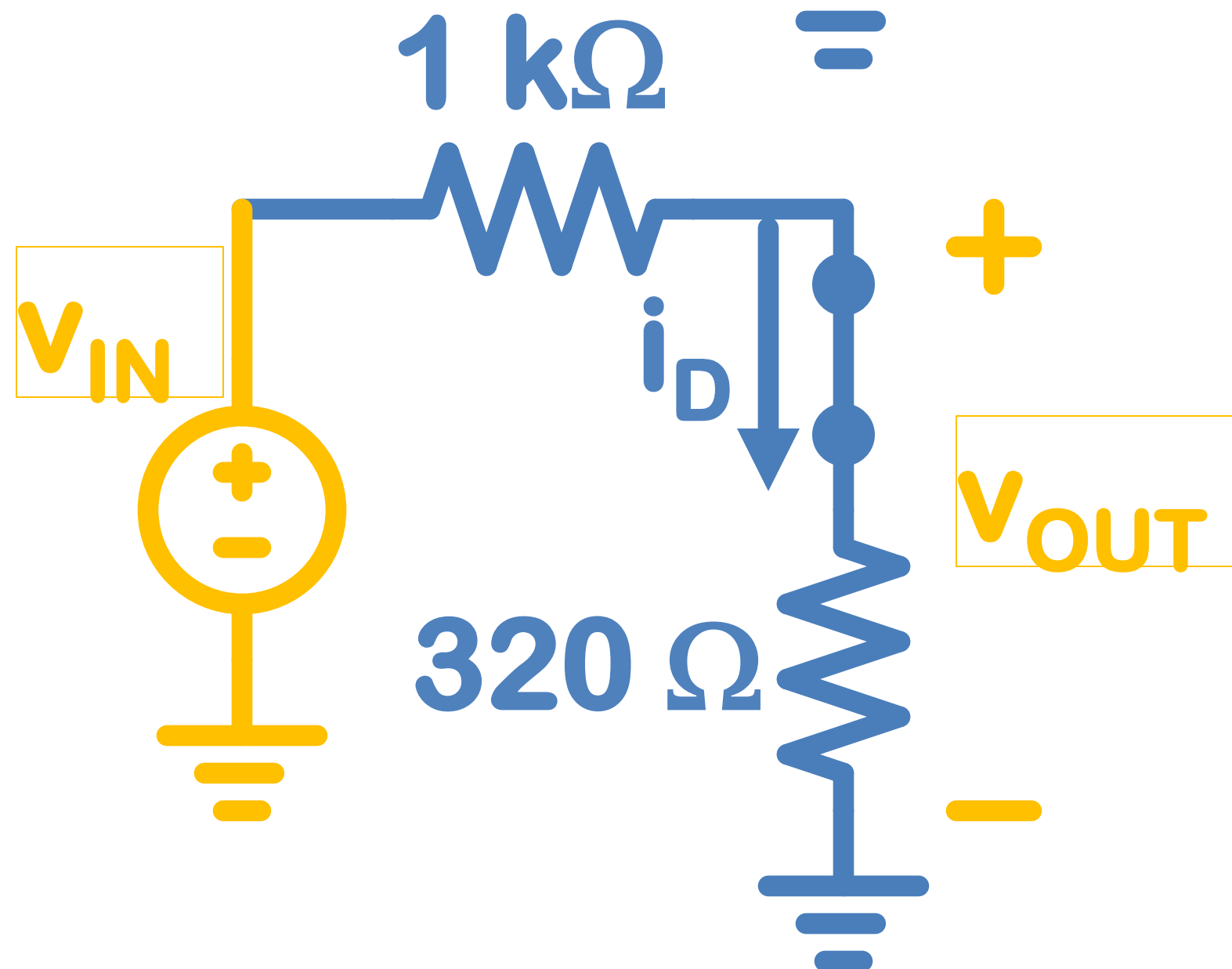


$$v_{OUT} = 0.24 v_{IN}$$

$$i_D = v_{IN} / 1320$$

$$i_D > 0, \text{ when } v_{IN} > 0$$

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(B)

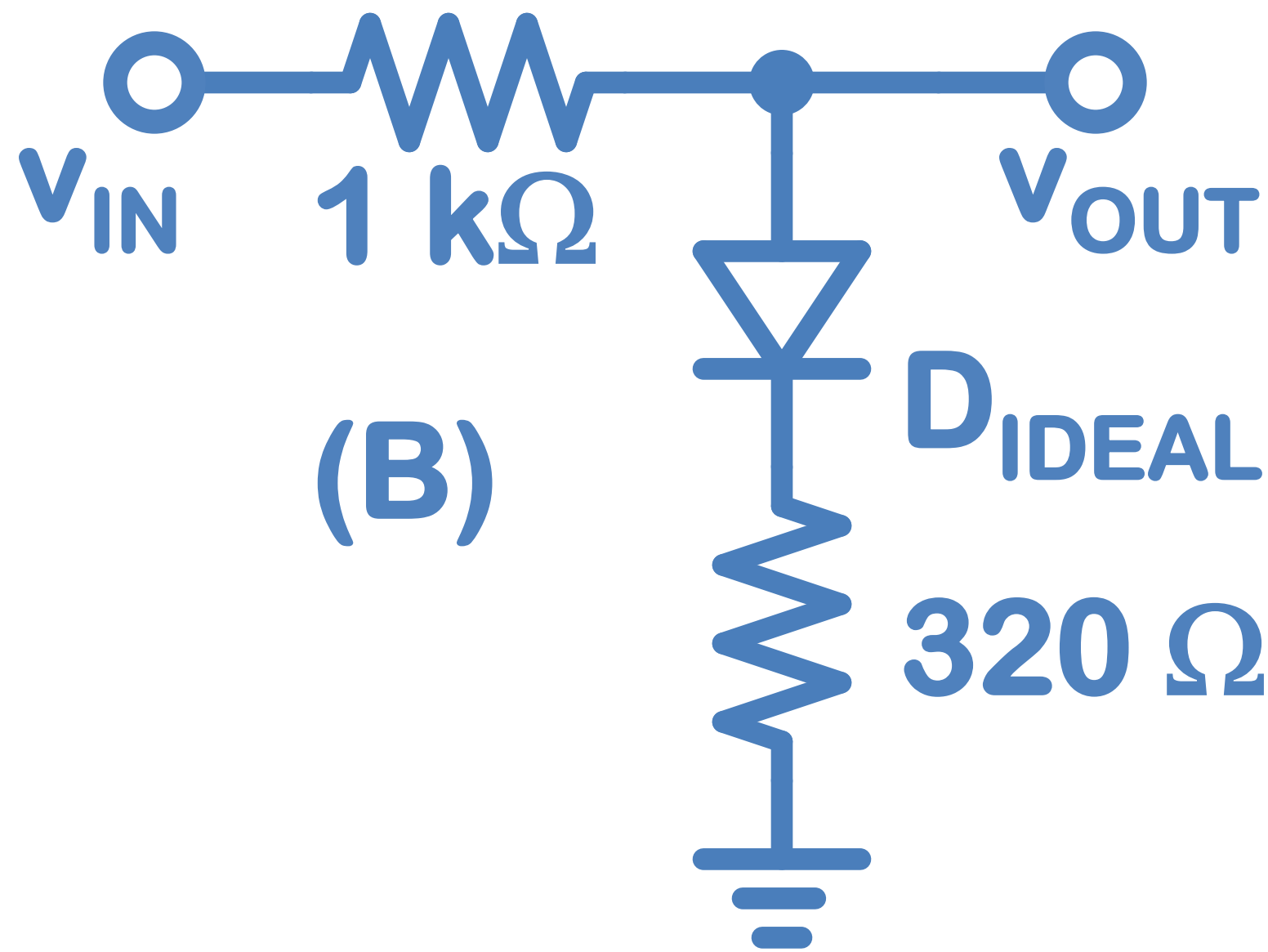

$$v_{OUT} = v_{IN}, \text{ when } v_{IN} < 0$$


$$v_{OUT} = 0.24v_{IN}, \text{ when } v_{IN} > 0$$

**the equal can go with either case*

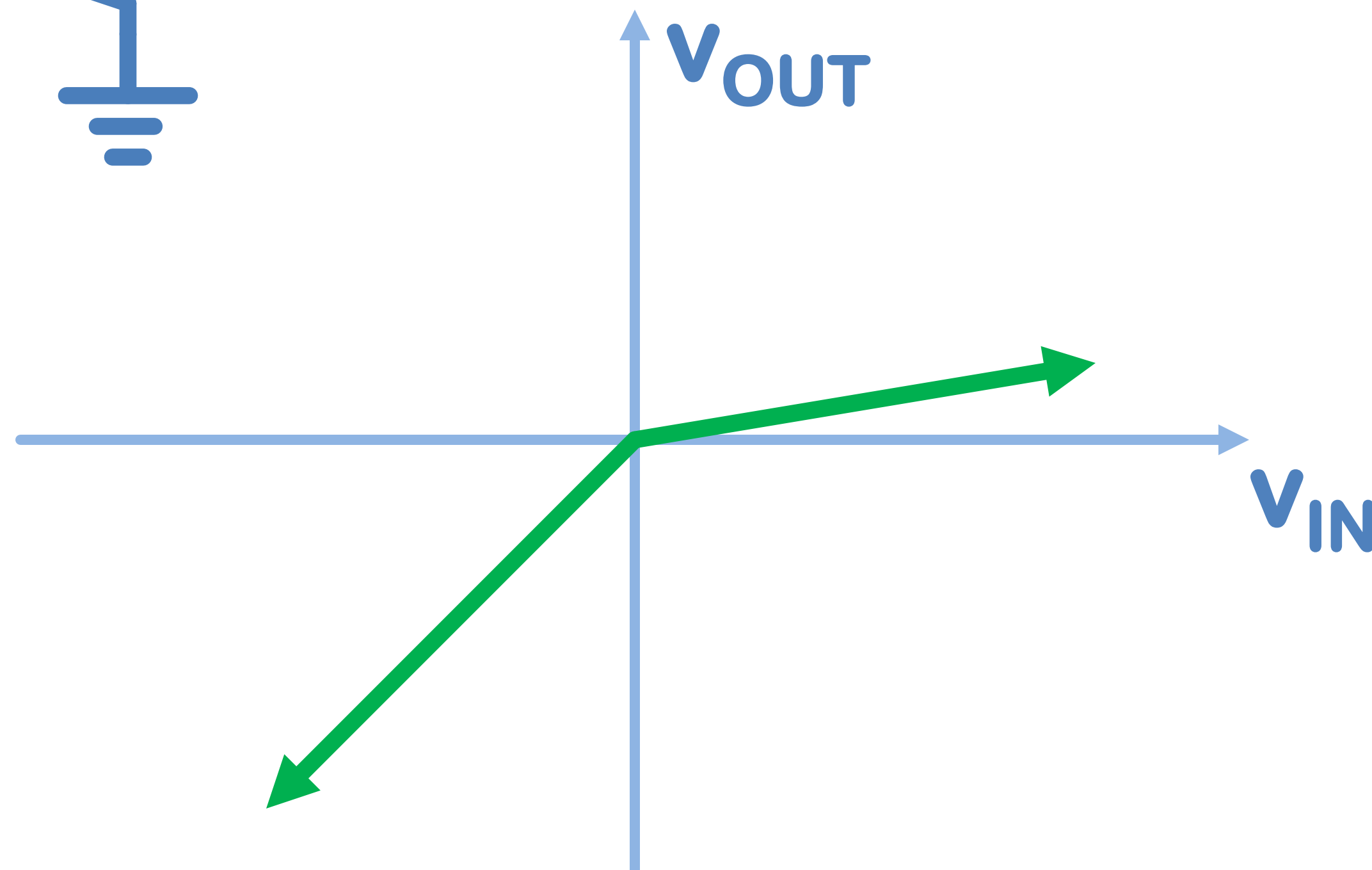

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(C) $900\ \Omega$

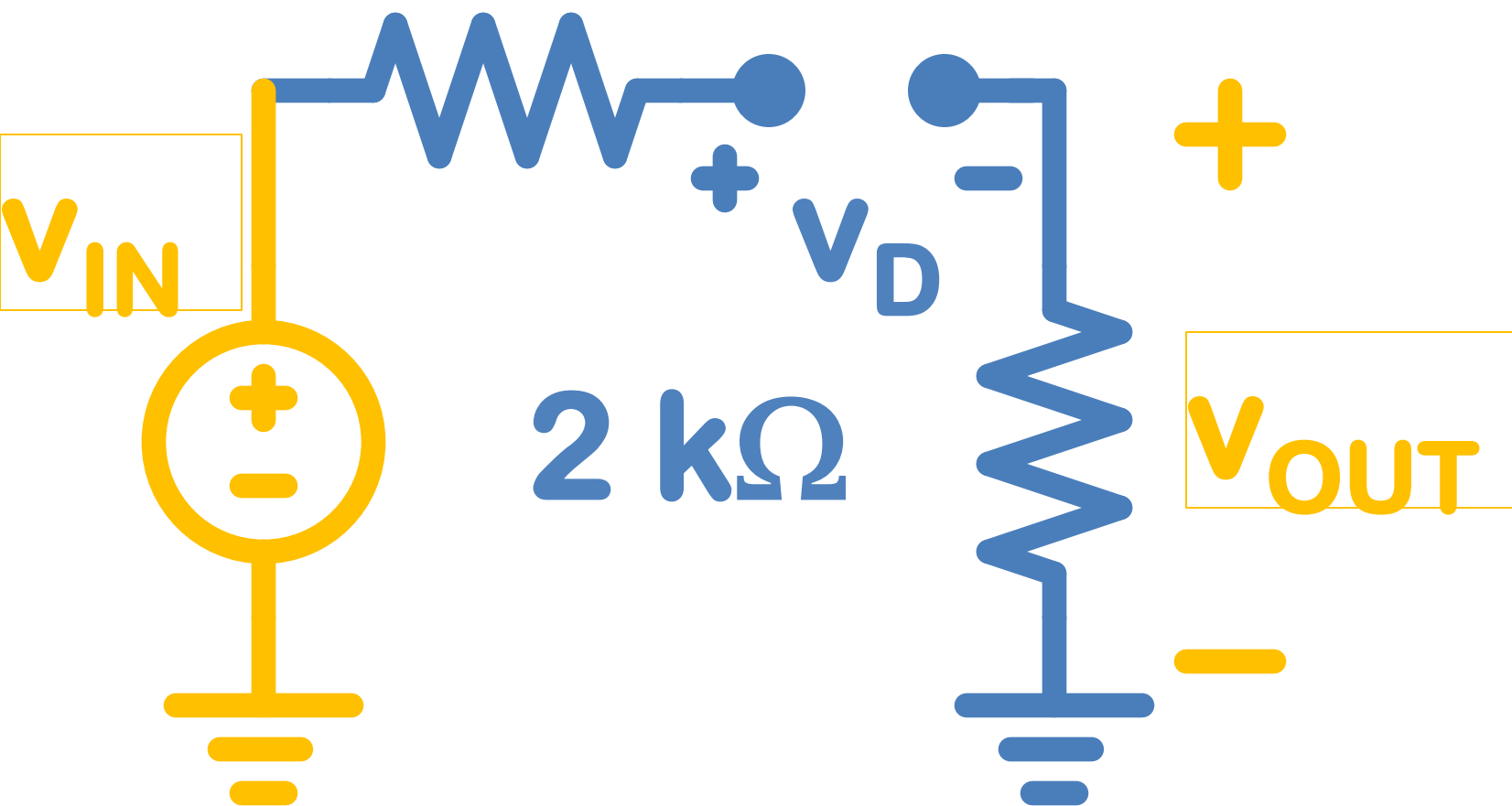

$$v_{OUT}=0$$

$$v_D=v_{IN}$$

$$v_D<0, \text{ when } v_{IN}<0$$

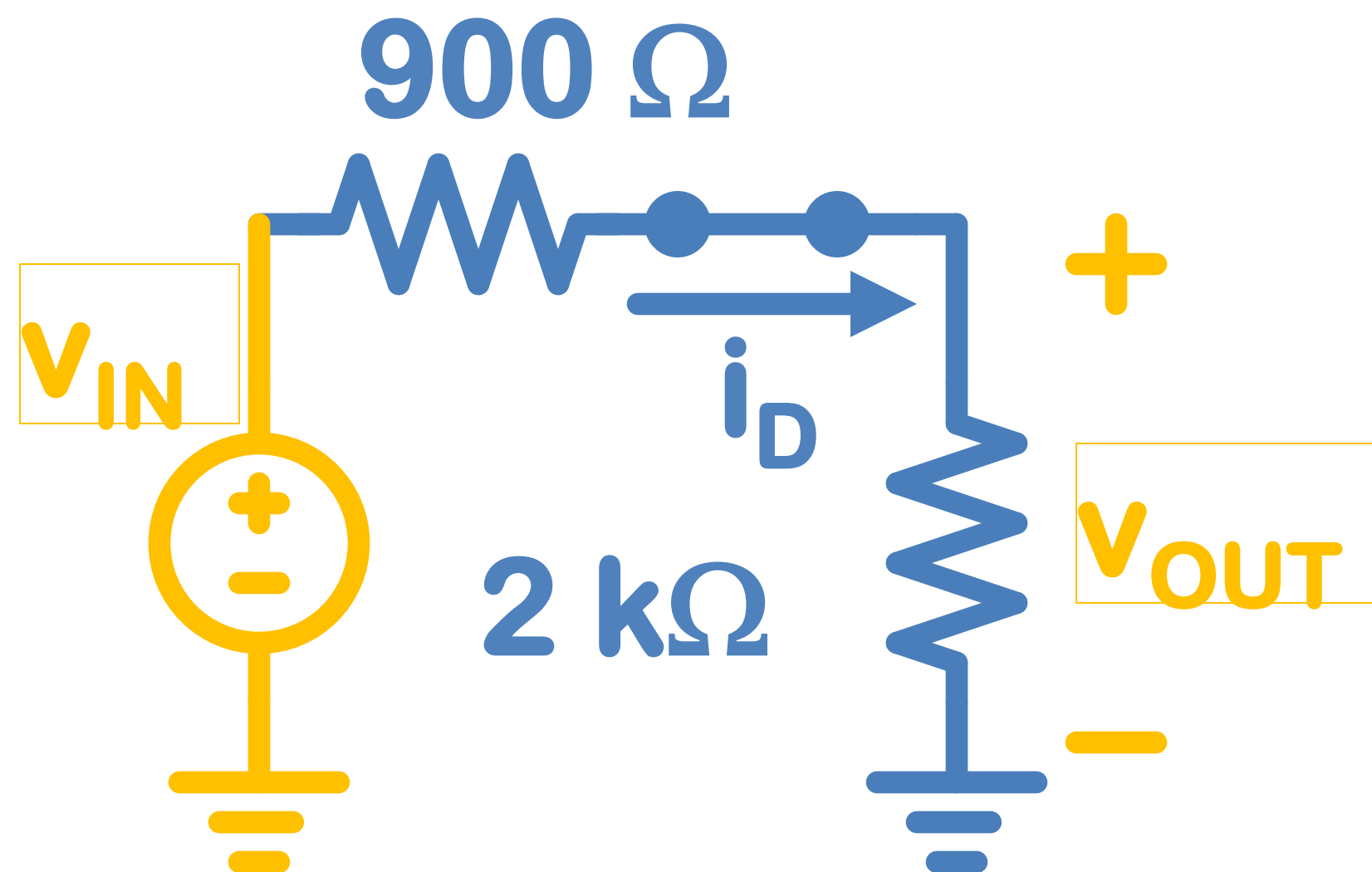


$$v_{OUT}=0.7v_{IN}$$

$$i_D=v_{IN}/2900$$

$$i_D>0, \text{ when } v_{IN}>0$$

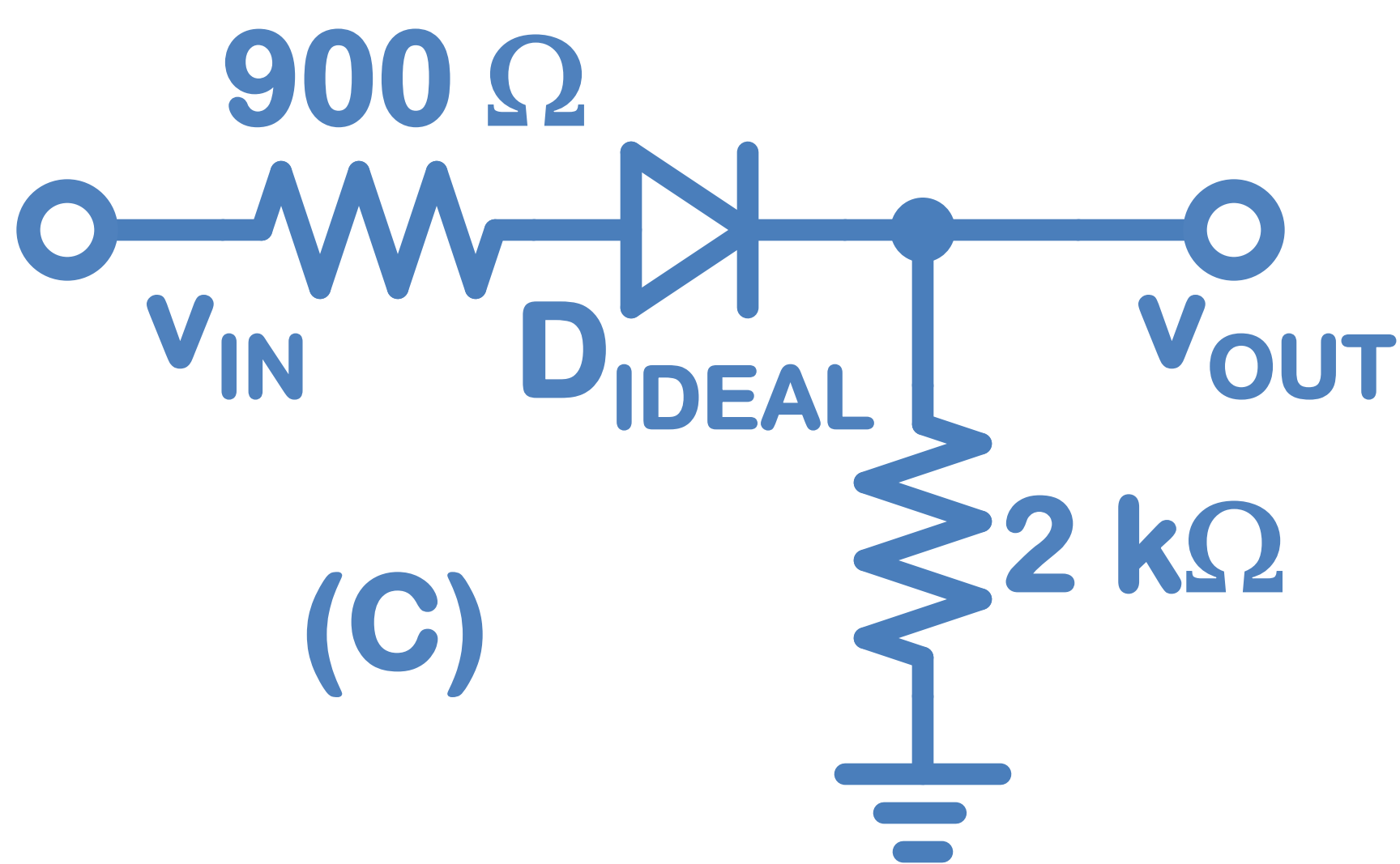
Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



$$v_{OUT} = 0.7v_{IN}, \text{ when } v_{IN} > 0$$


$$v_{OUT} = 0, \text{ when } v_{IN} < 0$$

**the equal can go with either case*

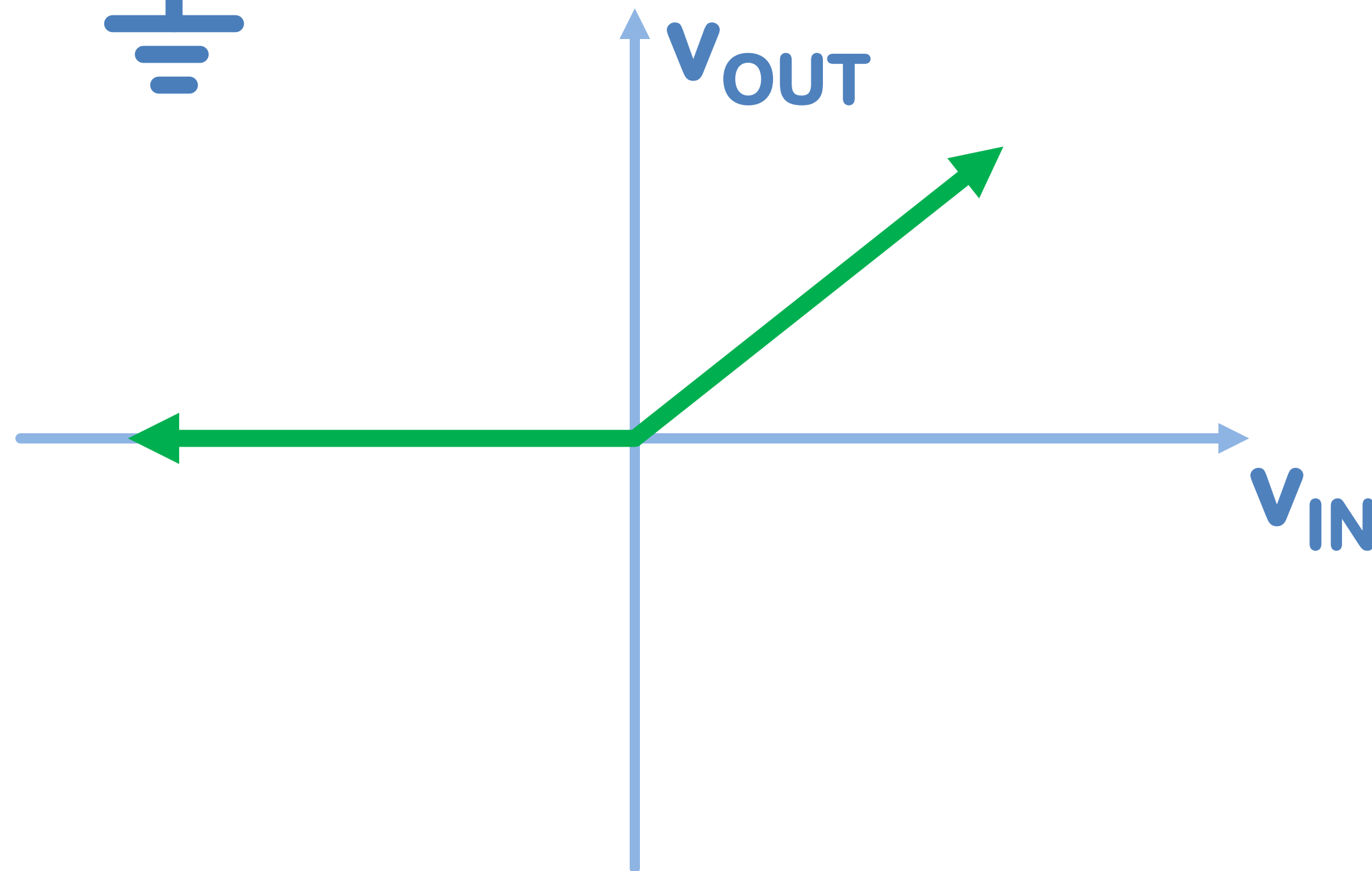

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(D)

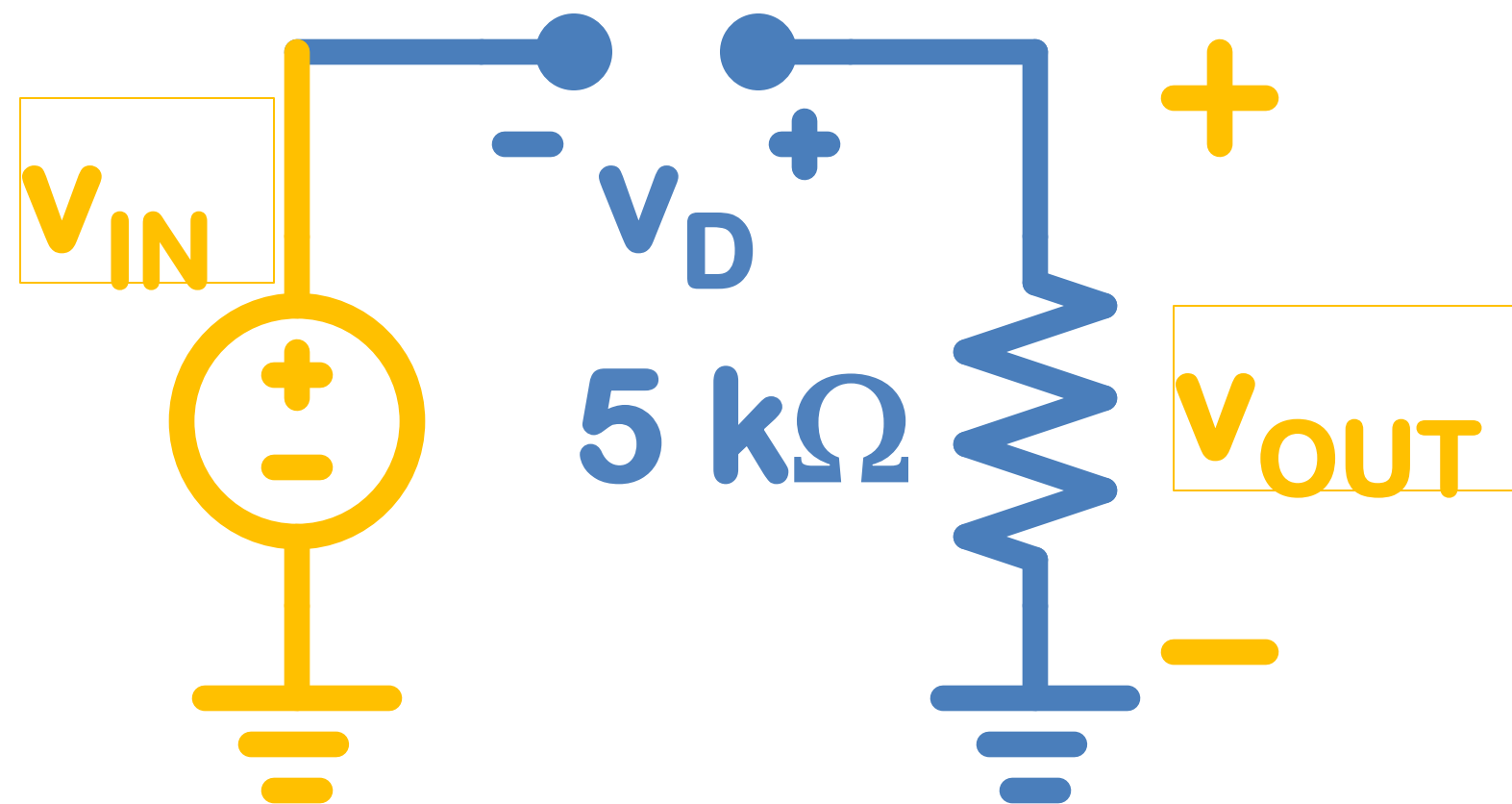

$$v_{OUT}=0$$

$$v_D = -v_{IN}$$

$$v_D < 0, \text{ when } v_{IN} > 0$$

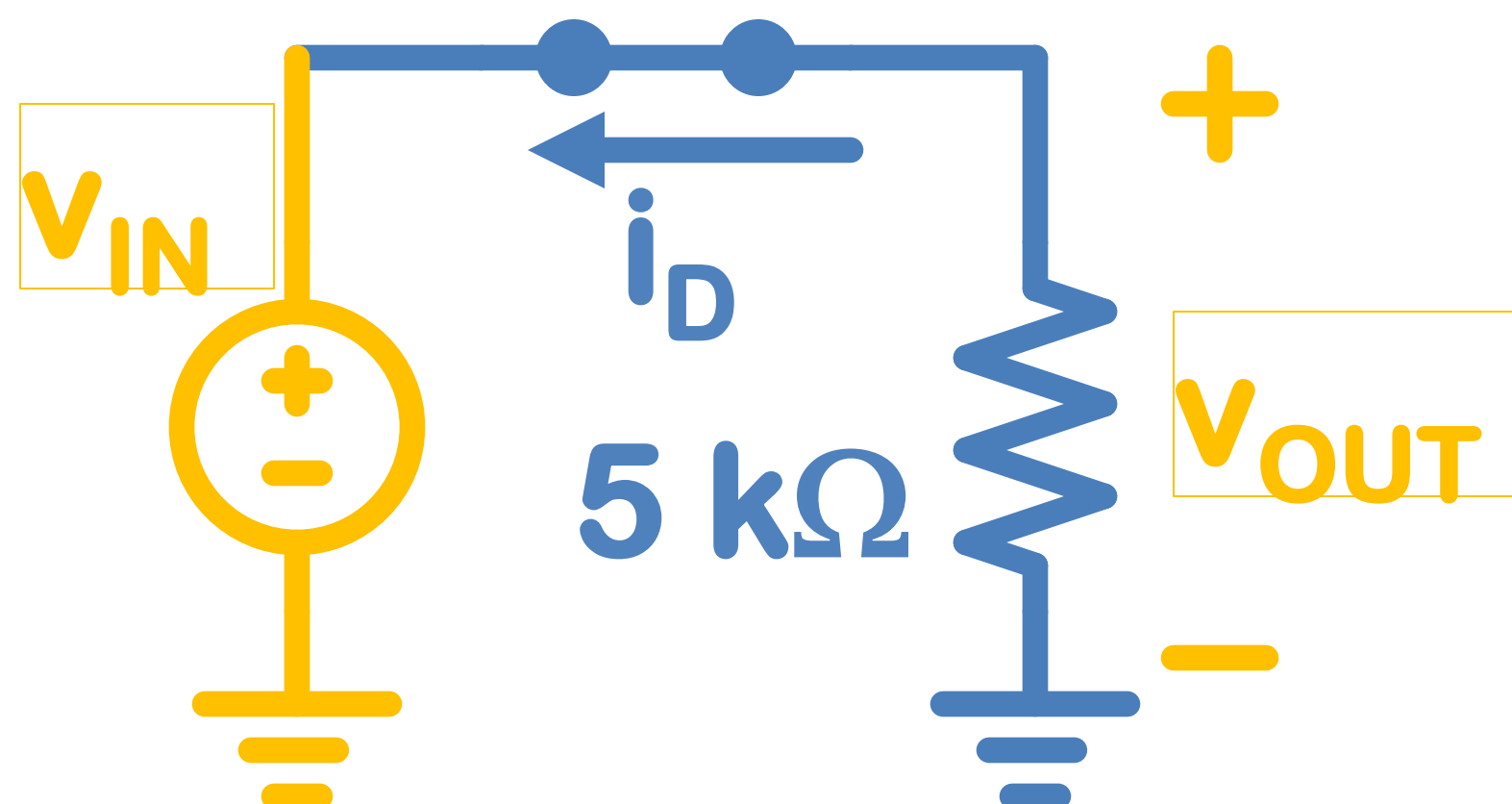


$$v_{OUT}=v_{IN}$$

$$i_D = -v_{IN}/5000$$


$$i_D > 0, \text{ when } v_{IN} < 0$$

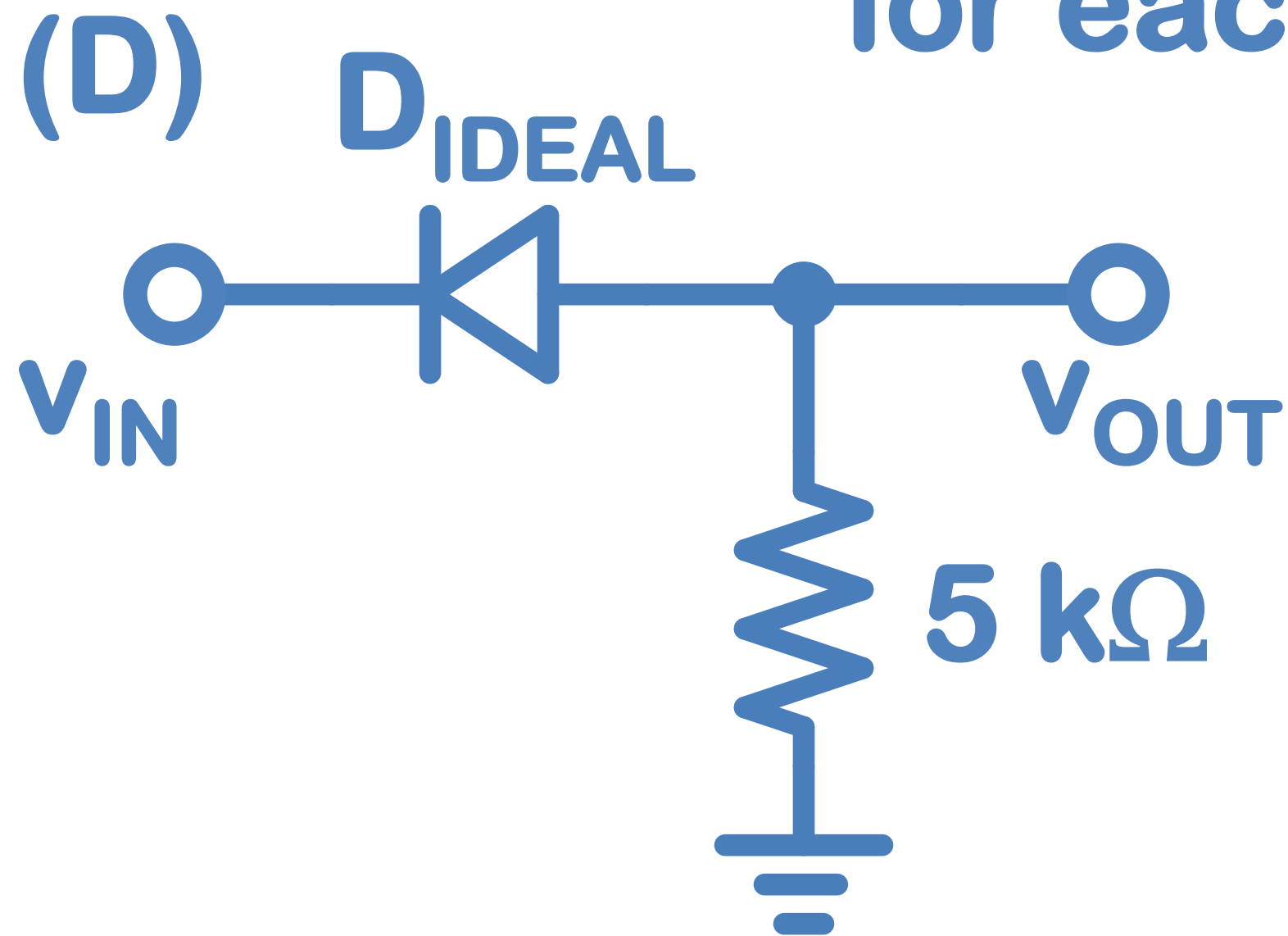Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.





$$v_{OUT}=0, \text{ when } v_{IN}>0$$
$$v_{OUT}=v_{IN}, \text{ when } v_{IN}<0$$

**the equal can go with either case*

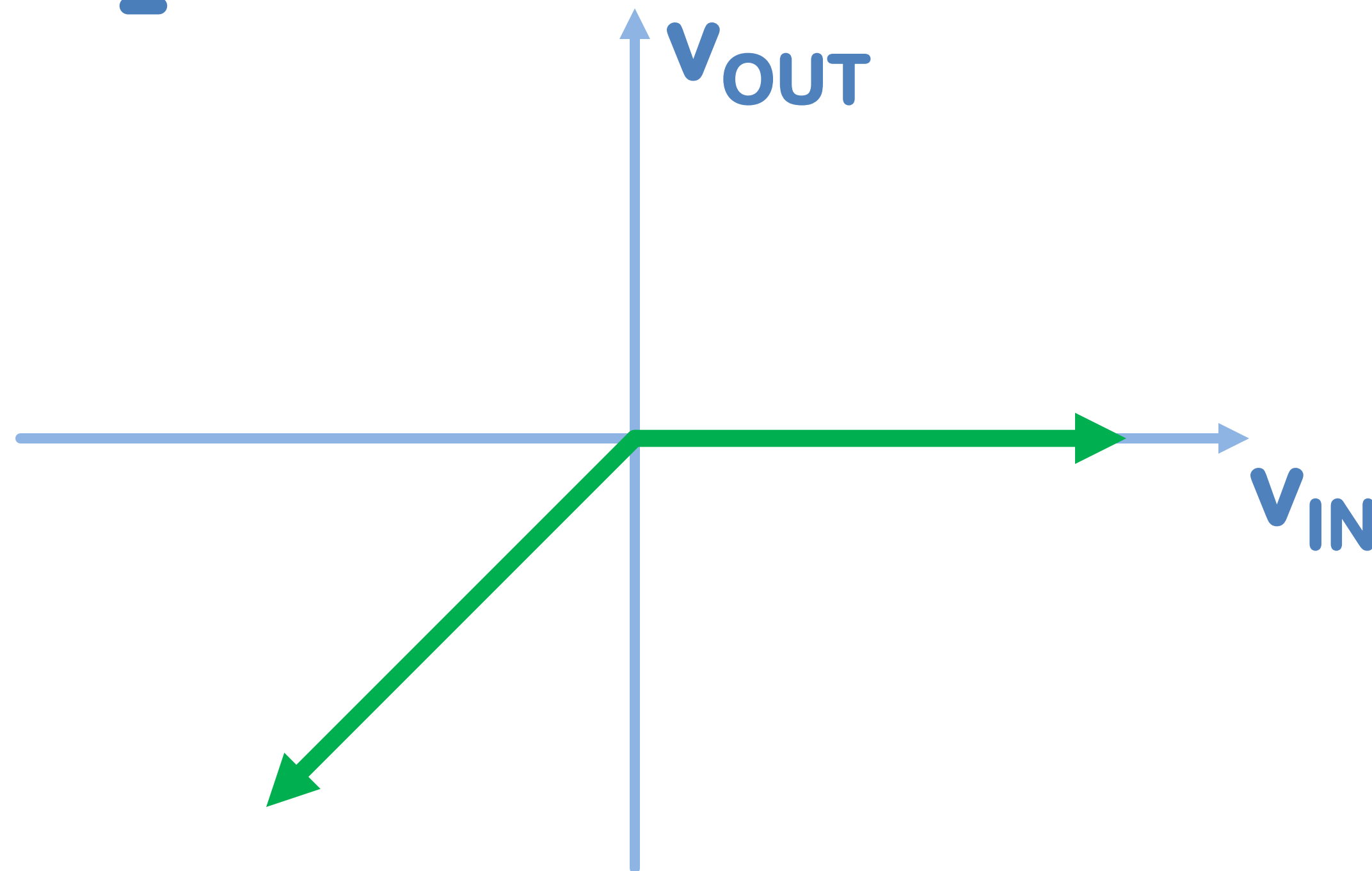


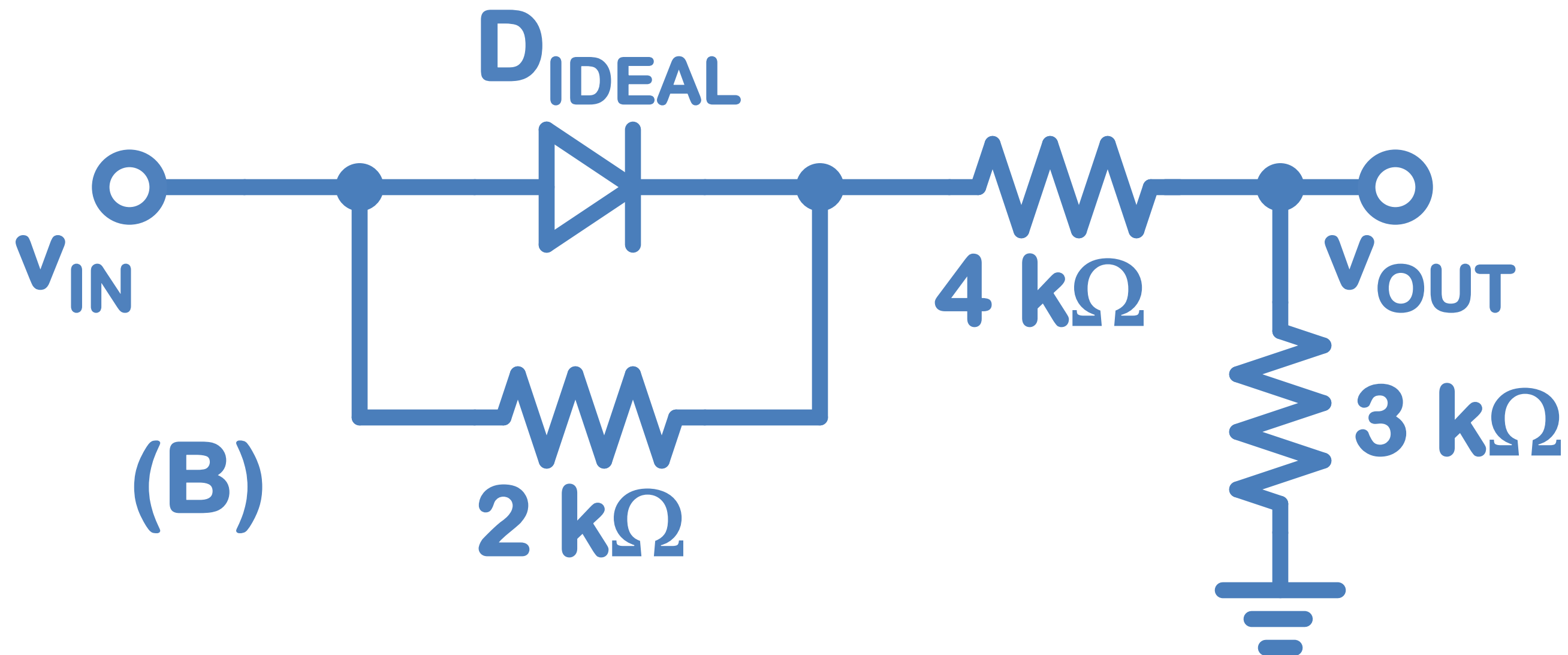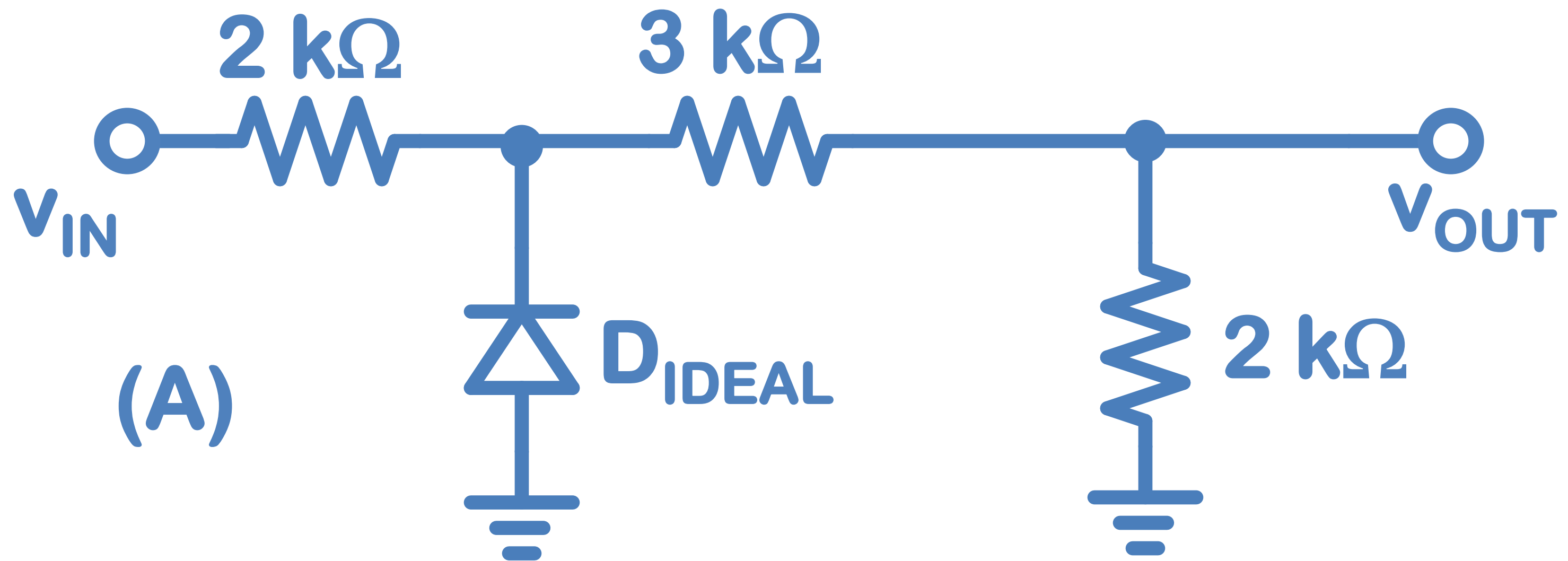- a) Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.
b) Plot the $v_{OUT}(t)$ if $v_{IN}(t)=2\sin(2\pi t)$ for each circuit.



Find the equation and plot $v_{OUT}(v_{IN})$
for each circuit.


(A)

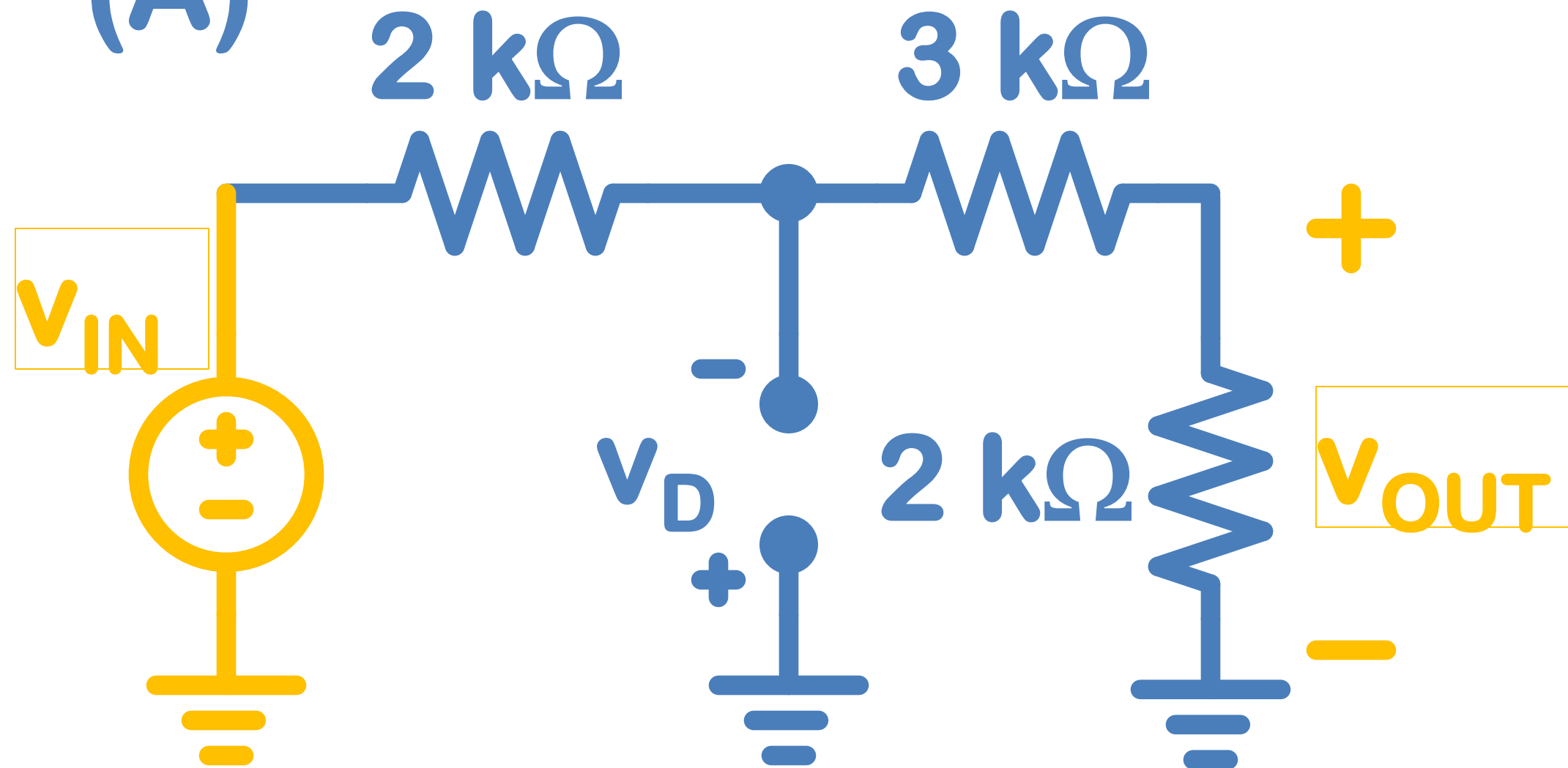

$$v_{OUT} = 0.286v_{IN}$$

$$v_D = -0.714v_{IN}$$

$$v_D < 0, \text{ when } v_{IN} > 0$$

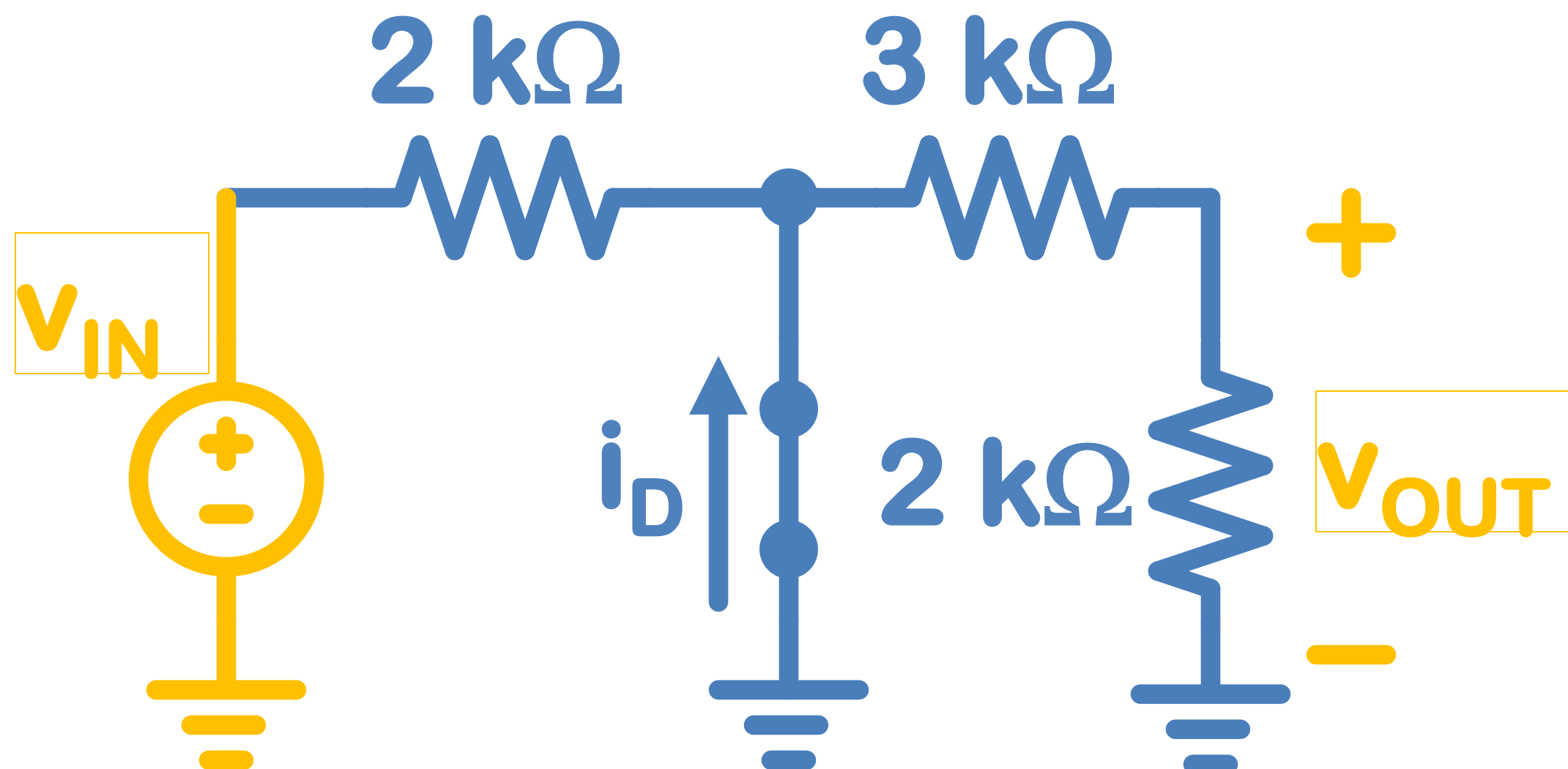


$$v_{OUT} = 0$$

$$i_D = -v_{IN}/2000$$

$$i_D > 0, \text{ when } v_{IN} < 0$$

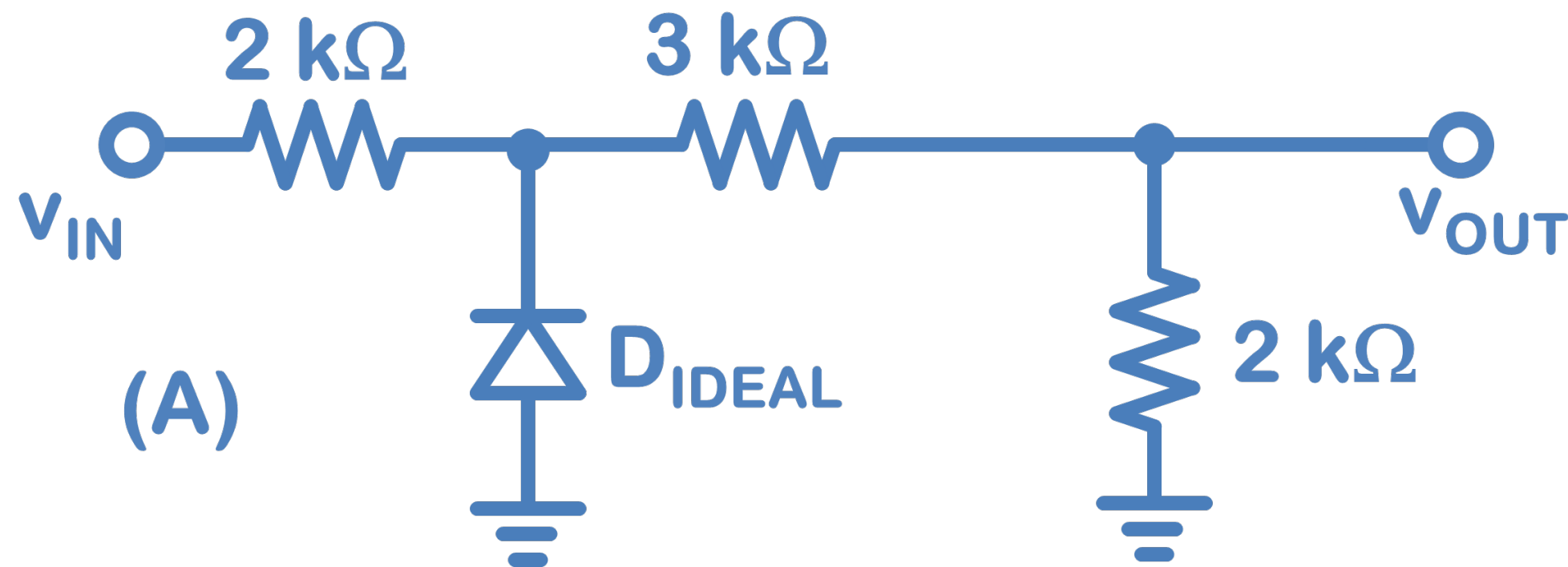
Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



$$v_{OUT}=0, \text{ when } v_{IN}<0$$


$$v_{OUT}=0.286v_{IN}, \text{ when } v_{IN}>0$$

*the equal can go with either case

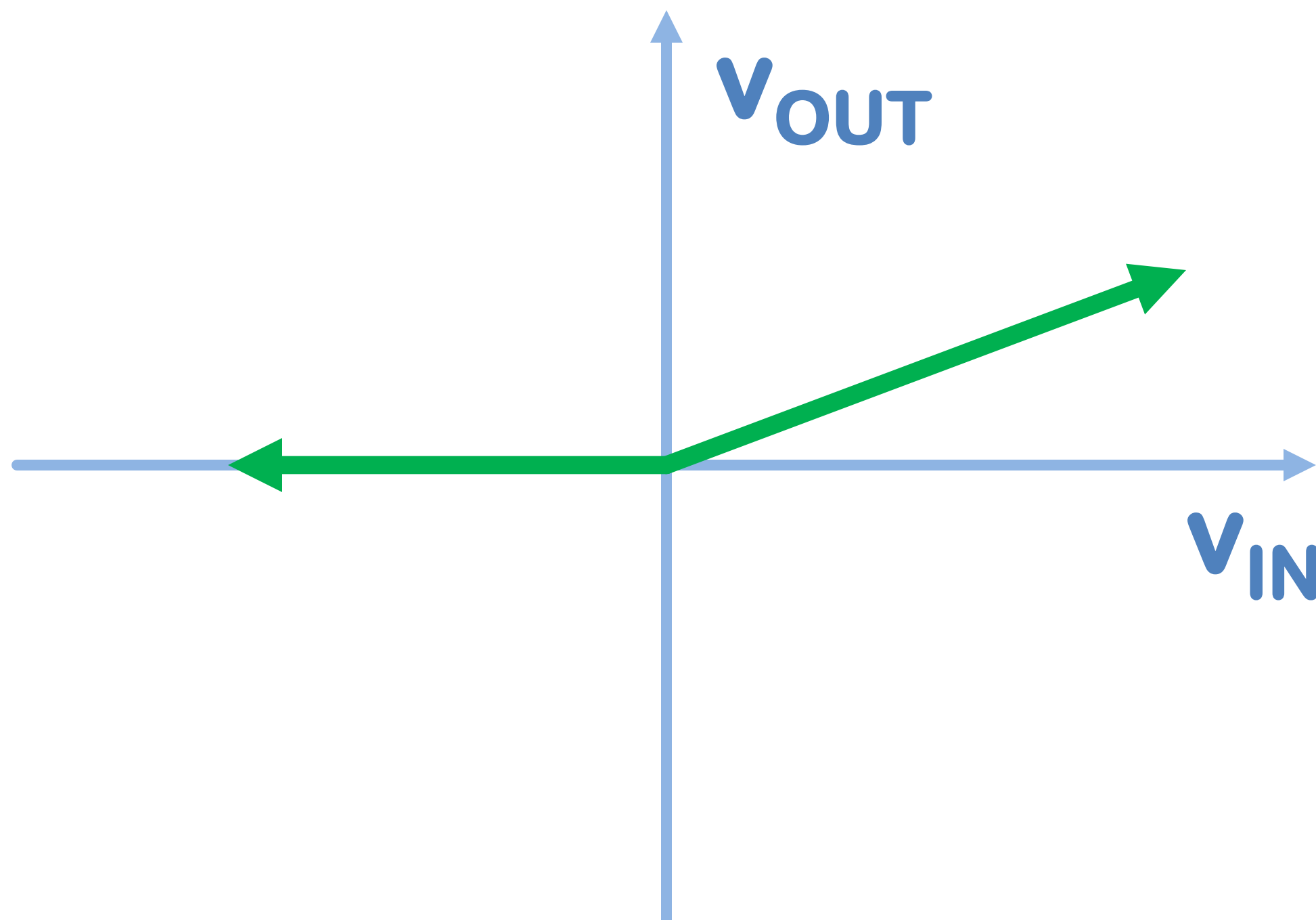

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(A)

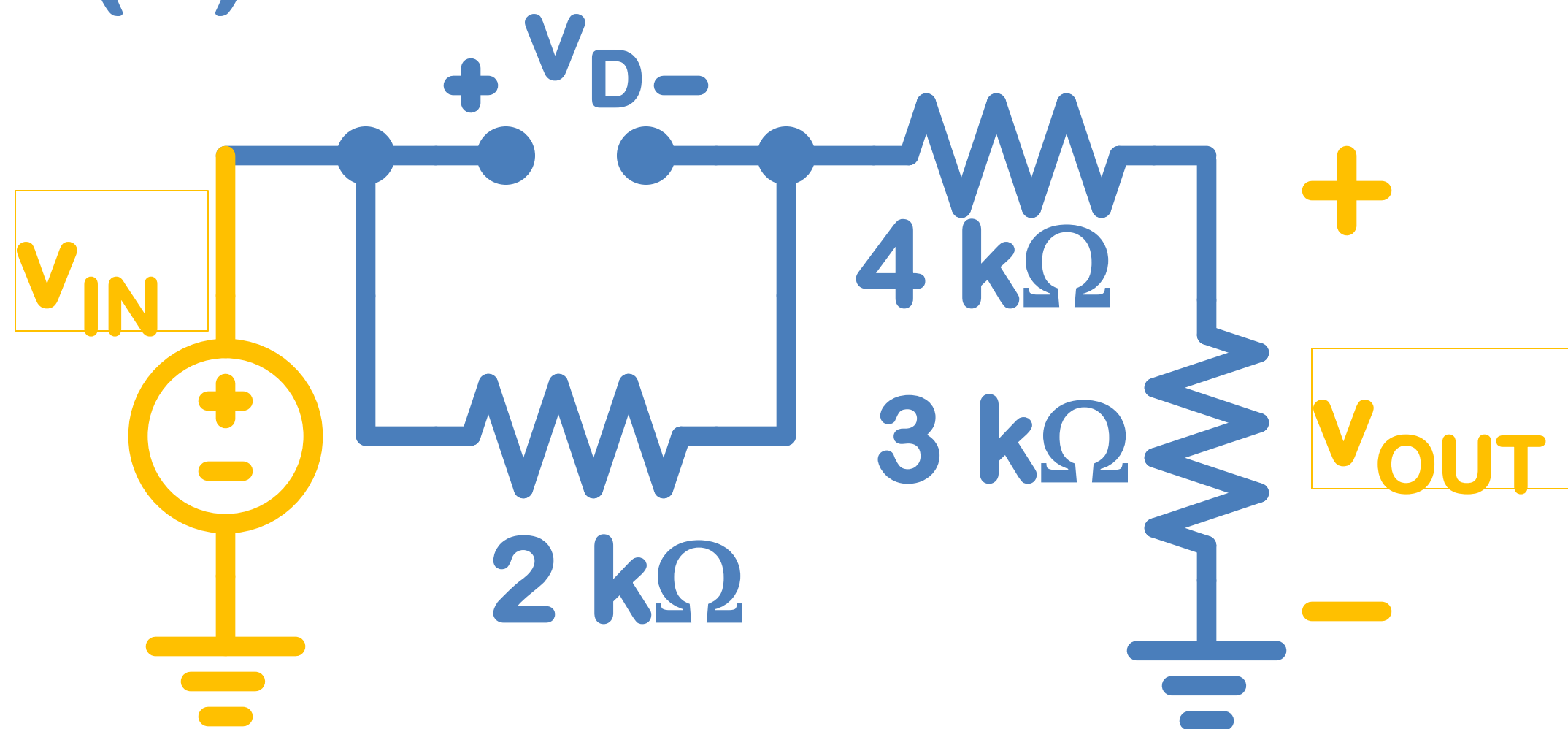

$$v_{OUT} = (3/9)v_{IN}$$

$$v_D = (2/9)v_{IN}$$

$$v_D < 0, \text{ when } v_{IN} < 0$$

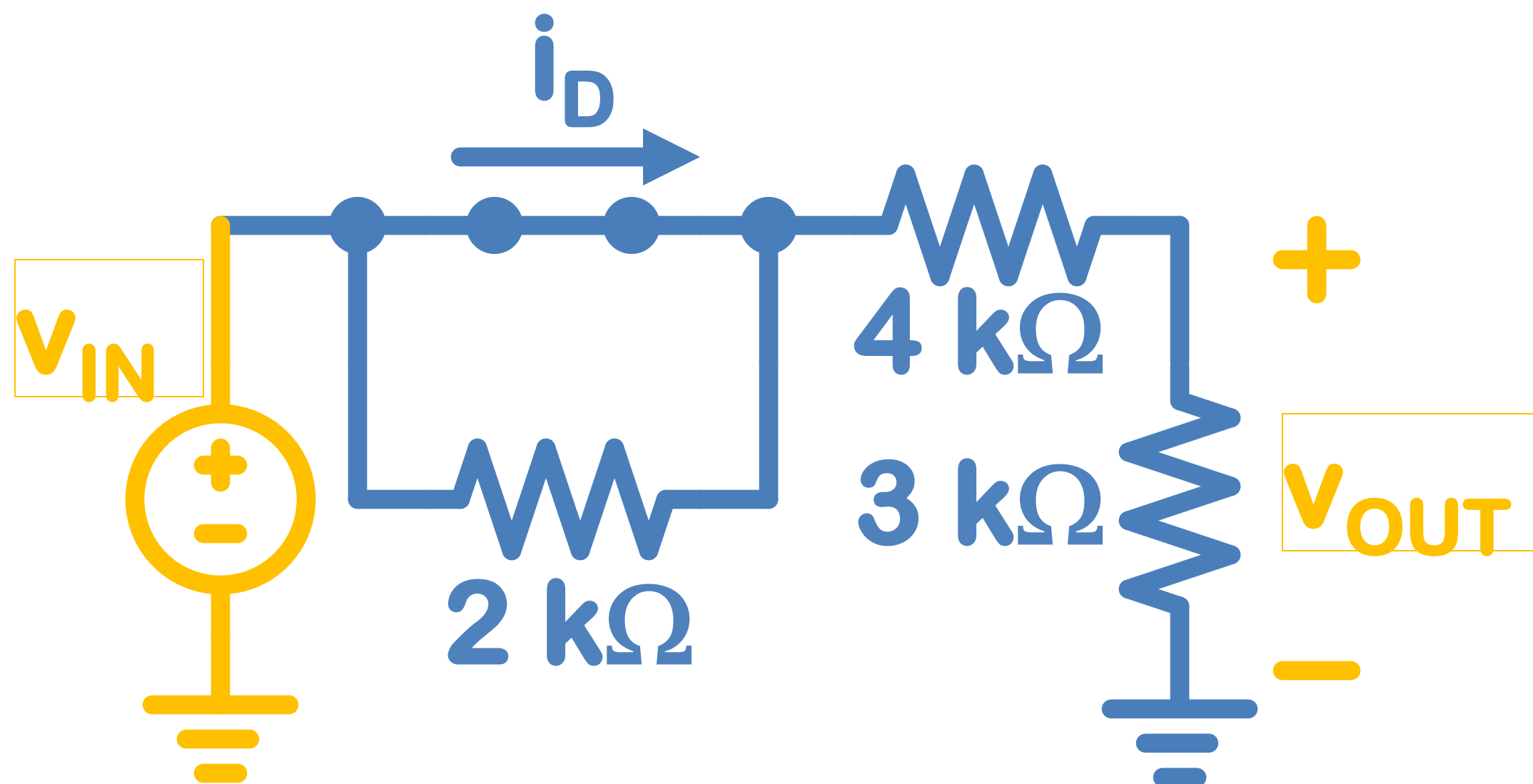


$$v_{OUT} = (3/7)v_{IN}$$

$$i_D = v_{IN}/7000$$

$$i_D > 0, \text{ when } v_{IN} > 0$$

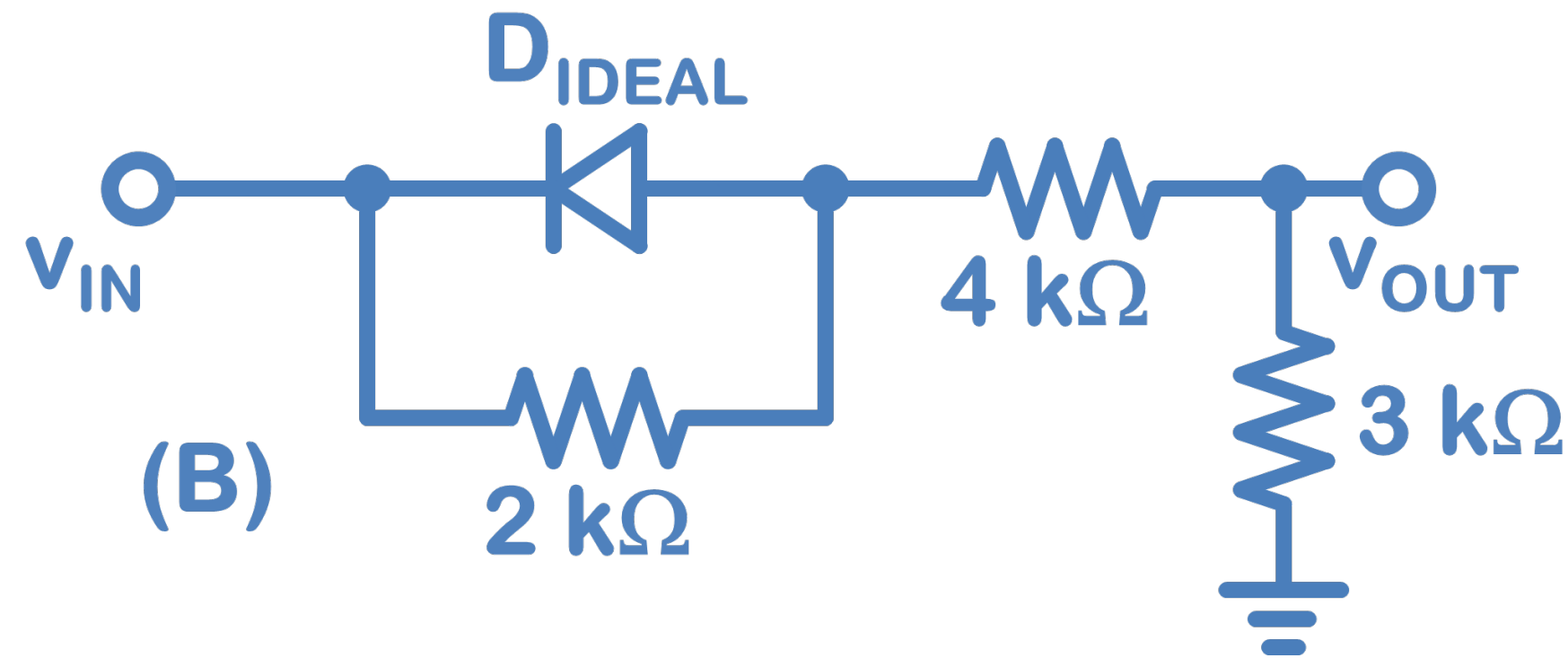
Find the equation and plot $v_{OUT}(v_{IN})$
 D_{IDEAL} for each circuit.



$$v_{OUT} = (1/3)v_{IN}, \text{ when } v_{IN} < 0$$


$$v_{OUT} = (3/7)v_{IN}, \text{ when } v_{IN} > 0$$

*the equal can go with either case

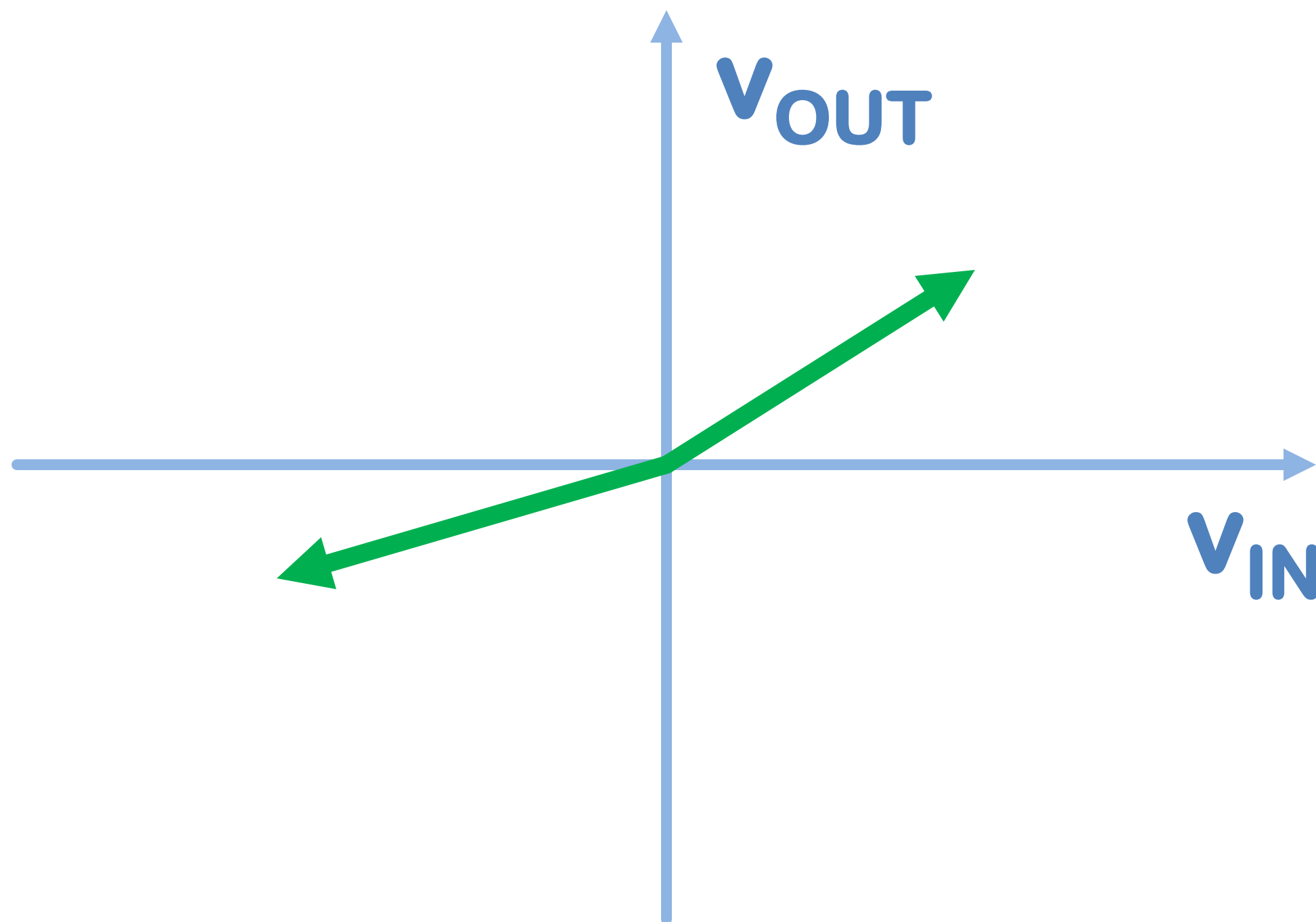


Problem 4.

a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.

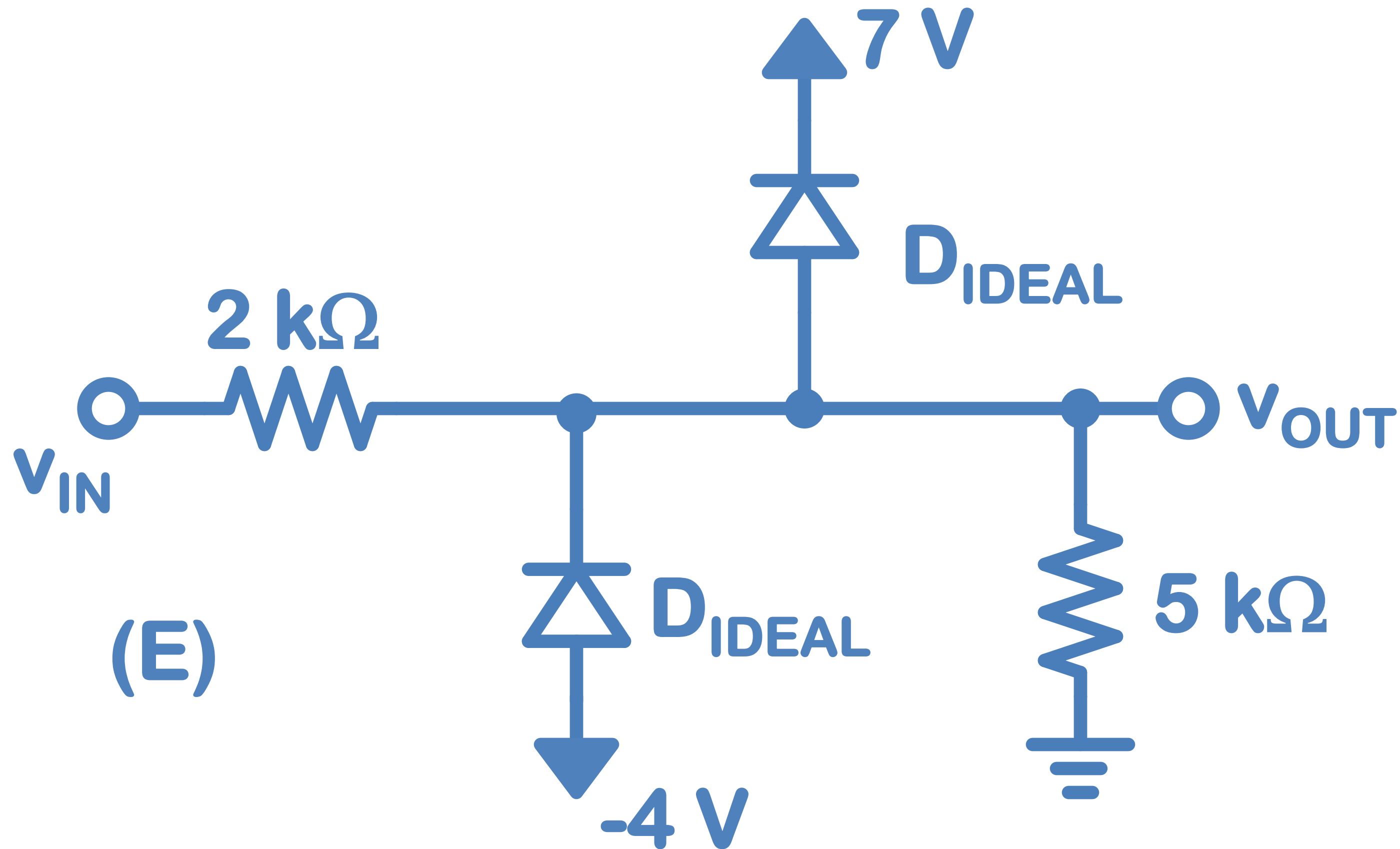

Problem 4.

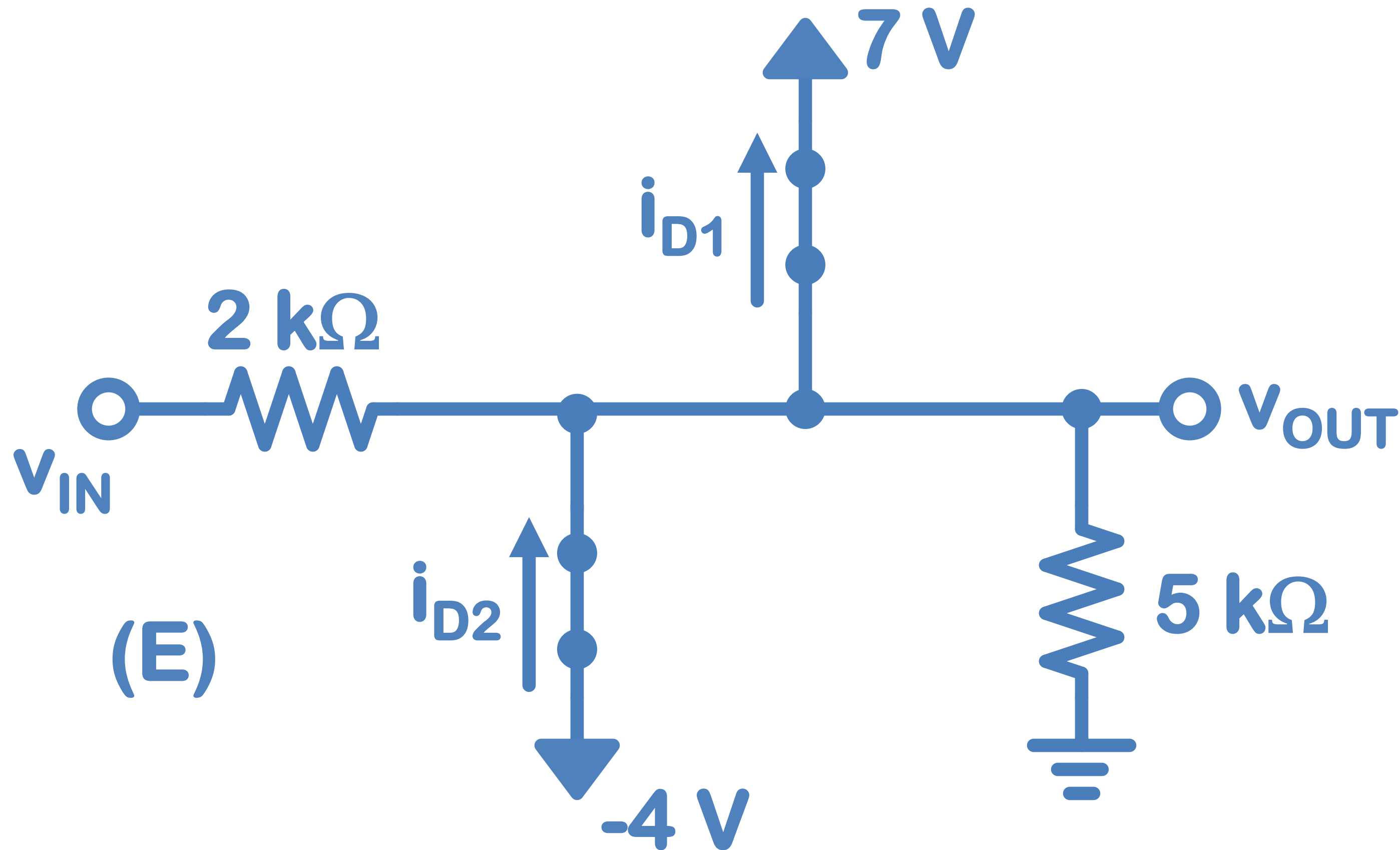
a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.



$i_{D1}=i_{D2}=-11/0=\text{neg. infinity}$
Never > 0 for FB,FB

Problem 4.

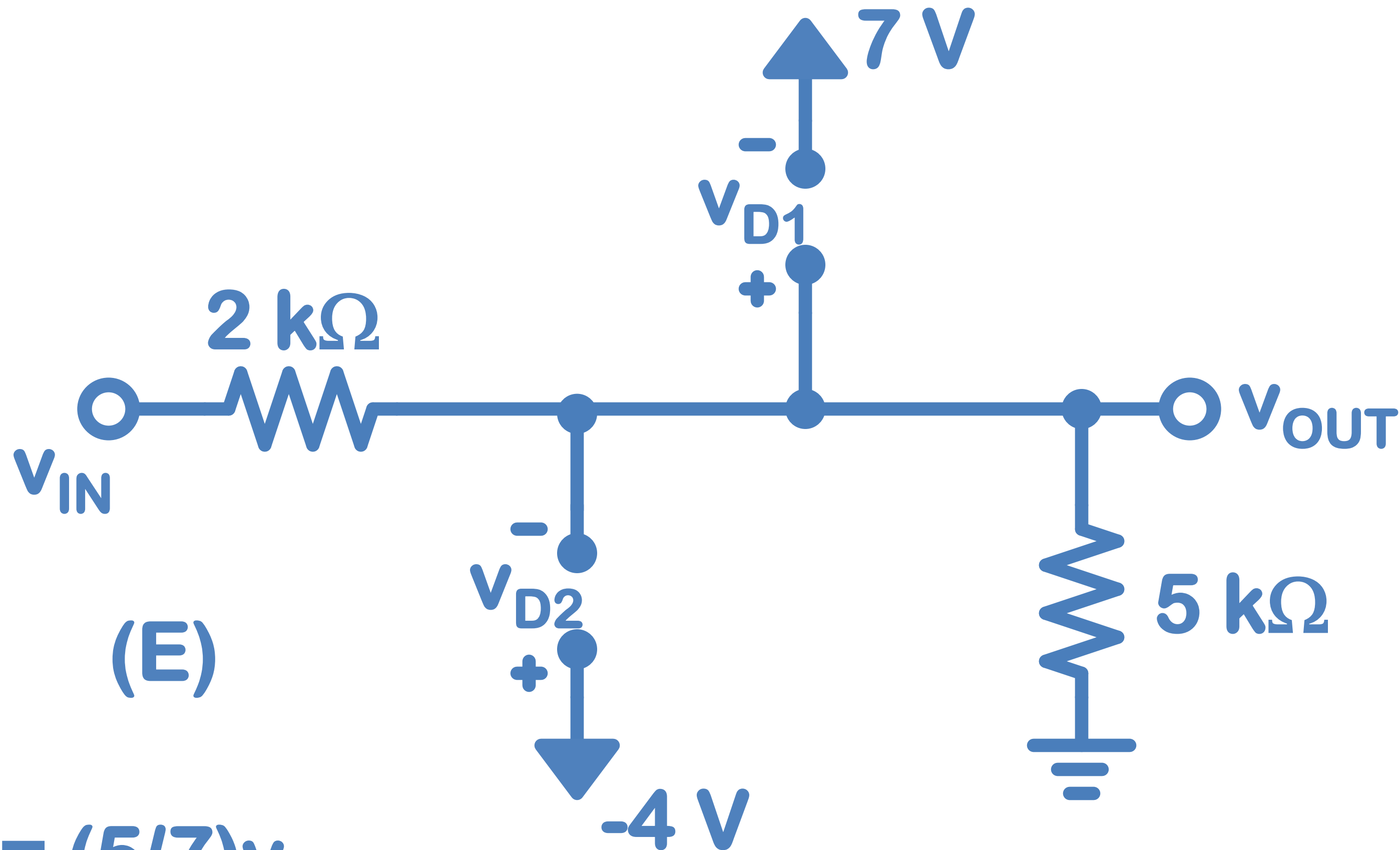a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.



$$v_{OUT} = (5/7)v_{IN}$$


$$v_{D1} = (5/7)v_{IN} - 7 < 0; v_{IN} < (49/5)$$

$$v_{D2} = -4 - (5/7)v_{IN} < 0; v_{IN} > -(28/5)$$

$$-(28/5) < v_{IN} < (49/5)$$

Problem 4.

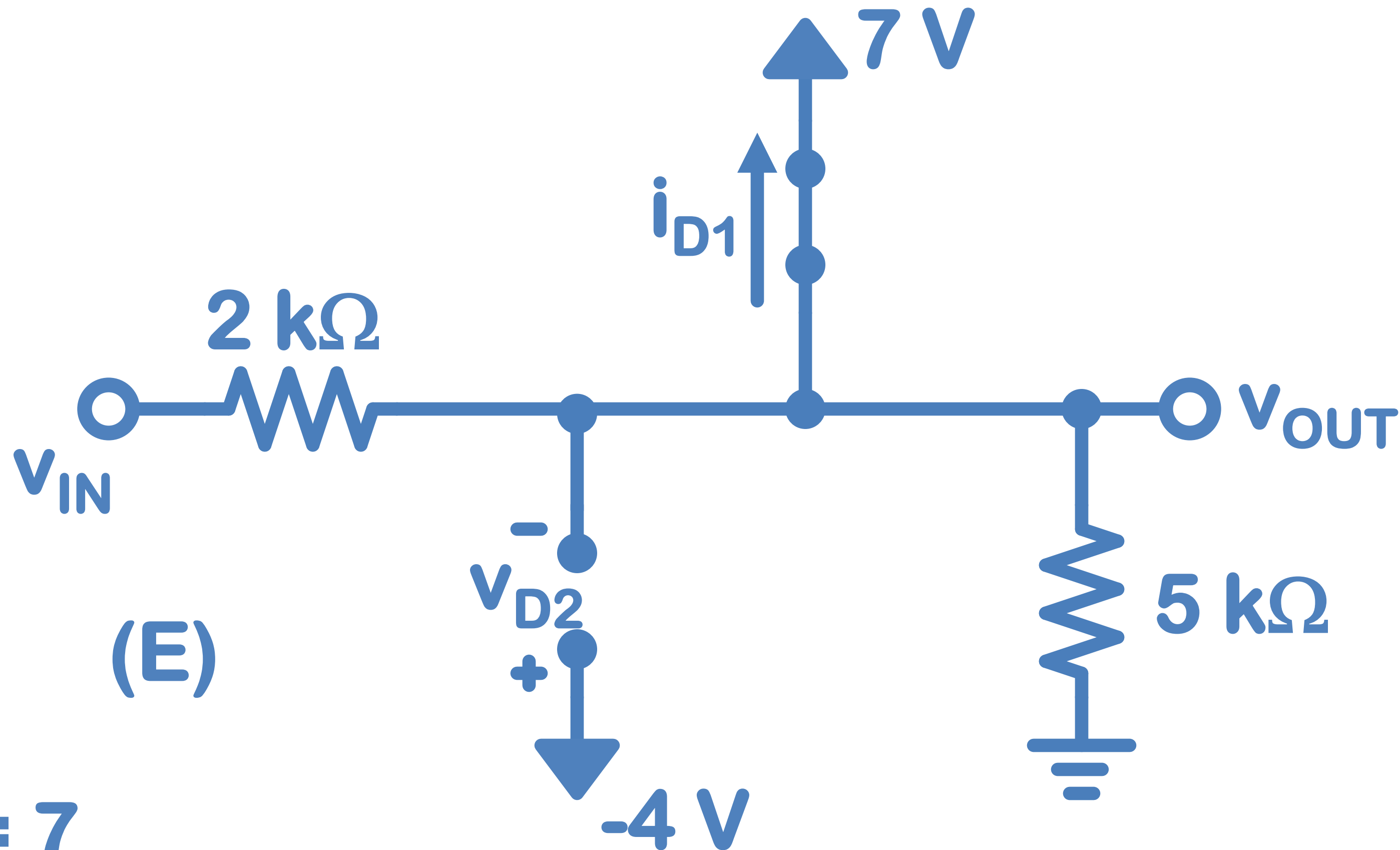a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.



$$v_{OUT} = 7$$


$$i_{D1} = (v_{IN} - 7)/2000 + -7/5000 > 0; v_{IN} > 49/5$$

$$v_{D2} = -4 - 7 < 0; \text{always}$$

$$v_{IN} > (49/5)$$

Problem 4.

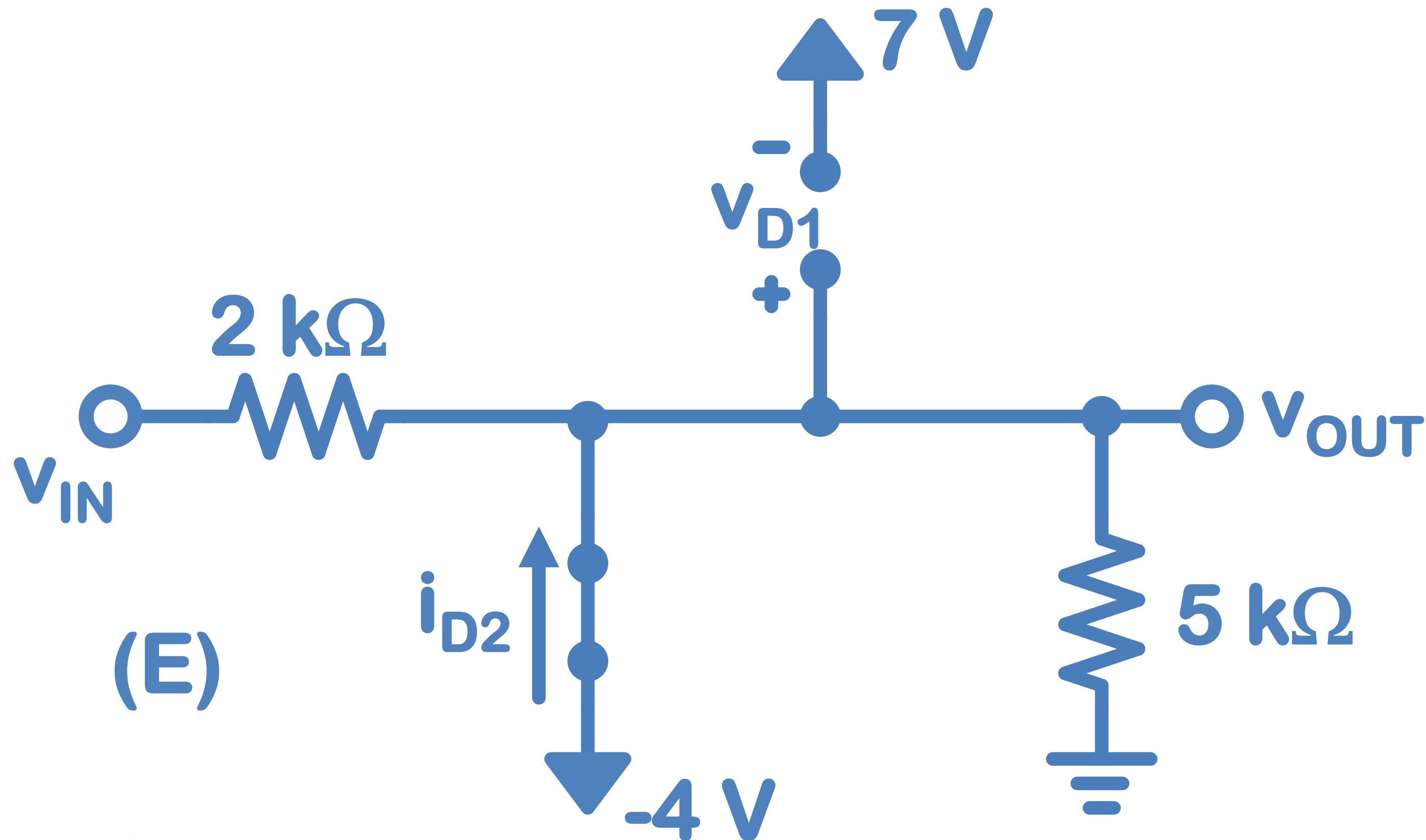a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.



$$v_{OUT} = -4$$


$$v_{D1} = -4 - 7 < 0; \text{ always}$$

$$i_{D2} = (-4 - v_{IN}) / 2000 - 4 / 5000 > 0; v_{IN} < -(28/5)$$

$$v_{IN} < -(28/5)$$

Problem 4.

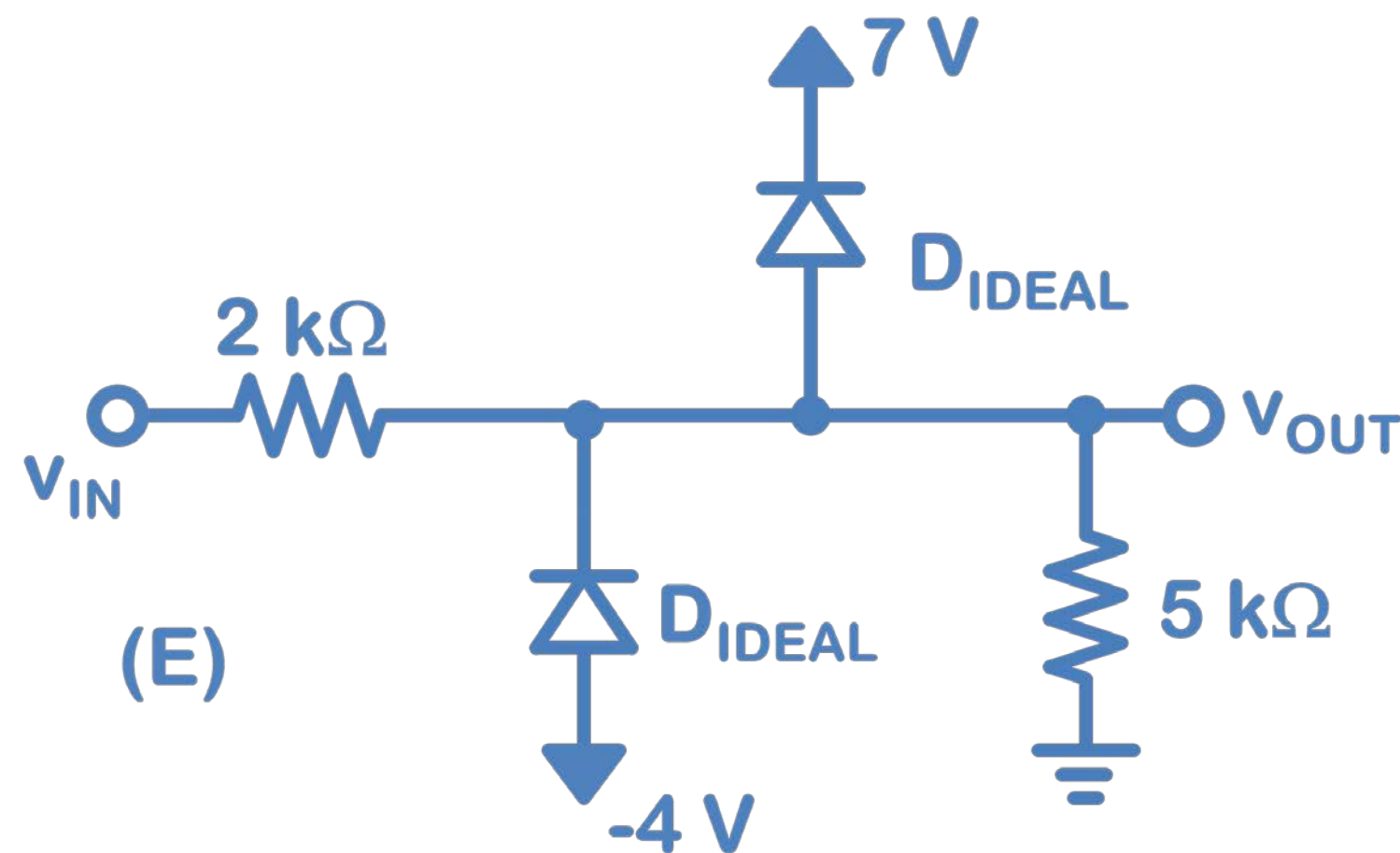a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.



$$\begin{aligned} v_{OUT} &= -4, \text{ when } v_{IN} < -28/5 \\ v_{OUT} &= (5/7)v_{IN}, \text{ when } -28/5 < v_{IN} < 49/7 \\ v_{OUT} &= 7, \text{ when } v_{IN} > 49/7 \end{aligned}$$

*the equal can go with either case

