

EECS 312 – Electronic Circuits I – Homework 3
Carl Leuschen – Spring 2025

1. Fill in the missing values in the table. Diodes A to F are Junction Diodes. Assume $V_T=25\text{mV}$.

Diode	I_S (A)	n	V_D (V)	I_D (mA)	P_D (mW)
A	1×10^{-14}	1.2	0.65		
B	1×10^{-9}	1.7		3	
C	3×10^{-12}		0.68	2	
D		1.9	0.5	.01	
E		1.1		1.3	1
F	1×10^{-13}		.67		20

2. A Junction Diode with $n=1.3$ conducts 0.8mA at 0.7V , $I_D(V_D=0.7\text{V})=0.8\text{mA}$.
a. How much does the device conduct (find I_D) at $V_D=0.8\text{V}$? 0.6V ? 0.5V ?

b. What voltage (find V_D) would produce a current of $I_D=80\mu\text{A}$? 8mA ? 80mA ?

3. Find the I_1 and V_1 in the following circuit. Use $I_S=7 \times 10^{-13}\text{A}$ and $n=1.5$ for the diodes.

