

EECS 312 – Electronic Circuits I – Homework 3
Carl Leuschen – Spring 2025

1. Fill in the missing values in the table. Diodes A to F are Junction Diodes. Assume $V_T=25\text{mV}$.

Diode	I_S (A)	n	V_D (V)	I_D (mA)	P_D (mW)
A	1×10^{-14}	1.2	0.65	.025	.017
B	1×10^{-9}	1.7	.634	3	1.9
C	3×10^{-12}	1.34	0.68	2	1.4
D	2.68×10^{-10}	1.9	0.5	.01	0.005
E	9.24×10^{-16}	1.1	.77	1.3	1
F	1×10^{-13}	1.01	.67	29	20

2. A Junction Diode with $n=1.3$ conducts 0.8mA at 0.7V , $I_D(V_D=0.7\text{V})=0.8\text{mA}$.

a. How much does the device conduct (find I_D) at $V_D=0.8\text{V}$? 0.6V ? 0.5V ?
 $V_2 - V_1 = n \cdot V_T \cdot \ln(I_2/I_1)$ or $I_2 = I_1 \cdot \exp((V_2 - V_1)/(nV_T))$


17.4mA, 0.0369mA, 0.0017mA

b. What voltage (find V_D) would produce a current of $I_D=80\mu\text{A}$? 8mA ? 80mA ?

0.6252V, 0.7748V, 0.8497V

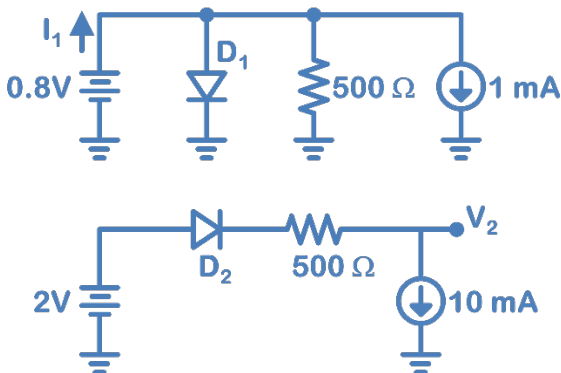3. Find the I_1 and V_1 in the following circuit. Use $I_S=7 \times 10^{-13}\text{A}$ and $n=1.5$ for the diodes.

$$I_1 = I_S \cdot \exp(.8/nV_T) + .8/500 + .001 = 3.9\text{mA}$$



$$V_2 = 2 - n \cdot V_T \cdot \ln(.01/I_S) - 500 \cdot .01 = -3.87\text{V}$$