

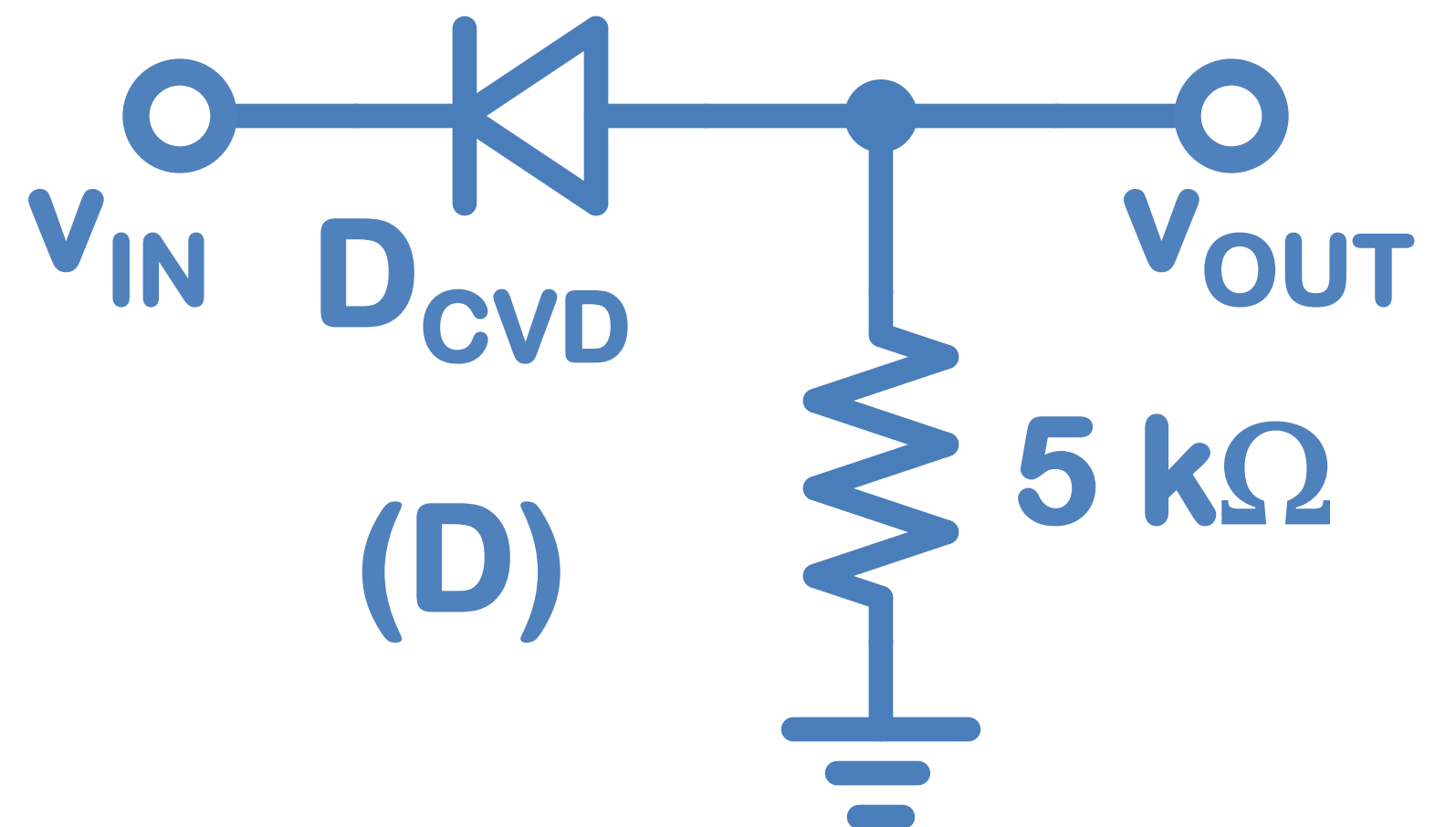
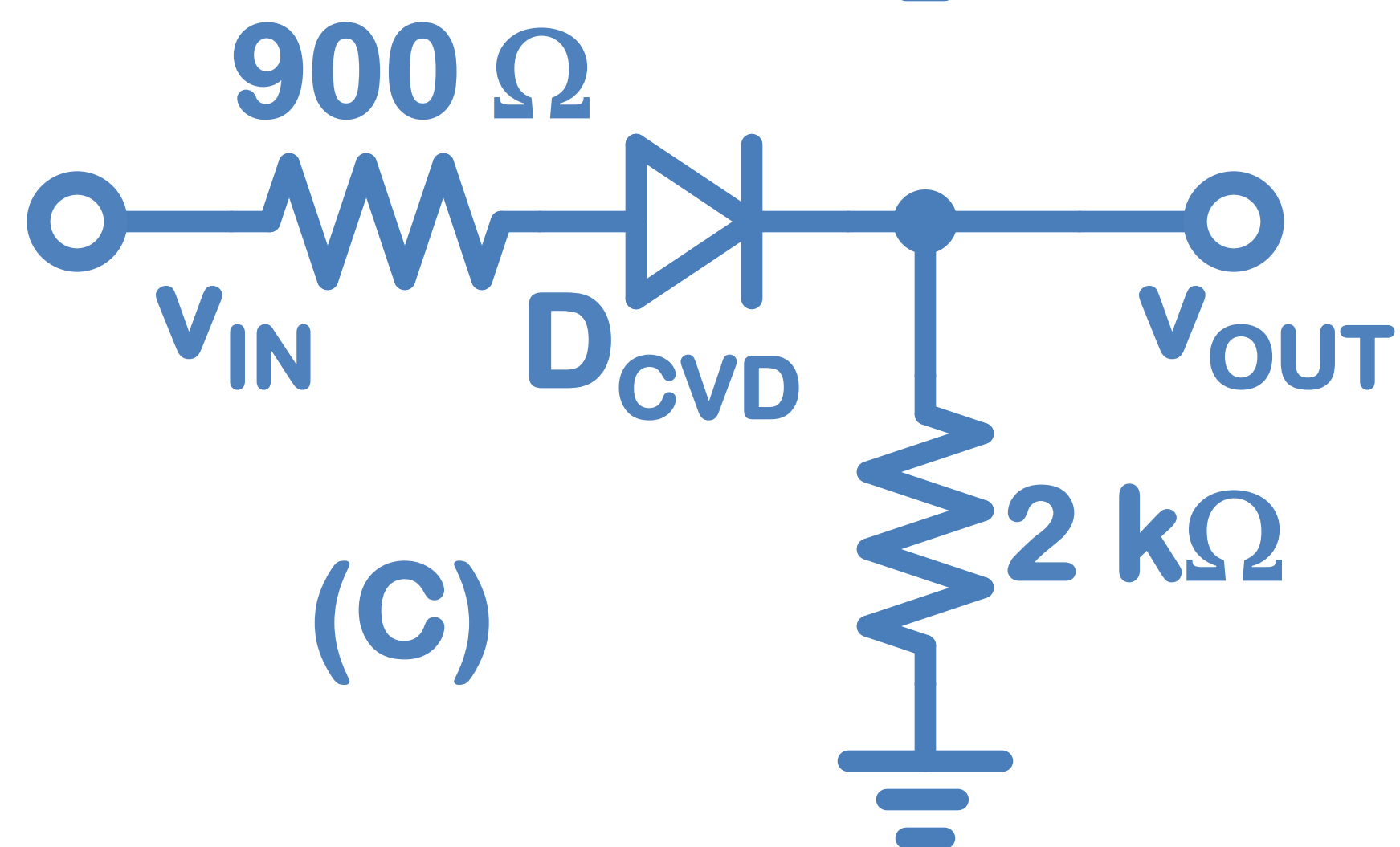
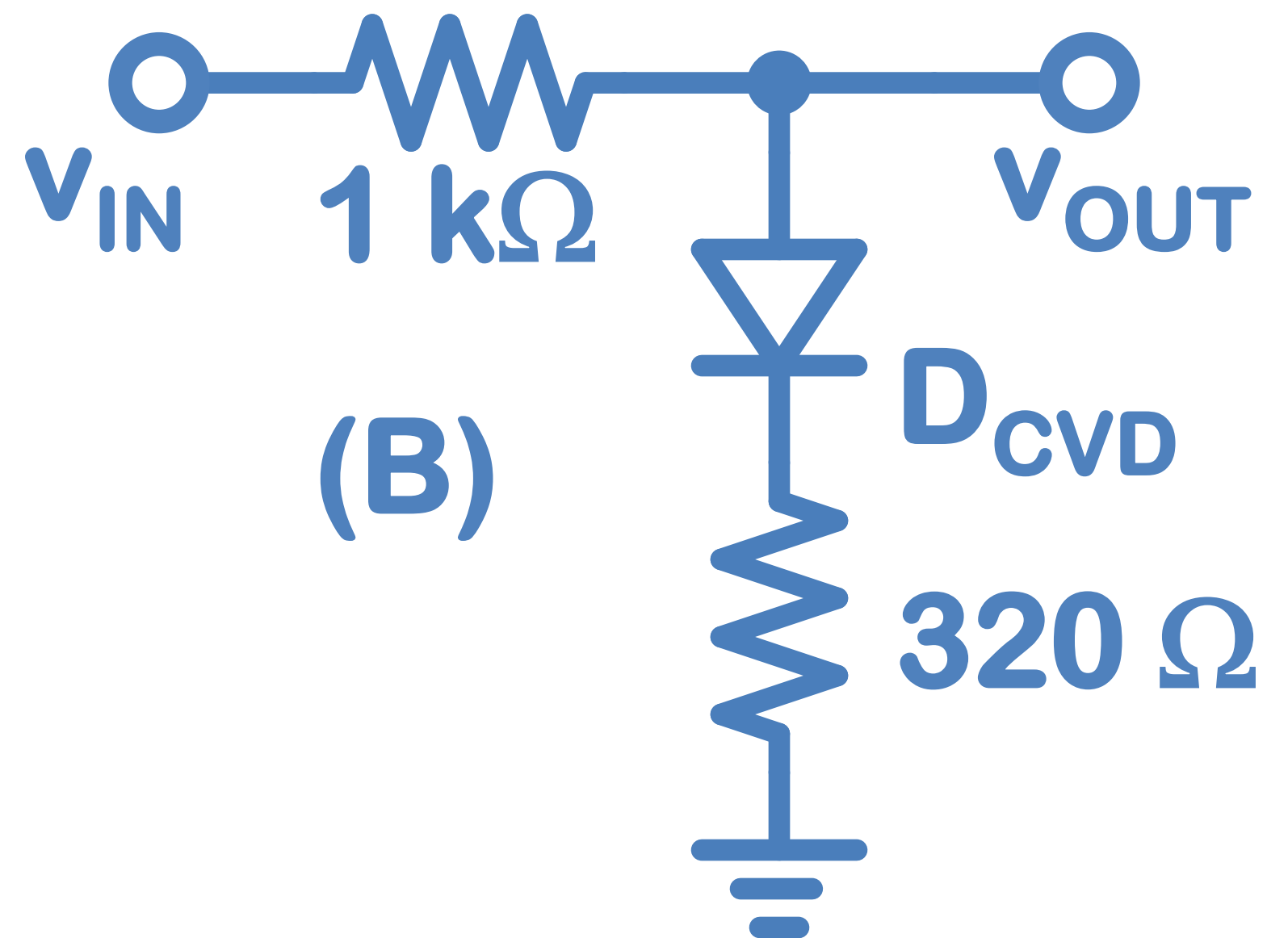


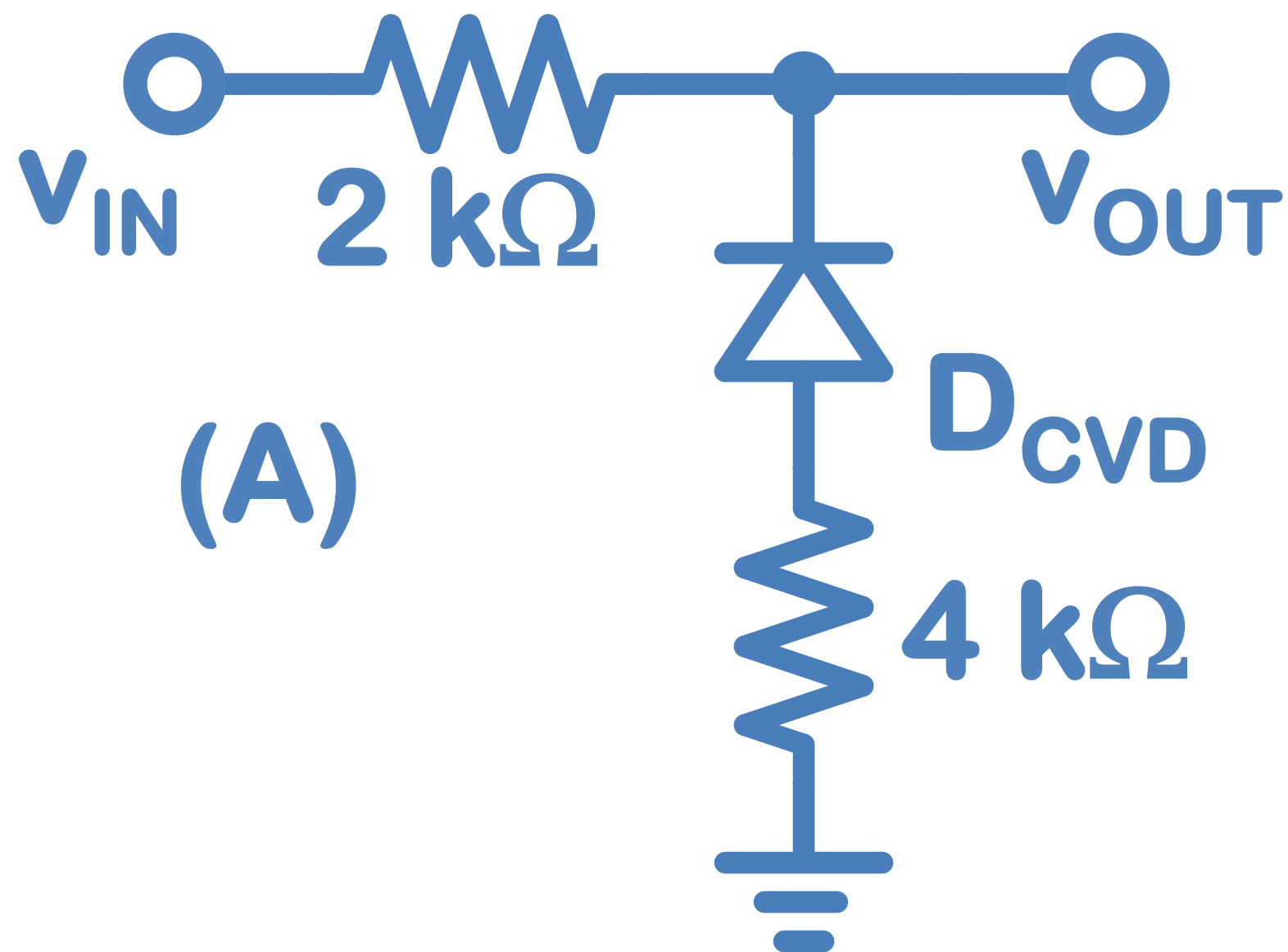Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(A)

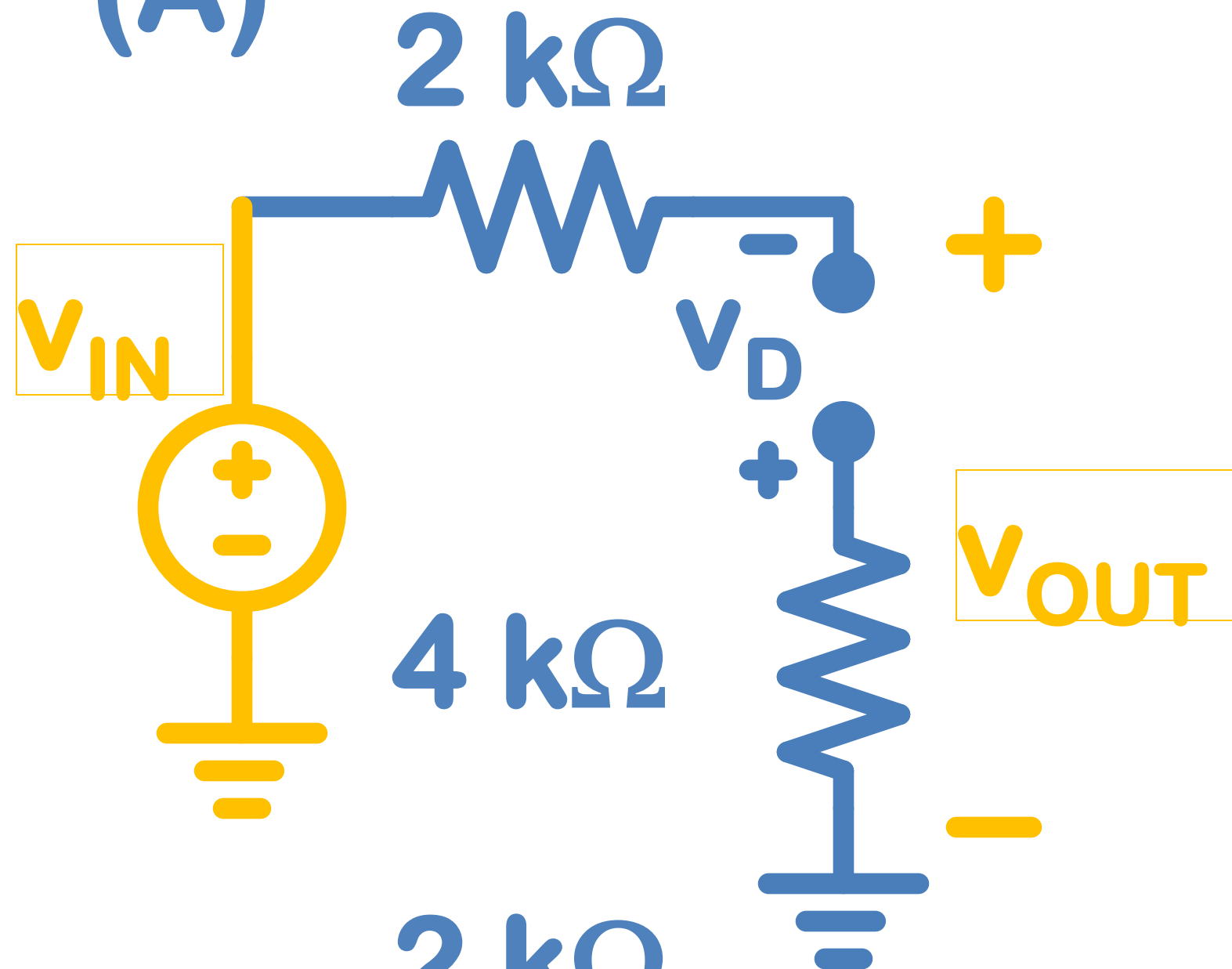

$$v_{OUT} = v_{IN}$$

$$v_D = -v_{IN}$$
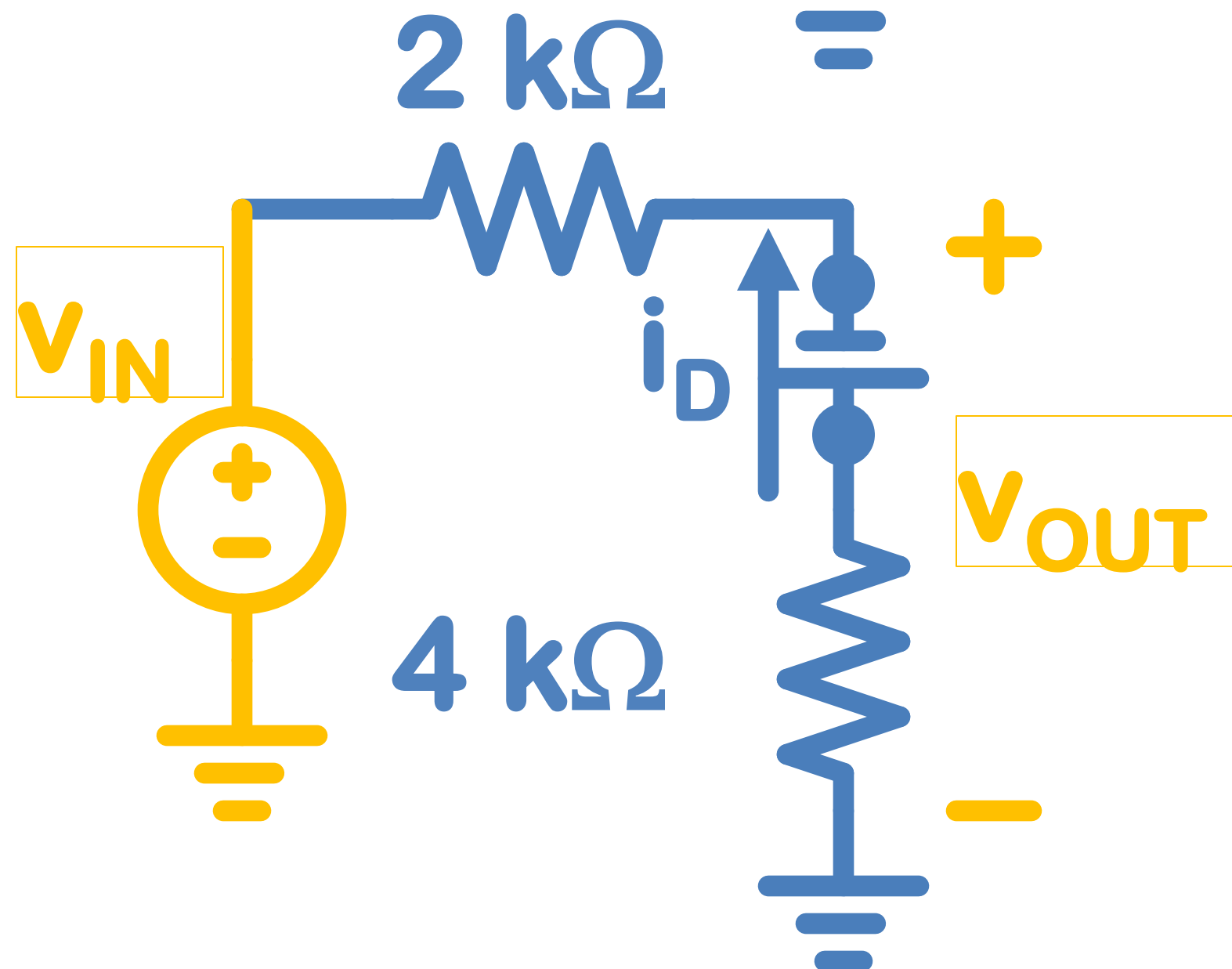
$$v_D < 0.7, \text{ when } v_{IN} > -0.7$$



$$v_{OUT} = 0.67(v_{IN} + 0.7) - 0.7$$


$$v_{OUT} = 0.67v_{IN} - 0.233$$

$$i_D = -(v_{IN} + 0.7)/6000$$

$$i_D > 0, \text{ when } v_{IN} < -0.7$$

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(A)

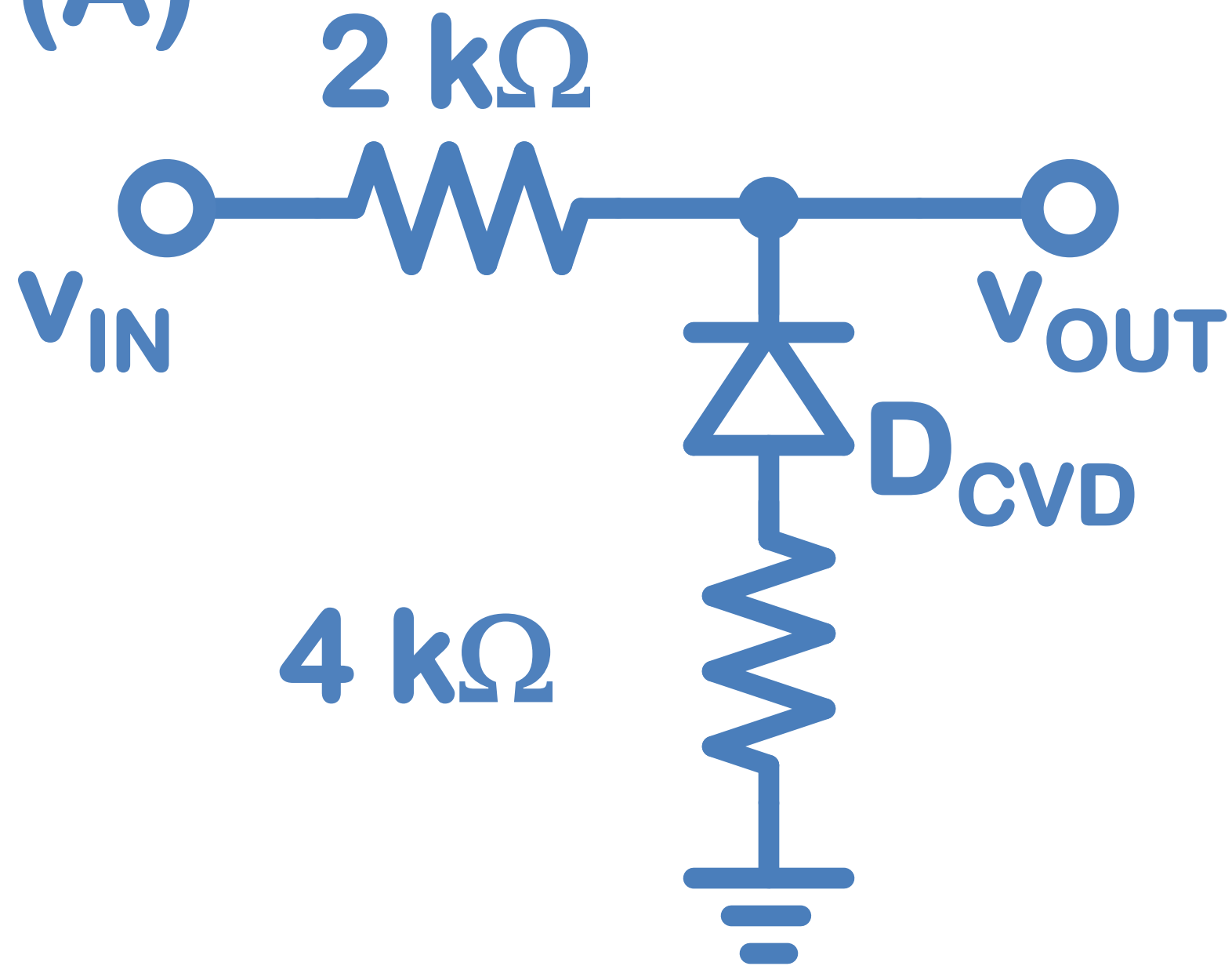

$$v_{OUT} = .67v_{IN}, -.23 \text{ when } v_{IN} < -0.7$$


$$v_{OUT} = v_{IN}, \text{ when } v_{IN} > -0.7$$

*the equal can go with either case

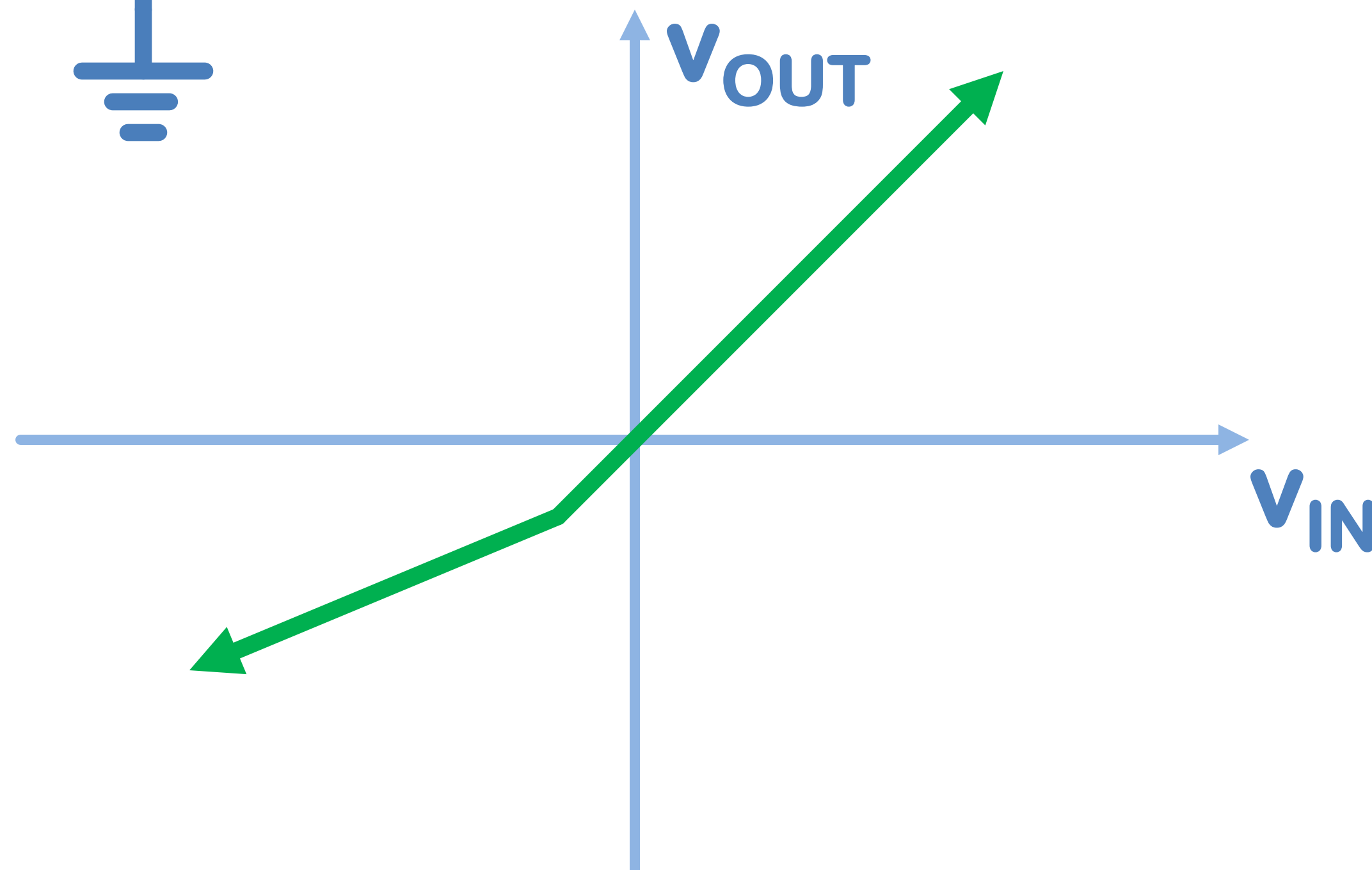

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(B)

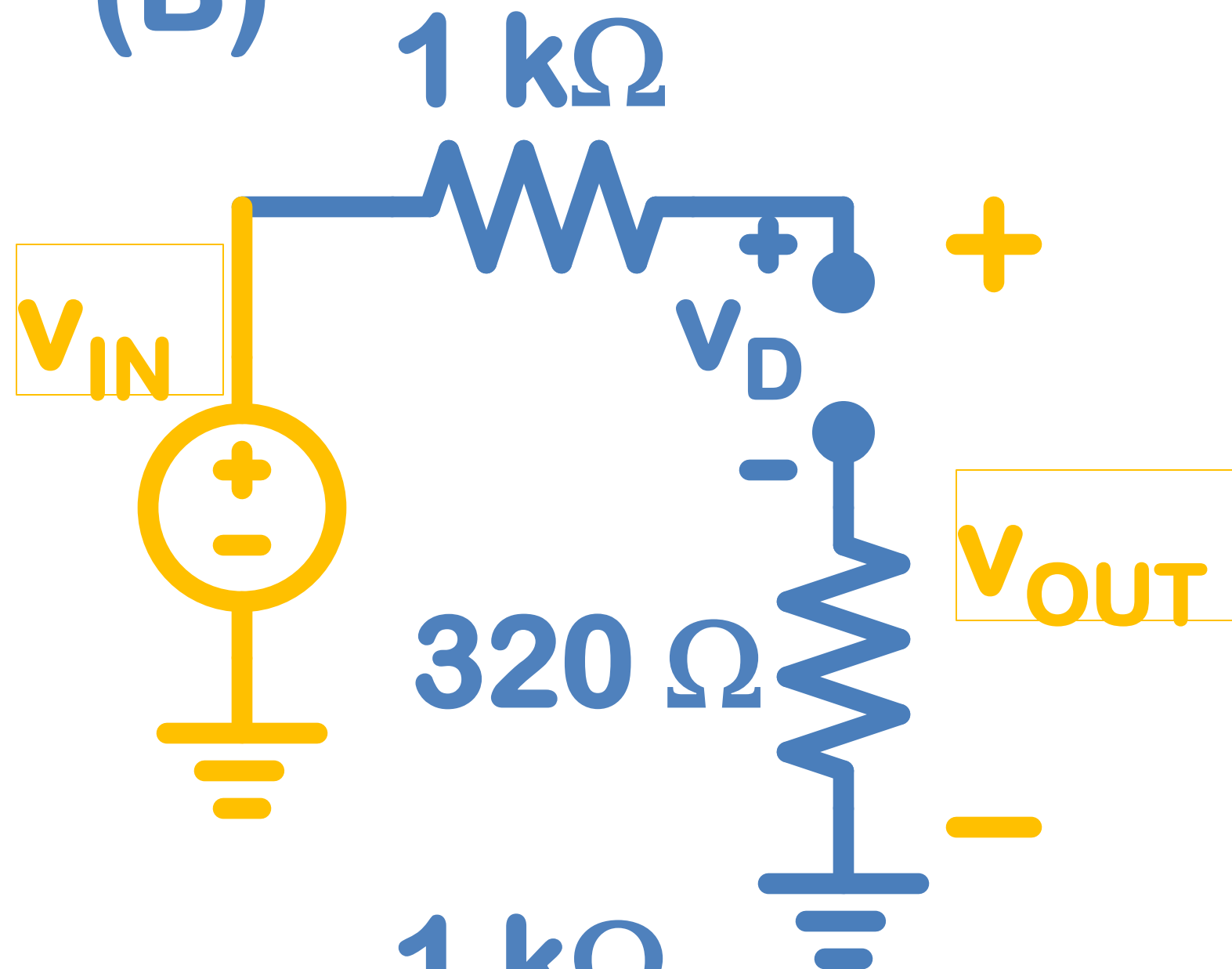

$$v_{OUT} = v_{IN}$$

$$v_D = v_{IN}$$
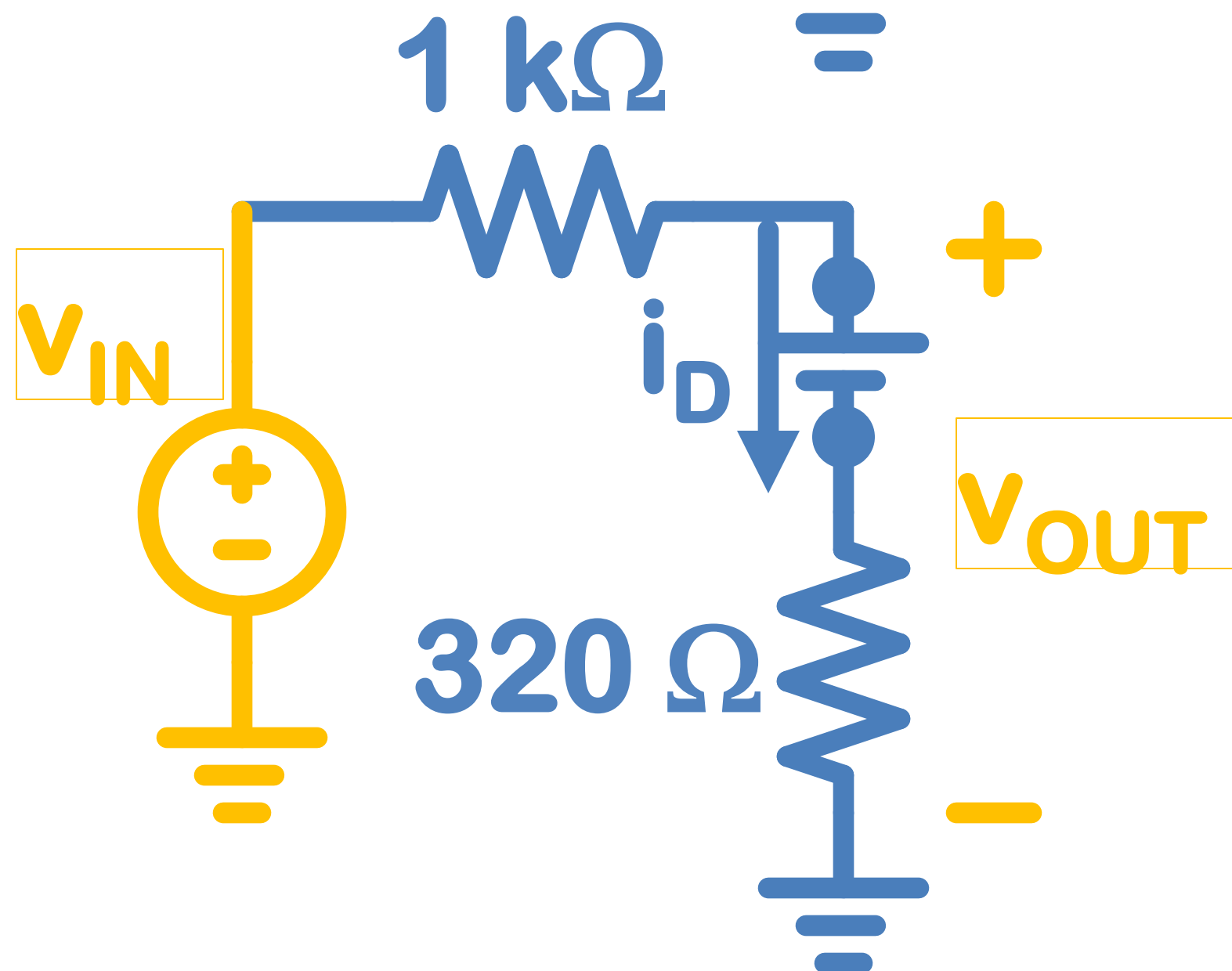
$$v_D < 0.7, \text{ when } v_{IN} < 0.7$$



$$v_{OUT} = 0.24(v_{IN} - 0.7) + 0.7$$


$$v_{OUT} = 0.24v_{IN} + 0.53$$

$$i_D = (v_{IN} - 0.7) / 1320$$

$$i_D > 0, \text{ when } v_{IN} > 0.7$$

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(B)

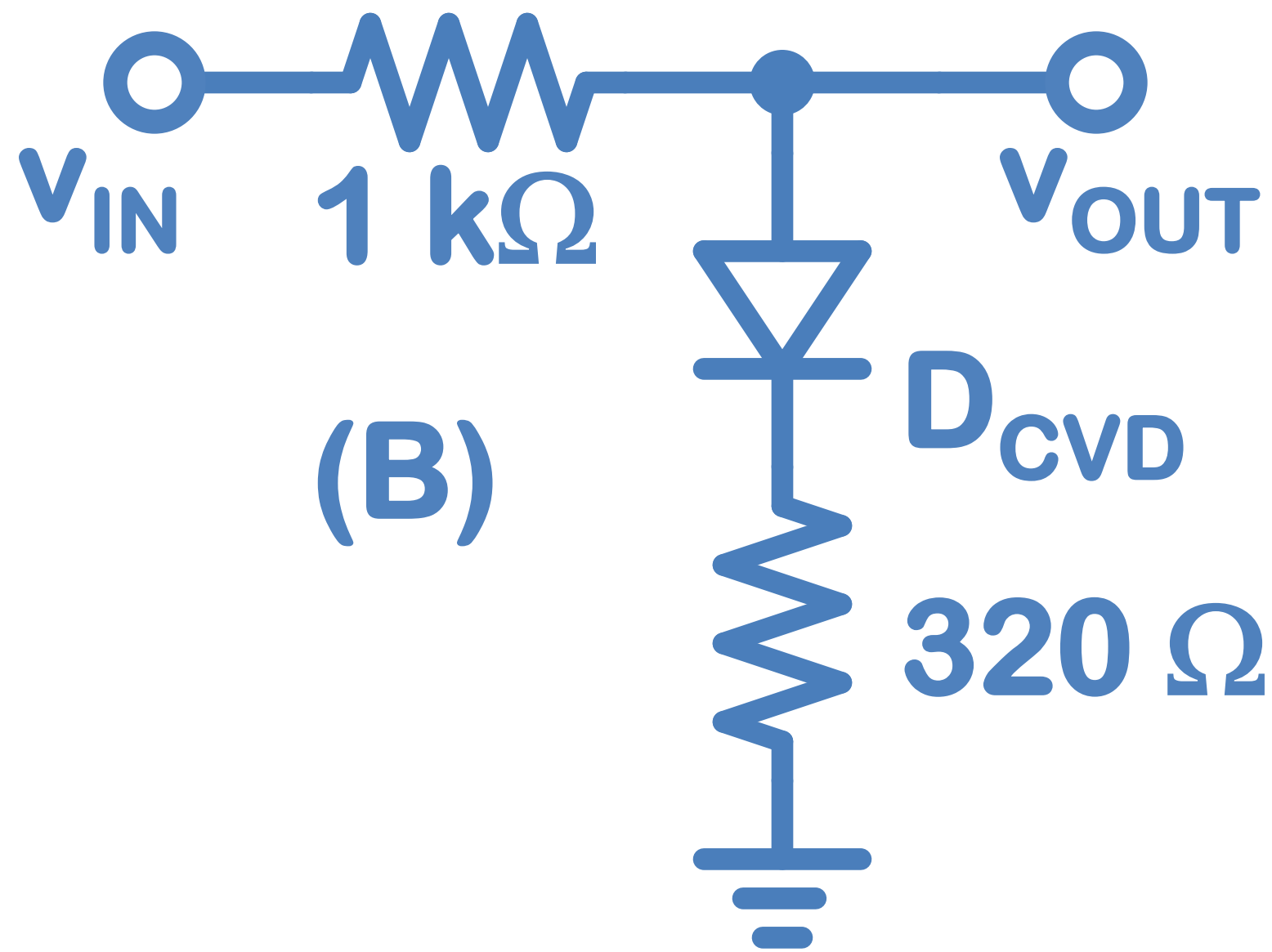

$$v_{OUT} = v_{IN}, \text{ when } v_{IN} < 0.7$$


$$v_{OUT} = 0.24v_{IN} + 0.53 \text{ when } v_{IN} > 0.7$$

*the equal can go with either case

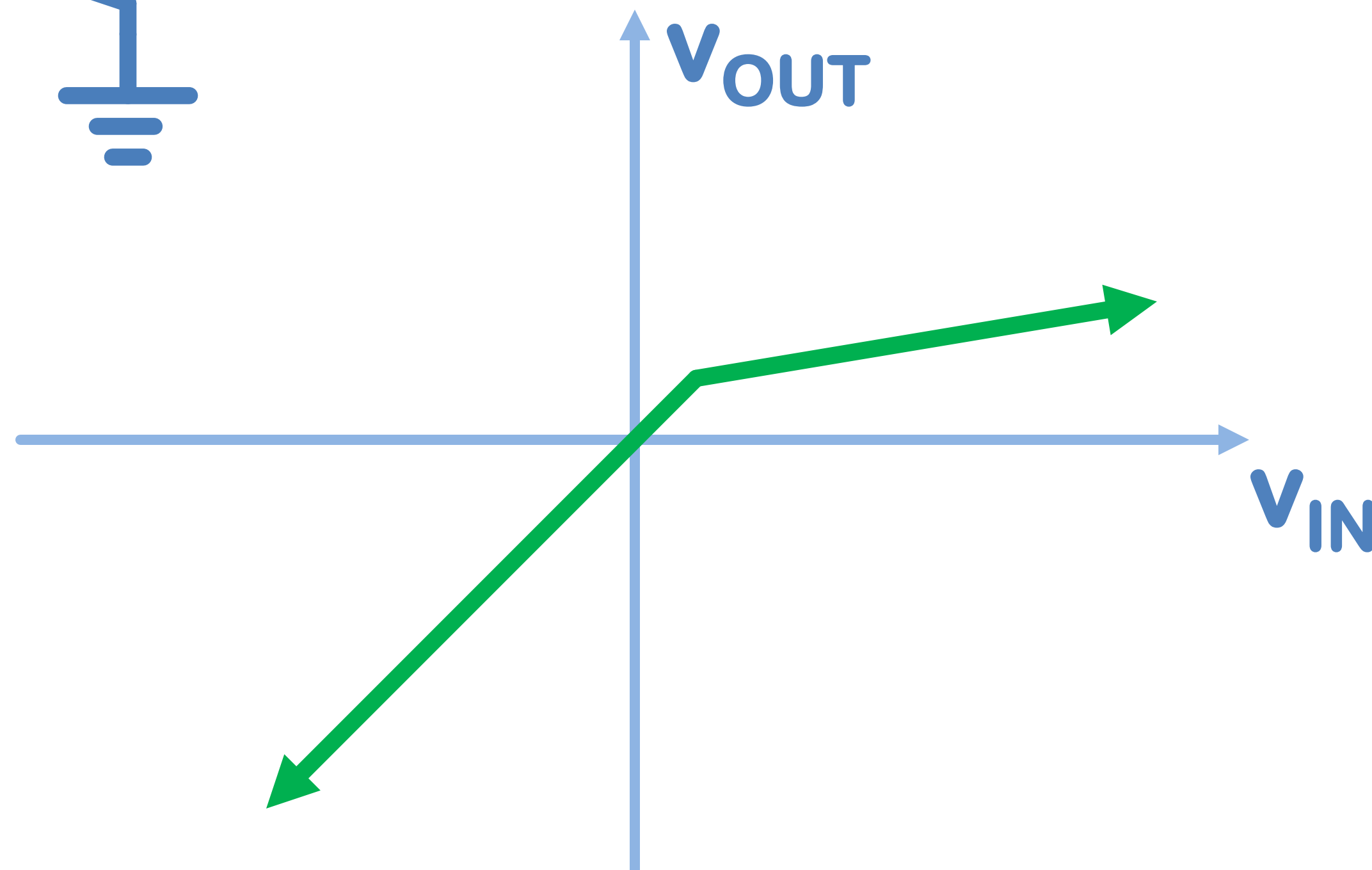

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(C) $900\ \Omega$

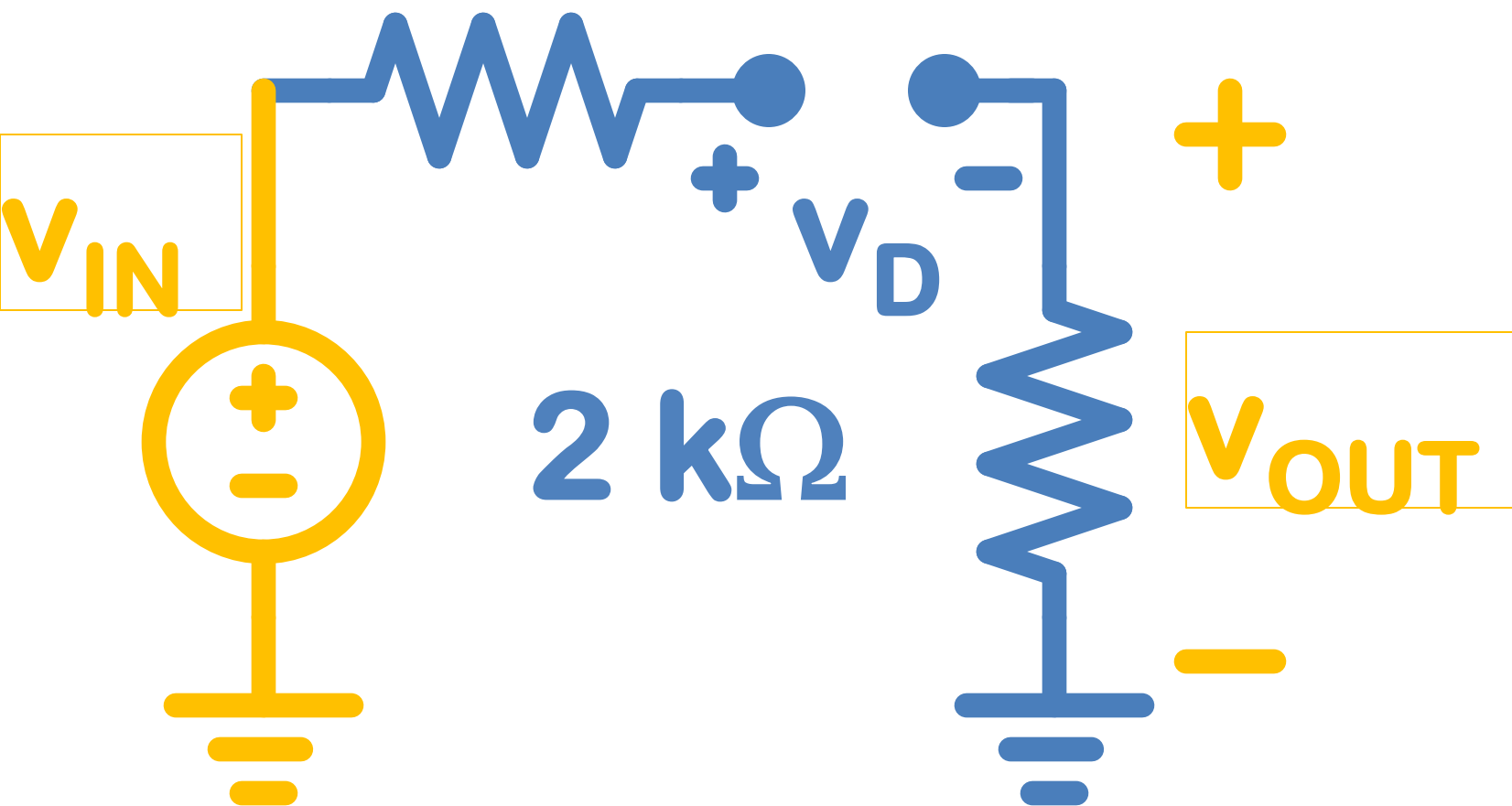

$$v_{OUT}=0$$

$$v_D=v_{IN}$$
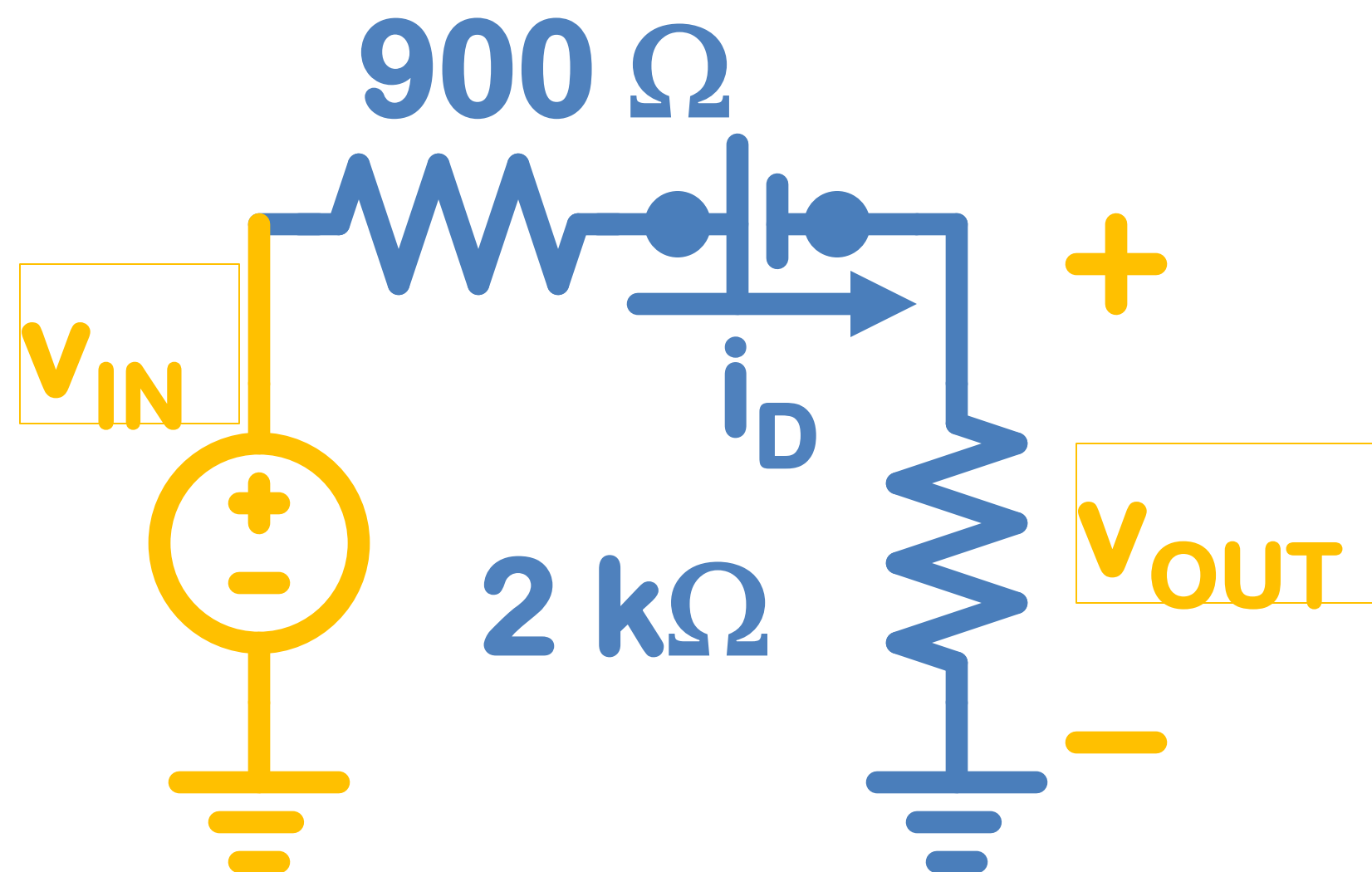
$$v_D < 0.7, \text{ when } v_{IN} < 0.7$$




$$v_{OUT}=0.7(v_{IN}-0.7)$$

$$i_D=(v_{IN}-0.7)2900$$

$$i_D > 0, \text{ when } v_{IN} > 0.7$$

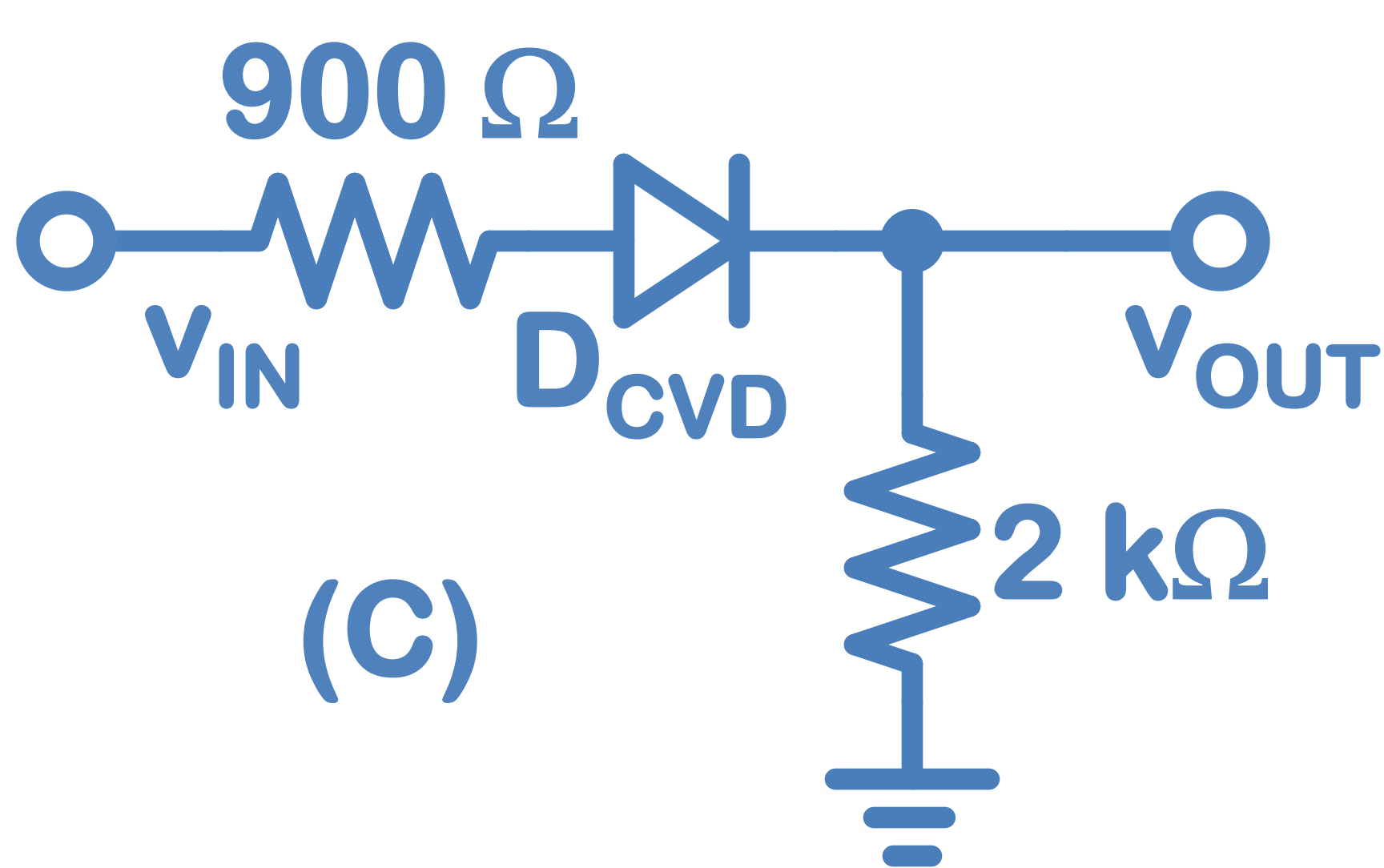
Find the equation and plot $v_{OUT}(v_{IN})$
for each circuit.



$$v_{OUT} = 0.7(v_{IN} - 0.7) \text{ when } v_{IN} > 0.7$$


$$v_{OUT} = 0, \text{ when } v_{IN} < 0.7$$

*the equal can go
with either case

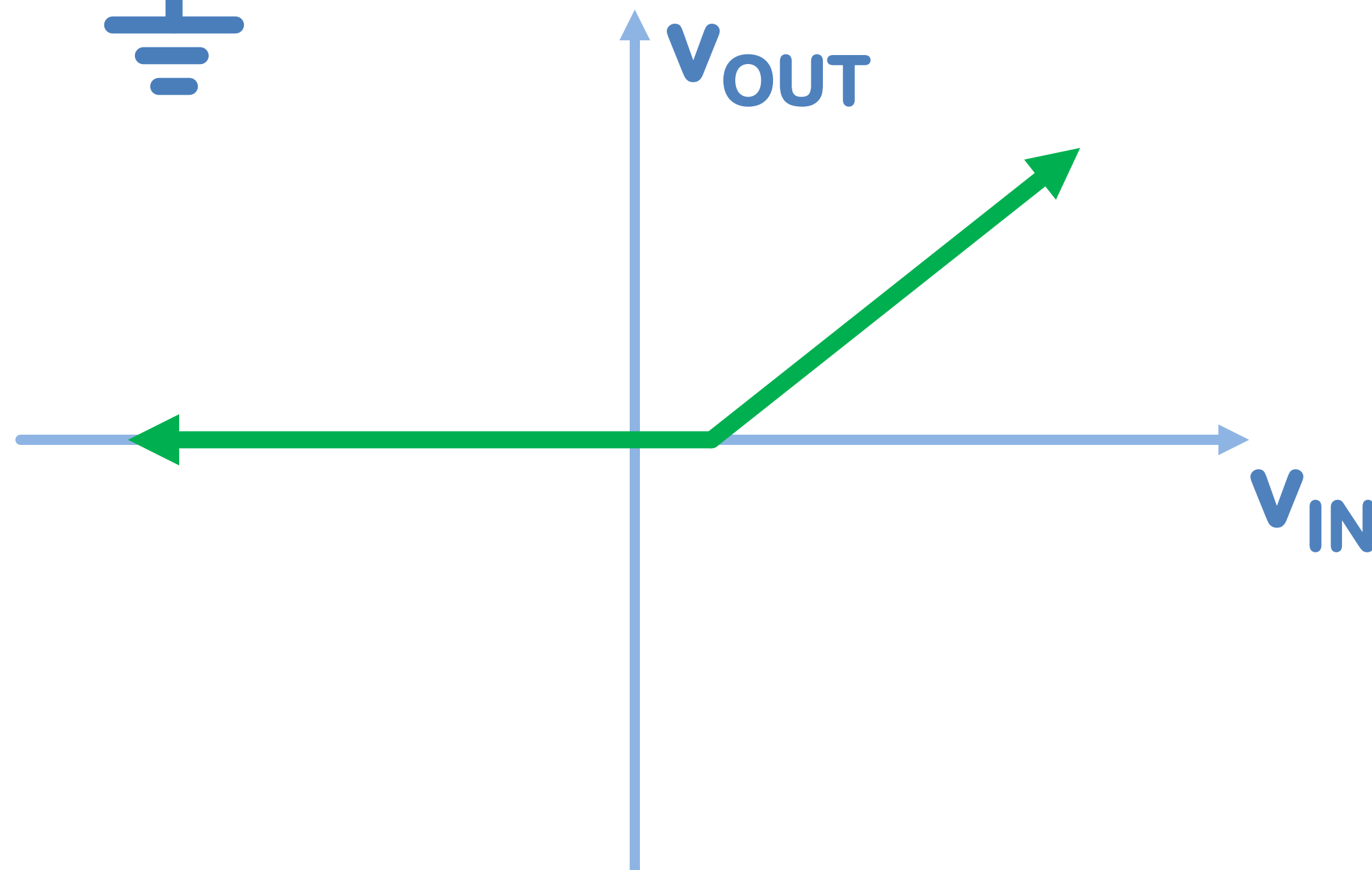

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(D)

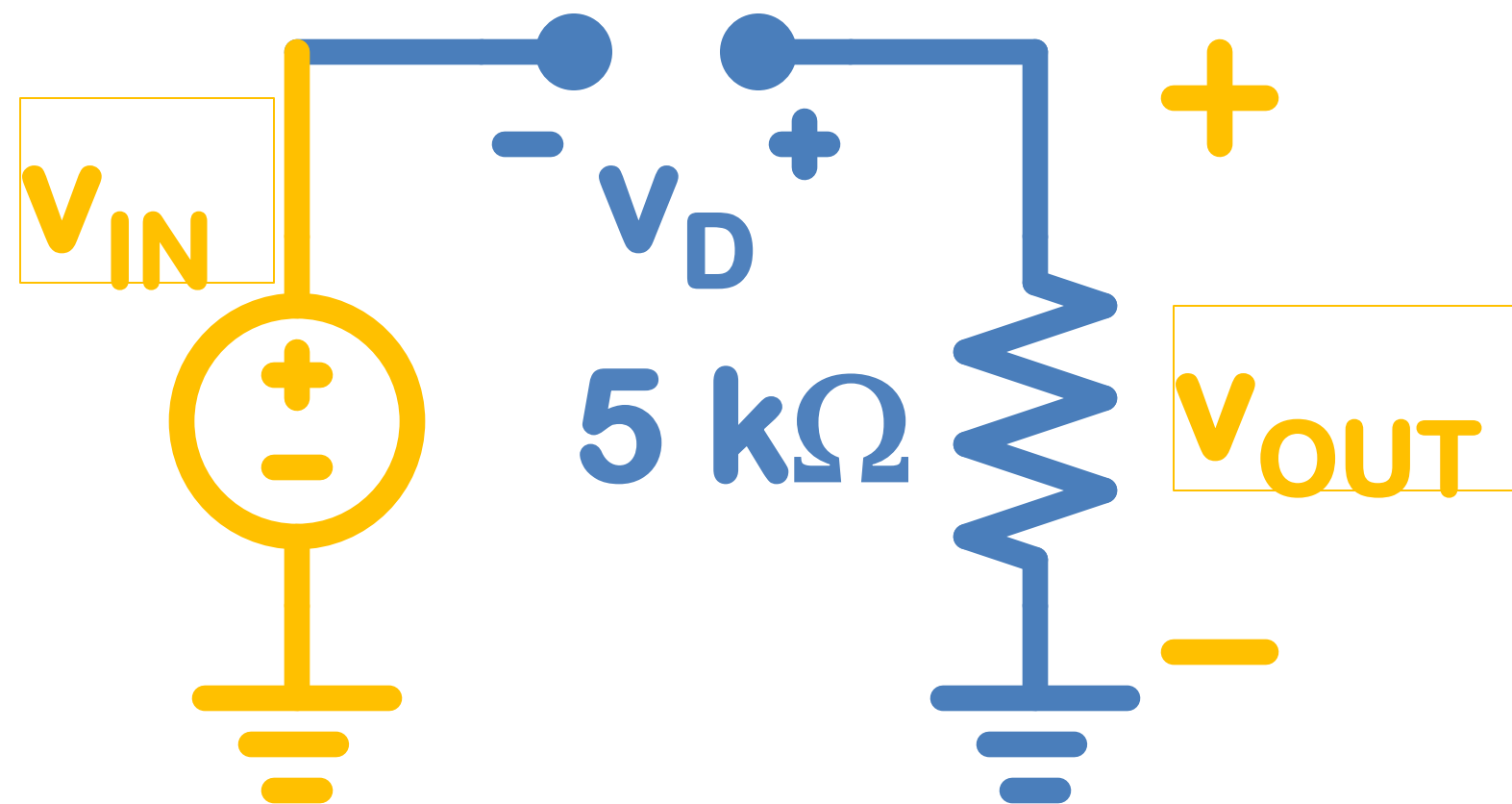

$$v_{OUT}=0$$

$$v_D = -v_{IN}$$
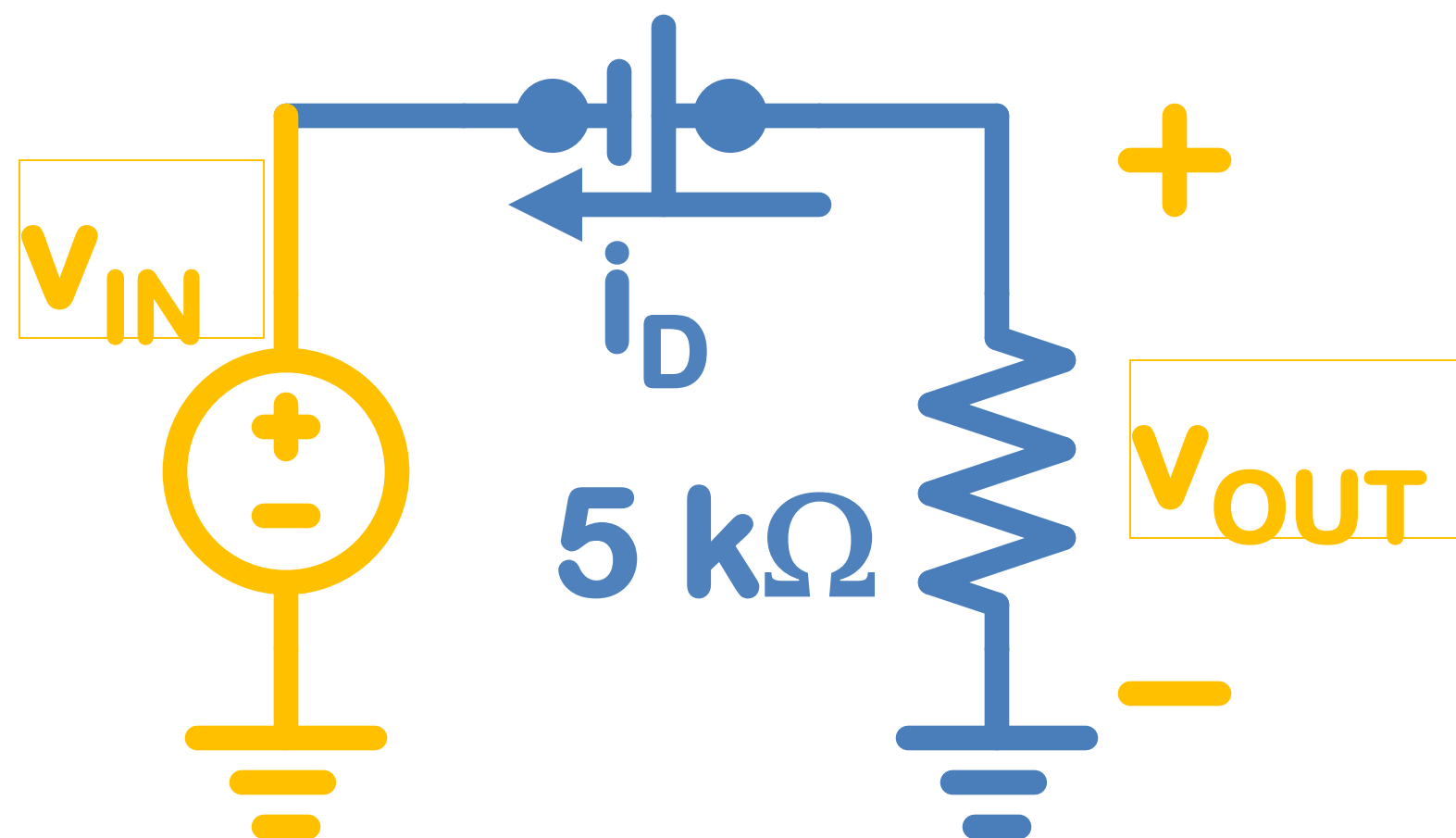
$$v_D < 0.7, \text{ when } v_{IN} > -0.7$$




$$v_{OUT} = v_{IN} + 0.7$$

$$i_D = -(v_{IN} + 0.7) / 5000$$


$$i_D > 0, \text{ when } v_{IN} < -0.7$$

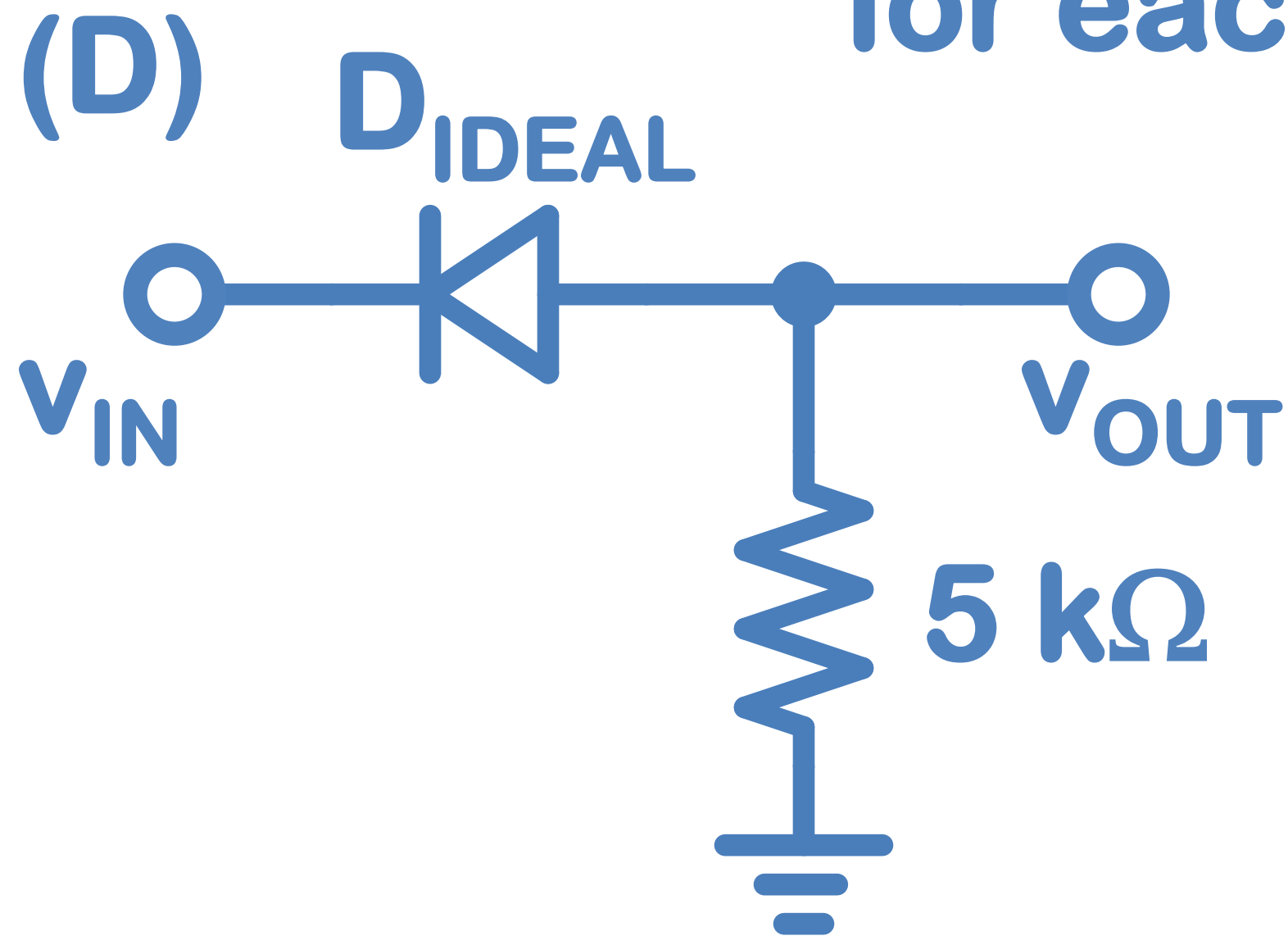Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.





$$v_{OUT}=0, \text{ when } v_{IN} > -0.7$$
$$v_{OUT}=v_{IN}+.7 \text{ when } v_{IN} < -0.7$$

*the equal can go with either case

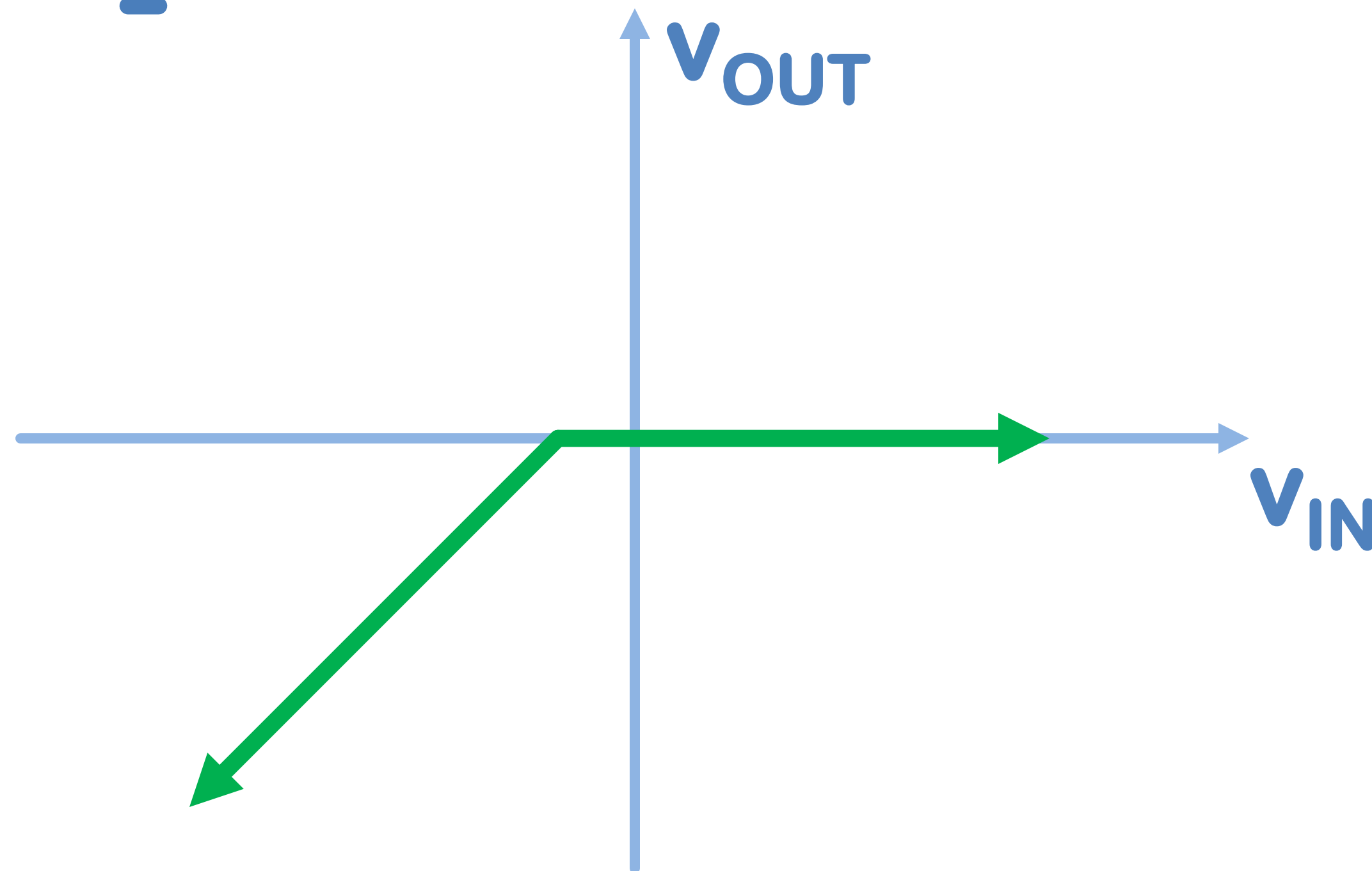


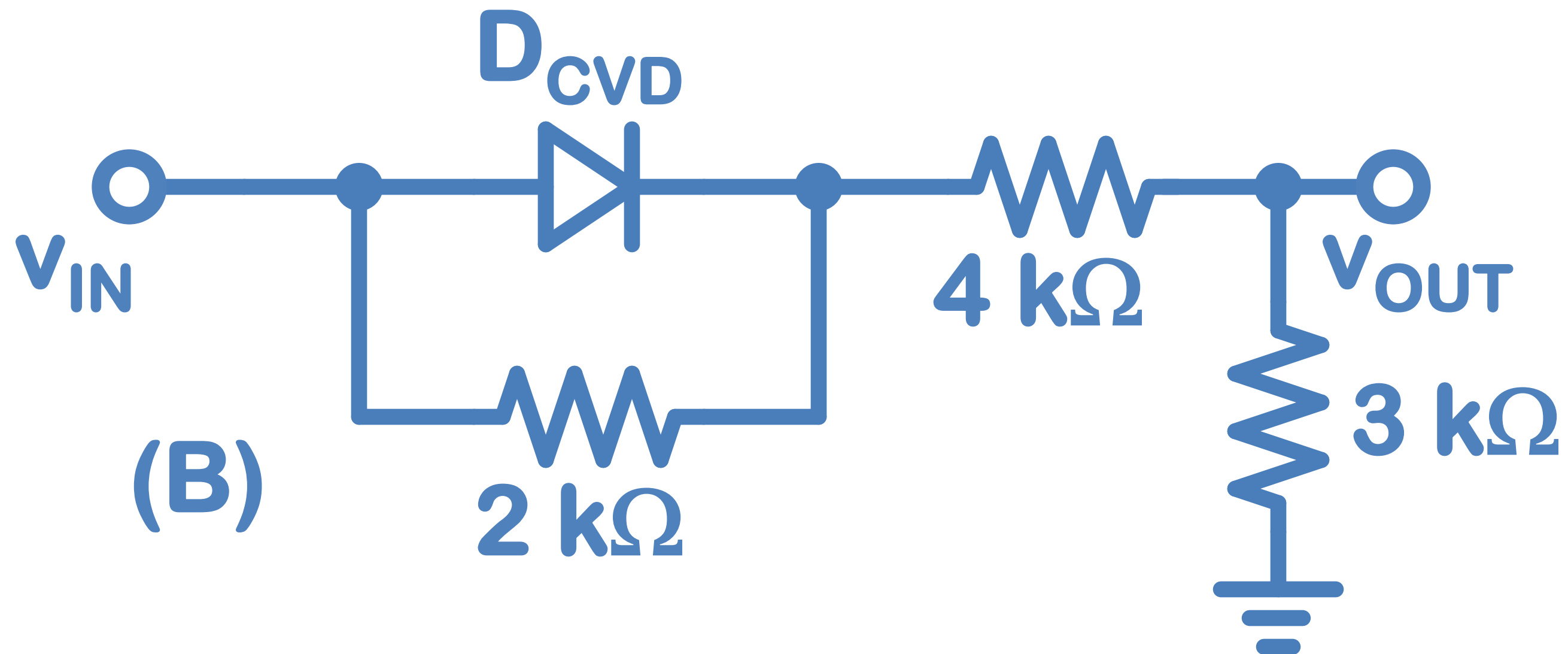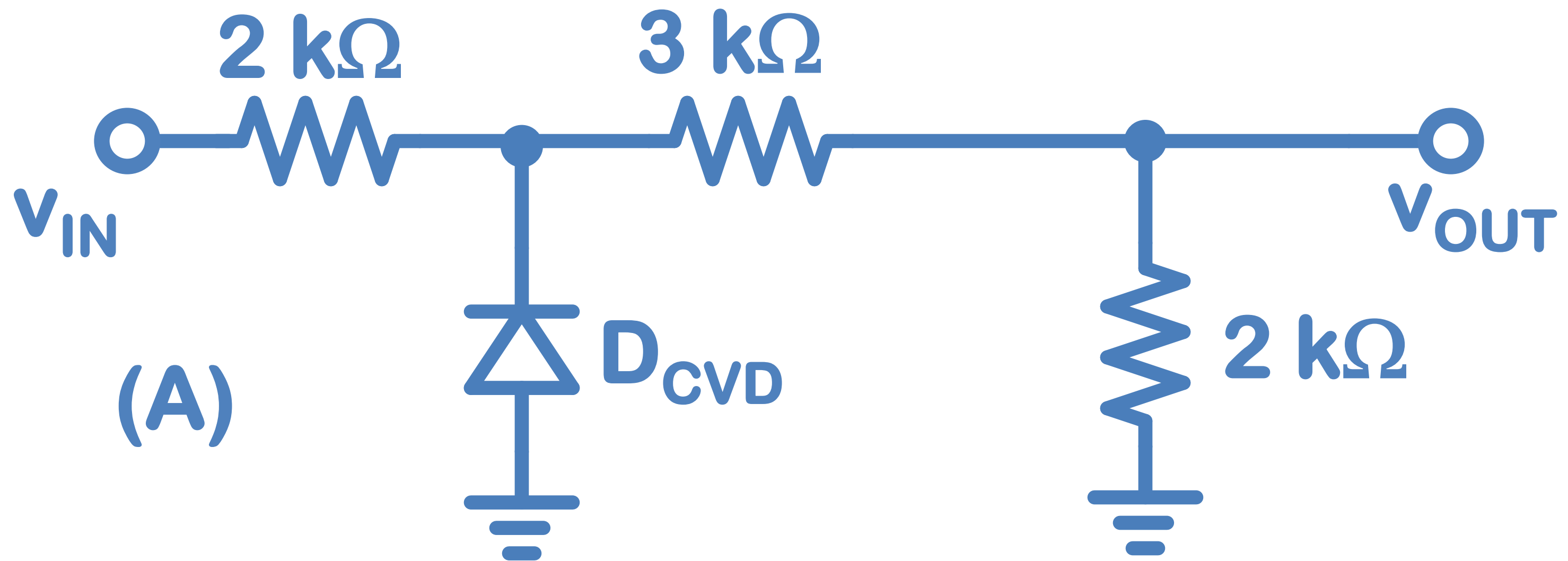Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(A)

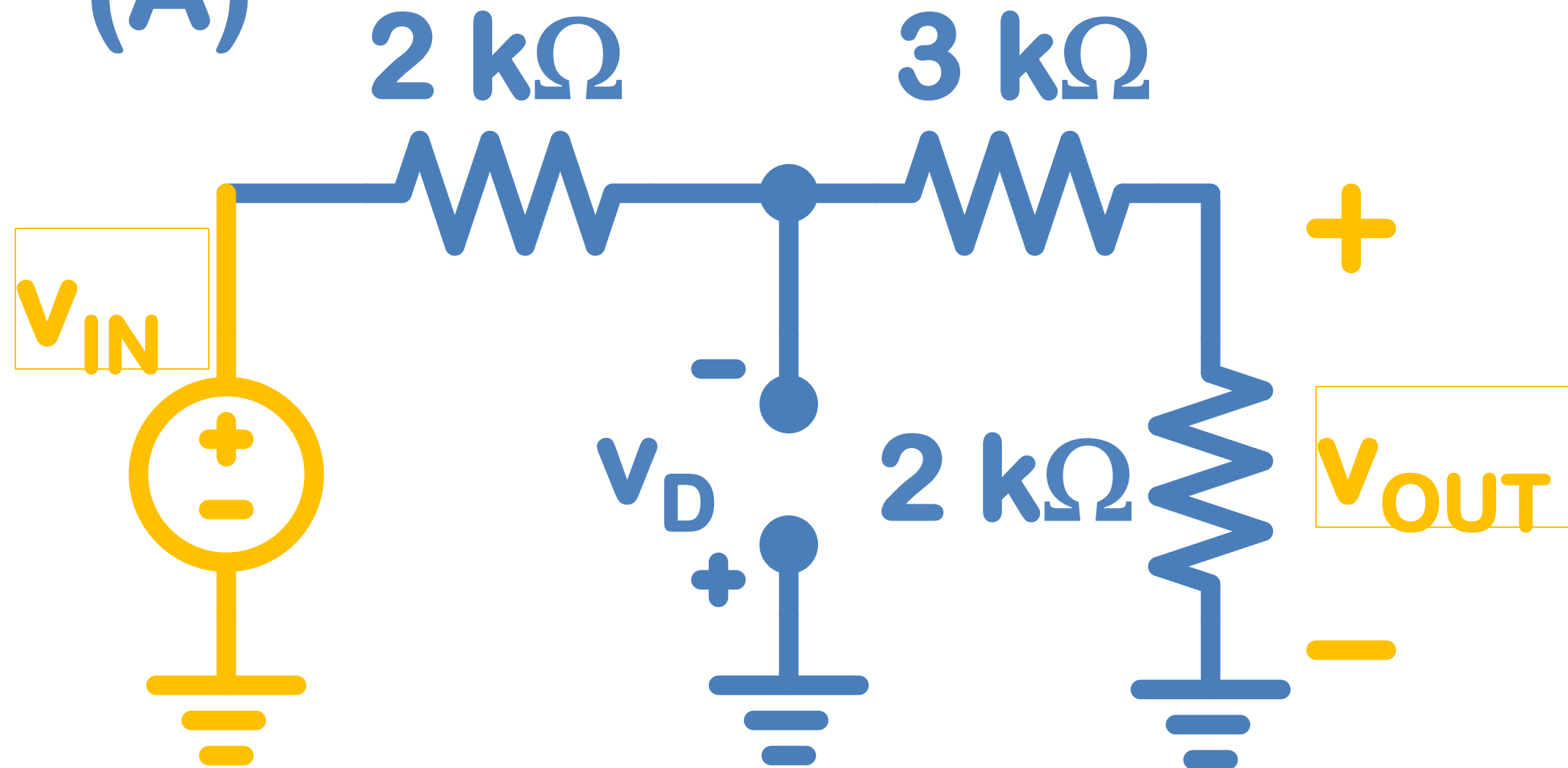

$$v_{OUT} = 0.286v_{IN}$$

$$v_D = -0.714v_{IN}$$
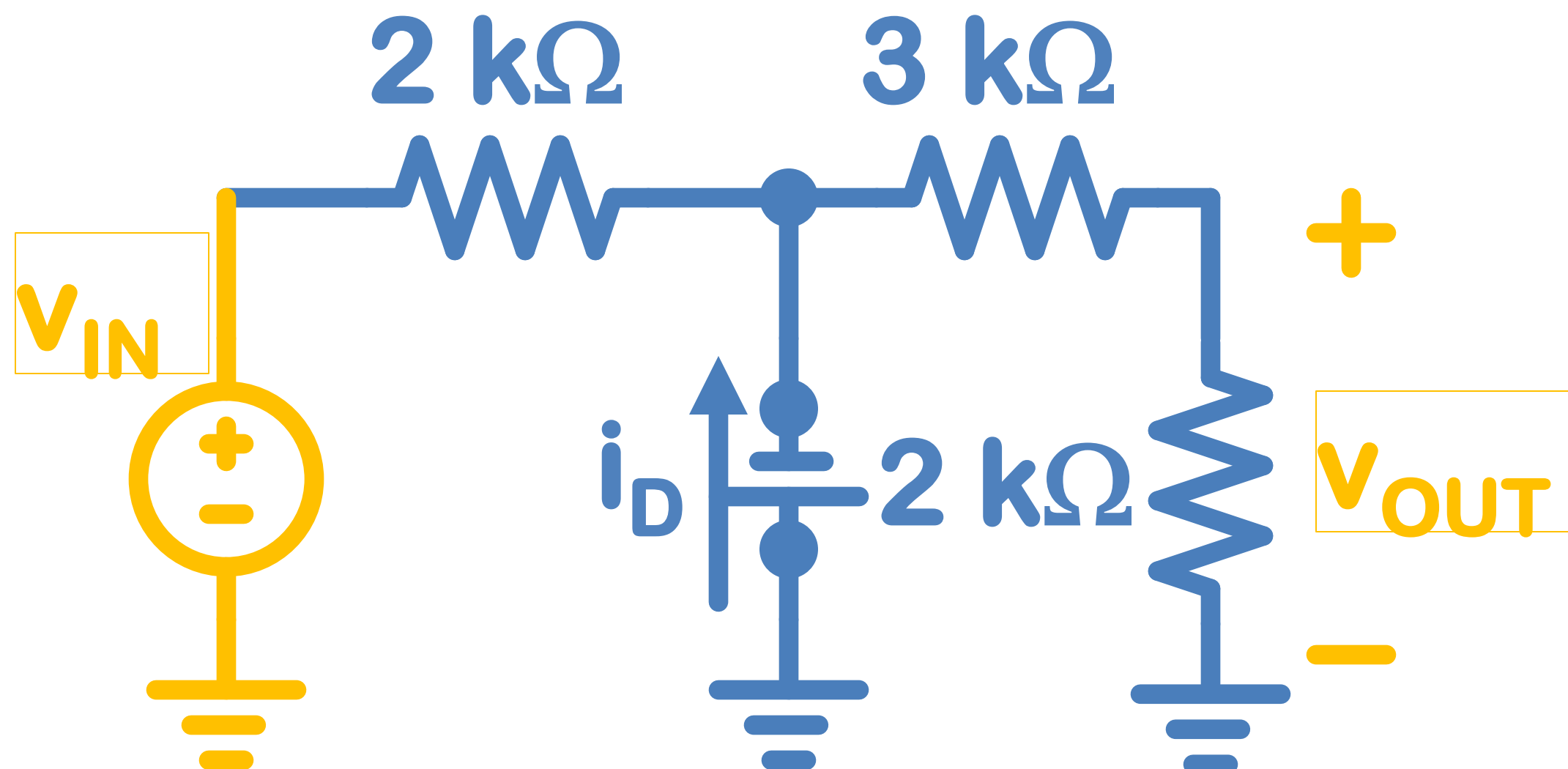
$$v_D < 0.7, \text{ when } v_{IN} > -0.98$$




$$v_{OUT} = -0.7(2/5) = 0.28$$

$$i_D = -(v_{IN} + 0.7)/2000 - 0.7/5000$$

$$i_D > 0, \text{ when } v_{IN} < -0.98$$

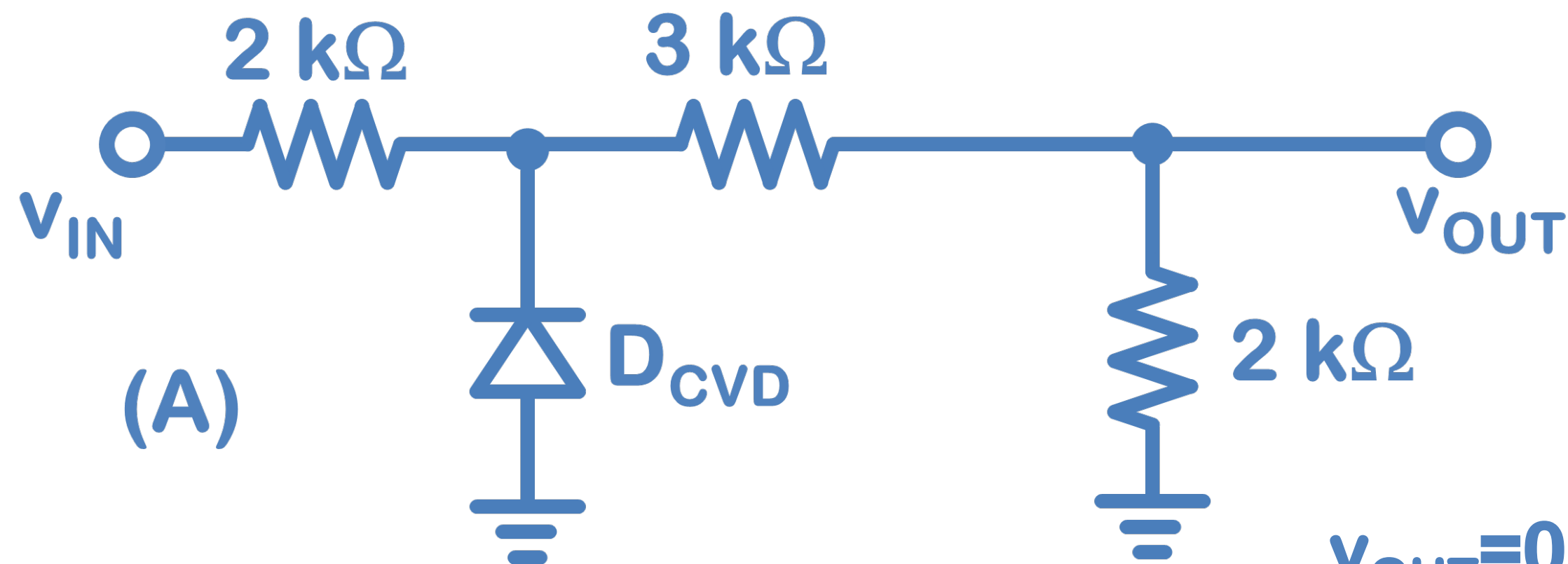
Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



$$v_{OUT} = 0.28, \text{ when } v_{IN} < -0.98$$


$$v_{OUT} = 0.286v_{IN}, \text{ when } v_{IN} > -0.98$$

*the equal can go with either case

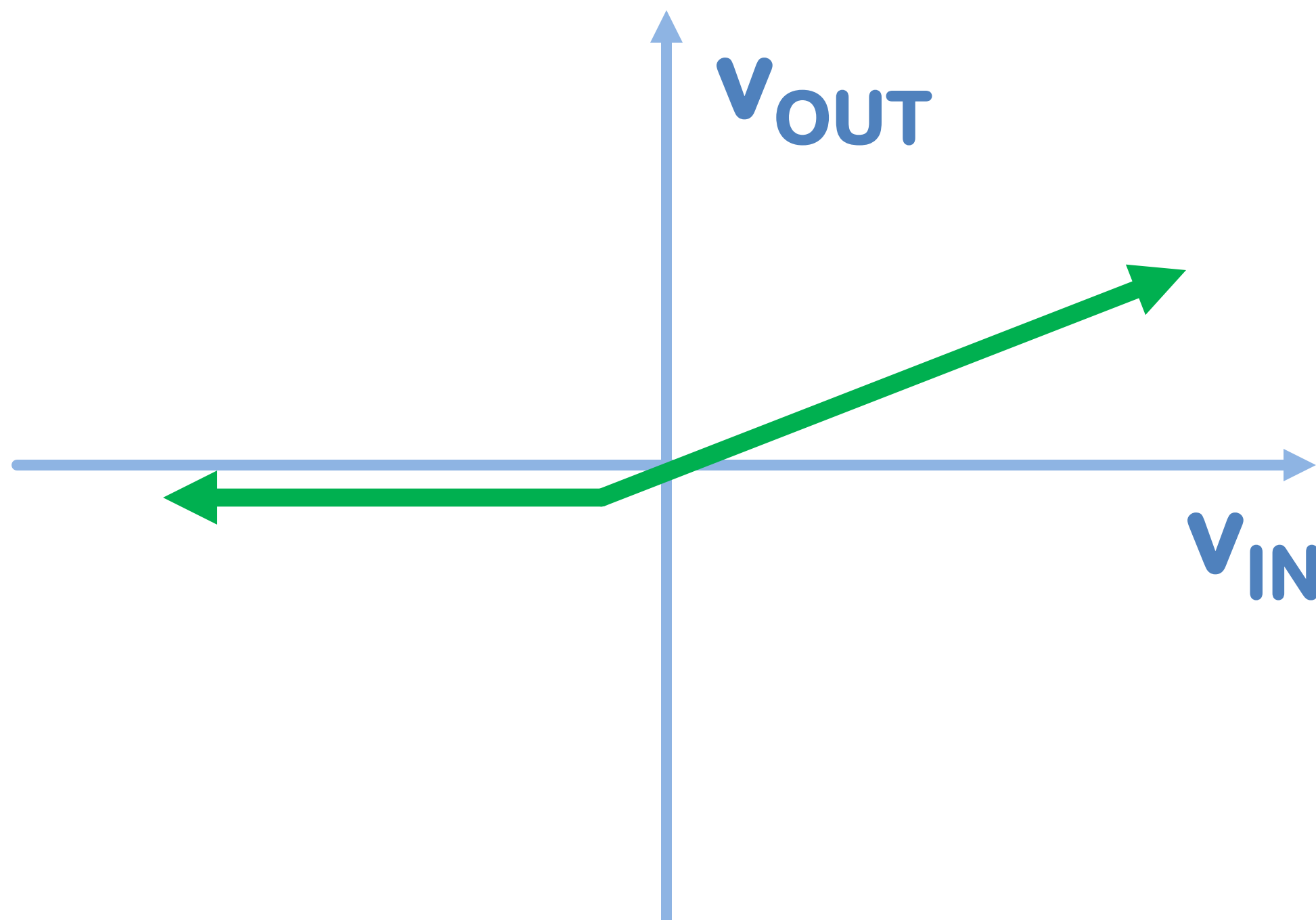

Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.


(A)

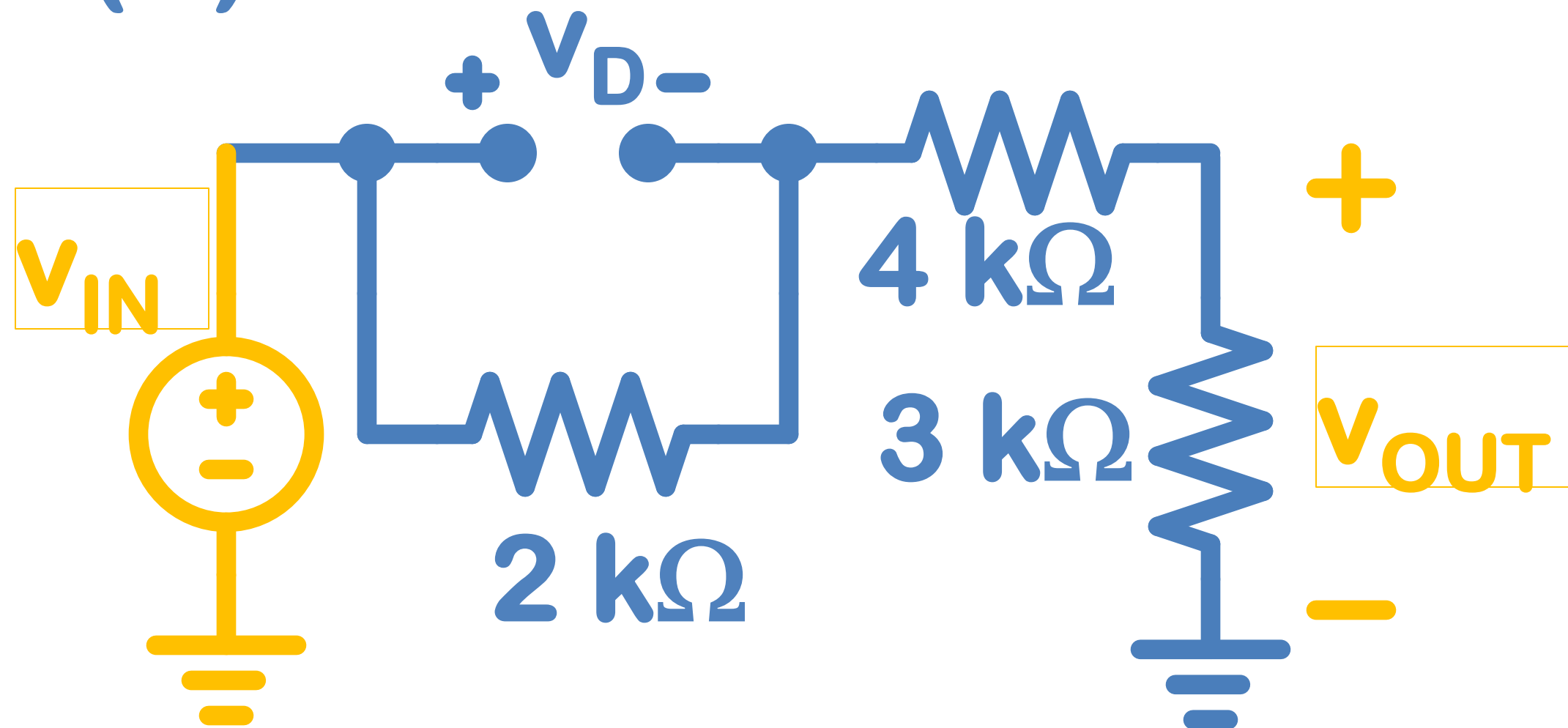

$$v_{OUT} = (3/9)v_{IN}$$

$$v_D = (2/9)v_{IN}$$
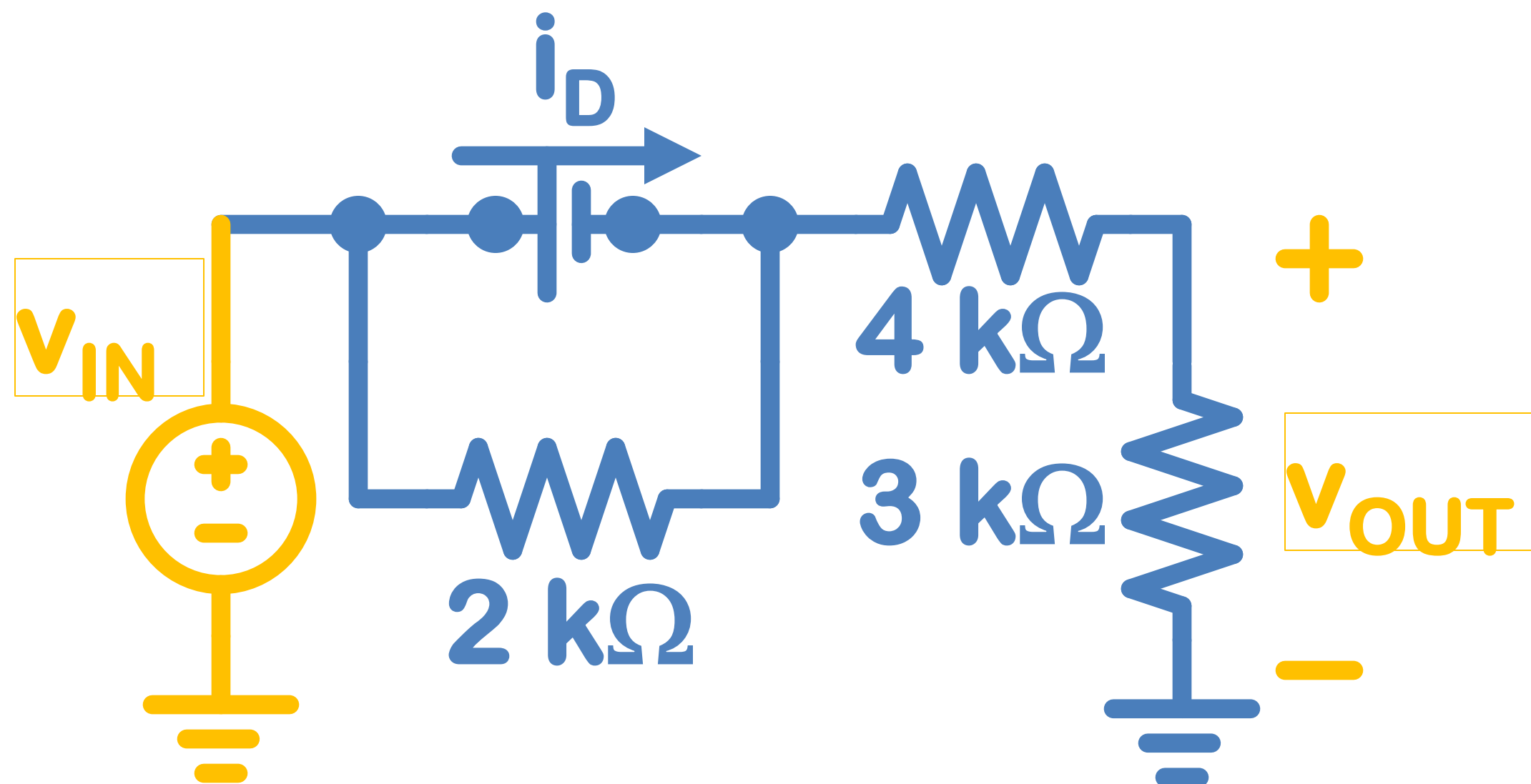
$$v_D < 0.7, \text{ when } v_{IN} < 3.15$$




$$v_{OUT} = (3/7)(v_{IN} - 0.7)$$

$$i_D = (v_{IN} - 0.7)/7000 - 0.7/2000$$

$$i_D > 0, \text{ when } v_{IN} > 3.15$$

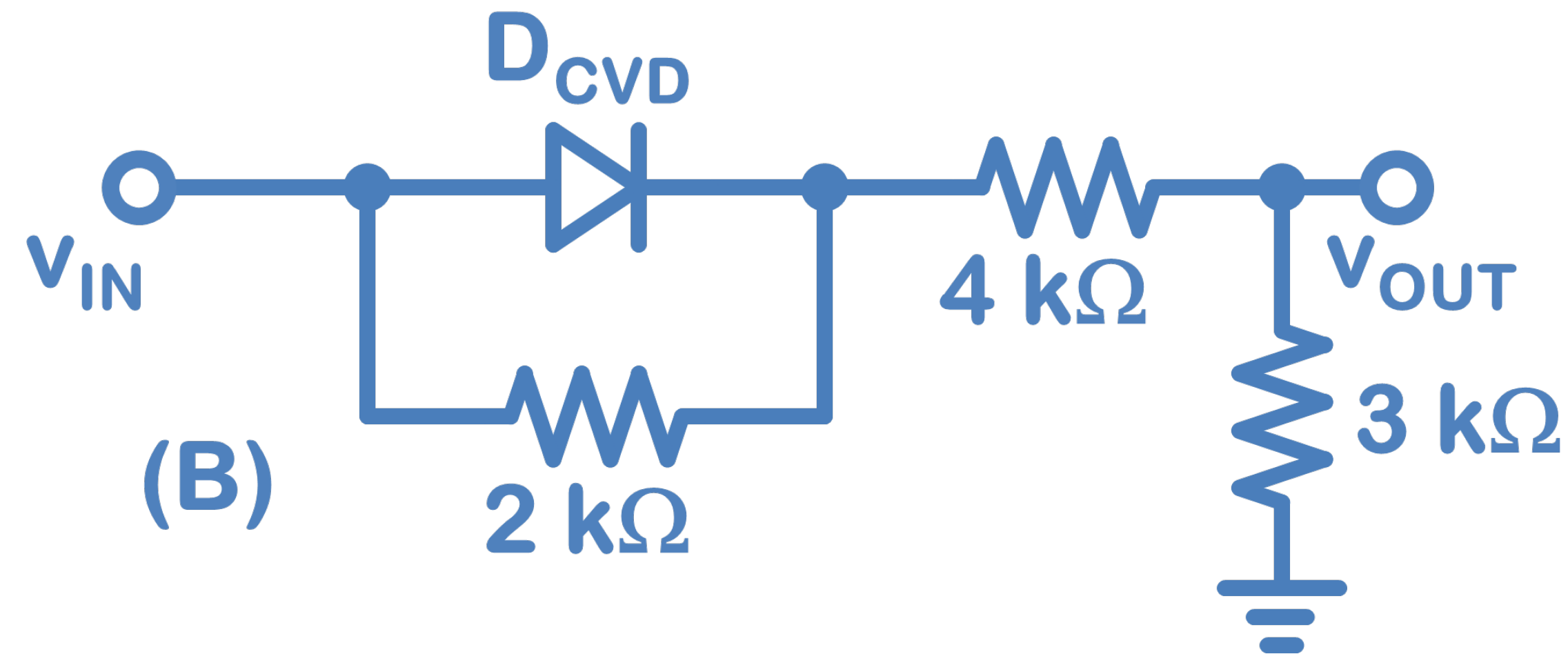Find the equation and plot $v_{OUT}(v_{IN})$
 D_{IDEAL} for each circuit.



$$v_{OUT} = (1/3)v_{IN}, \text{ when } v_{IN} < 3.15$$

$$v_{OUT} = (3/7)(v_{IN} - 0.7), \text{ when } v_{IN} > 3.15$$

*the equal can go
with either case

