


Small Signal Analysis

For the circuit below, using $n=2$.


1) Draw the large signal circuit (do not solve).

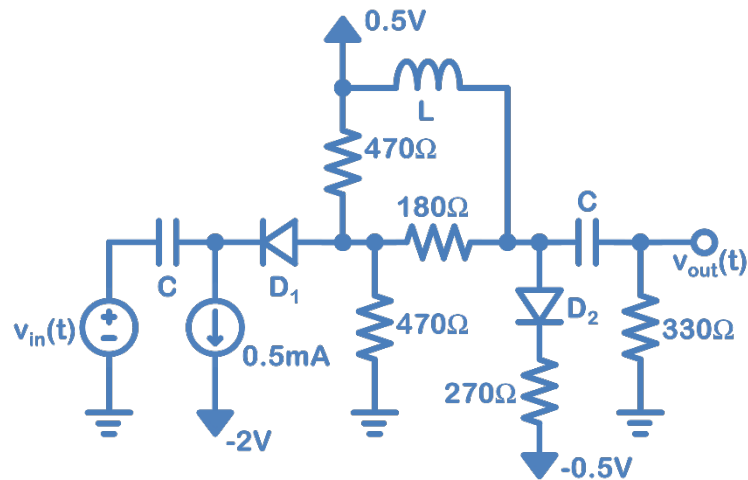2) Draw the small signal circuit and find v_{out}/v_{in} .

Assume large signal diode currents of $I_{D1} = 0.5 \text{ mA}$ and $I_{D2} = 1.0 \text{ mA}$.




LSC

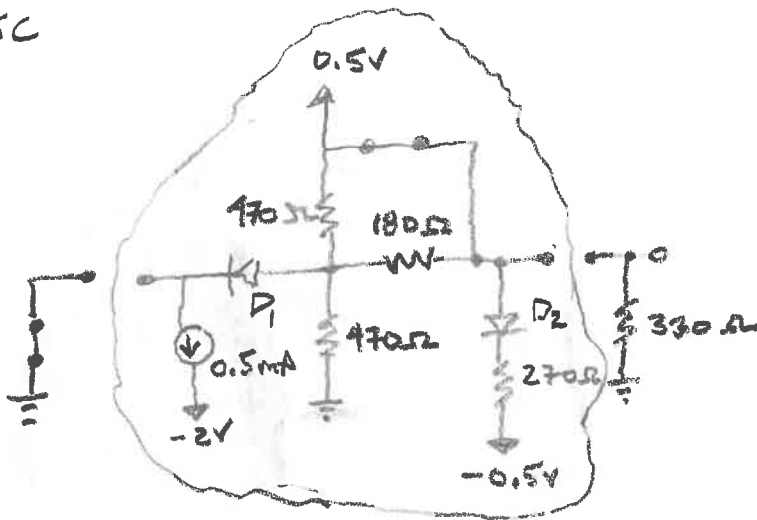

$$r_{d1} = \frac{2 \cdot 0.025}{0.0005} = 100 \Omega$$

$$r_{d2} = \frac{2 \cdot 0.025}{0.001} = 50 \Omega$$

SSC

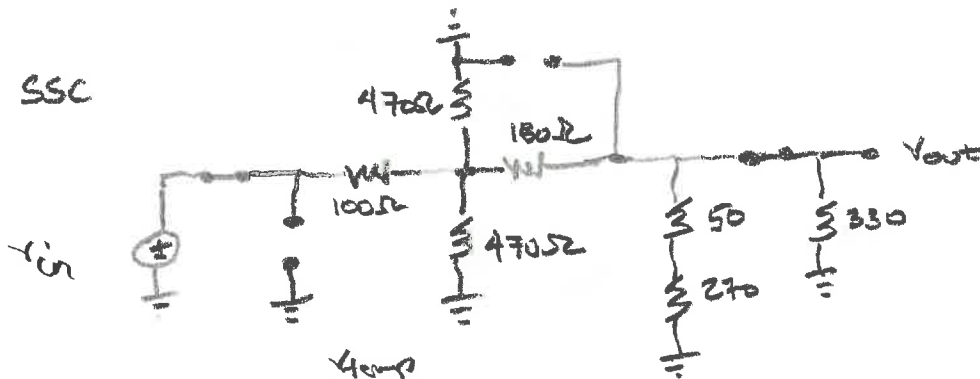


$$50 + 270 = 320 \Omega$$

$$330 \parallel 320 = 162 \Omega$$


$$162 + 180 = 342$$

$$342 \parallel 235 = 139$$

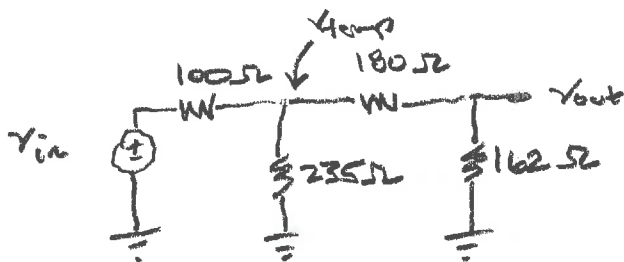

$$\frac{V_{temp}}{V_{in}} = \frac{139}{100 + 139} = 0.58$$

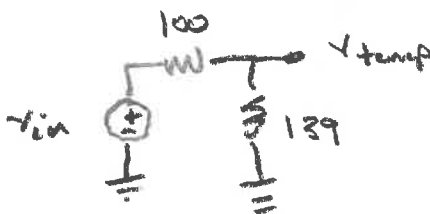
$$\frac{V_{out}}{V_{temp}} = \frac{162}{162 + 180} = 0.47$$



$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_{temp}} \cdot \frac{V_{temp}}{V_{in}} = \underline{0.273}$$

The figure below shows a circuit for an improved Waugh Voltage Controlled Attenuator, where V_C and $V_+(5V)$ are the large-signal voltage sources.

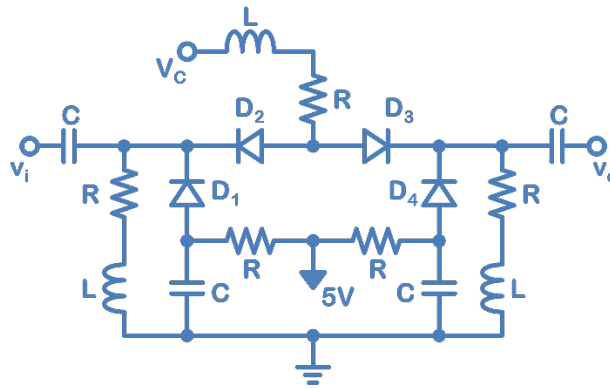Reference: <https://www.microwaves101.com/encyclopedias/waugh-attenuator>



Large-Signal Sources.

V_C is the “constant” control voltage.

5V is a constant voltage.

Small-Signal Source.

The small signal input v_i is on the left.

Small-Signal probe.

The small signal output v_o is on the right.

Assume all capacitors and inductors are very large, $R=500\Omega$, and $n=1$ for all diodes.

1. Draw the large-signal circuit.

2. Using the 0.7V CVD model, find the large signal diode currents for large signal control voltages:

$V_C = 3V, 5V, 7V, 9V, 11V, 13V$

hint: The circuit is symmetrical, so you can just analyze half.

Split the top resistor into two parallel resistors with values $2R=1k\Omega$.


$I_{D1}=I_{D4}$, and $I_{D2}=I_{D3}$


3. Calculate the small signal resistances for the diodes for each control voltage.


4. Draw the small-signal circuit.


5. Find the small signal ratio, v_o/v_i , for each control voltage.

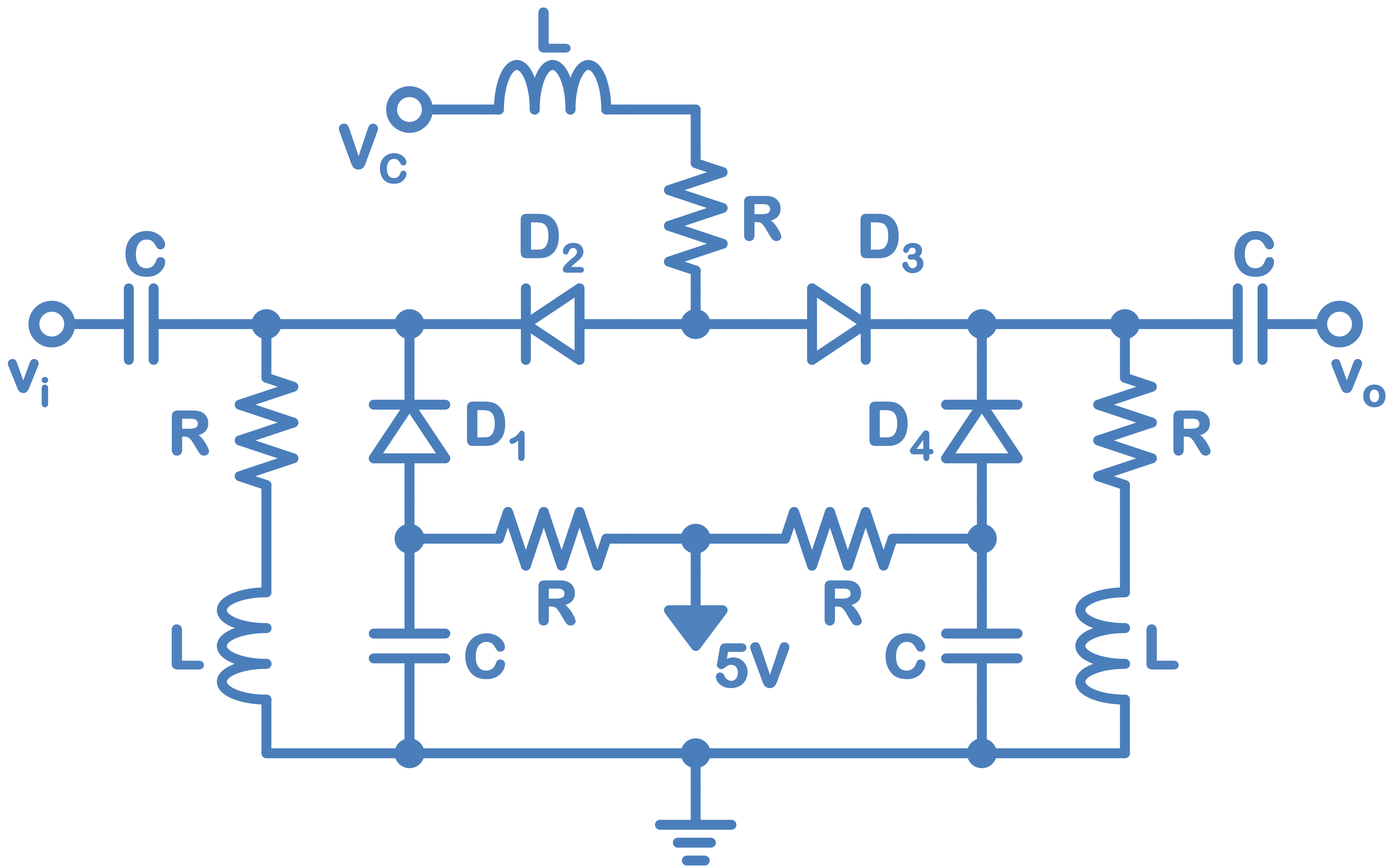
6. Generate a plot of the small signal ratio in terms of V_C using your points.



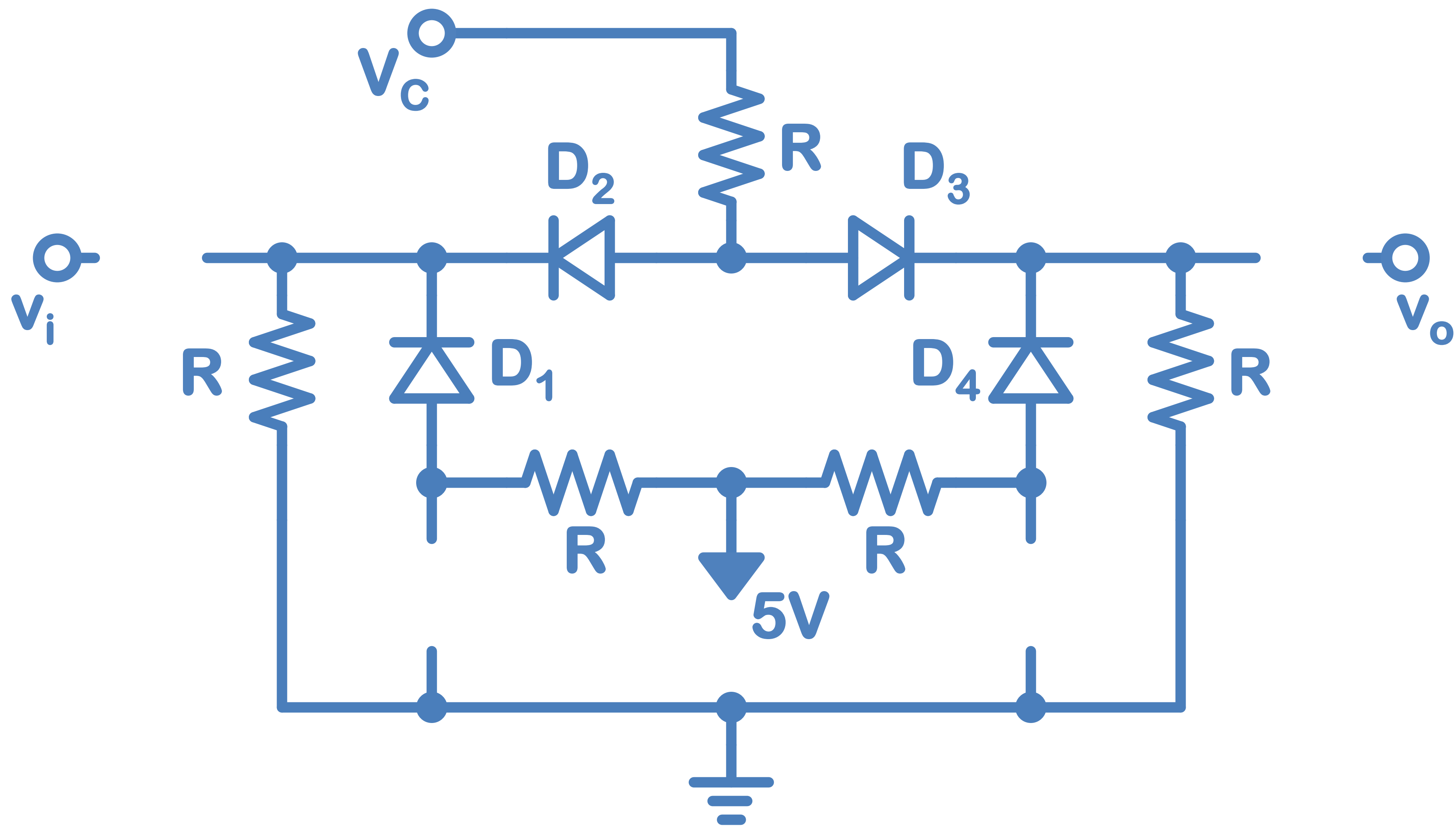

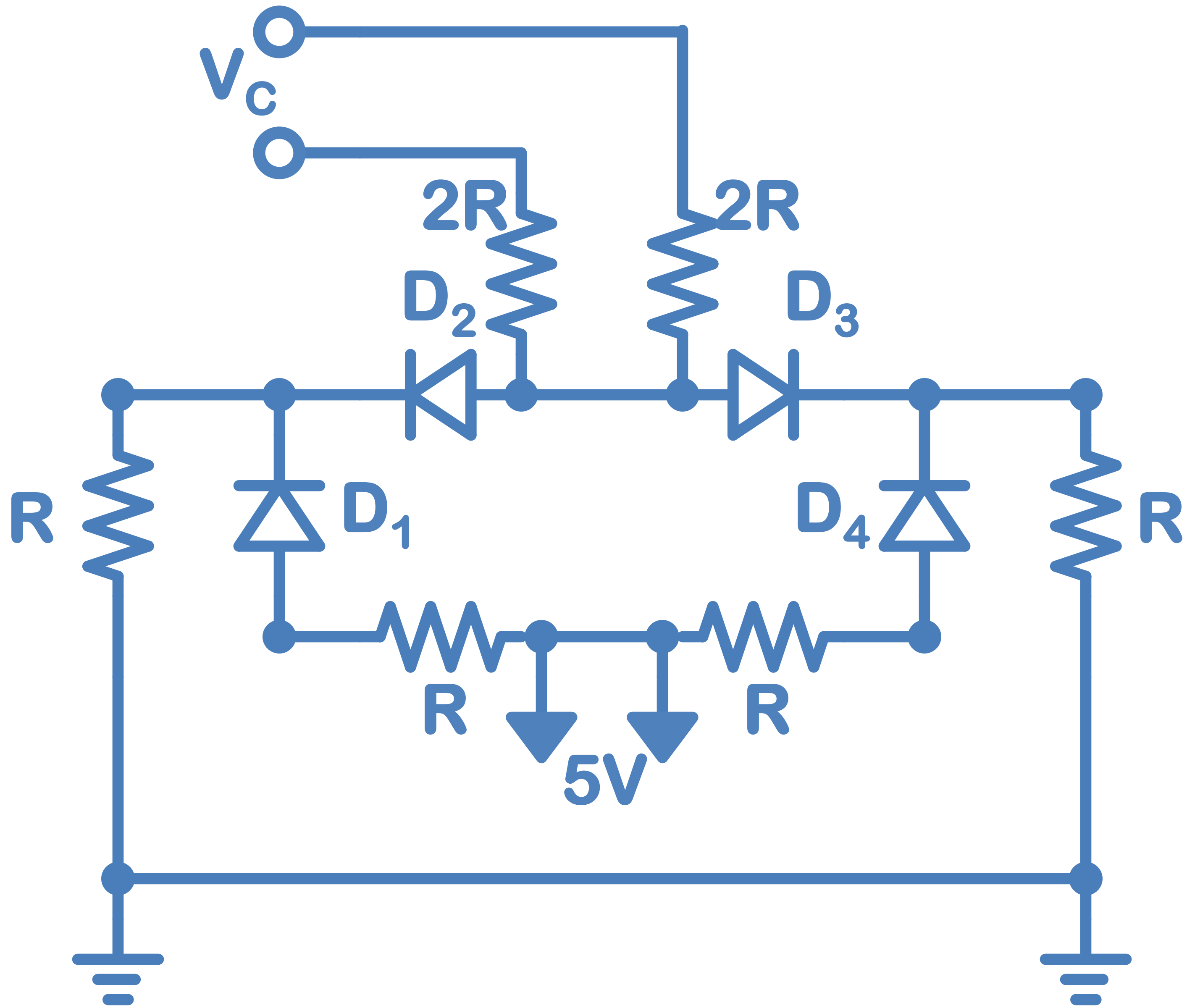

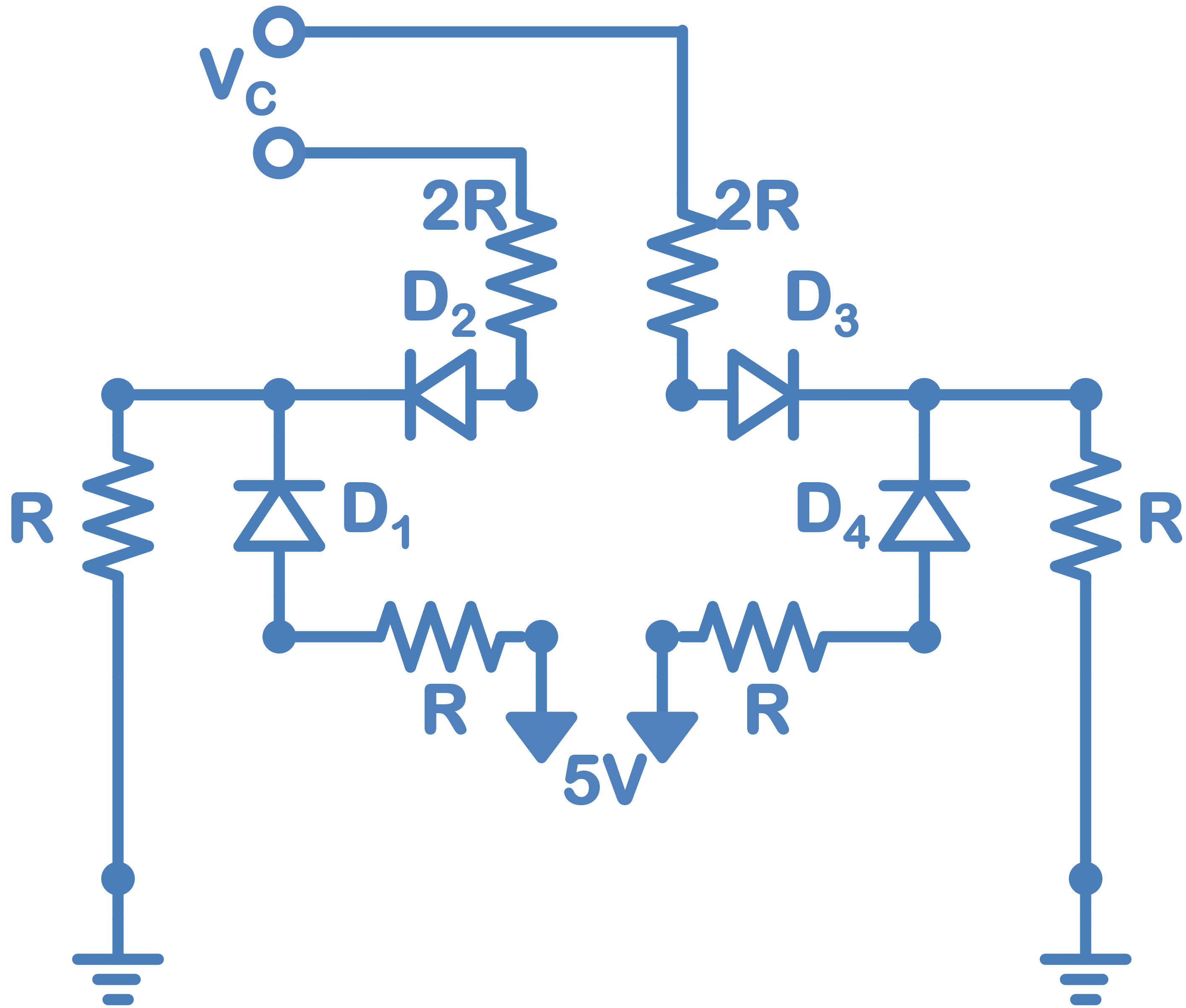

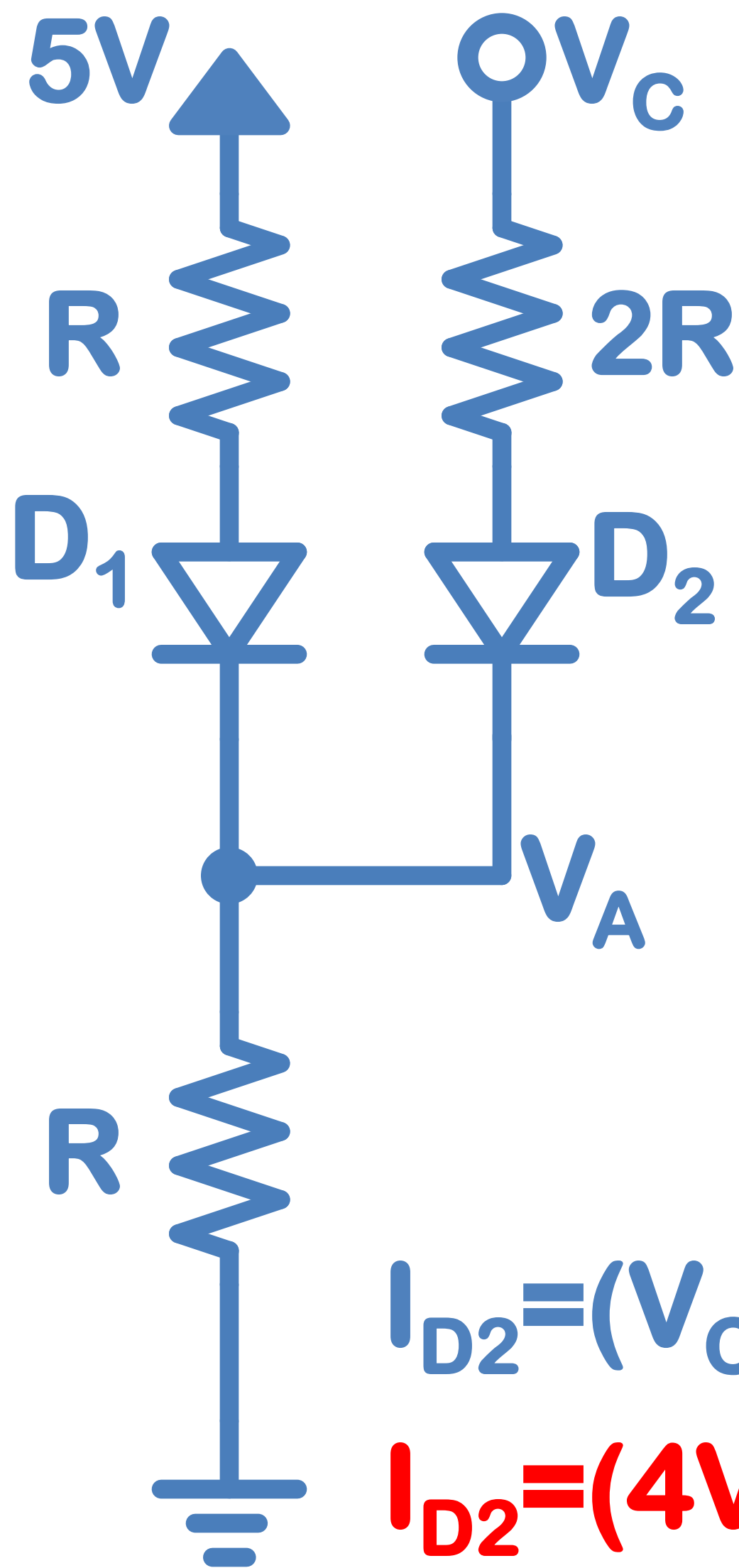

KCL

$$(5 - 0.7 - V_A)/R + (V_C - 0.7 - V_A)/2R = V_A/R$$

$$(10 - 1.4 - 2V_A) + (V_C - 0.7 - V_A) = 2V_A$$

$$5V_A = 10 + V_C - 2.1$$


$$V_A = (7.9 + V_C)/5$$

$$I_{D1} = (4.3 - V_A)/R = (4.3 - (7.9 + V_C)/5)/R$$

$$I_{D1} = (13.6 - V_C)/2.5k$$

$$I_{D2} = (V_C - 0.7 - V_A)/2R = (V_C - 0.7 - (7.9 + V_C)/5)/2R$$

$$I_{D2} = (4V_C - 11.4)/5k$$

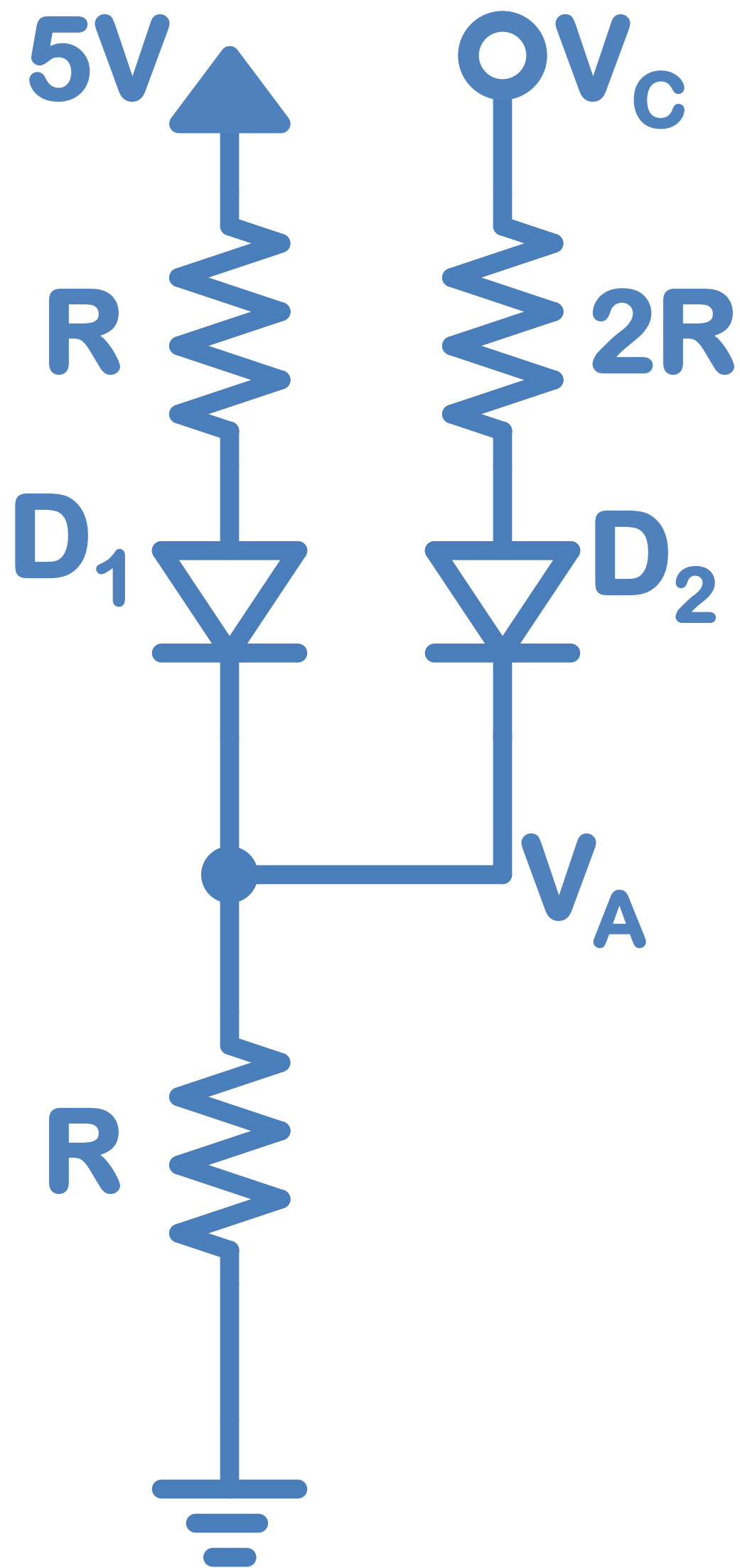



$$I_{D1} = (13.6 - V_c) / 2.5k$$


$$r_{d1} = 62.5 / (13.6 - V_c)$$


$$I_{D2} = (4V_c - 11.4) / 5k$$


$$r_{d2} = 125 / (4V_c - 11.4)$$

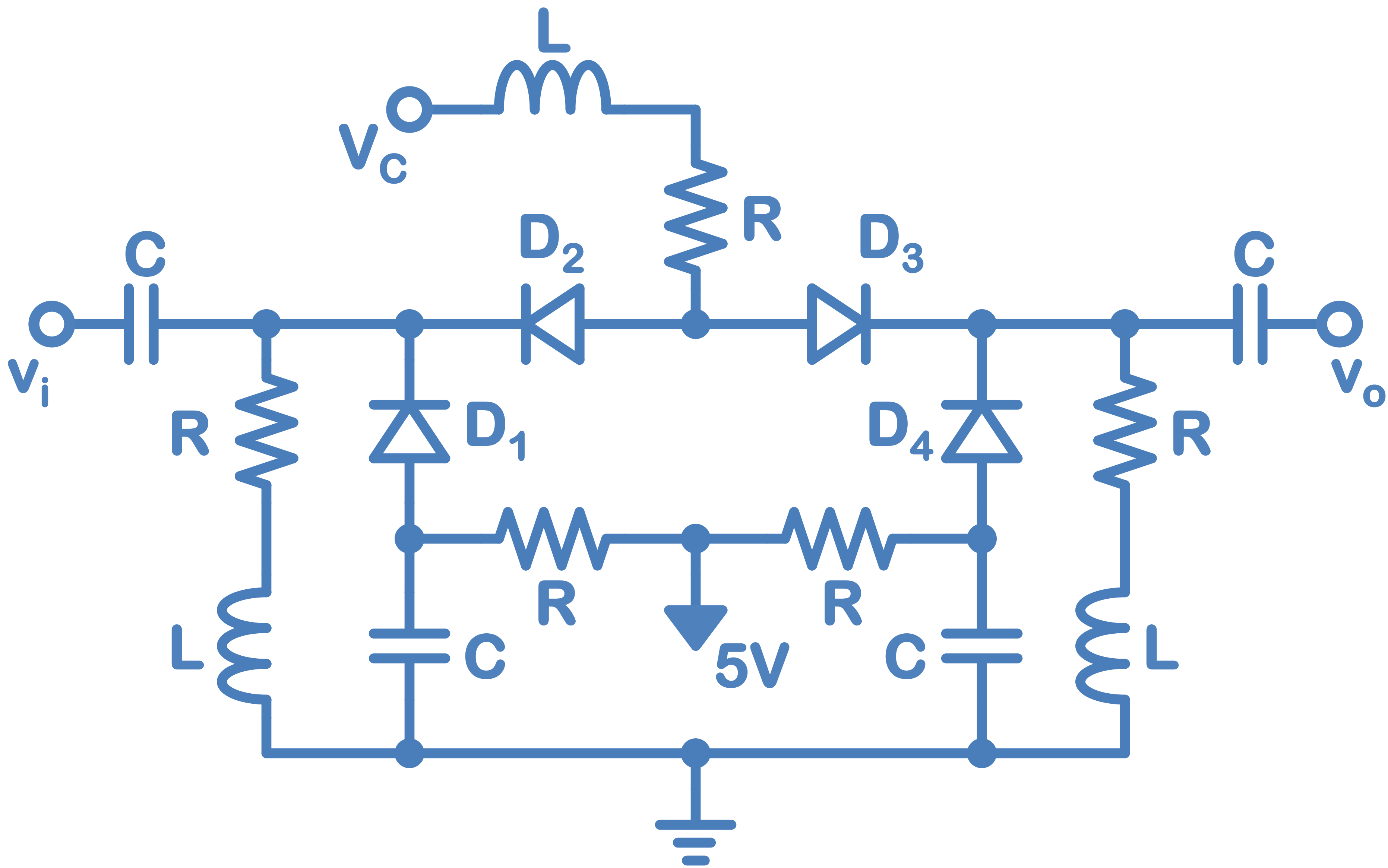

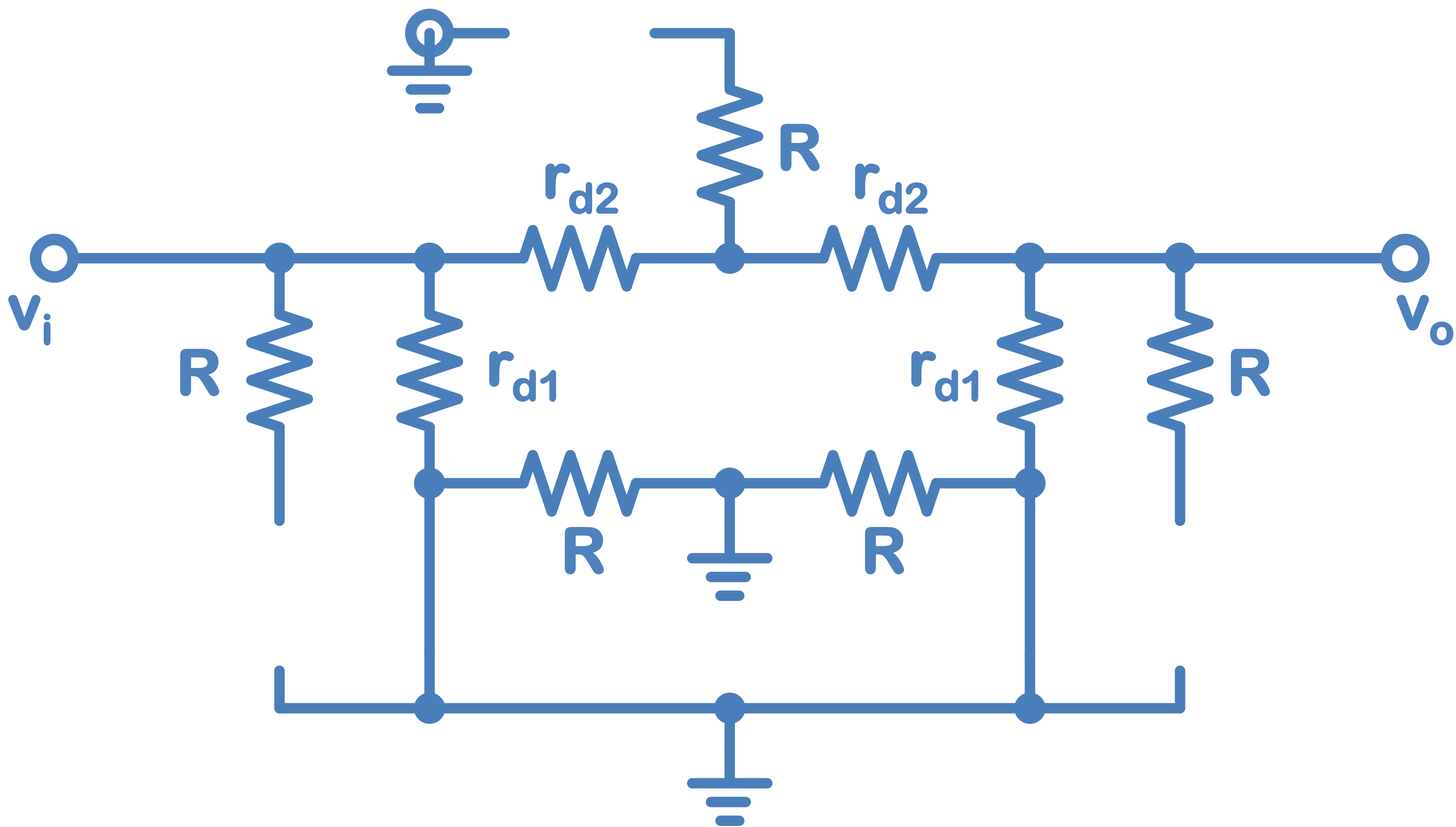

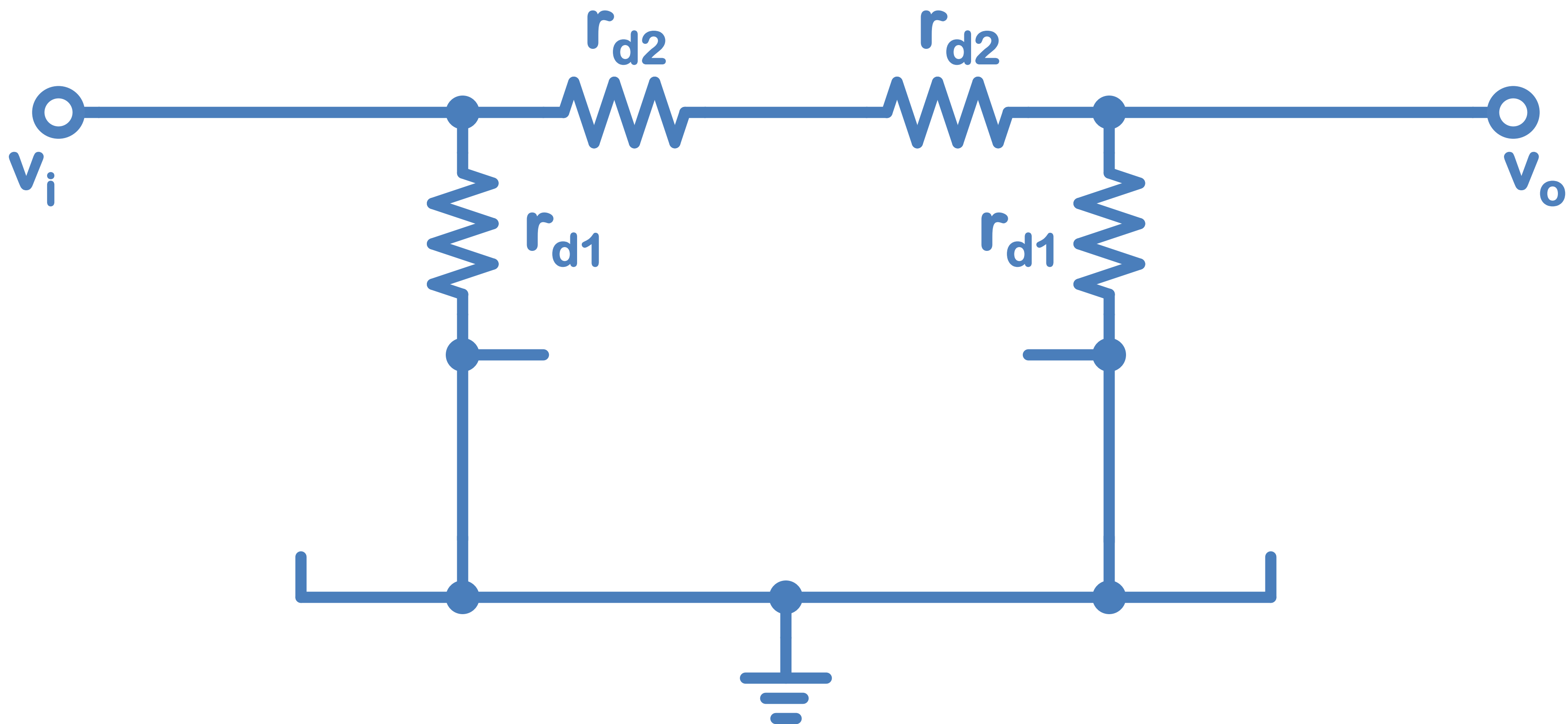

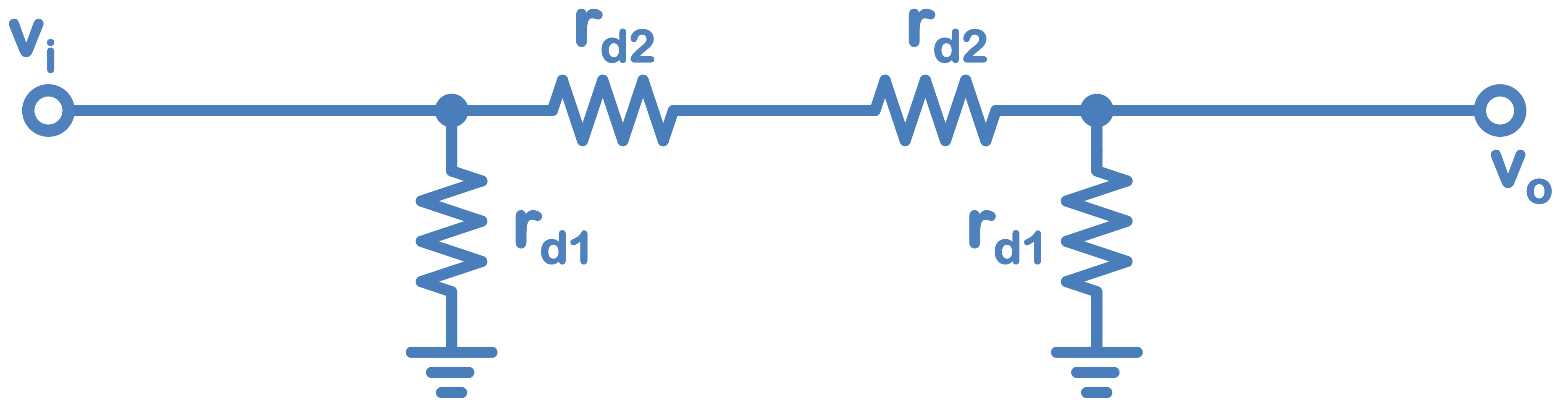

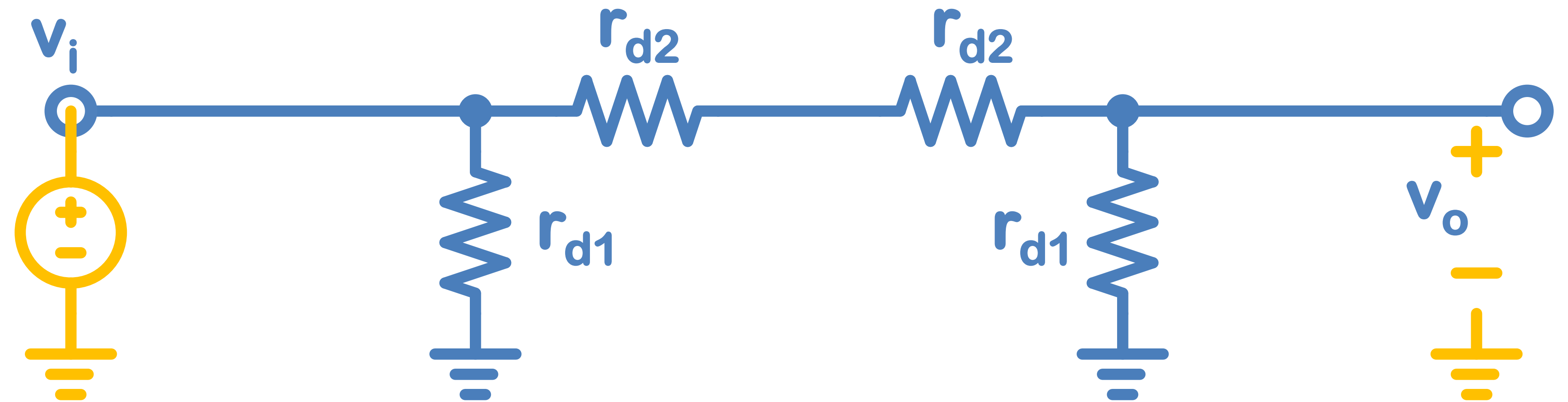

$$v_o/v_i = r_{d1}/(2r_{d2}+r_{d1})$$

$$v_o/v_i = 62.5/(13.6-V_C)/(250/(4V_C-11.4)+62.5/(13.6-V_C))$$

$$v_o/v_i = 62.5(4V_C-11.4) / (250(13.6-V_C)+62.5(4V_C-11.4))$$

$$v_o/v_i = (250V_C-712.5) / (3400-250V_C+250V_C-712.5)$$

$$v_o/v_i = (250V_C-712.5) / (2687.5)$$

$$v_o/v_i = 0.093V_C - 0.2651$$

$$I_{D1} = (13.6 - V_C) / 2.5k$$

$$r_{d1} = 62.5 / (13.6 - V_C)$$

$$I_{D2} = (4V_C - 11.4) / 5k$$

$$r_{d2} = 125 / (4V_C - 11.4)$$

$$v_o / v_i = 0.093V_C - 0.2651$$

VC	ID1 (mA)	ID2 (mA)	rd1	rd2	vo/vi
3	4.24	0.12	5.896226	208.3333	0.0139
4	3.84	0.92	6.510417	27.17391	0.1069
5	3.44	1.72	7.267442	14.53488	0.1999
6	3.04	2.52	8.223684	9.920635	0.2929
7	2.64	3.32	9.469697	7.53012	0.3859
8	2.24	4.12	11.16071	6.067961	0.4789
9	1.84	4.92	13.58696	5.081301	0.5719
10	1.44	5.72	17.36111	4.370629	0.6649
11	1.04	6.52	24.03846	3.834356	0.7579
12	0.64	7.32	39.0625	3.415301	0.8509
13	0.24	8.12	104.1667	3.078818	0.9439