

Perform Small Signal Analysis on the Circuits.


1. Find v_{out}/v_{in} .

Q_n :

$$k_n = 20 \text{ mA/V}^2$$

$$V_{tn} = 2 \text{ V}$$

$$V_A = 40 \text{ V}$$

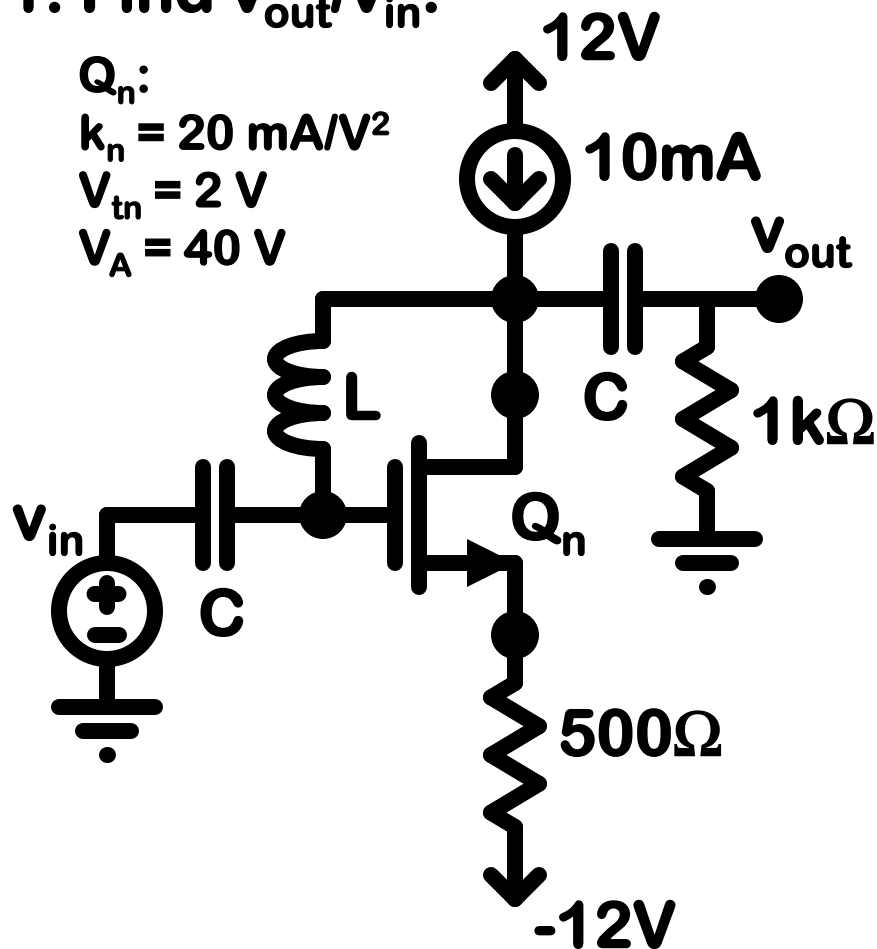

Draw the equivalent
PMOS circuit.


2. Find i_{out}/v_{in} .

Q_p :

$$k_p = 5 \text{ mA/V}^2$$


$$V_{tp} = -1 \text{ V}$$

$$V_A = -50 \text{ V}$$

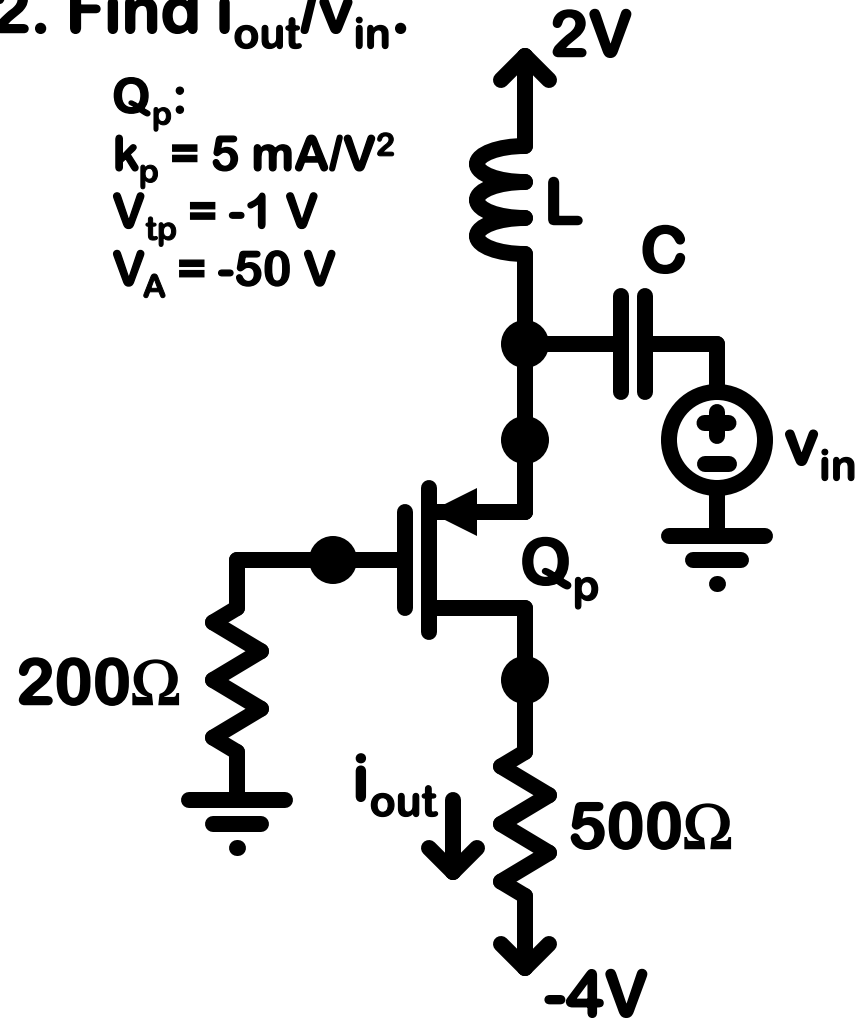


Draw the equivalent
NMOS circuit.

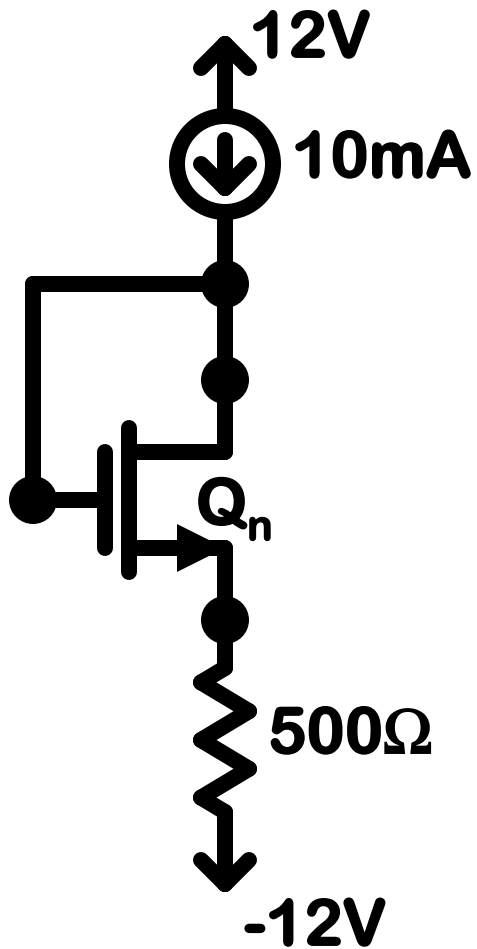Perform Small Signal Analysis on the Circuits.



LSC

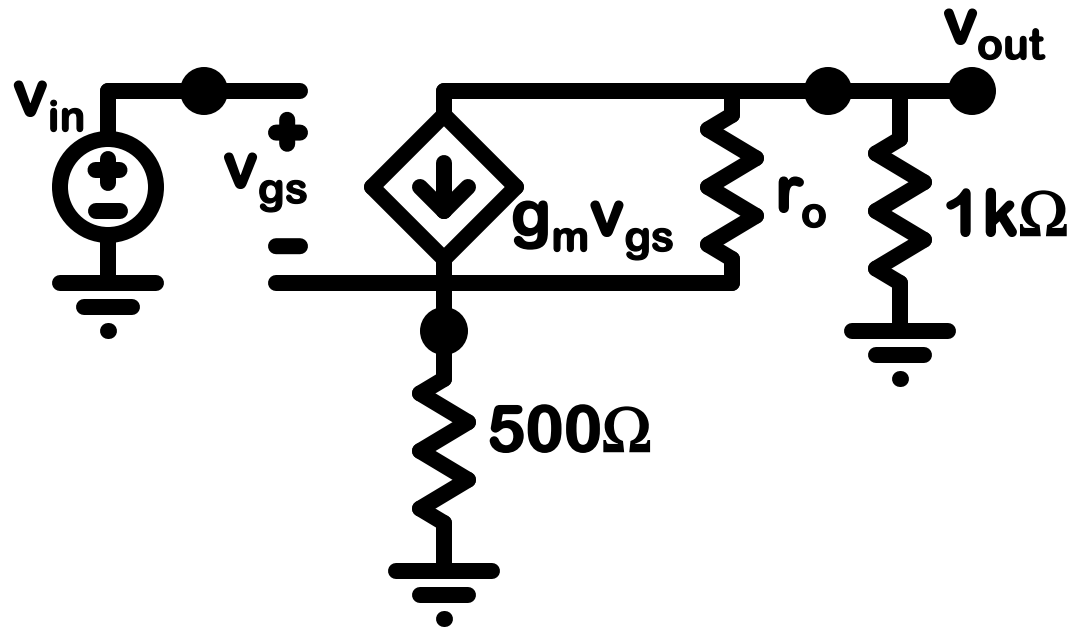

SSC

Perform Small Signal Analysis on the Circuits.


1. Find v_{out}/v_{in} .

Q_n :

$$k_n = 20 \text{ mA/V}^2$$

$$V_{tn} = 2 \text{ V}$$

$$V_A = 40 \text{ V}$$

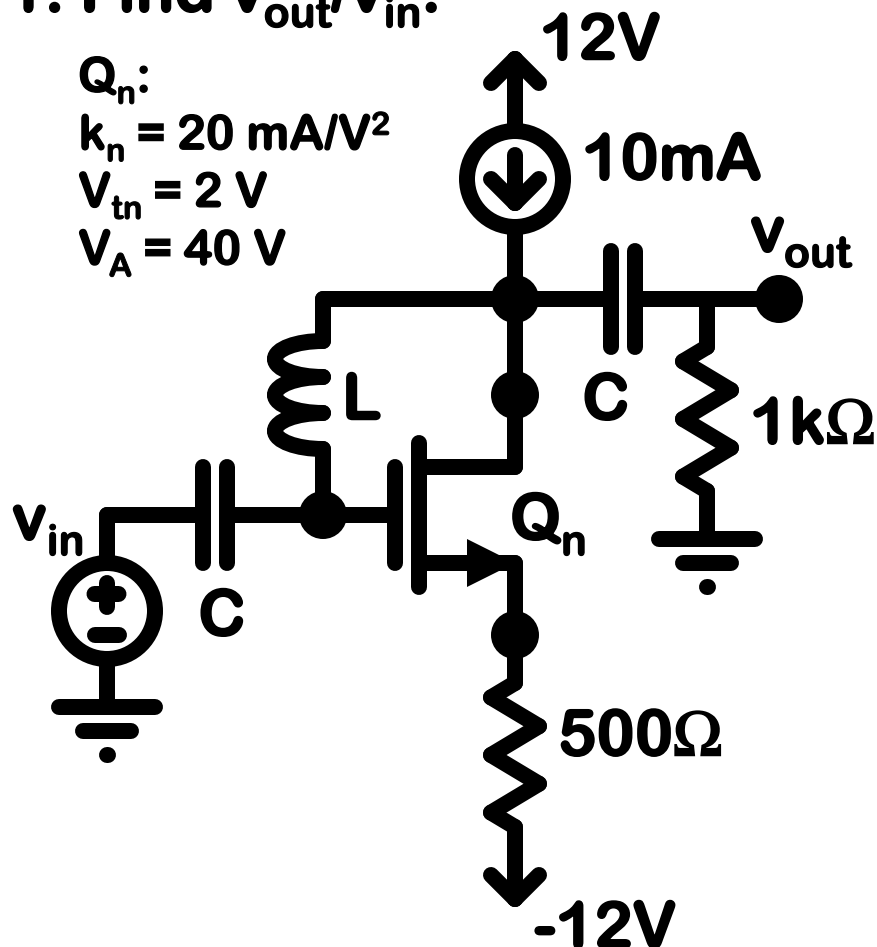

1. LSC

2. $I_D = 10\text{mA}$

$$V_{GS} = \sqrt{2 \cdot 10 / 20} + 2 = 3\text{V}$$

3. $g_m = 20\text{mA/V}$

$$r_o = 40 / 0.01 = 4\text{k}\Omega$$

4. SSC

5. Solve

$$v_o / 1000 = -v_s / 500, v_s = -v_o / 2$$

$$-v_o / 1\text{k} = 0.02(v_i - v_s) + (v_o - v_s) / 4\text{k}$$

$$-8v_o = 160(v_i + v_o / 2) + 2(v_o + v_o / 2)$$

$$v_o / v_i = -160 / 91 \text{ (V/V)}$$

$$v_o / v_i = -1.758 \text{ (V/V)}$$

Perform Small Signal Analysis on the Circuits.


1. Find v_{out}/v_{in} .

Q_n :

$$k_n = 20 \text{ mA/V}^2$$

$$V_{tn} = 2 \text{ V}$$

$$V_A = 40 \text{ V}$$

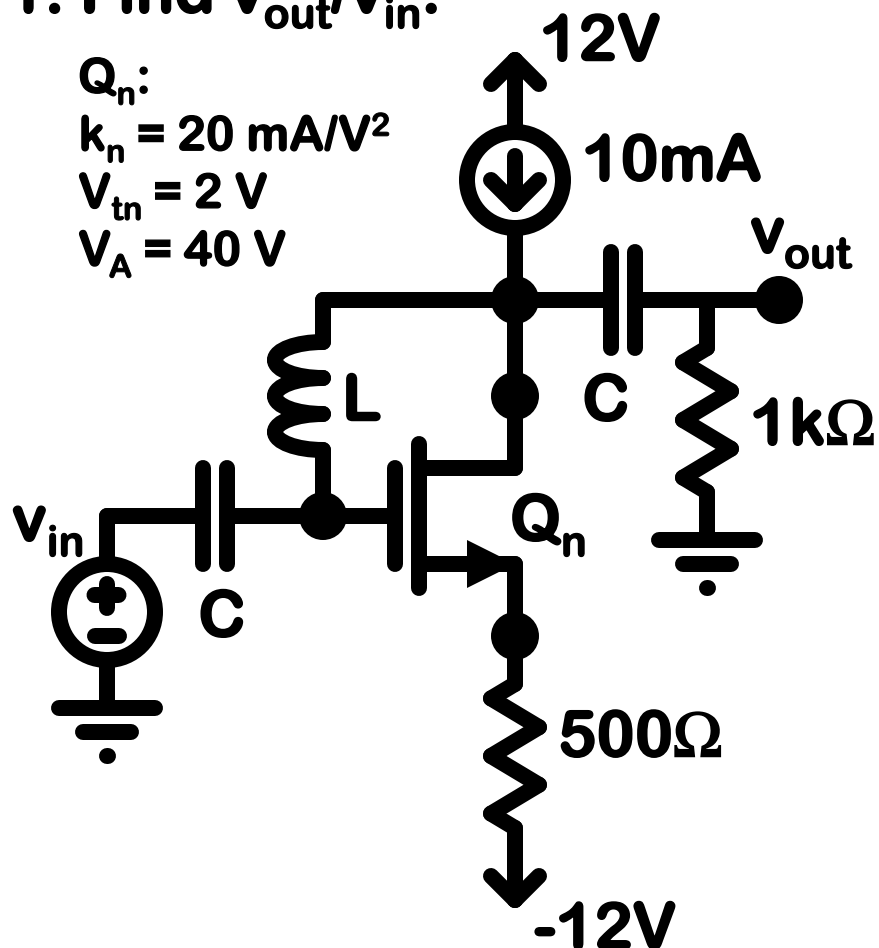


2. Find i_{out}/v_{in} .

Q_p :


$$k_p = 5 \text{ mA/V}^2$$

$$V_{tp} = -1 \text{ V}$$


$$V_A = -50 \text{ V}$$

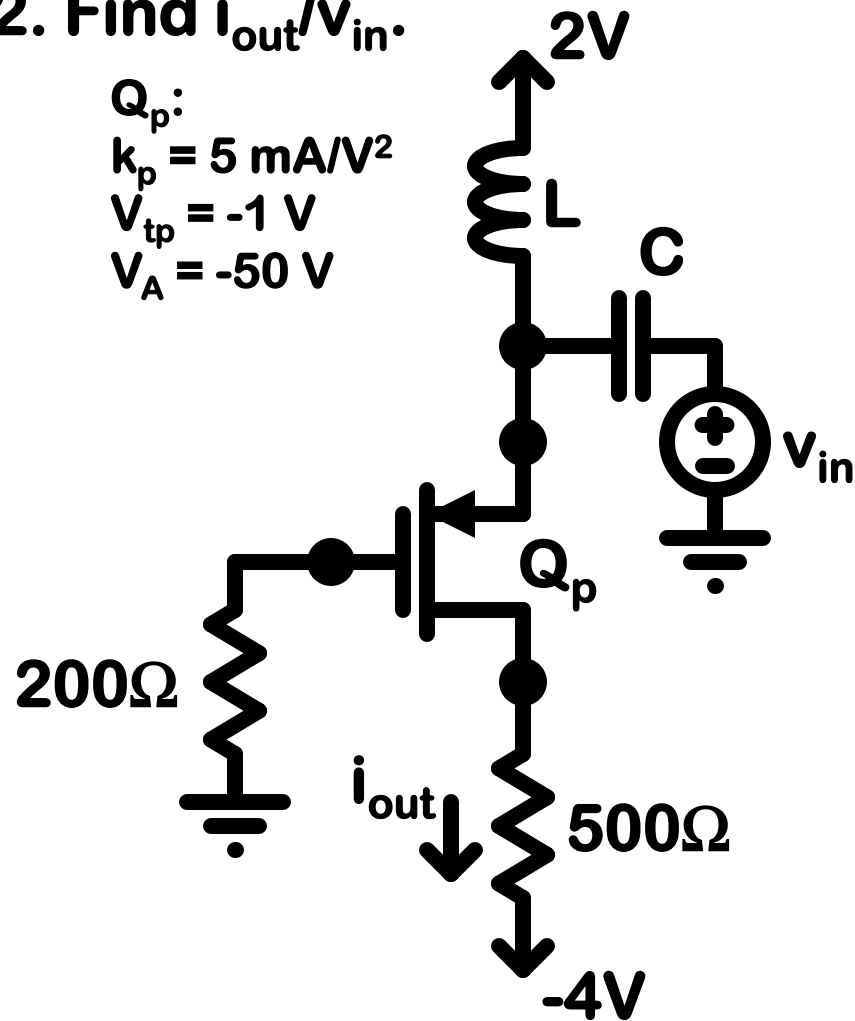

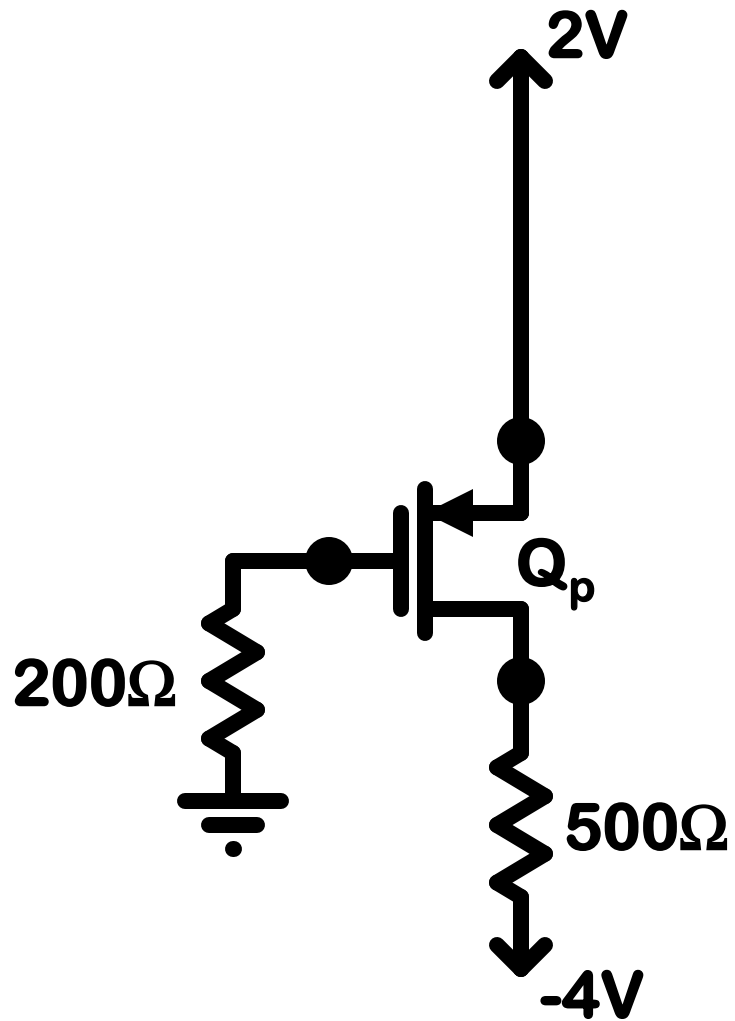Perform Small Signal Analysis on the Circuits.



LSC

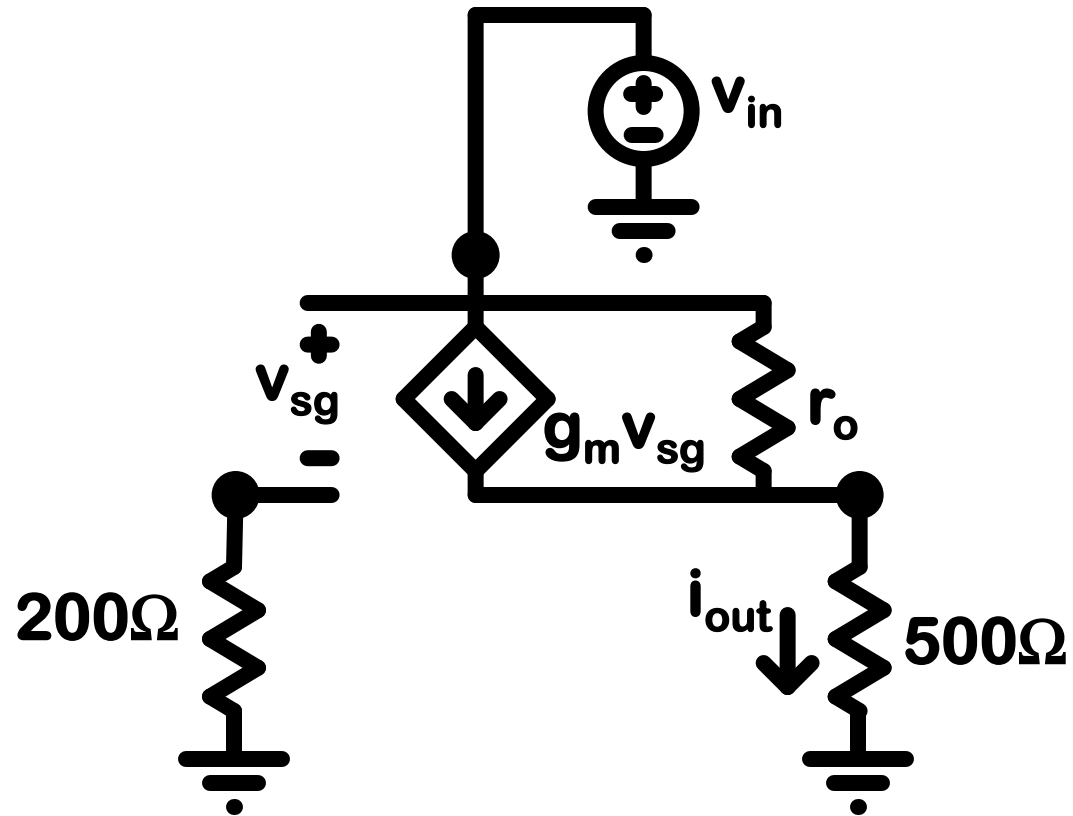

SSC

Perform Small Signal Analysis on the Circuits.

1. LSC

2. $V_{SG} = 2V$

$$I_D = 0.0025(2-1)^2 = 2.5mA$$

3. $g_m = 5mA/V$

$$r_o = 50/.0025 = 20k\Omega$$

4. SSC

5. Solve

$$v_{sg} = v_i$$

$$.005v_i = (v_i - v_o)/20k = v_o/.5k$$

$$100v_i = v_i - v_o = 40v_o$$

$$v_o/v_i = 101/41 \text{ (V/V)}$$

$$i_o/v_i = (101/41)/500 \text{ (1/}\Omega\text{)} = 4.93 \text{ mA/V}$$


2. Find i_{out}/v_{in} .

Q_p :


$$k_p = 5 \text{ mA/V}^2$$


$$V_{tp} = -1 \text{ V}$$


$$V_A = -50 \text{ V}$$

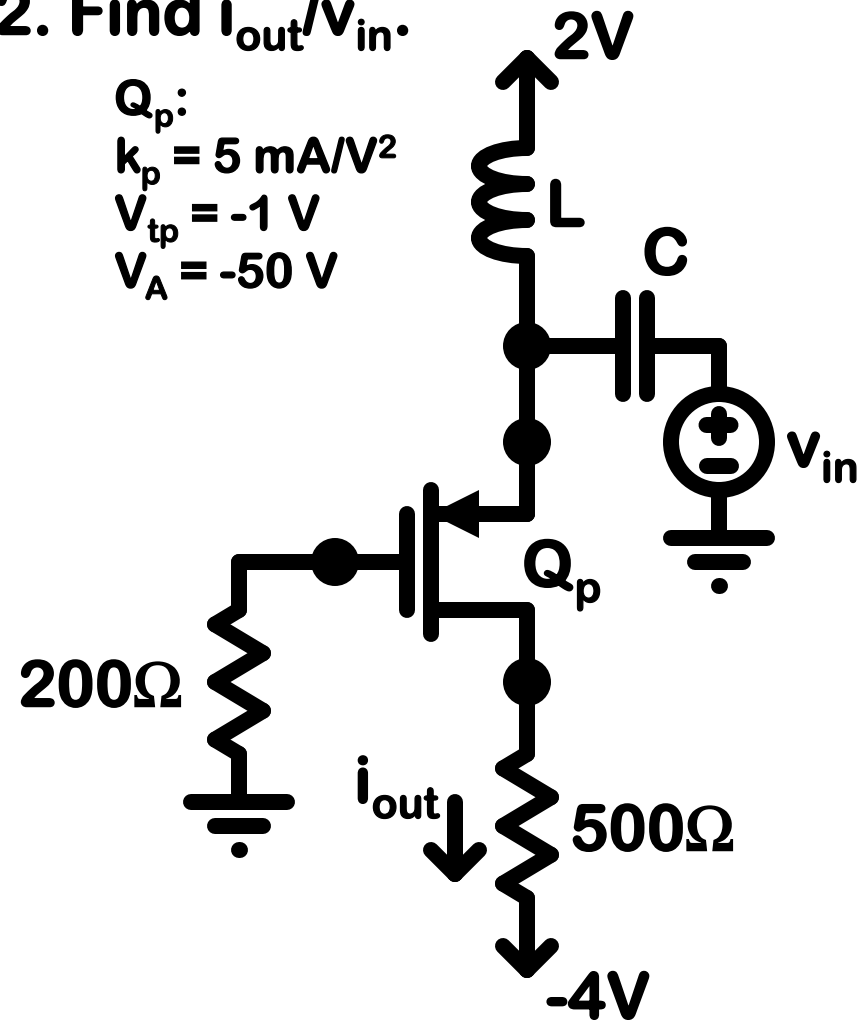

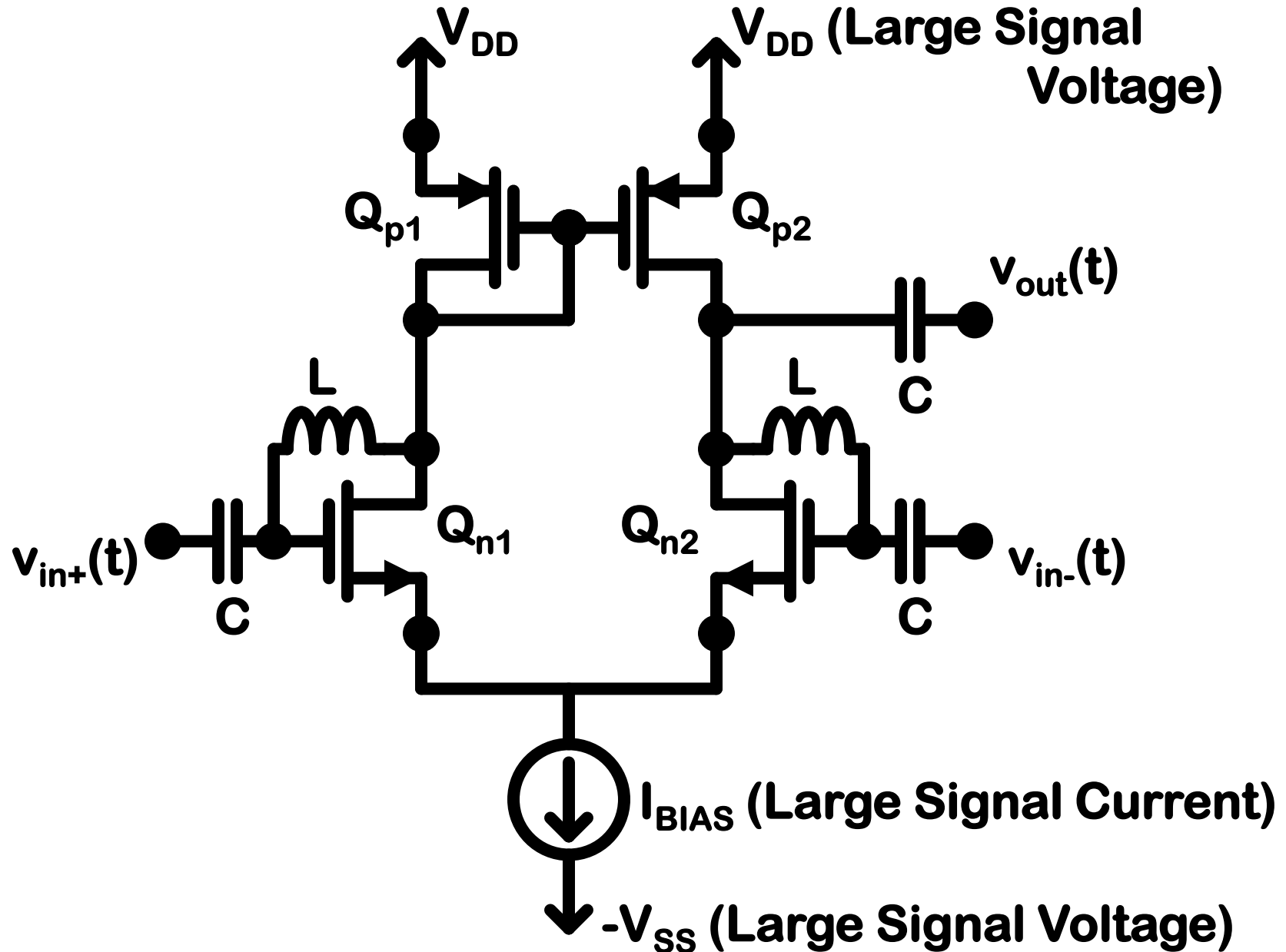
**Draw the Large and Small Signal Circuits.
Include r_o in the Small Signal Circuit.**



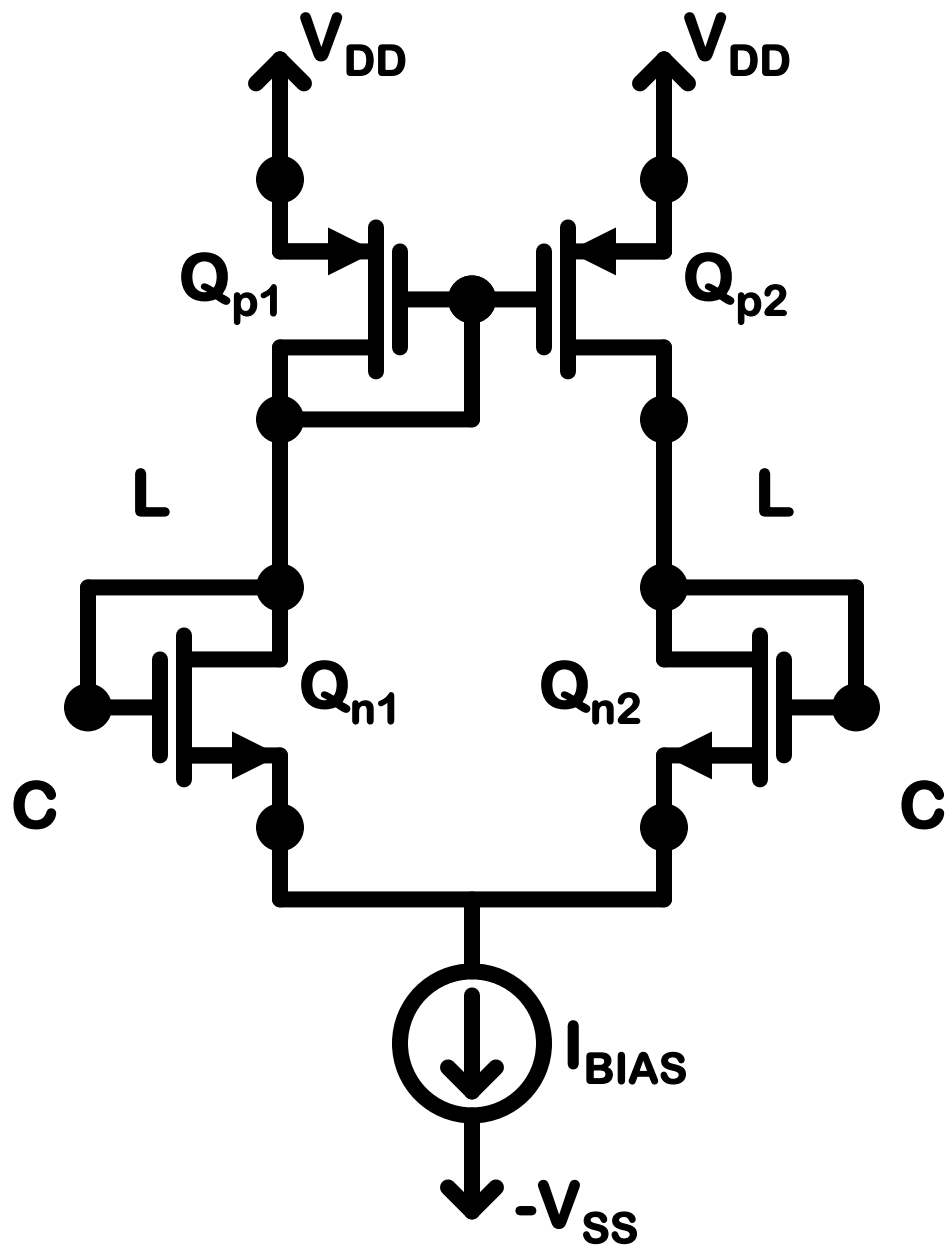

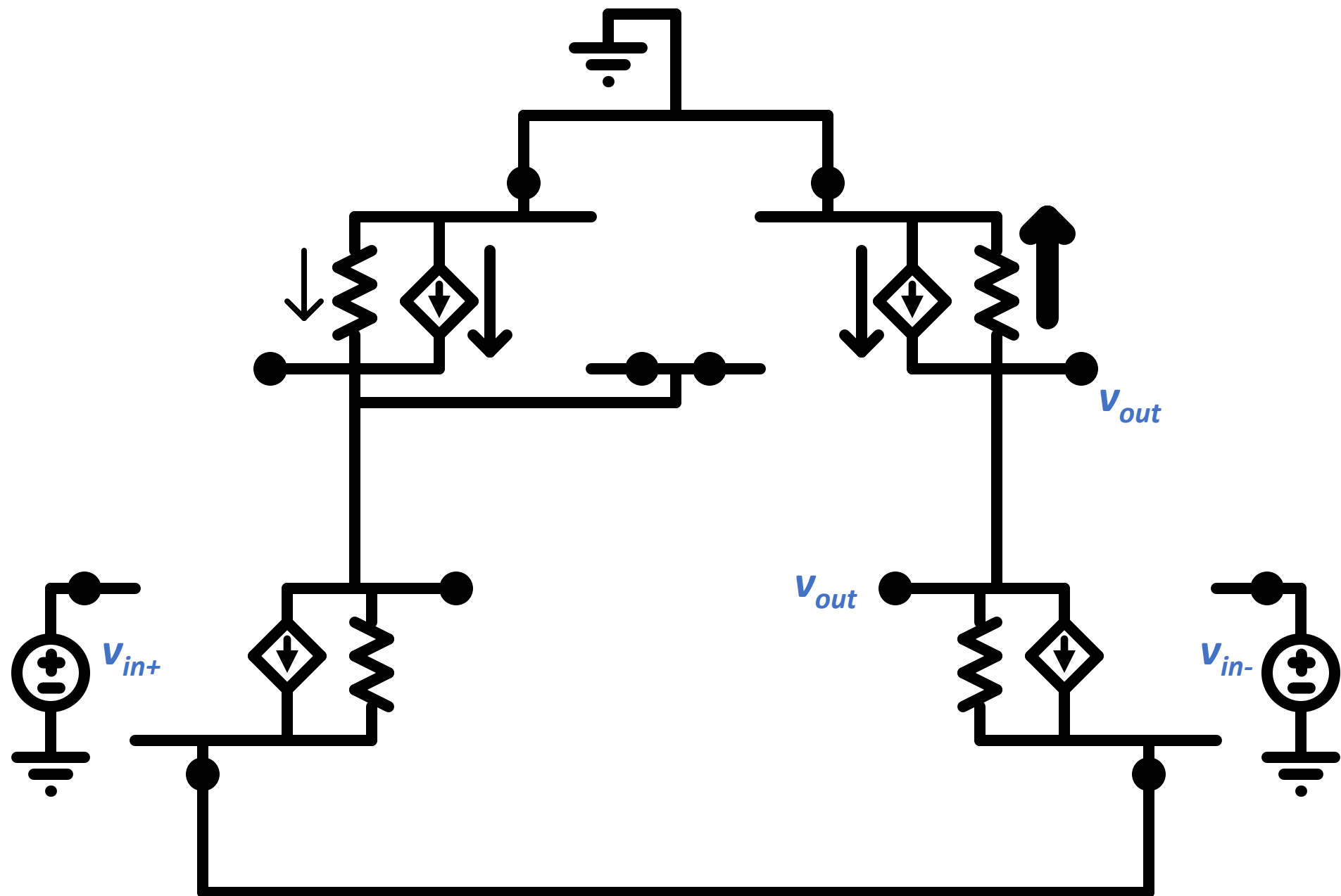

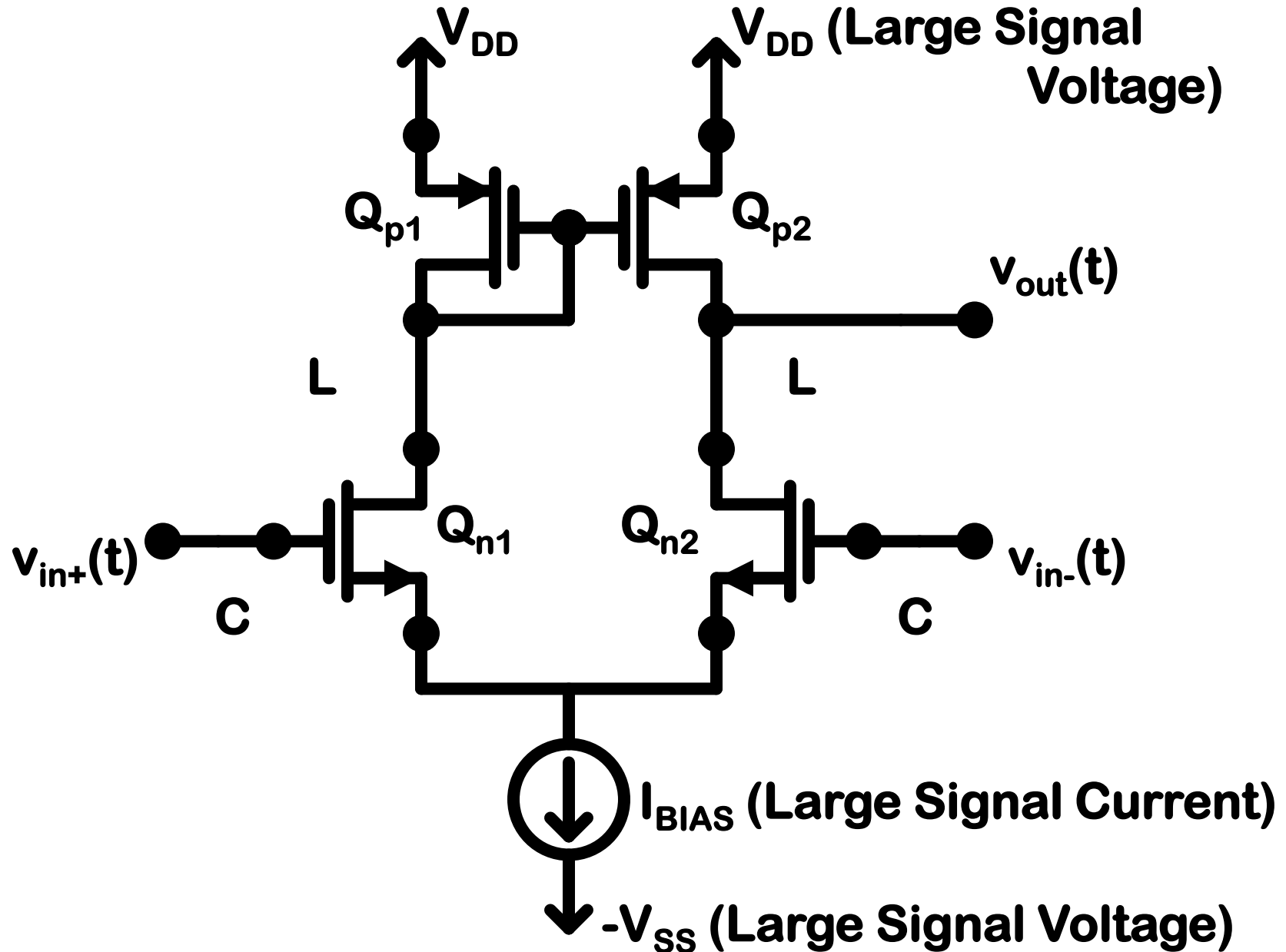**Draw the Large and Small Signal Circuits.
Include r_o in the Small Signal Circuit.**



Find:

$$V_{OH} \quad 3.6 + 1.1 = 4.7$$

$$V_{OL} \quad 1.2 - 0.7 + (-1/6) * (5 - 3.8) = 0.3$$

$$V_{IH} \quad 3.8 - 0.7 * \sqrt{2} / 2 = 3.3$$

$$V_{IL} \quad 1.9 + 1.1 * \sqrt{2} / 2 = 2.68$$

$$NM_L \quad 2.68 - 0.3 = 2.38$$

$$NM_H \quad 4.7 - 3.3 = 1.4$$

$$NM \quad 1.4$$

