

1. For the following logic functions:

- a. Design the PUN and PDN.
- b. Identify the input combinations that the PUN will be conducting and for each combination determine the PUN resistance, r_{PUN} , in terms of r_{SDP} of a single PMOS component.
- c. Identify the input combinations that the PDN will be conducting and for each combination determine the PDN resistance, r_{PDN} , in terms of r_{DSN} of a single NMOS component.
- d. Using $k_n=k_p=4\text{mA/V}^2$, $V_{tn}=|V_{tp}|=0.8\text{V}$, and $V_{DD}=3\text{V}$, determine r_{DSN} and r_{SDP} .
- e. For an output capacitance of $C=50\text{pF}$, determine the maximum value of T_{PLH} and T_{PHL} .
- f. Determine the necessary sizes for all the transistors in terms of the the $(W/L)_{INV}$ that meets timing (n, and p).

$$Y = \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{D} \cdot \overline{B}$$

$$Y = \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{D} + \overline{B}$$

2. A one-bit full adder with carry in/out has three inputs and two outputs.

Inputs:

- A: First coefficient.
- B: Second coefficient.
- C_{IN} : Carry input from previous stage.

Outputs

- S: Sum.
- C_{OUT} : Carry output.

- a. Determine the logic functions for S and C_O in terms of A, B, and C_I . Remember, for CMOS design you can only use ANDs, ORs, and NOTs in your logic functions.
- b. Implement each logic function in CMOS.
- c. Determine how many PMOS and NMOS transistors are required.
- d. Using $k_n=k_p=20\text{mA/V}^2$, $V_{tn}=|V_{tp}|=0.8\text{V}$, and $V_{DD}=2.5\text{V}$, determine r_{DSN} , r_{SDP} .
- e. For an output capacitance of $C=40\text{pF}$, determine the maximum propagation delay for carry output, C_{OUT} , based on the maximum PUN or PDN resistance.
- f. What would the maximum net delay be for an 8-bit adder and resulting maximum clock rate?

note: If you need to use an inverter to satisfy the function syntax for the PUN or PDN, just use the inverter symbol in part b and assume (1 PMOS and 1 NMOS) per inverter in part c.