
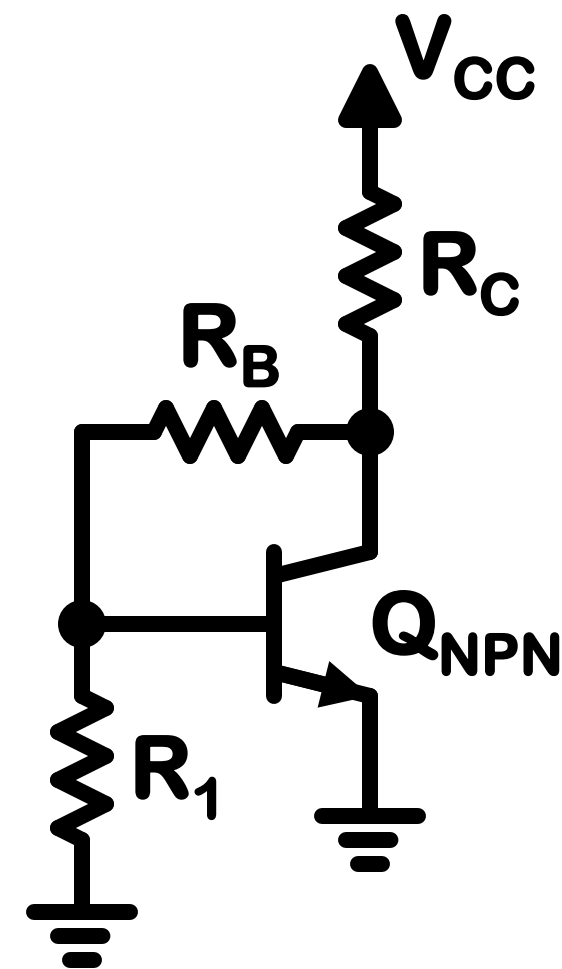
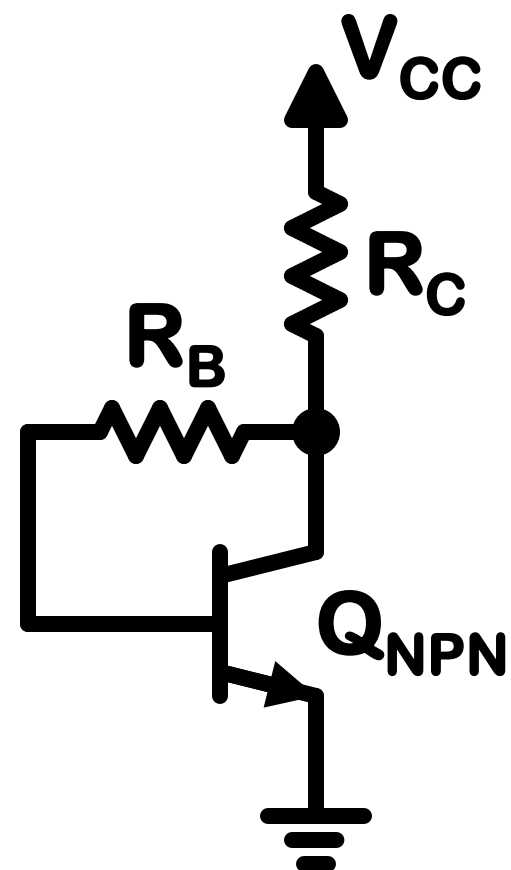
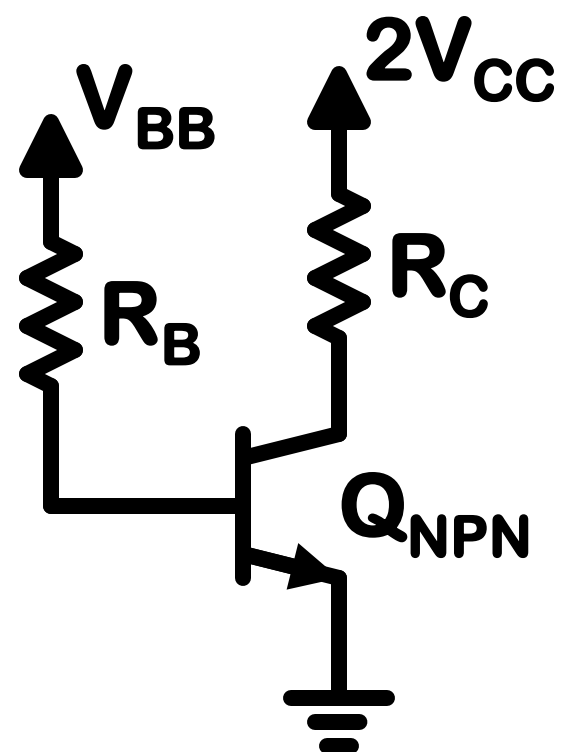


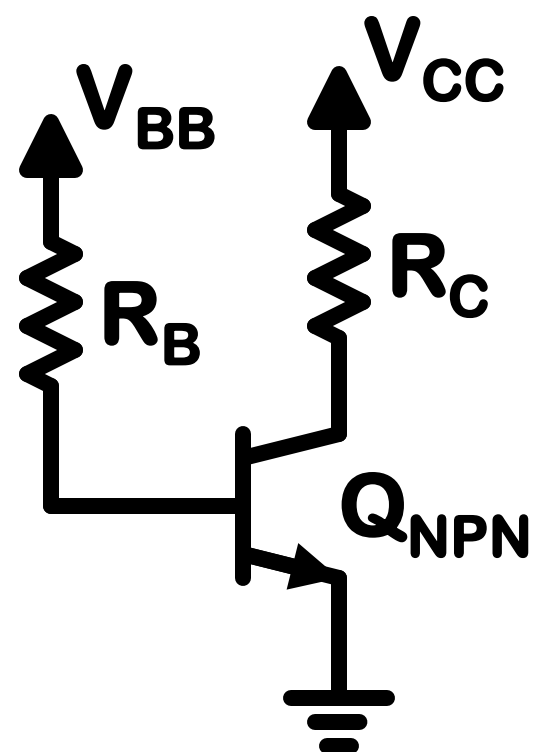

$V_{CC} = 6V$
 $V_{BB} = 4V$
 $R_B = 10k\Omega$
 $R_C = 500\Omega$
 $R_E = 200\Omega$
 $R_1 = 10k\Omega$
 $\beta = 50$





A: Saturation

B: Active

C: Active

D: Active

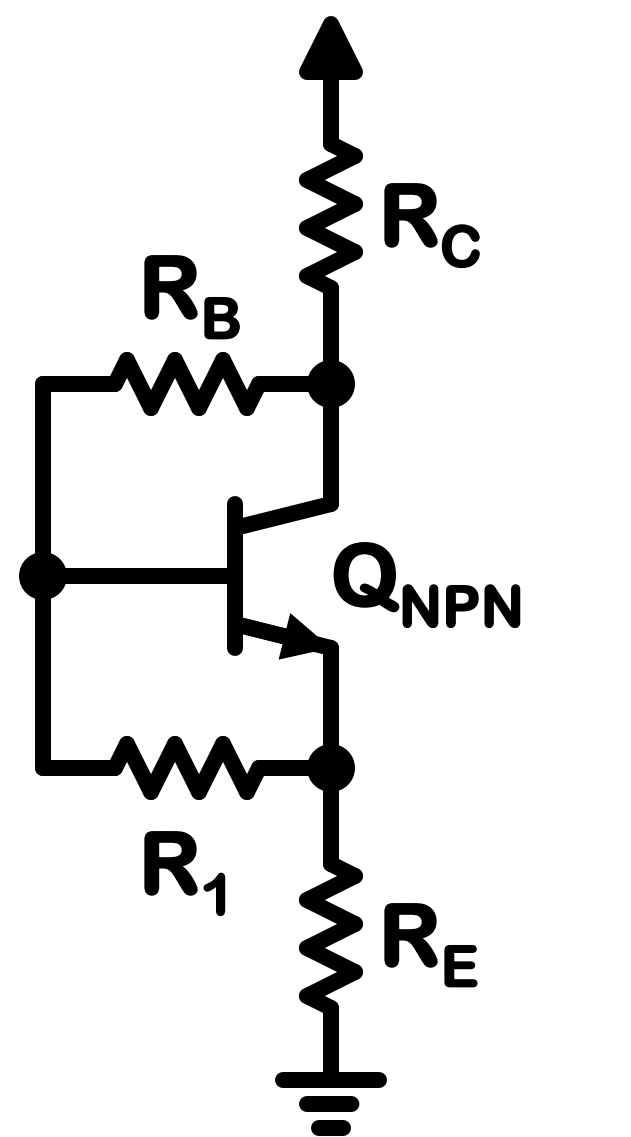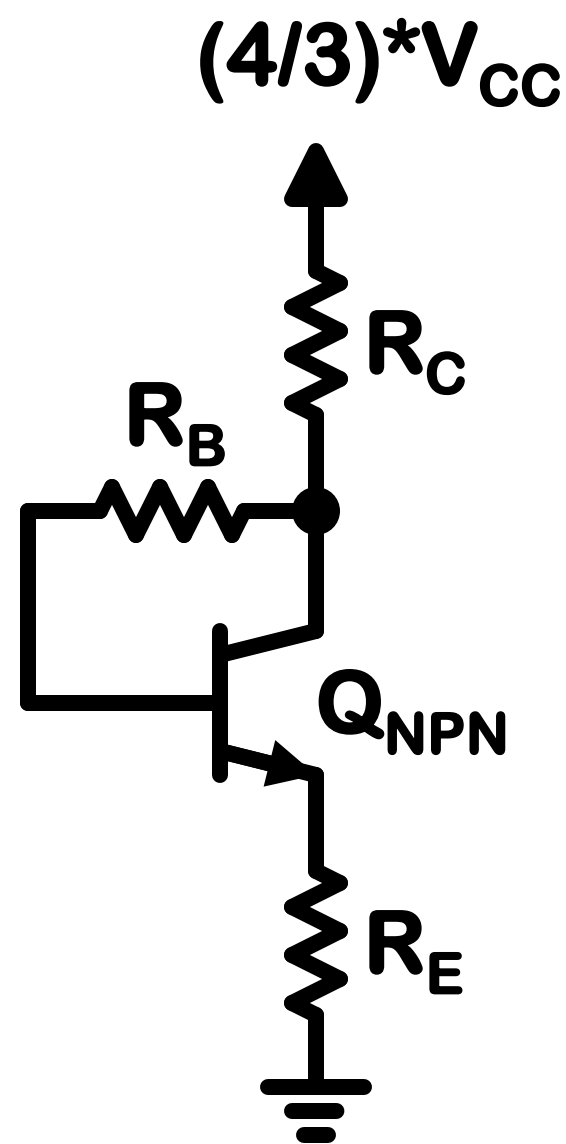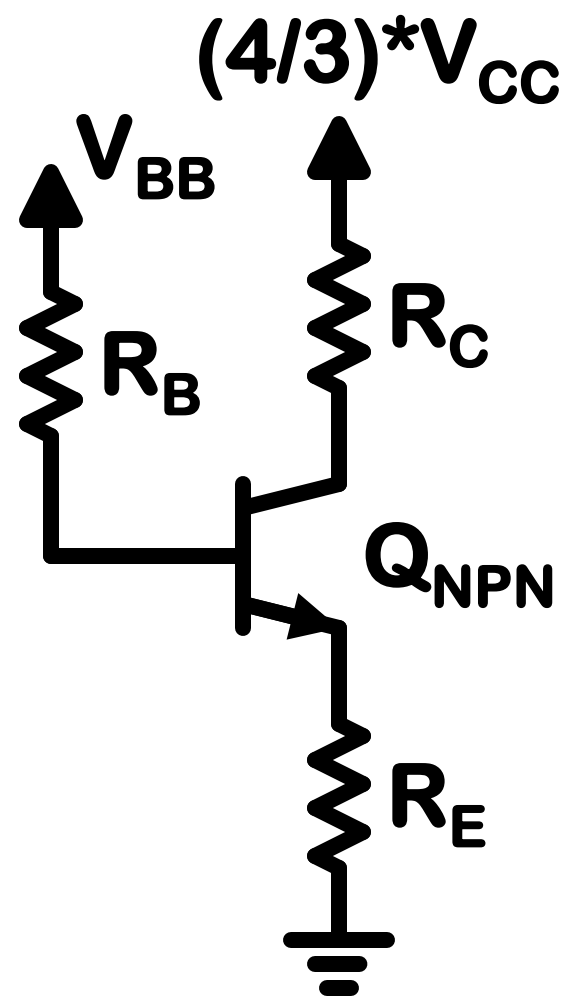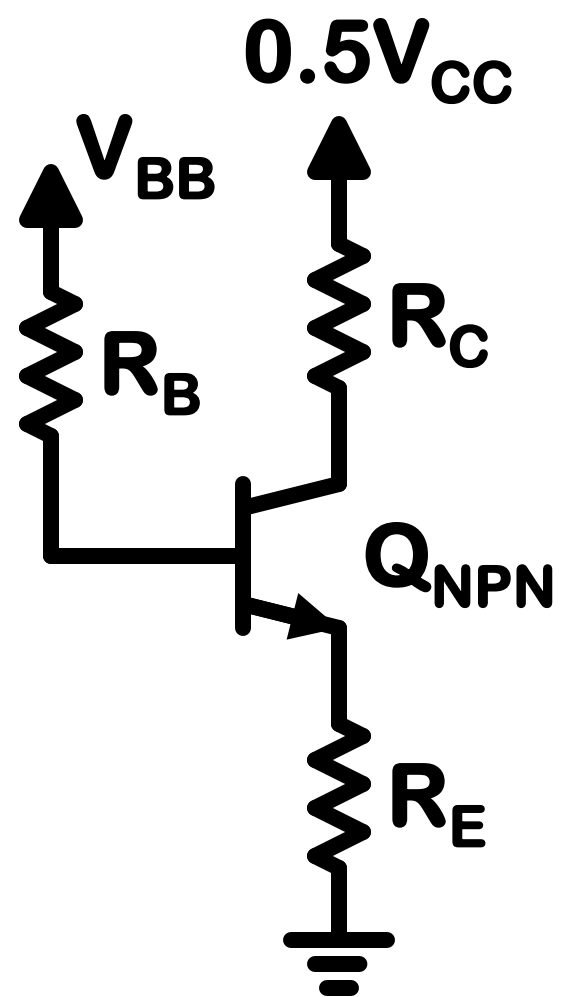- Find the collector current, i_C , for each device.
- Verify the mode which is given for each circuit.
- Draw PNP equivalent.




E: Saturation

F: Active

G: Active

H: Active

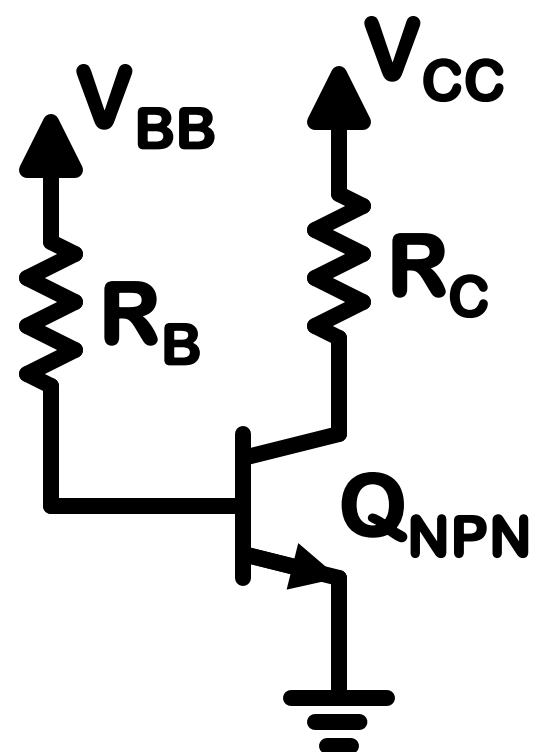

1. Saturation

2. Enforce (device equation)

$$v_{BE} = 0.7V, v_{CE} = 0.2V$$


3. Solve


$$i_B = (4.0 - 0.7)/10k = 0.33mA$$

$$i_C = (6.0 - 0.2)/500 = 11.6mA$$

4. Check

$$i_C/i_B = 11.6/0.33 = 35 < 50$$

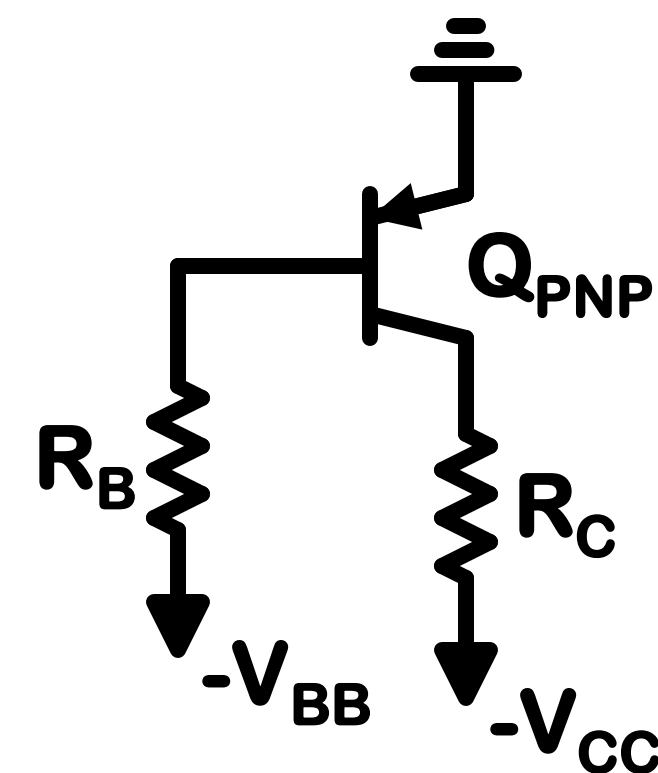

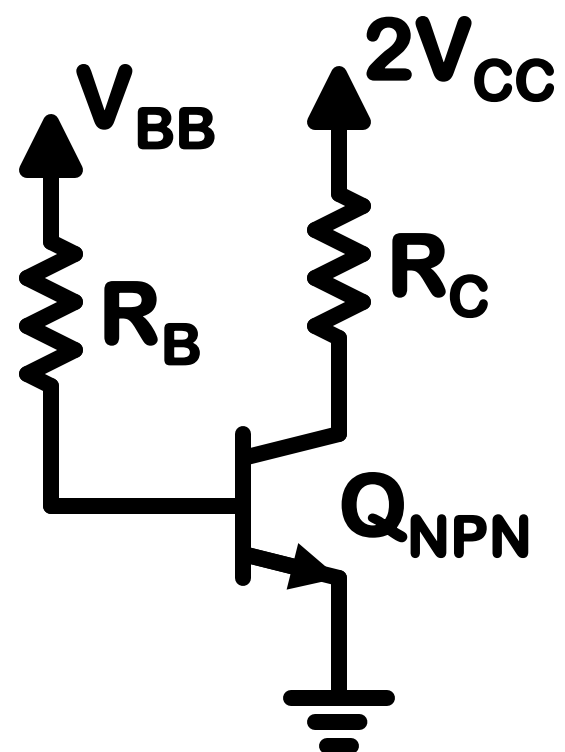

1. Active

2. Enforce (device equation)

$$V_{BE} = 0.7V, i_C = \beta \cdot i_B$$


3. Solve


$$i_B = (4.0 - 0.7)/10k = 0.33mA$$

$$i_C = 50i_B = 16.5mA$$

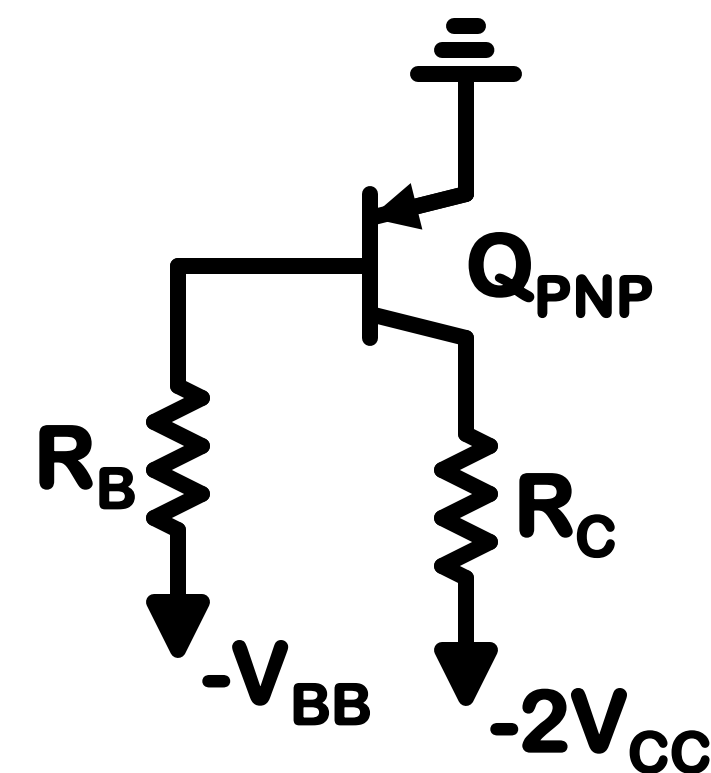4. Check

$$V_{CE} = 12 - 500 \cdot 0.0165 = 3.75V > 0.2V$$



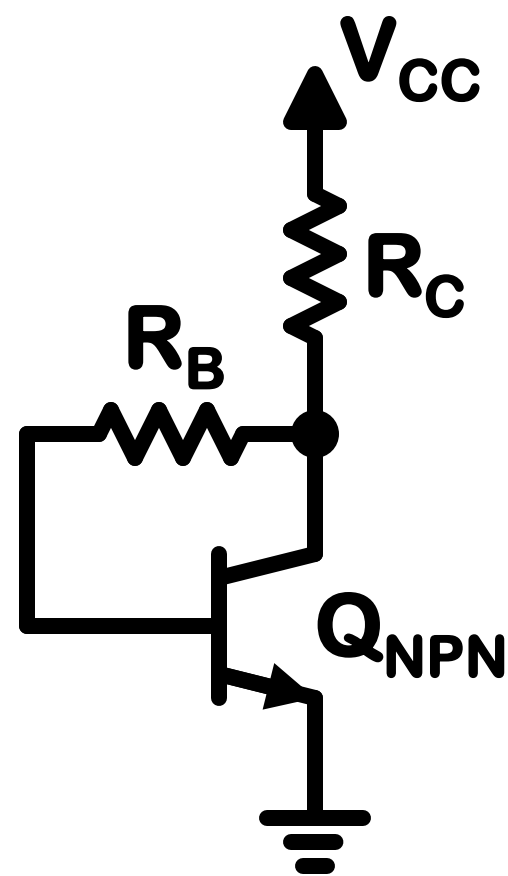

1. Active

2. Enforce (device equation)

$$V_{BE} = 0.7V, i_C = \beta \cdot i_B$$

3. Solve

$$6 - 500i_E - 10000i_B - 0.7 = 0$$

$$6 - 500(50+1)i_B - 10000i_B - 0.7 = 0$$


$$i_B = (6-0.7)/(500(50+1) + 10000)$$


$$i_B = 0.15 \text{ mA}$$

$$i_C = 7.46 \text{ mA}$$

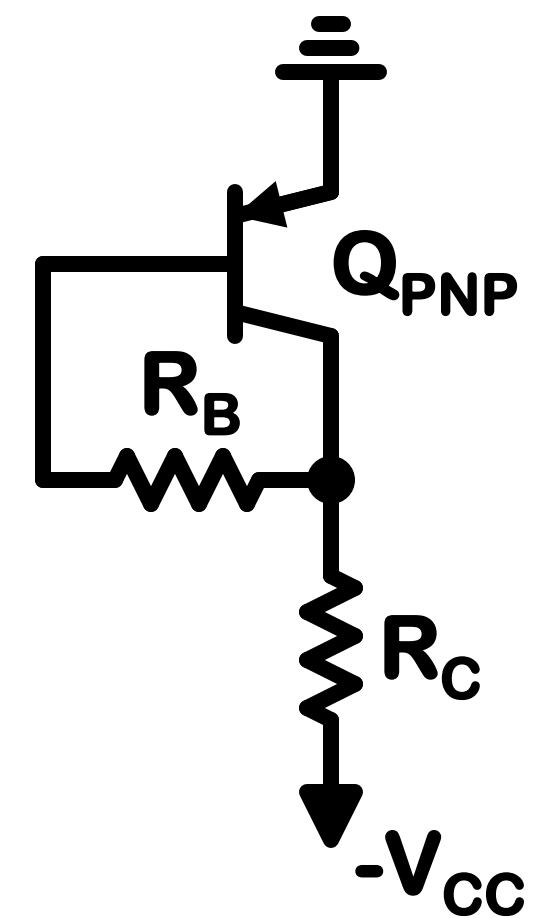4. Check

$$V_{CE} = 6 - 500 \cdot 0.00761 = 2.19V > 0.2V$$



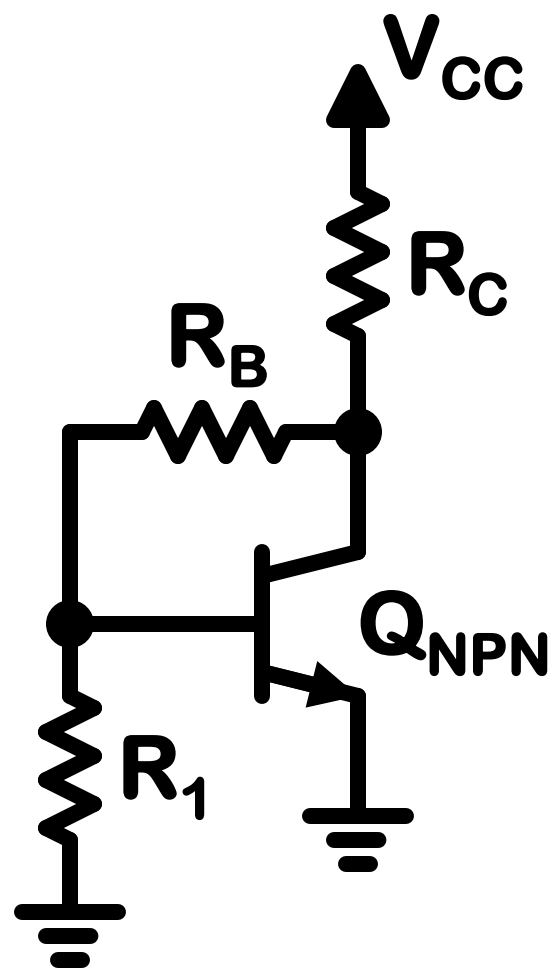

1. Active

2. Enforce (device equation)

$$V_{BE} = 0.7V, i_C = \beta \cdot i_B$$

3. Solve

$$6 - 500(i_E + 0.7/10000) - 10000(i_B + 0.7/10000) - 0.7 = 0$$


$$6 - 500((50+1)i_B + 0.00007) - 10000(i_B + 0.00007) - 0.7 = 0$$


$$i_B = (6 - 0.7 - 10500 \cdot 0.00007) / (500(51) + 10000) = 0.129 \text{ mA}$$

$$i_C = 6.43 \text{ mA}$$

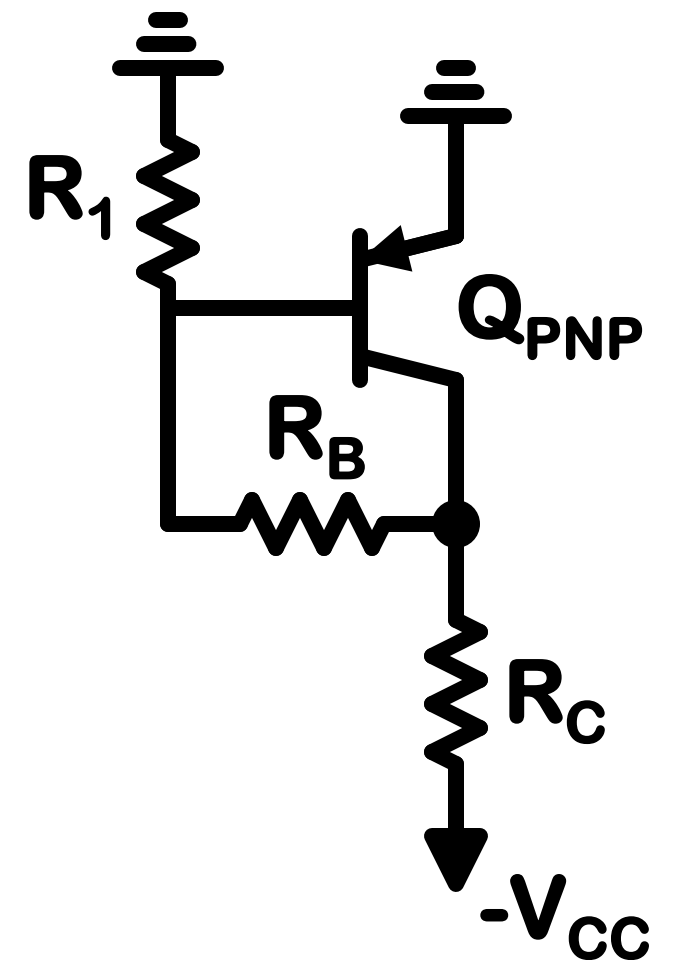4. Check

$$V_{CE} = 6 - 500 \cdot 0.00656 = 2.72V > 0.2V$$



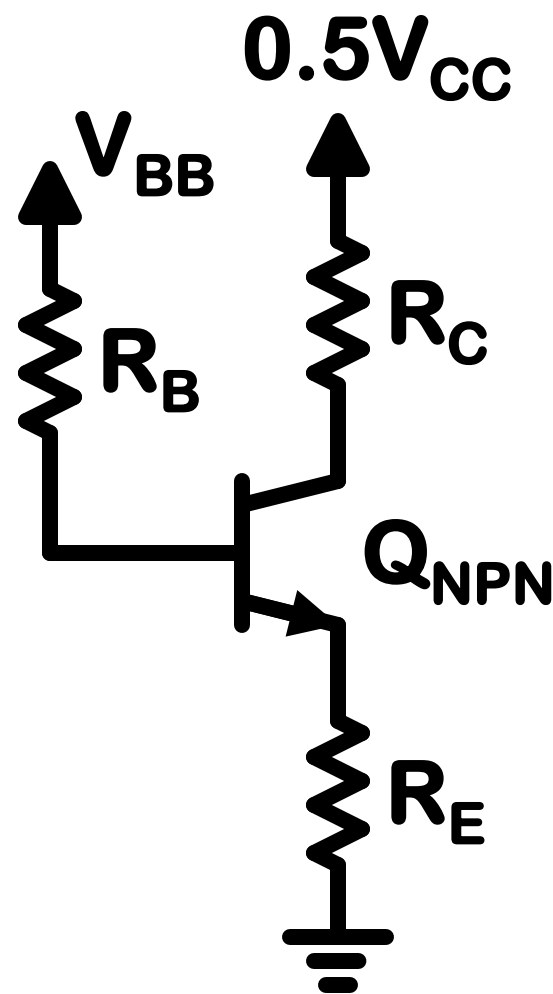

1. Saturation

2. Enforce (device equation)

$$v_{BE} = 0.7V, v_{CE} = 0.2V$$

3. Solve

$$i_E = i_B + i_C$$

$$v_E/200 = (4 - (v_E + 0.7))/10000 + (3 - (v_E + 0.2))/500$$

$$50v_E = 4 - v_E - 0.7 + 60 - 20v_E - 4$$

$$71v_E = 59.3$$

$$v_E = 0.835V$$


$$i_E = 0.835/200 = 4.175 \text{ mA}$$


$$i_B = (4 - (0.835 + 0.7))/10000 = 0.246 \text{ mA}$$

$$i_C = (3 - (0.835 + 0.2))/500 = 3.93 \text{ mA}$$

4. Check

$$i_C/i_B = 16 < 50$$

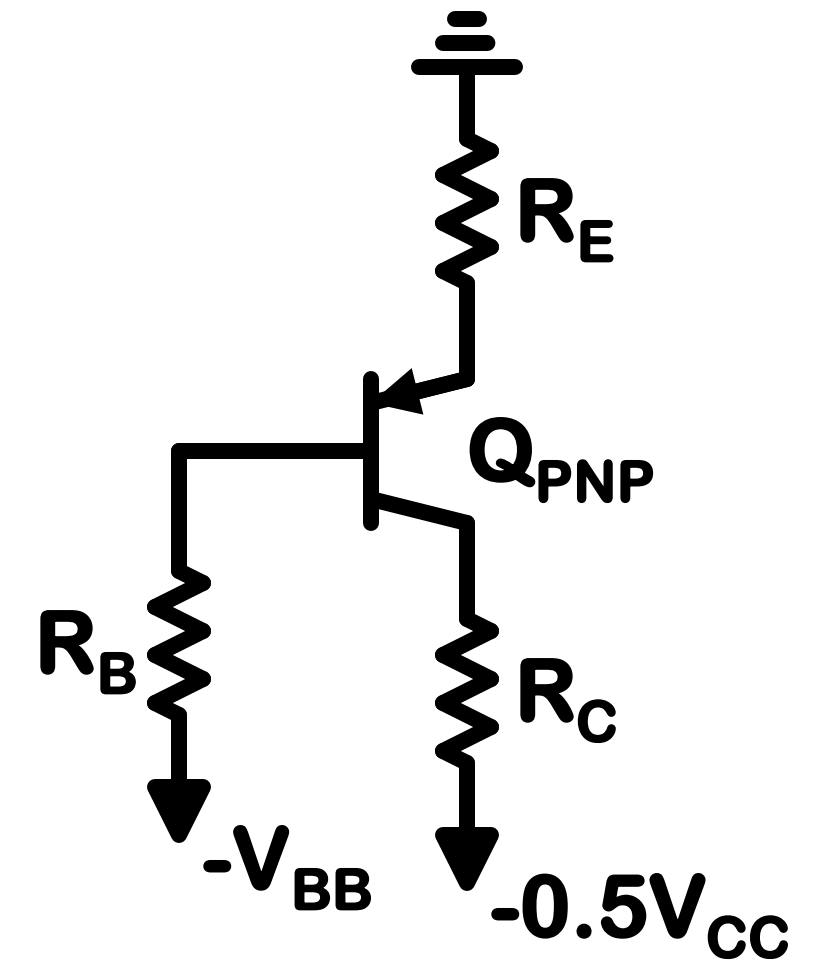

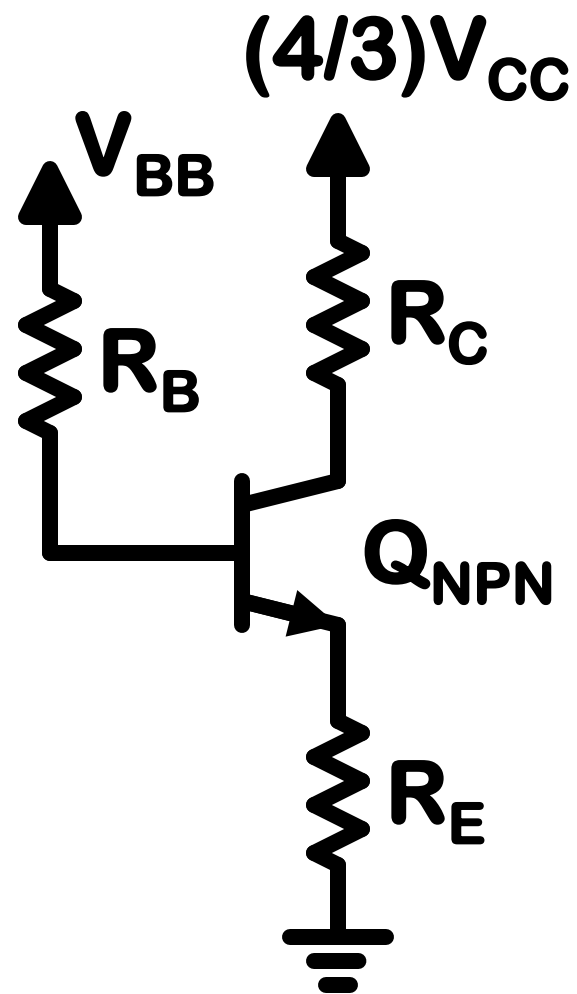

1. Active

2. Enforce (device equation)

$$V_{BE} = 0.7V, i_C = \beta \cdot i_B$$

3. Solve

$$4 - 10000i_B - 0.7 - 200i_E = 0$$

$$4 - 10000i_B - 0.7 - 200(50+1)i_B = 0$$


$$i_B = (4-0.7)/(10000 + 200(50+1)) = 0.163 \text{ mA}$$


$$i_C = 50 \cdot 0.163 = 8.168 \text{ mA}$$

$$i_E = 8.332 \text{ mA}$$

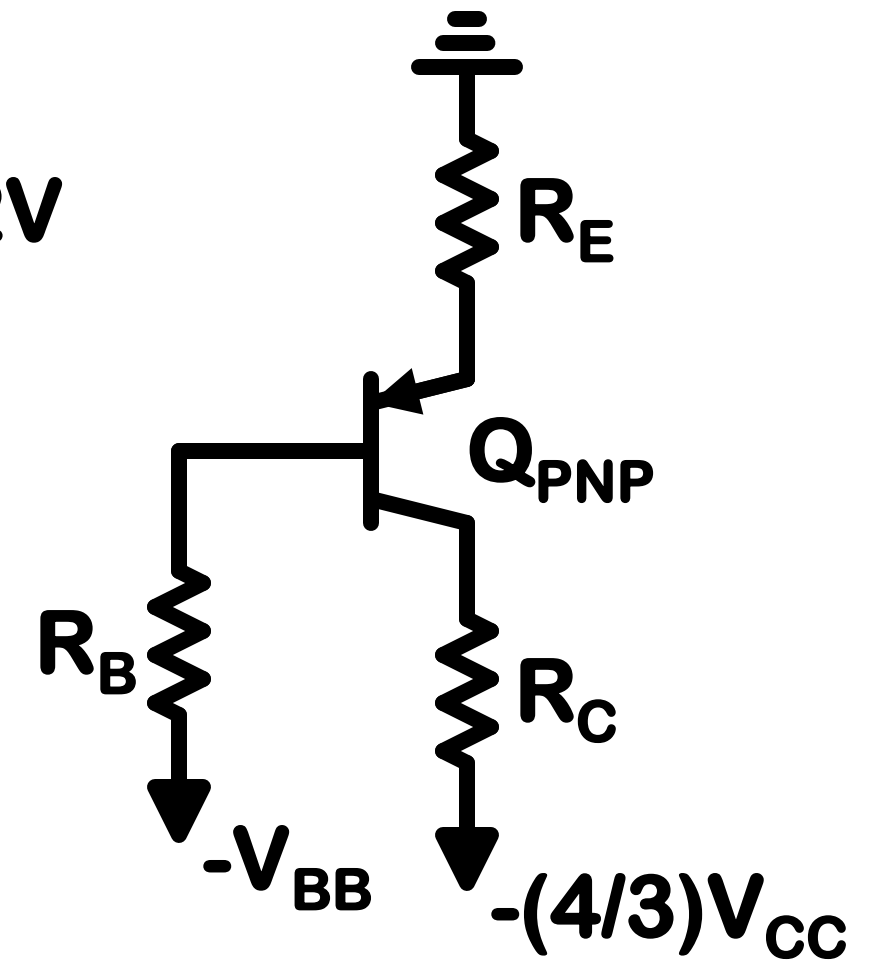4. Check

$$V_{CE} = 8 - 8.168\text{m} \cdot 500 - 8.332\text{m} \cdot 200 = 2.25V > 0.2V$$



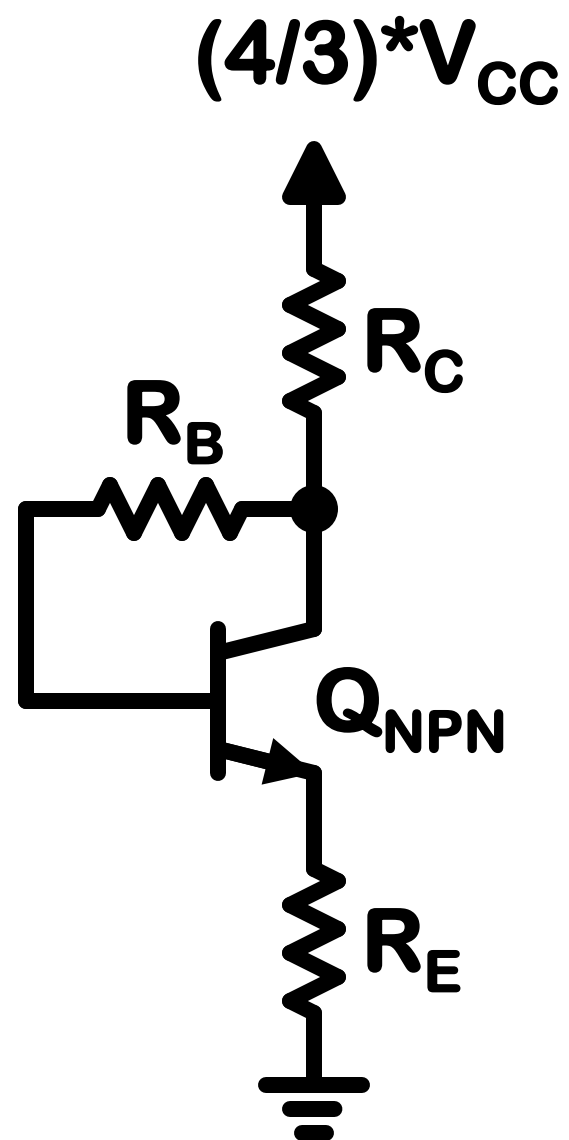

1. Active

2. Enforce (device equation)

$$V_{BE} = 0.7V, i_C = \beta \cdot i_B$$

3. Solve

$$8 - (500+200)i_E - 10000i_B - 0.7 = 0$$

$$8 - 700(50+1)i_B - 10000i_B - 0.7 = 0$$


$$i_B = (8-0.7)/(700(50+1) + 10000)$$

$$i_B = 0.16 \text{ mA}$$

$$i_C = 7.99 \text{ mA}$$

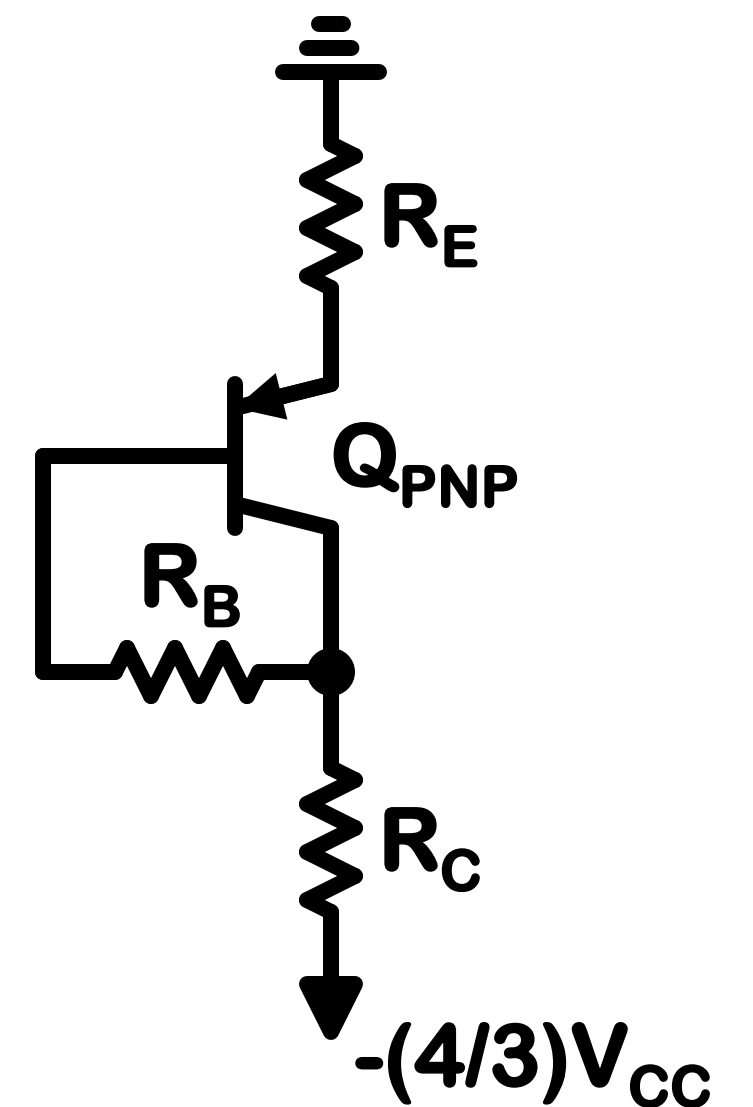4. Check

$$V_{CE} = 8 - 700*0.00815 = 2.3V > 0.2V$$



1. Active

2. Enforce (device equation)

$$V_{BE} = 0.7V, i_C = \beta \cdot i_B$$

3. Solve

$$8 - 700(i_E + 0.7/10000) - 10000(i_B + 0.7/10000) - 0.7 = 0$$



$$8 - 700((50+1)i_B + 0.00007) - 10000(i_B + 0.00007) - 0.7 = 0$$



$$i_B = (8 - 0.7 - 10700 \cdot 0.00007) / (700(51) + 10000) = 0.143 \text{ mA}$$

$$i_C = 7.167 \text{ mA}$$

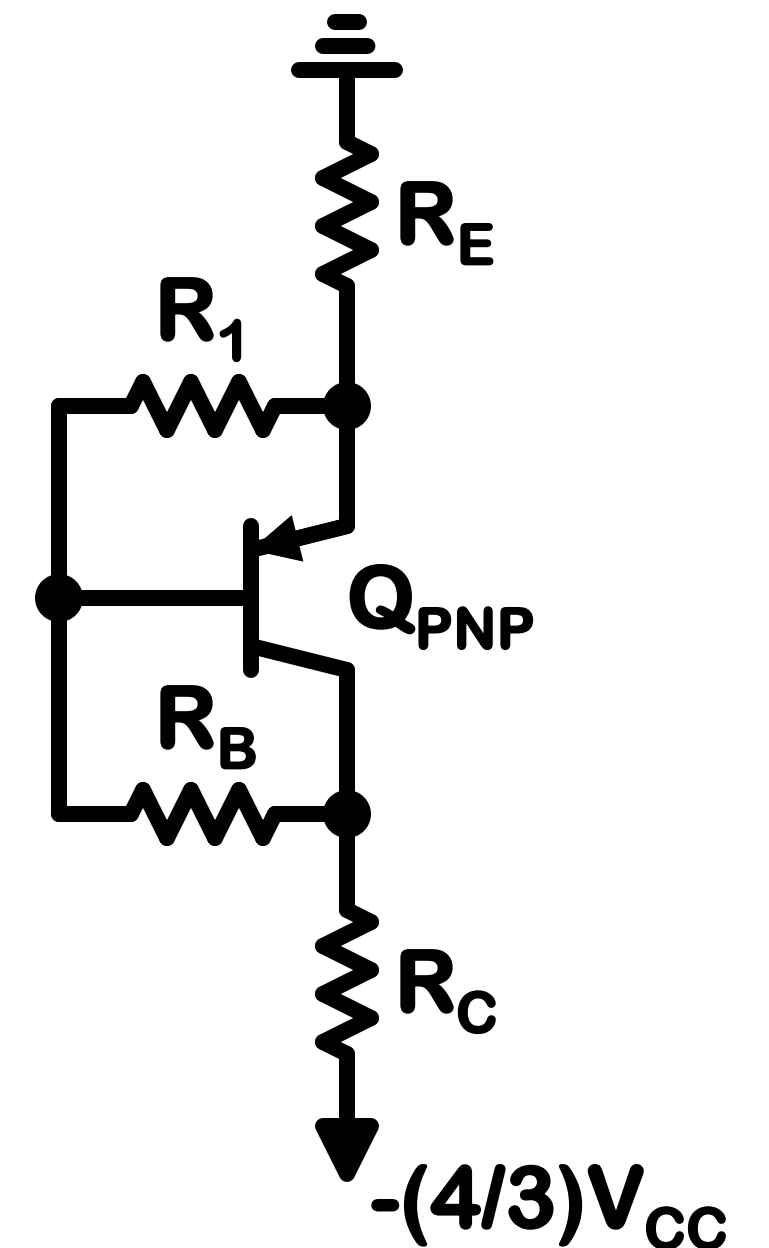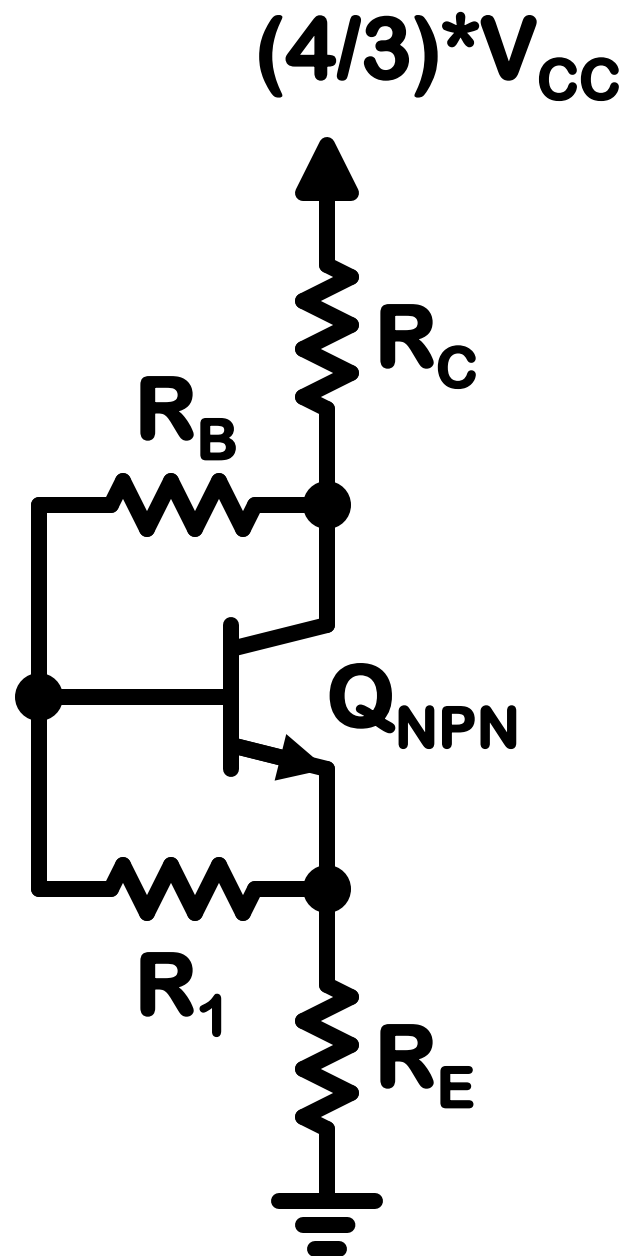4. Check

$$V_{CE} = 8 - 700 \cdot 0.00731 = 2.883V > 0.2$$



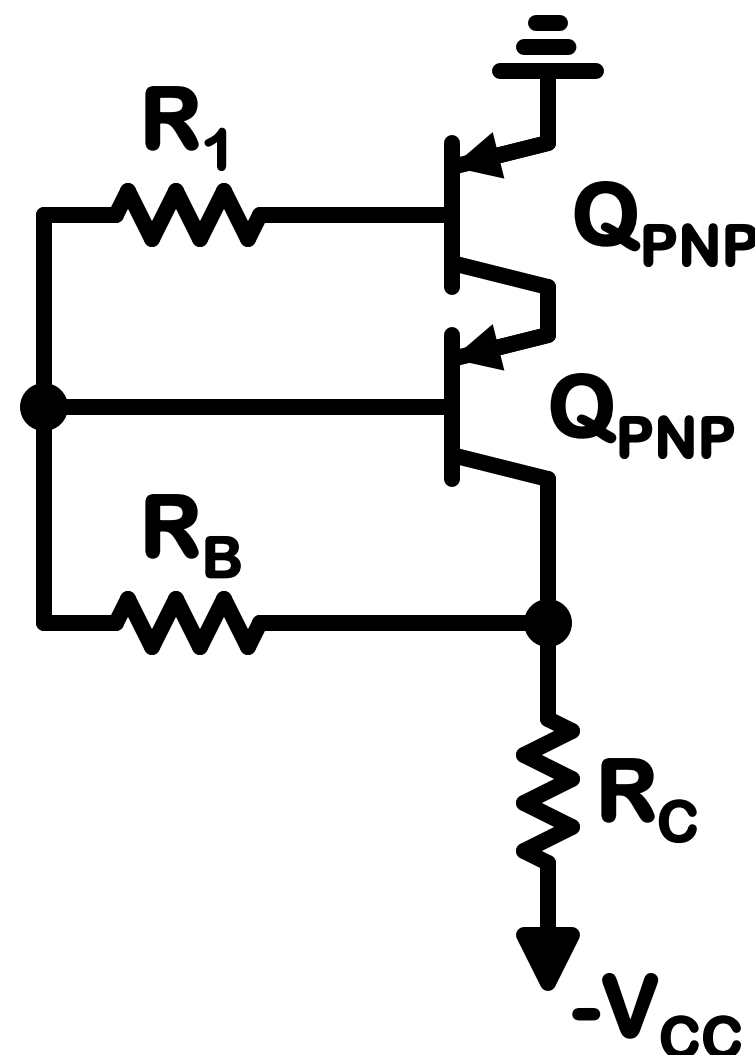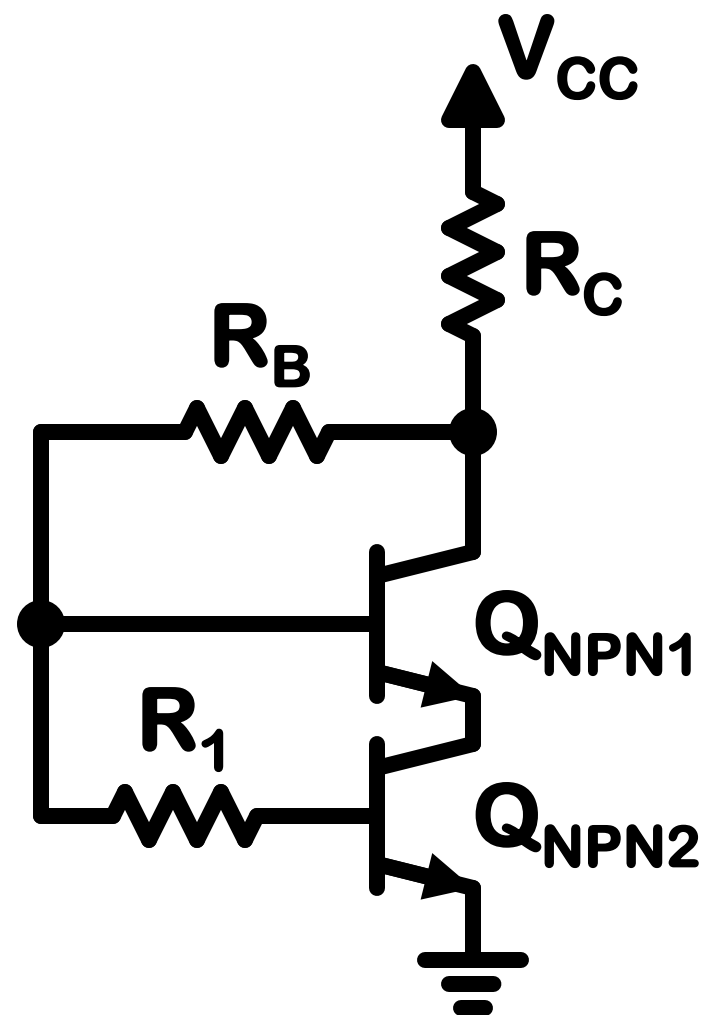

1. Active & Saturation

2. Enforce (device equation)

$$v_{BE1} = 0.7V, i_{C1} = 50i_{B1}$$

$$v_{BE2} = 0.7V, v_{CE2} = 0.2V$$

3. Solve

$$v_{B2} = 0.7V, v_{C2} = v_{E1} = 0.2V, v_{B1} = 0.9V$$

$$i_{B2} = 0.2/10000 = 0.00002mA$$

$$6 - 500(i_{E1} + .00002) - 10000(i_{B1} + .00002) = 0.9V$$

$$6 - 500(i_{E1} + .00002) - 10000(i_{E1}/51 + .00002) = 0.9V$$

$$6 - 0.9 - 10500*.00002 = (500 + 10000/51)i_{E1}$$

$$i_{E1} = 7.025mA$$

$$i_{B1} = 0.138mA$$

$$i_{C1} = 6.887mA$$

$$i_{C2} = i_{E1} = 7.025mA$$

$$i_{B2} = 0.02mA$$

$$i_{E2} = 7.045mA$$

Check: $v_{CE} = 6 - 500i_{E2} - 0.2 = 2.278 > .2$

$i_{C2}/i_{B2} = 351$ not less than 50 - wrong