
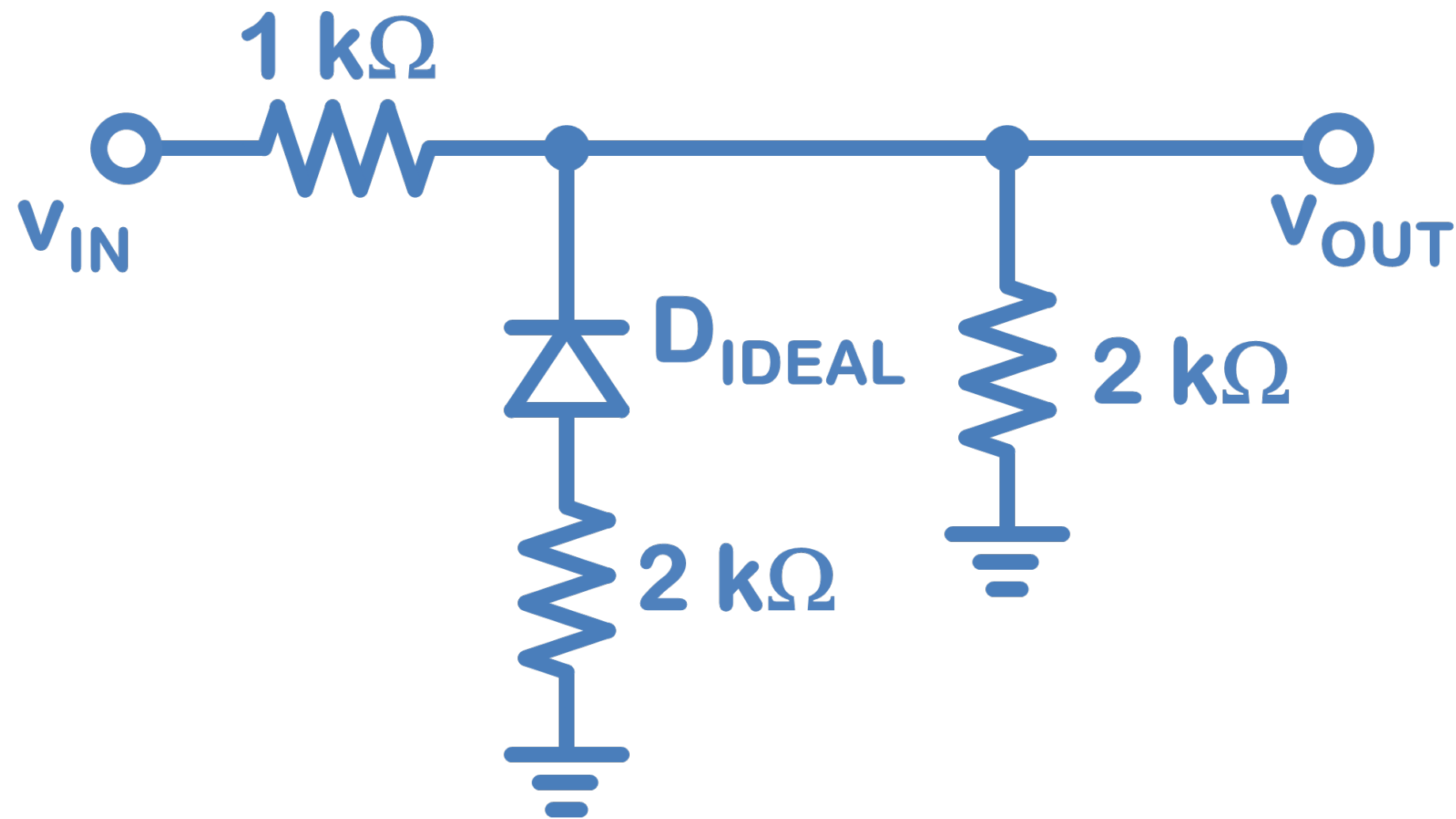


EECS312 Quiz 2

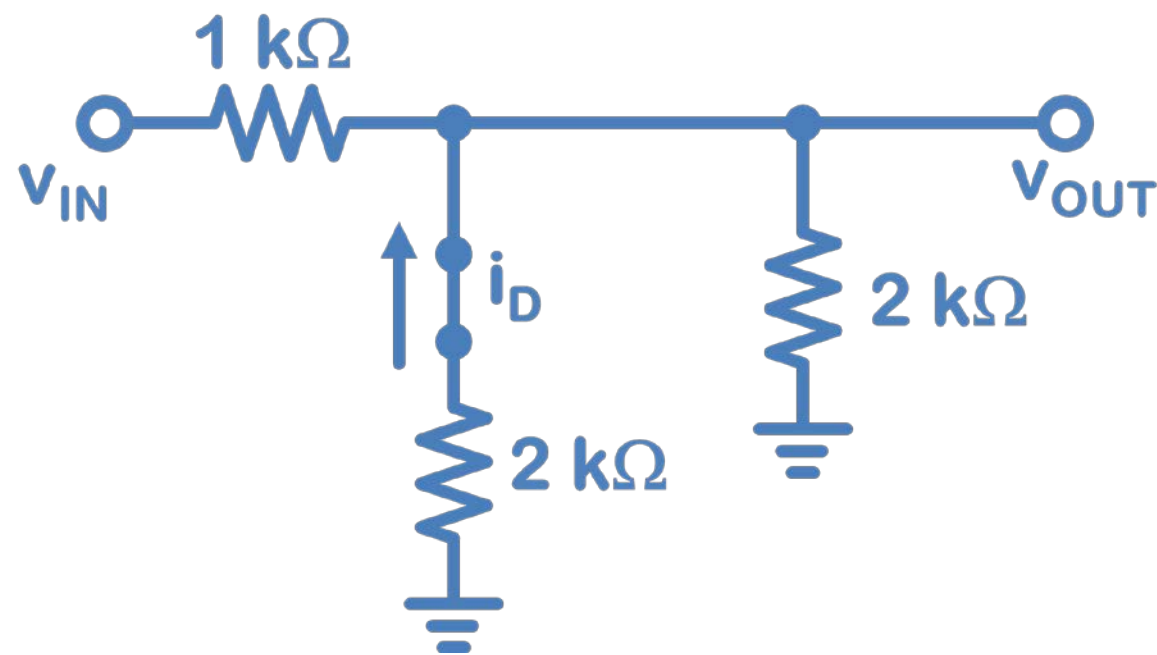

Find $v_{OUT}(v_{IN})$ and the range of v_{IN} . Do both FB and RB.

EECS312 Quiz 2



Find $v_{OUT}(v_{IN})$ and the range of v_{IN} that Reverse Bias is valid.

FB: open:

find $v_{out}(v_{in})$ using resistive divider between and $1k\Omega$ and $1k\Omega$.


$$v_{out}(v_{in}) = (1/2)v_{in}$$

$$\text{find } i_D(v_{in}) = -1/2v_{in}/2k = -(1/4k)v_{in}$$

Apply inequality condition. $-(1/4k)v_{in} > 0$.

Valid: $v_{in} < 0$.
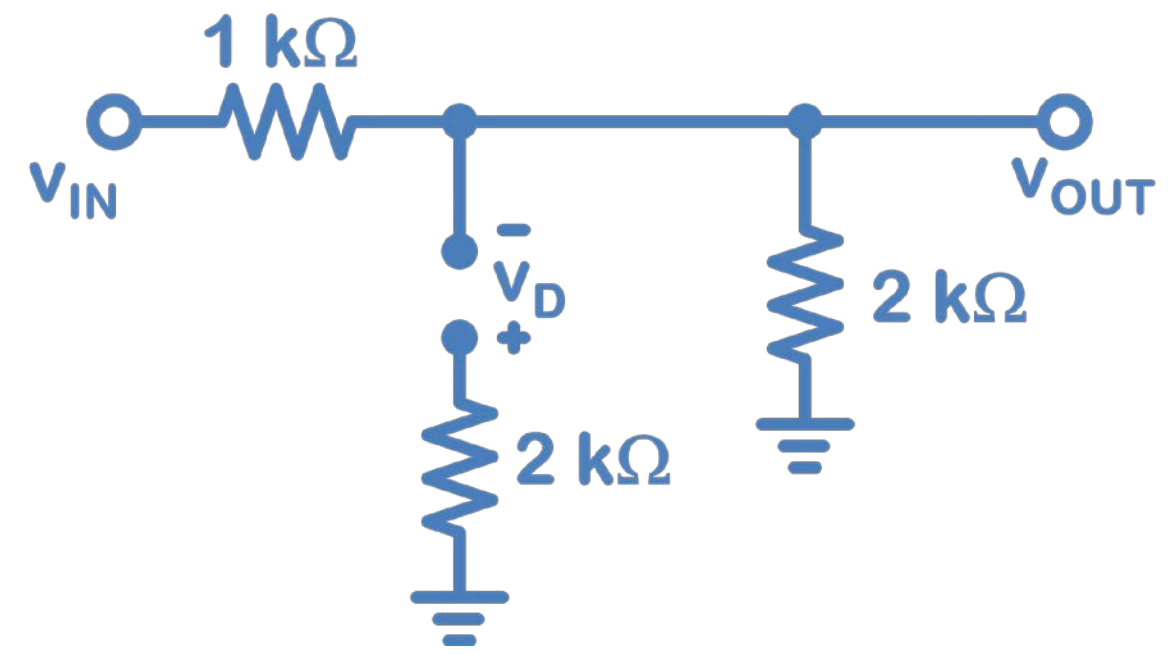
$$v_{out}(v_{in}) = (1/2)v_{in} \text{ for } v_{in} < 0$$



RB: open:

find $v_{out}(v_{in})$ using resistive divider between and $2k\Omega$ and $1k\Omega$.

$$v_{out}(v_{in}) = (2/3)v_{in}$$

$$\text{find } v_D(v_{in}) = 0 - v_{out} = -(2/3)v_{in}$$

Apply inequality condition. $-(2/3)v_{in} < 0$.

Valid: $v_{in} > 0$.

$$v_{out}(v_{in}) = (2/3)v_{in} \text{ for } v_{in} > 0$$