

EECS312-Quiz #3

1. Give the junction diode i-v equation that describes forward and reverse bias.



$$i_D(v_D) = \underline{\hspace{2cm}}$$

2. A junction diode with $n=2$ is biased at a large signal current of $I_D = 2.5\text{mA}$. What is the small signal resistance?

$$r_d = \underline{\hspace{2cm}}$$

3. For the circuits below, find the diode voltage (v_D) and diode current (i_D). Assume the diode in (a) is Forward Biased and the diode in (b) is Reverse Biased.

$$V_{Da} = \underline{\hspace{2cm}} \quad i_{Da} = \underline{\hspace{2cm}} \quad V_{Db} = \underline{\hspace{2cm}} \quad i_{Db} = \underline{\hspace{2cm}}$$

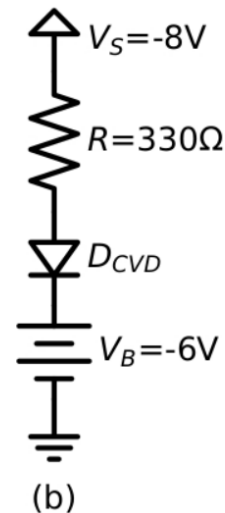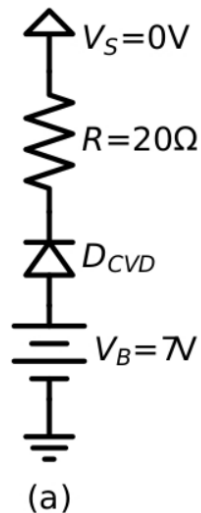

EECS312-Quiz #3

1. Give the junction diode i-v equation that describes forward and reverse bias.

$$i_D(v_D) = I_S(\exp(v_D/nV_T)-1)$$

2. A junction diode with $n=2$ is biased at a large signal current of $I_D = 2.5\text{mA}$. What is the small signal resistance?

$$r_d = nV_T/I_D = 2 \cdot 0.025 / 0.0025 = 20\Omega$$

3. For the circuits below, find the diode voltage (v_D) and diode current (i_D). Assume the diode in (a) is Forward Biased and the diode in (b) is Reverse Biased.

$$v_{Da} = 0.7V$$

$$i_{Da} = 6.3/20 \text{ [A]}$$

$$v_{Db} = -8 - -6 = -2V$$

$$i_{Db} = 0A$$

