

EECS312-Quiz 5

For the circuit to the right, the NMOS (Q_N) is characterized by:

$$k_n = 5 \text{ mA/V}^2$$


$$V_{tn} = 1\text{V}$$

Find the voltage V_1 using saturation mode:

$$i_D = 0.5k_n(v_{GS} - V_{tn})^2.$$

Verify whether saturation is correct.

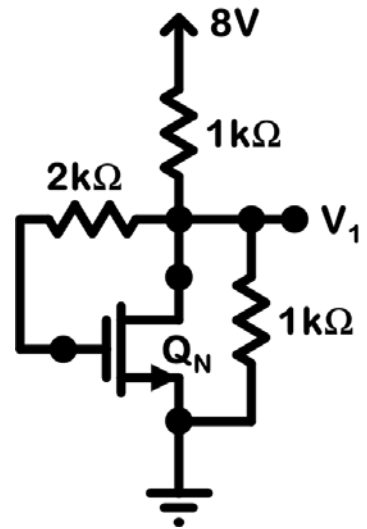Show your work for each step and label each step (steps 1 and 5 are completed for you).



1. Guess: Saturation

2. _____

3. _____

4. _____

5. Done:

EECS312-Quiz 5

For the circuit to the right, the NMOS (Q_N) is characterized by:

$$k_n = 5 \text{ mA/V}^2$$


$$V_{tn} = 1\text{V}$$

Find the voltage V_1 using saturation mode:

$$i_D = 0.5k_n(v_{GS}-V_{tn})^2.$$

Verify whether saturation is correct.

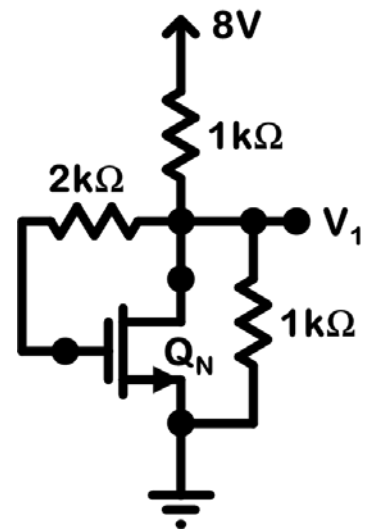Show you work for each step and label each step (steps 1 and 5 are completed for you).



1. Guess: Saturation

2. Enforce

$$i_D = 0.0025(v_{DS}-1)^2$$

3. Solve

$$i_D = i_1 - i_2$$

$$.0025(v_{DS}-1)^2 = (8-v_{DS})/1000 - v_{DS}/1000$$

$$2.5v_{DS}^2 - 5v_{DS} + 2.5 = 8 - 2v_{DS}$$

$$2.5v_{DS}^2 - 3v_{DS} - 5.5 = 0$$

$$v_{DS} = (3 \pm \sqrt{9 + 4 \cdot 2.5 \cdot 5.5})/5$$

$$v_{DS} = (3 \pm \sqrt{64})/5 = 11/5 \text{ or } -1 \text{ choose } 11/5 = 2.2$$

$$V_1 = v_{DS} = 2.2\text{V}$$

4. Check

$$v_{GS} > V_{tn}, 2.2 > 1, \text{ Yes}$$

$$v_{DS} > v_{GS} - V_{tn}, 2.2 > 1.2, \text{ Yes}$$

5. Done: