

Quiz: Solutions

Cutoff Mode

What are two equality equations for cutoff mode? (hint: three possibilities, but there are only 2 independent equations)

$$i_E = i_B = i_C = 0$$

What are two inequality equations for cutoff mode? (hint: think about how the PN junctions must be biased)

$$V_{BE} < 0.7$$

$$V_{BC} < 0.5$$

Saturation Mode

What is the equation for i_C in Saturation mode?

$$i_C = I_S \exp(V_{BE}/V_T) - (I_S/\alpha_R) \exp(V_{BC}/V_T)$$

$$i_C = I_S \exp(V_{BE}/V_T) (1 - (1/\alpha_R) \exp(-V_{CE}/V_T))$$

If you take i_C equation in Saturation mode and consider a large value of v_{CE} , how can you approximate it? (hint (maybe): if v_{CE} is a large positive value what does that do to v_{BC} ?)

Active Mode

What is the equation for i_C in active mode?

$$i_C = I_S \exp(V_{BE}/V_T)$$

What is another enforcing equation for active mode?

$$i_C = \beta i_B$$

What are two inequality equations for active mode? (hint: think about how the PN junctions must be biased)

$$V_{CE} > 0.2V \text{ and } i_B > 0$$