

Diode Content and Equations

Diode Symbol, Terminal Names, Voltage and Current Orientations

Ideal Diode:	Model	Eq. Var	Cond	Ineq. Var	Cond
FB:	$v_D = 0$, for $i_D > 0$	Short			
RB:	$i_D = 0$, for $v_D < 0$	Open			

Junction Diode: $i_D = I_S(\exp(v_D/nV_T) - 1)$, for both FB and RB

Range of values for I_S (1×10^{-8} to 1×10^{-15} [Amps]) and n (1 to 2).
 V_T is dependent on temperature (Typically 0.025V)

FB approximation ($v_D \gg nV_T$): $i_D = I_S \exp(v_D/nV_T)$

RB approximation ($v_D \ll -nV_T$): $i_D = -I_S$

0.7V CVD Model:	Ideal Diode in series with 0.7V Battery
FB:	$v_D = 0.7V$, for $i_D > 0$
RB:	$i_D = 0$, for $v_D < 0.7V$

PWL Model:	Ideal Diode in series with Resistor and Battery
FB:	$i_D = (v_D - V_{D0})/r_D$, for $v_D > V_{D0}$
RB:	$i_D = 0$, for $v_D < V_{D0}$

Small Signal Diode Model: $r_d = nV_T/I_D$

always assume the diode is FB for small signal analysis problems

Small Signal resistance given $i(v)r = 1/i'_D(v_D)$ evaluated at (V_D, I_D)

Know the table of devices and their Large Signal Model and Small Signal Model

Zener Diode (CVD Model):	Ideal Diode in series with a Battery
BD:	$v_Z = V_Z$, for $i_Z > 0$
RB:	$i_Z = 0$, for $v_Z < V_Z$

Zener Diode (PWL Model):	Ideal Diode in series with Resistor and Battery
BD:	$i_Z = (v_Z - V_{Z0})/r_Z$, for $v_Z > V_{Z0}$
RB:	$i_Z = 0$, for $v_Z < V_{Z0}$

Zener Symbol and Voltage & Current Orientations

Difference and Similarities between Zener and Junction Diodes

Diode Applications (what is the purpose, basic circuit and basic operation)

- Current Protection
- Simple Digital Logic
- Limiters (Circuit Protection) – Transfer Functions
- Rectifier Circuits (v_{OUT}/v_{IN} , PIV)
- Regulator (line regulation, load regulation)
- AC/DC Supply (approximation for ripple voltage)
- Voltage Controlled Attenuator
- Frequency Mixer

Semiconductors

Silicon lattice (intrinsic, covalent bonds).

Current (two types)

- Drift – charge moving due to electric field.

- Diffusion – charge moving due to heat and concentration gradient.

Doped Silicon

- N-Type: use Phosphorus to add extra electrons.

- P-Type: use Boron to add extra holes.

- Majority carriers

- Minority carriers

- Depleted

PN Junction and Bias States (FB, RB, Breakdown)

Exam I Organization

Around 4-5 Problem Sections

- Diode analysis at DC:** Given a circuit, assume a bias, find the answer, & verify bias.
- Diode Transfer Function:** Given a circuit, assume a bias, find the transfer function, and find the range of the independent variable.
- Diode Small Signal Analysis:** Large Signal Circuit, Small Signal Resistance, Small Signal Relationship.
- Short Answer Section:** True or False, Calculations (maybe using exponential model), General Application Questions (line regulation, Peak Inverse Voltage, Ripple Voltage, ...), AC/DC Supplies, Quick Analysis, Concept Understanding.
- Applications:** Given a circuit ... what is its purpose.