


Problem 1.

Find V_D and I_D for each circuit.



(A)

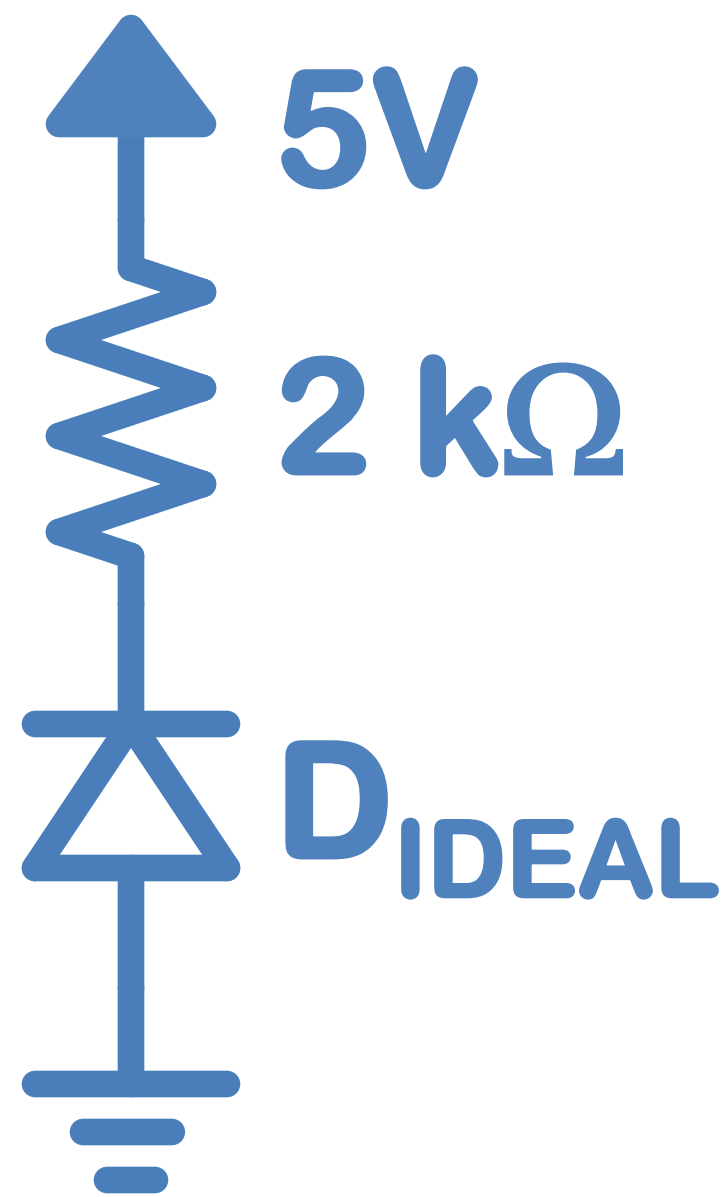1. FB:
2. short ($v_D=0$)
3. $i_D = 4/3.8k$
 $i_D = 1.05mA$
4. check $i_D > 0$
YES
5. Done




(B)

1. RB:
2. open ($i_D=0$)
3. $v_D = 0-5 = -5V$
4. check $v_D < 0$
YES
5. Done



(C)

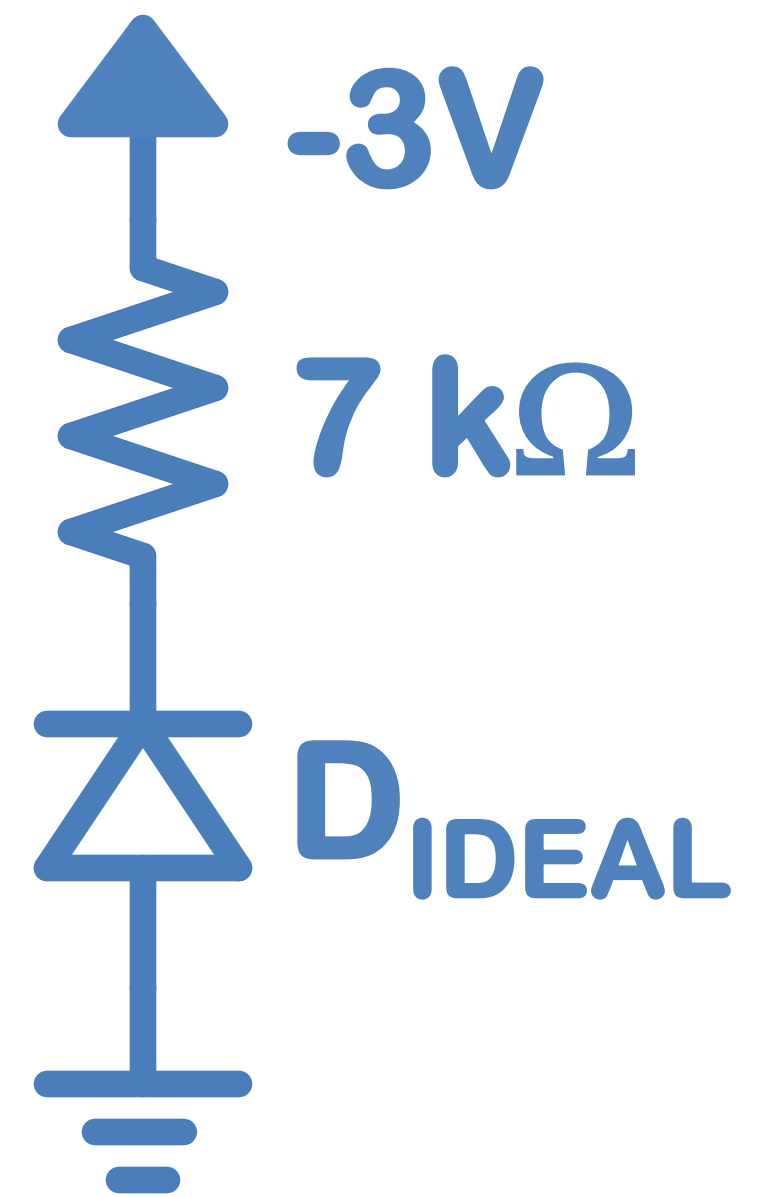1. RB:
2. open ($i_D=0$)
3. $v_D = -1-0 = -1V$
4. check $v_D < 0$
YES
5. Done



(D)

1. FB:
2. short ($v_D=0$)
3. $i_D = 0- -3/7k$
 $i_D = 0.43mA$
4. check $i_D > 0$
YES
5. Done

Problem 1.

Find V_D and I_D for each circuit.



(E)

1. FB:
2. short ($v_D=0$)
3. $i_D = 0 - -8/12k$
 $i_D = 0.67mA$
4. check $i_D > 0$
YES
5. Done




(F)

1. FB:
2. short ($v_D=0$)
3. $i_D = 4-0/2.3k$
 $i_D = 1.74mA$
4. check $i_D > 0$
YES
5. Done



(G)

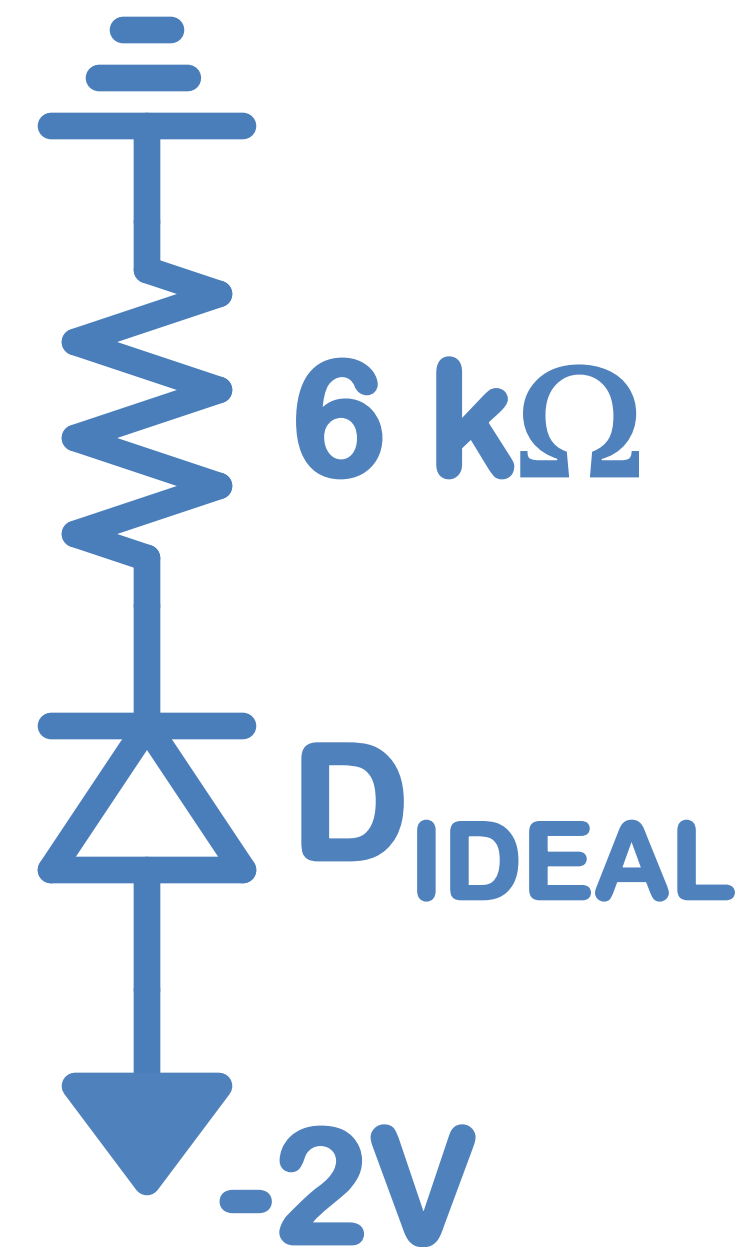
1. FB:
2. short ($v_D=0$)
3. $i_D = 0 - -5/11k$
 $i_D = 0.45mA$
4. check $i_D > 0$
YES
5. Done



(H)

1. RB:
2. open ($i_D=0$)
3. $v_D = -2-0 = -2V$
4. check $v_D < 0$
YES
5. Done

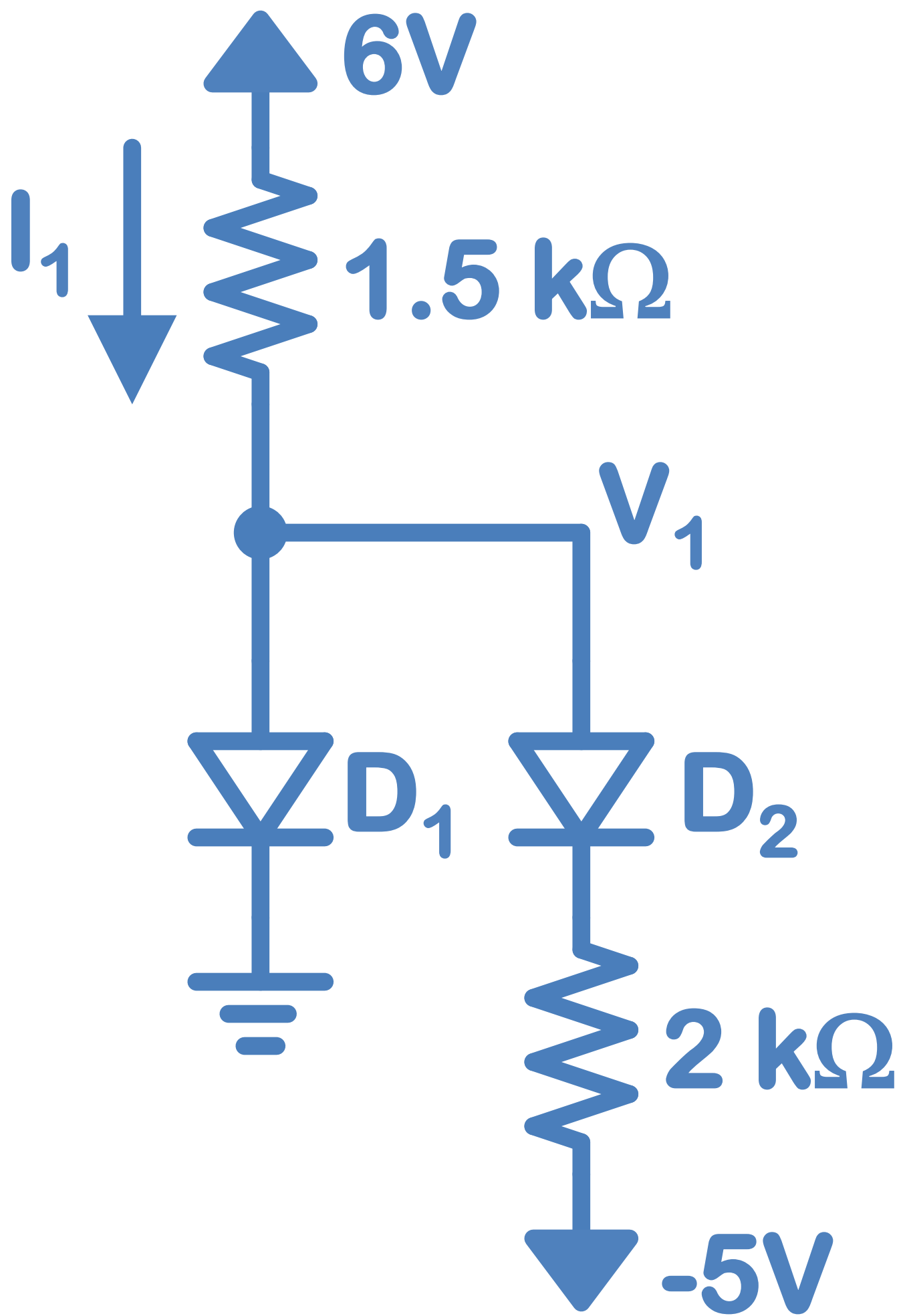Problem 2. Find $V_{1,2,3}$ and $I_{1,2,3}$ in the circuits below. All diodes are ideal.



(A)

1. FB, FB
2. shorts ($v_{D1}=0, v_{D2}=0$)
3. Find I_1, V_1, i_{D1}, i_{D2}

$$V_1 = 0$$

$$I_1 = \frac{6-0}{1.5k} = 4mA$$


$$i_{D2} = \frac{0-(-5)}{2k} = 2.5mA$$

$$i_{D1} = 4-2.5 = 1.5mA$$

4. check
 $i_{D1} > 0$ Yes
 $i_{D2} > 0$ Yes

5. Done

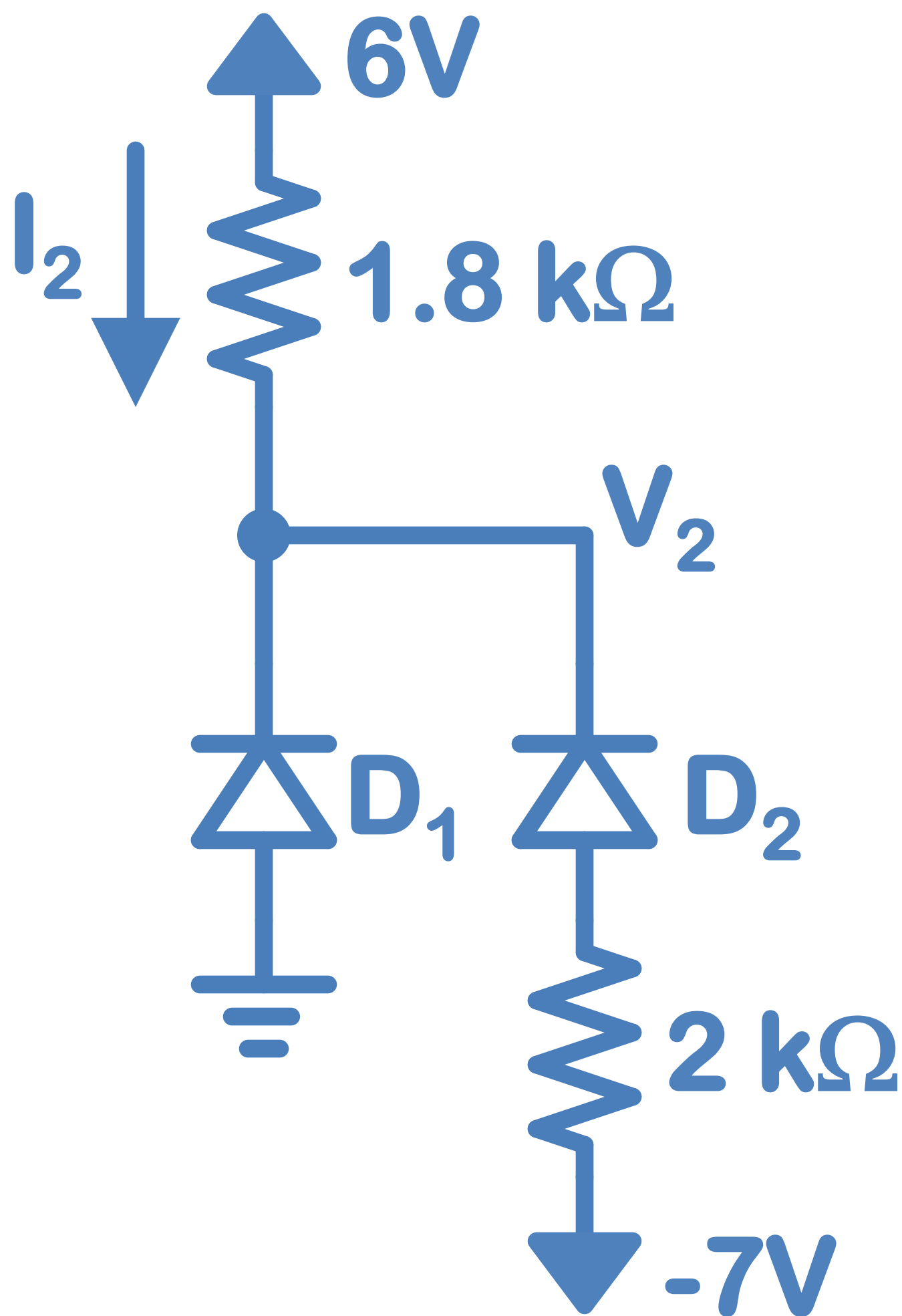Problem 2. Find $V_{1,2,3}$ and $I_{1,2,3}$ in the circuits below. All diodes are ideal.



(B)

1. RB, RB
2. opens ($i_{D1}=0, i_{D2}=0$)
3. Find I_2, V_2, v_{D1}, v_{D2}

$$V_2 = 6$$

$$I_2 = 0$$


$$v_{D1} = 0 - 6 = -6V$$

$$v_{D2} = -7 - 6 = -13V$$

4. check
 $v_{D1} < 0$ Yes
 $v_{D2} < 0$ Yes

5. Done

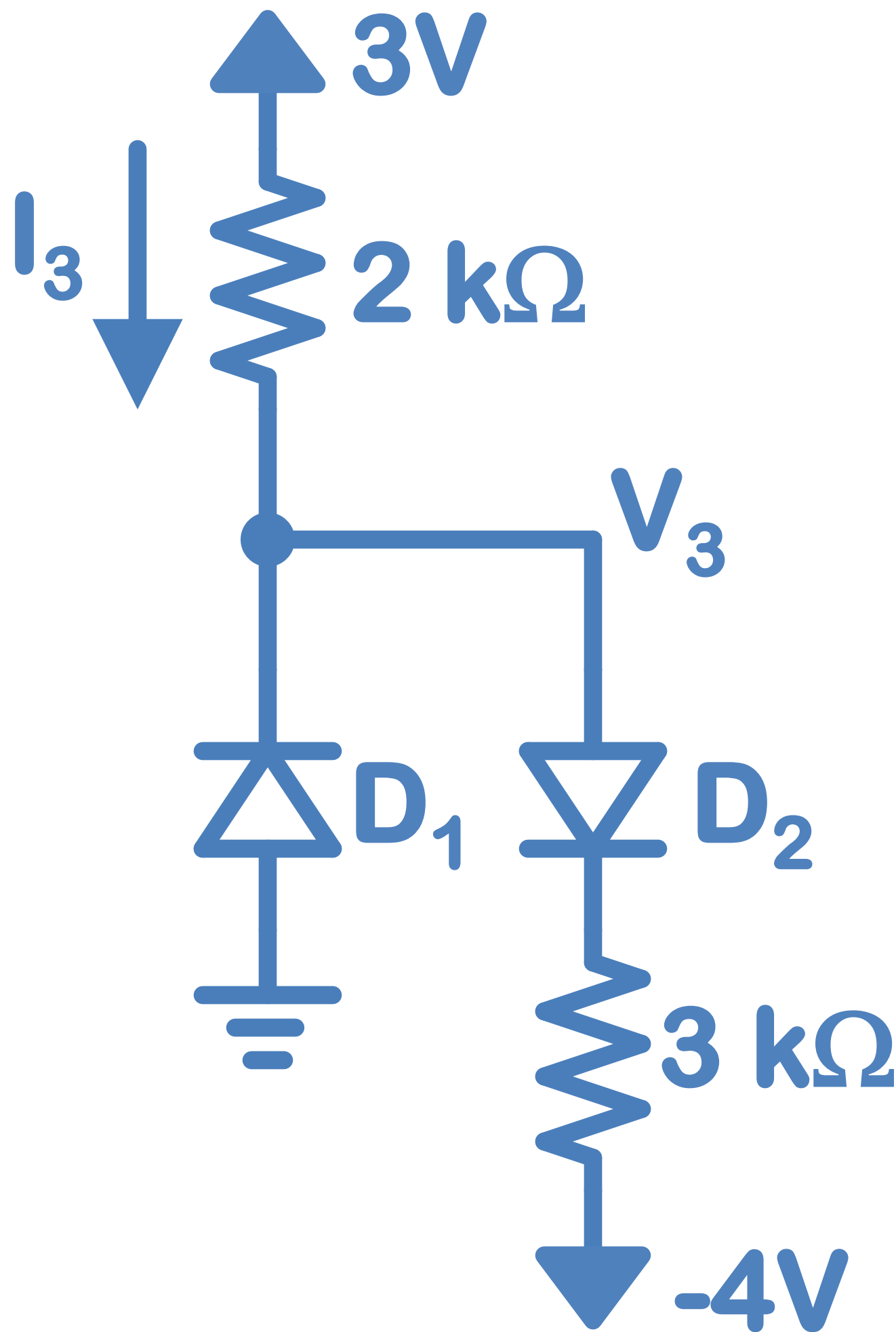Problem 2. Find $V_{1,2,3}$ and $I_{1,2,3}$ in the circuits below. All diodes are ideal.



(C)

1. RB, FB
2. open, short ($i_{D1}=0$, $v_{D2}=0$)
3. Find I_3 , V_3 , i_{D1} , i_{D2}

$$I_3 = (3 - -4) / (2k + 3k) = 7 / 5k = 1.4mA$$

$$V_3 = 3 - 2k * 1.4m = 0.2V$$



$$v_{D1} = 0 - 0.2 = -0.2V$$

$$i_{D2} = I_3 = 1.4mA$$

4. check
 $v_{D1} < 0$ Yes
 $i_{D2} > 0$ Yes

5. Done

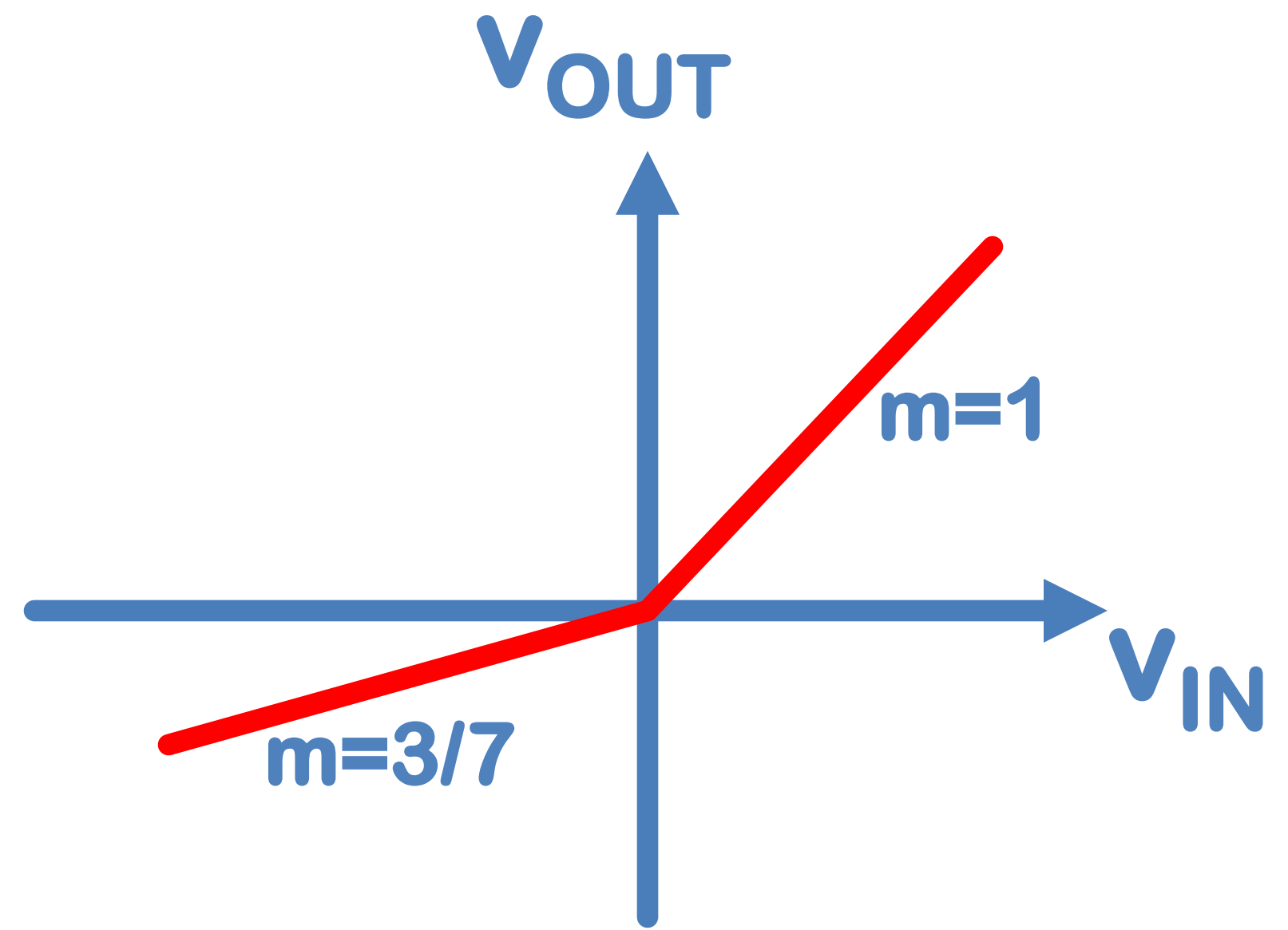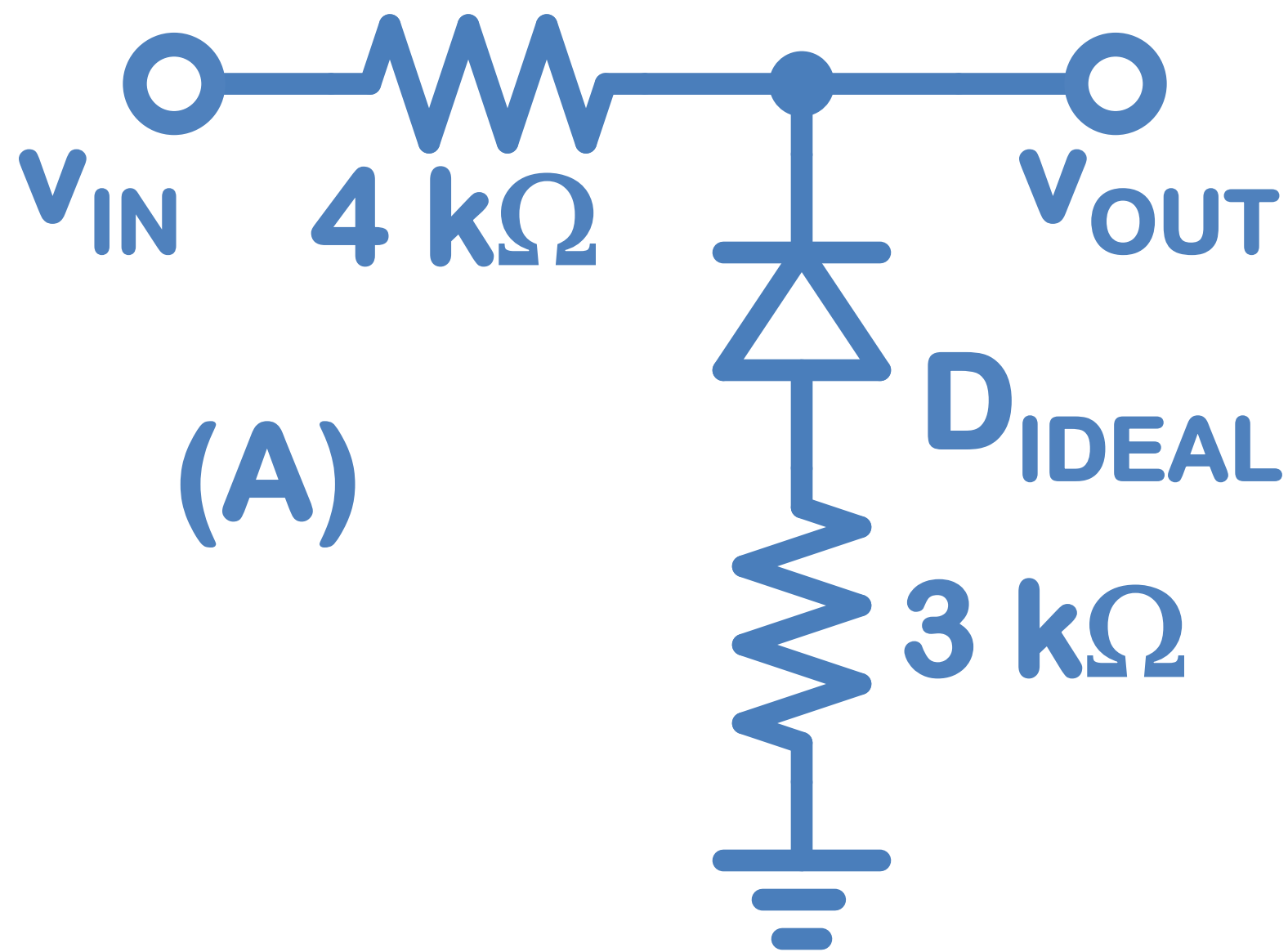Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



1. FB case:
2. short ($v_D=0$)
3. $v_{OUT}=(3/(3+4))v_{IN}$
 $v_{OUT} = (3/7)v_{IN}$
 $i_D = (0-v_{IN})/(4k+3k)$
4. apply $i_D>0$, therefore $v_{IN} < 0$
5. Next



1. RB case:
2. open ($i_D=0$)
3. $v_{OUT}=v_{IN}$
 $v_D = (0-v_{IN})$
4. apply $v_D<0$, therefore $v_{IN} > 0$
5. Done

answer:

$$v_{OUT} = (3/7)v_{IN}, v_{IN} < 0$$

$$v_{OUT} = v_{IN}, v_{IN} > 0$$

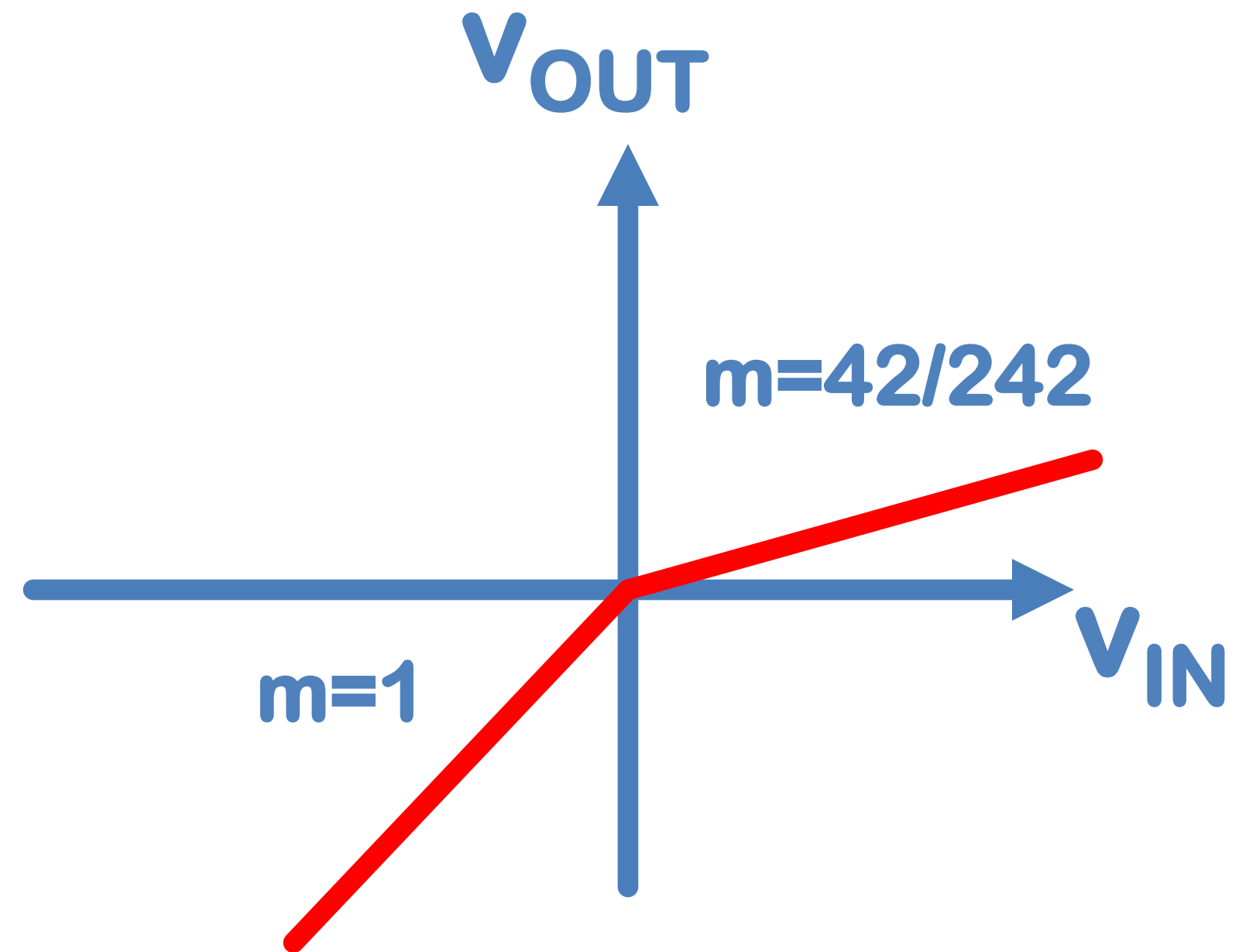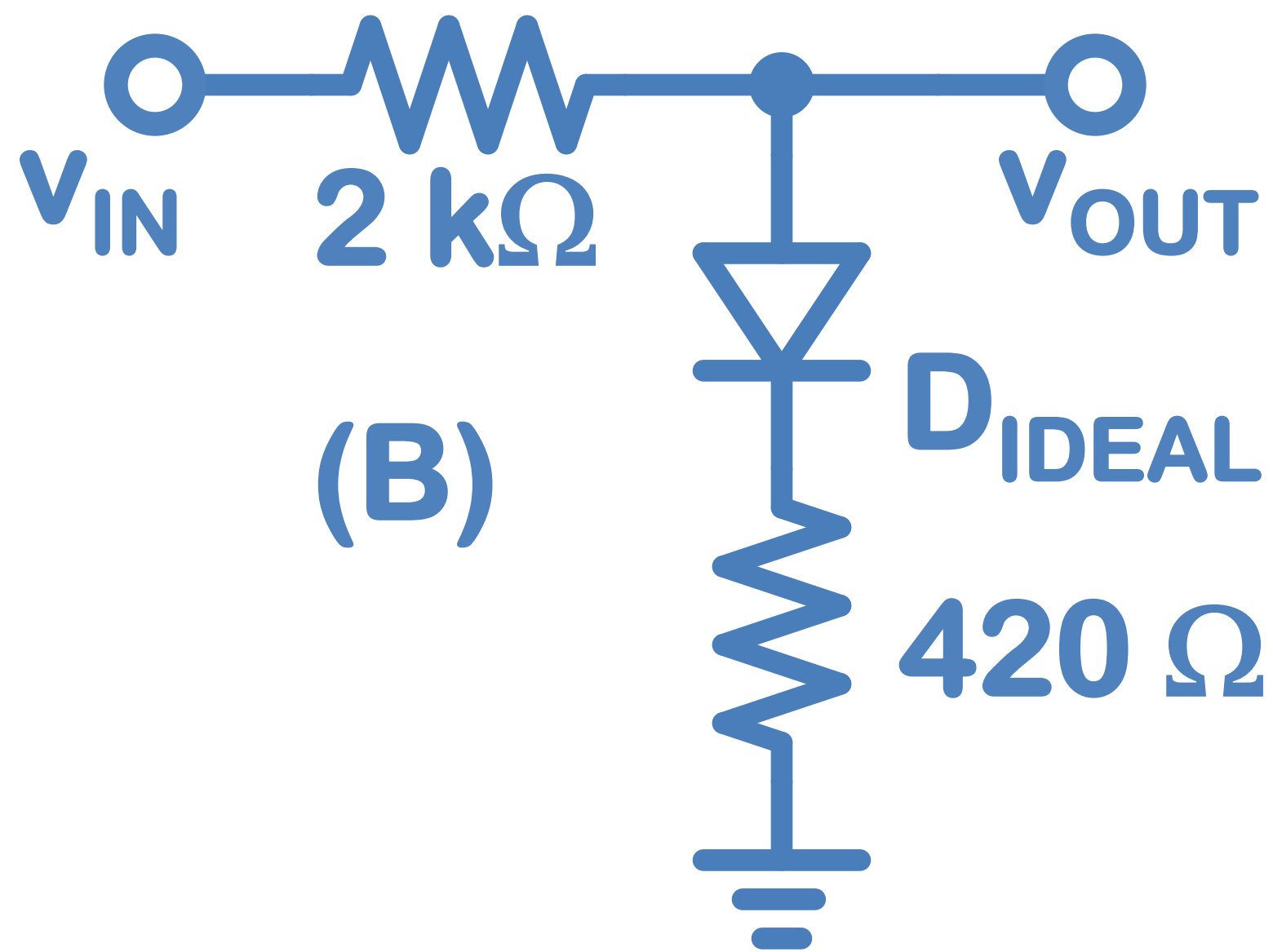Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



1. FB case:

2. short ($v_D=0$)

3. $v_{OUT} = (420/(420+2k))v_{IN}$

$v_{OUT} = (42/242)v_{IN}$

$i_D = (v_{IN}-0)/(2420)$

4. apply $i_D > 0$, therefore

$v_{IN} > 0$

5. Next

1. RB case:

2. open ($i_D=0$)

3. $v_{OUT} = v_{IN}$

$v_D = (v_{IN}-0)$

4. apply $v_D < 0$, therefore

$v_{IN} < 0$



5. Done

answer:

$v_{OUT} = (42/242)v_{IN}, v_{IN} > 0$

$v_{OUT} = v_{IN}, v_{IN} < 0$

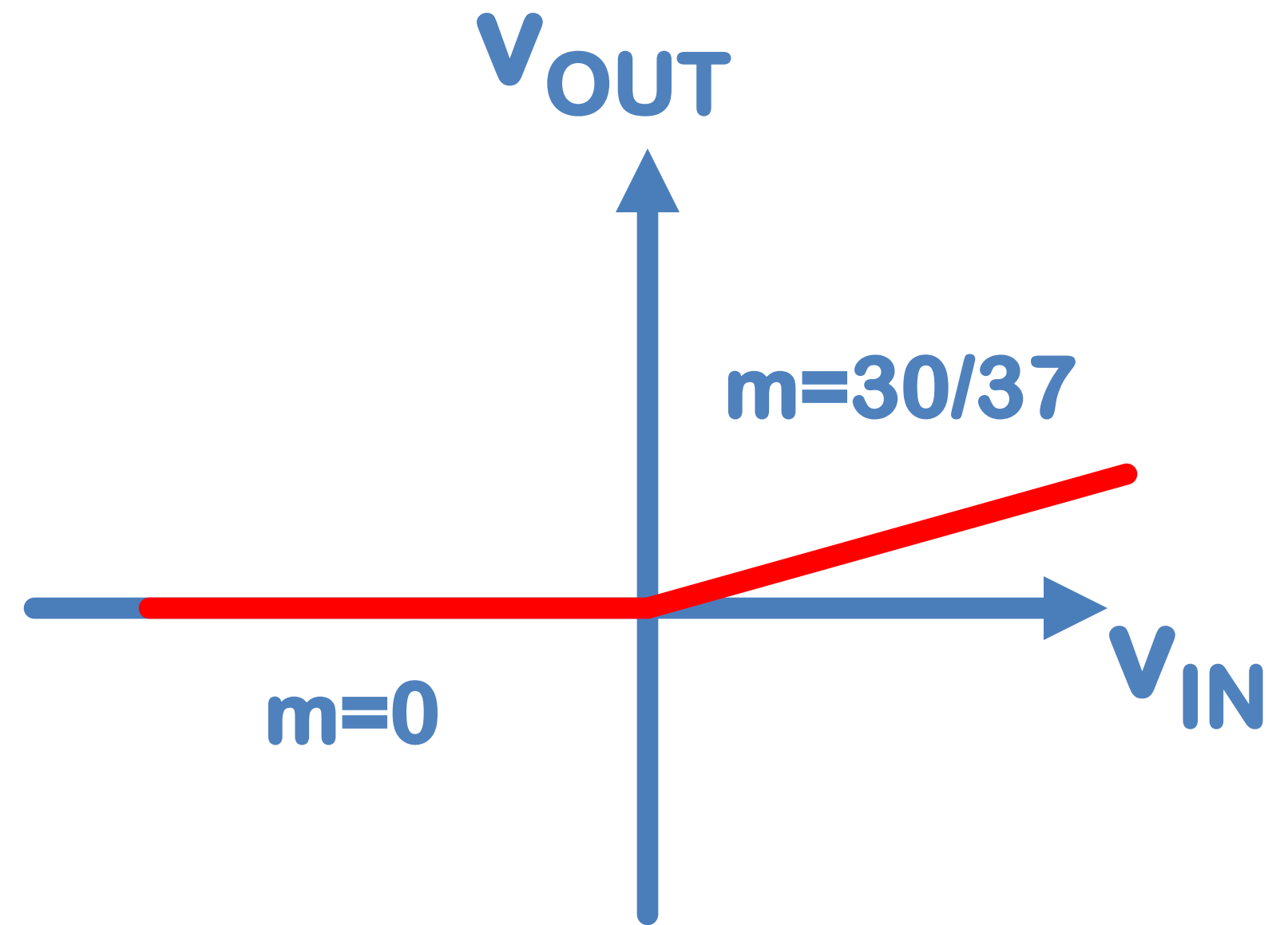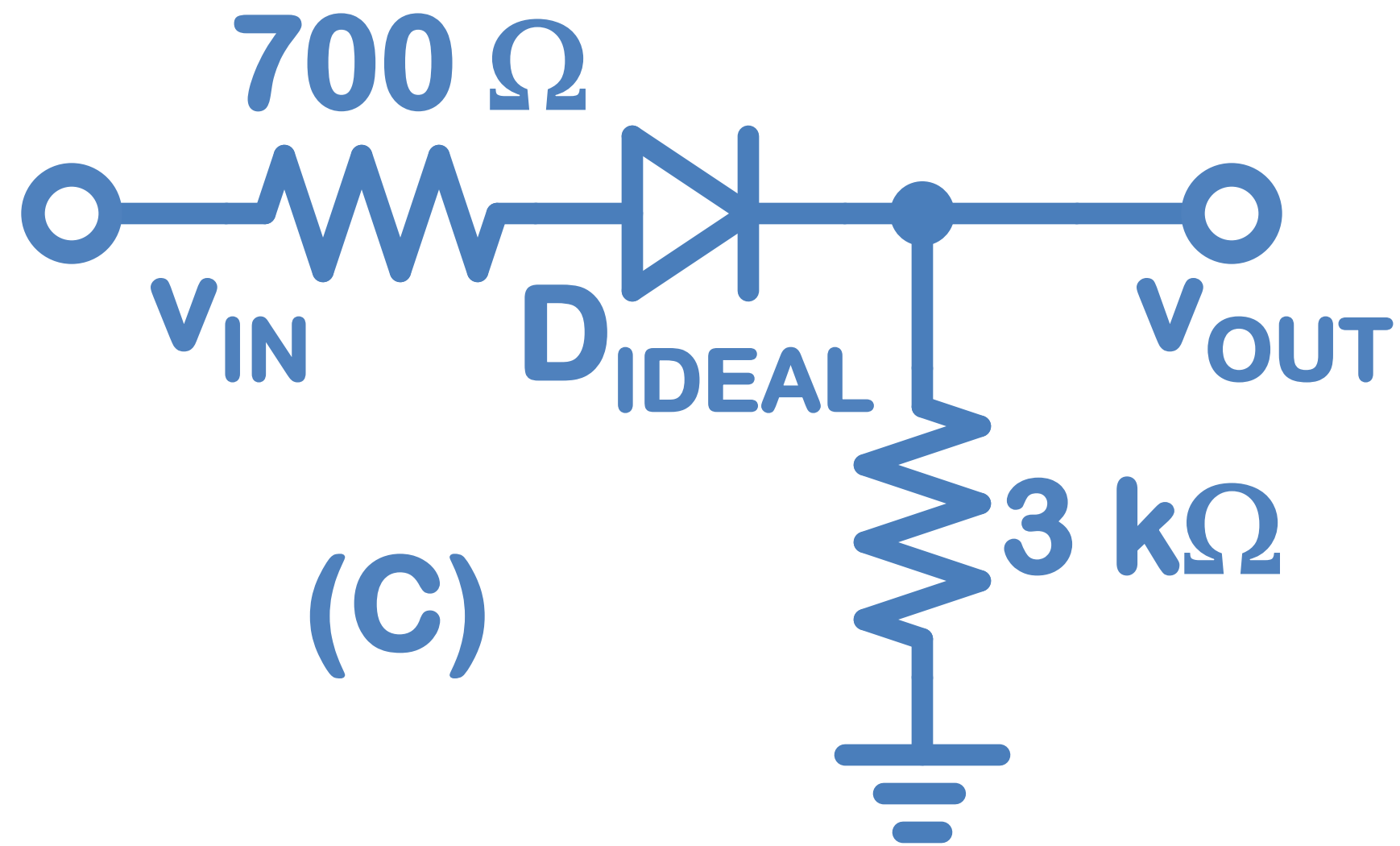Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



1. FB case:

2. short ($v_D=0$)

3. $v_{OUT} = (3k / (700 + 3k)) v_{IN}$

$$v_{OUT} = (30/37) v_{IN}$$

$$i_D = (v_{IN} - 0) / (3700)$$

4. apply $i_D > 0$, therefore

$$v_{IN} > 0$$

5. Next

1. RB case:

2. open ($i_D=0$)

3. $v_{OUT}=0$

$$v_D = v_{IN} - v_{OUT}$$

$$v_D = v_{IN} - 0$$

4. apply $v_D < 0$, therefore

$$v_{IN} < 0$$



5. Done

answer:

$$v_{OUT} = (30/37) v_{IN}, v_{IN} > 0$$

$$v_{OUT} = 0, v_{IN} < 0$$

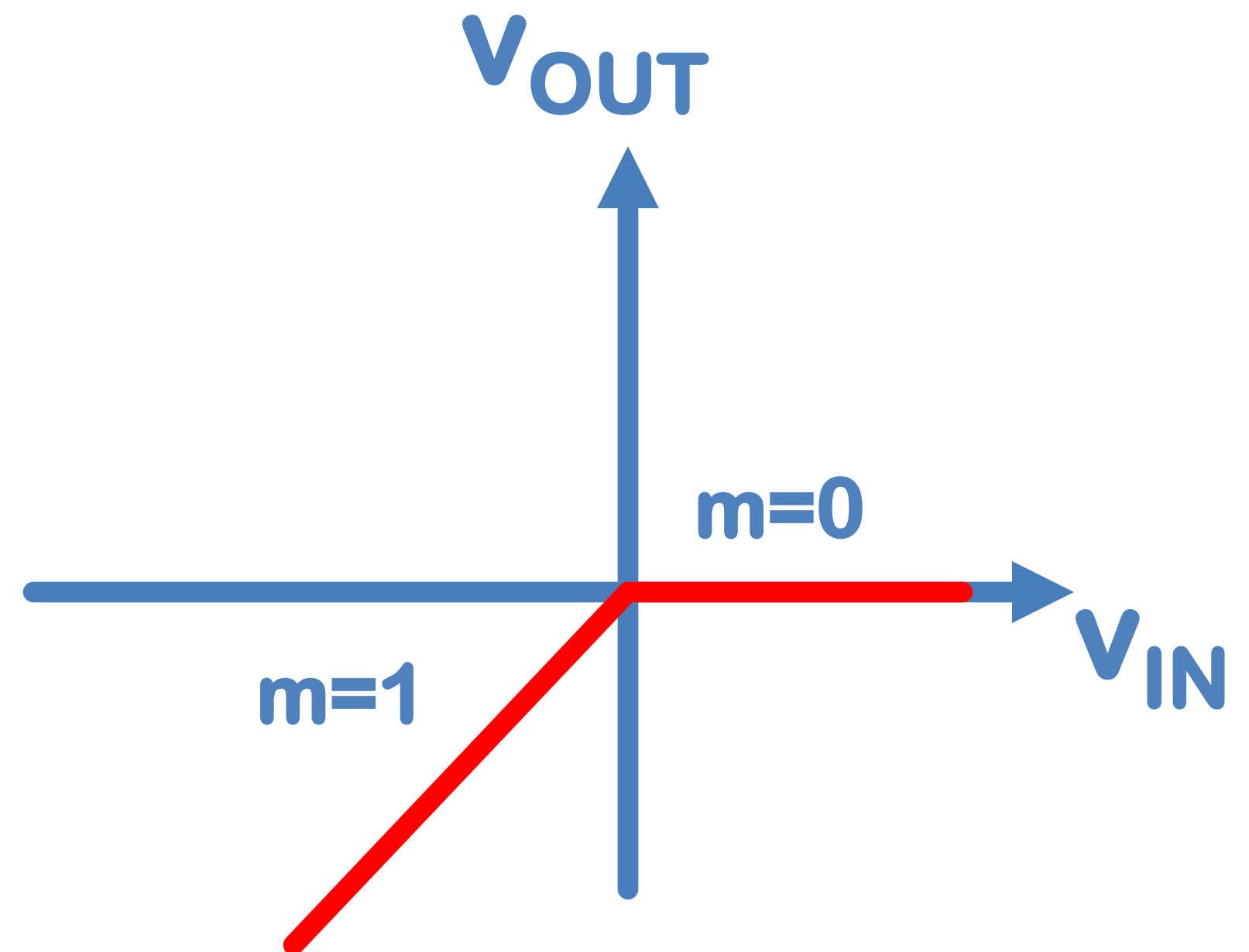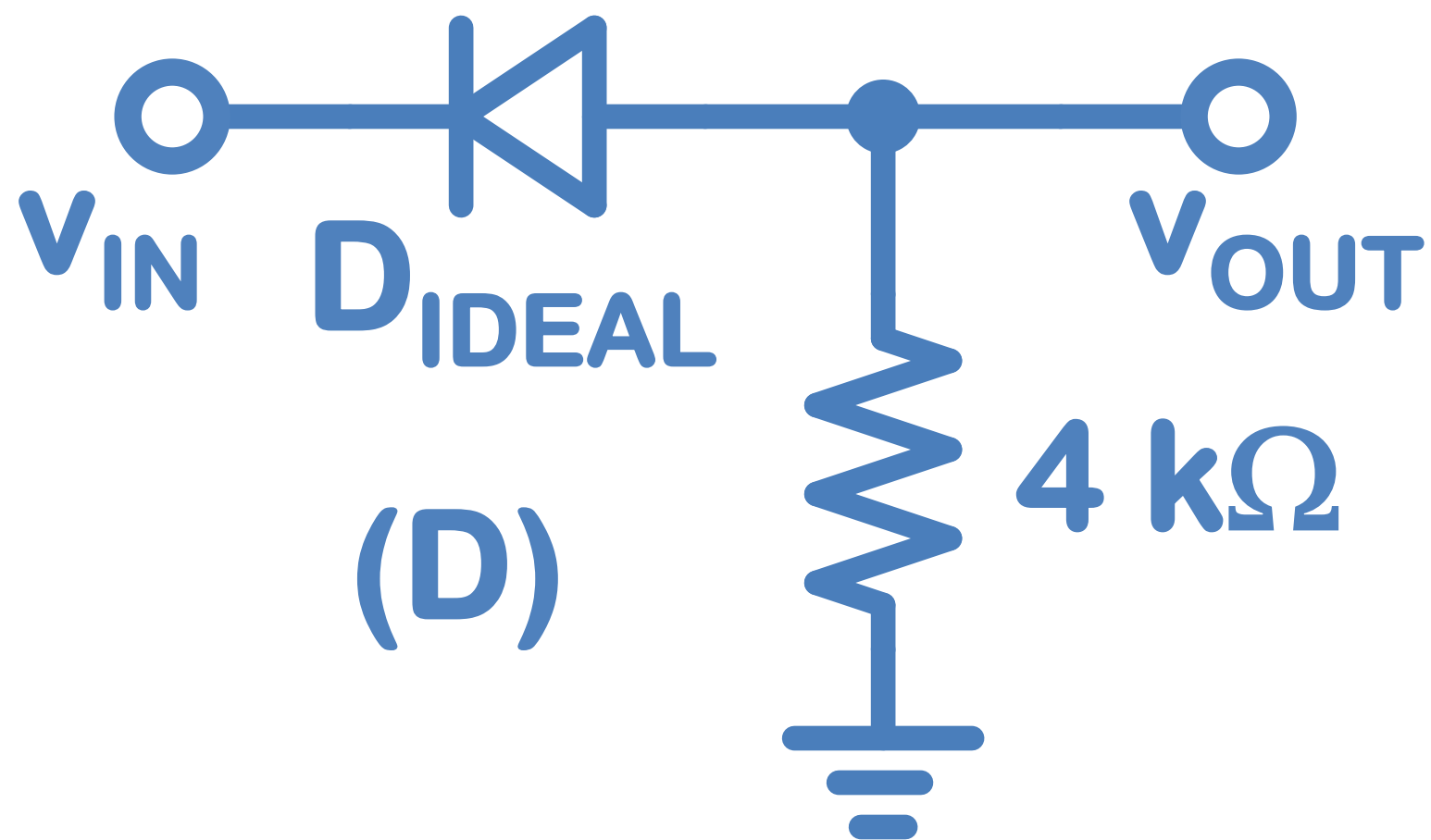Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.





1. FB case:
2. short ($v_D=0$)
3. $v_{OUT}=v_{IN}$
 $i_D = (0-v_{IN})/(4k)$
4. apply $i_D > 0$, therefore
 $v_{IN} < 0$
5. Next

1. RB case:
2. open ($i_D=0$)
3. $v_{OUT}=0$
 $v_D = v_{OUT}-v_{IN}$
 $v_D = -v_{IN}$
4. apply $v_D < 0$, therefore
 $v_{IN} > 0$
5. Done

answer:
 $v_{OUT} = v_{IN}, v_{IN} < 0$
 $v_{OUT} = 0, v_{IN} > 0$

Problem 3.

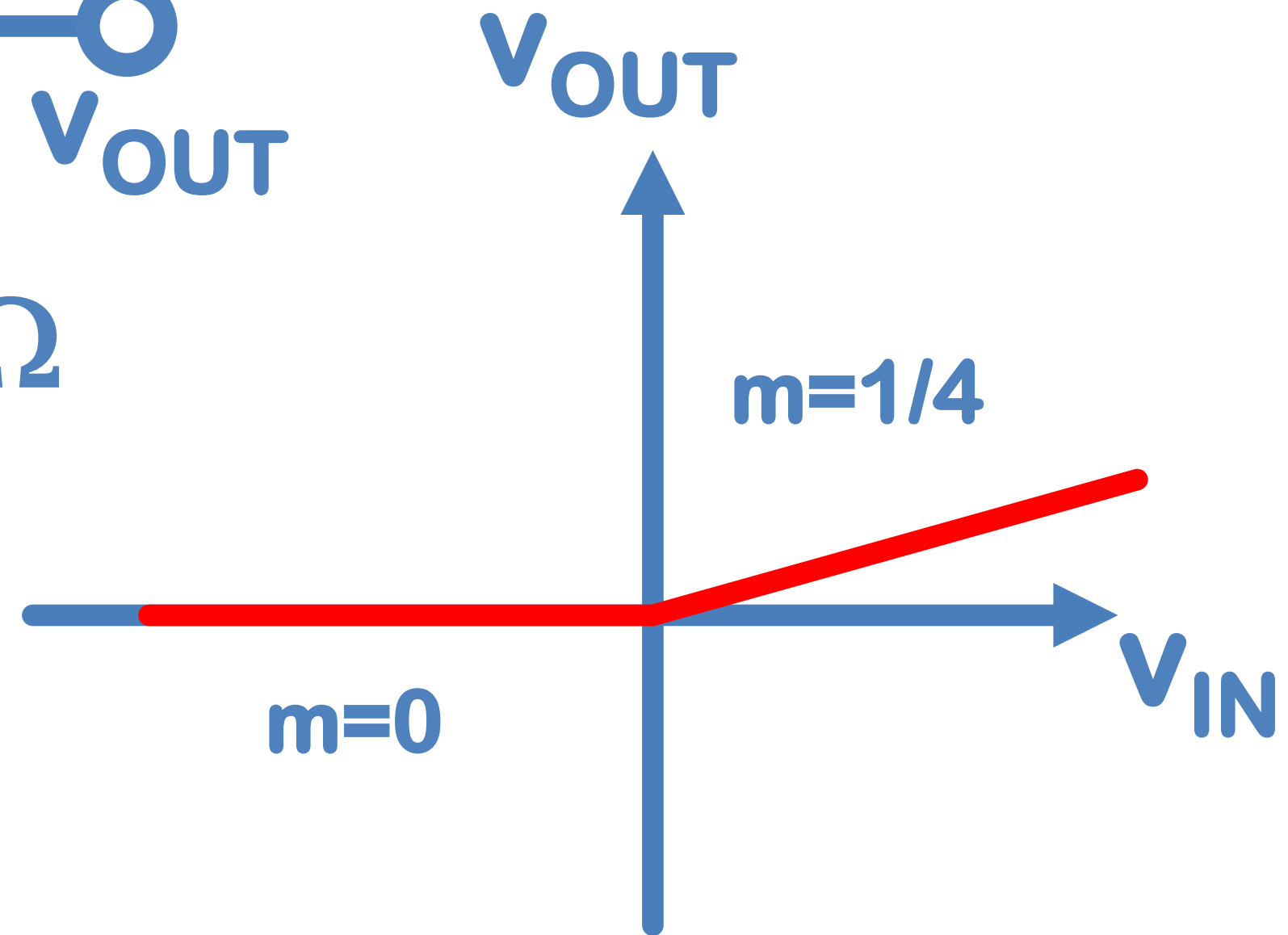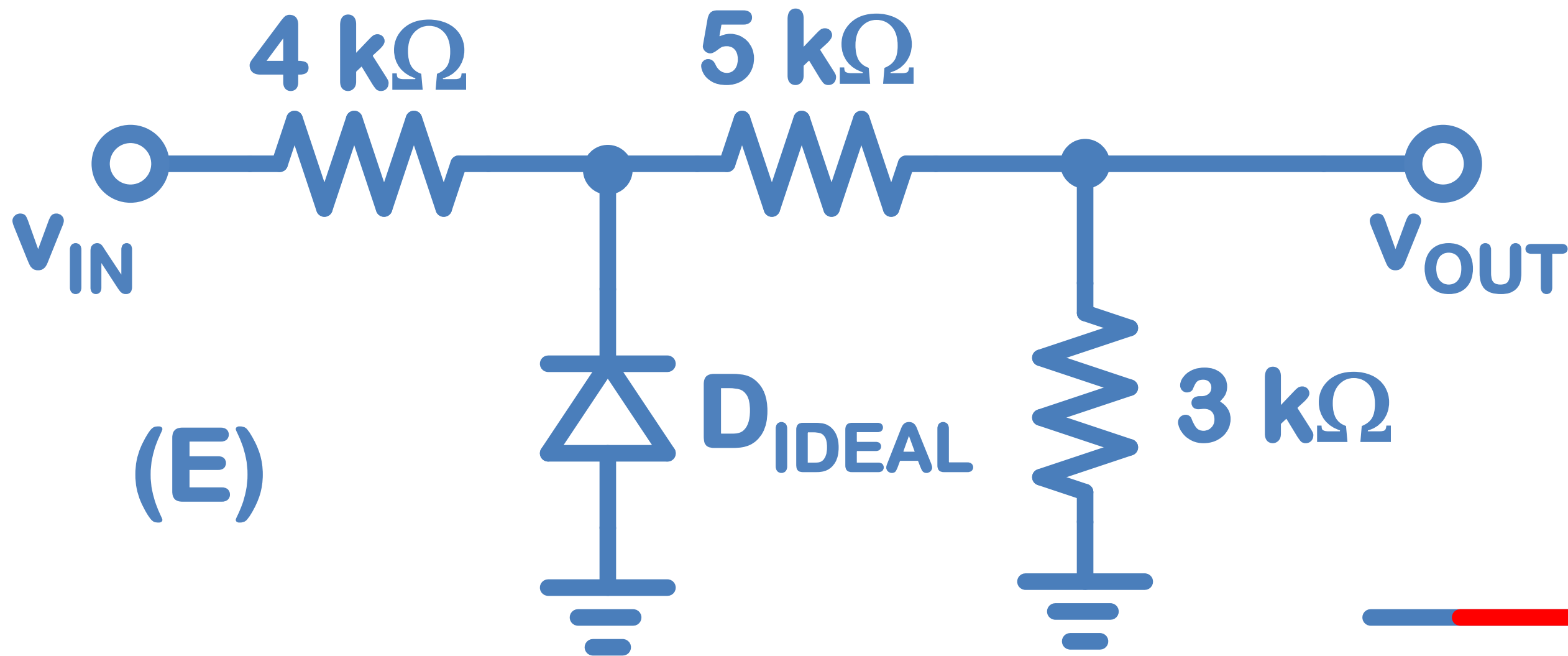a) Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



(E)



1. FB case:
2. short ($v_D=0$)
3. $v_{OUT}=0$
 $i_D = (0-v_{IN})/(4k)$
4. apply $i_D > 0$, therefore $v_{IN} < 0$
5. Next

1. RB case:
2. open ($i_D=0$)
3. $v_{OUT} = (3k/(4k+5k+3k))v_{IN}$
 $v_{OUT} = (1/4)v_{IN}$
 $v_D = (8k/12k)v_{IN}$
 $v_D = 0 - (2/3)v_{IN}$
4. apply $v_D < 0$, therefore $v_{IN} > 0$
5. Done

answer:
 $v_{OUT} = 0, v_{IN} < 0$
 $v_{OUT} = (1/4)v_{IN}, v_{IN} > 0$

Problem 3.

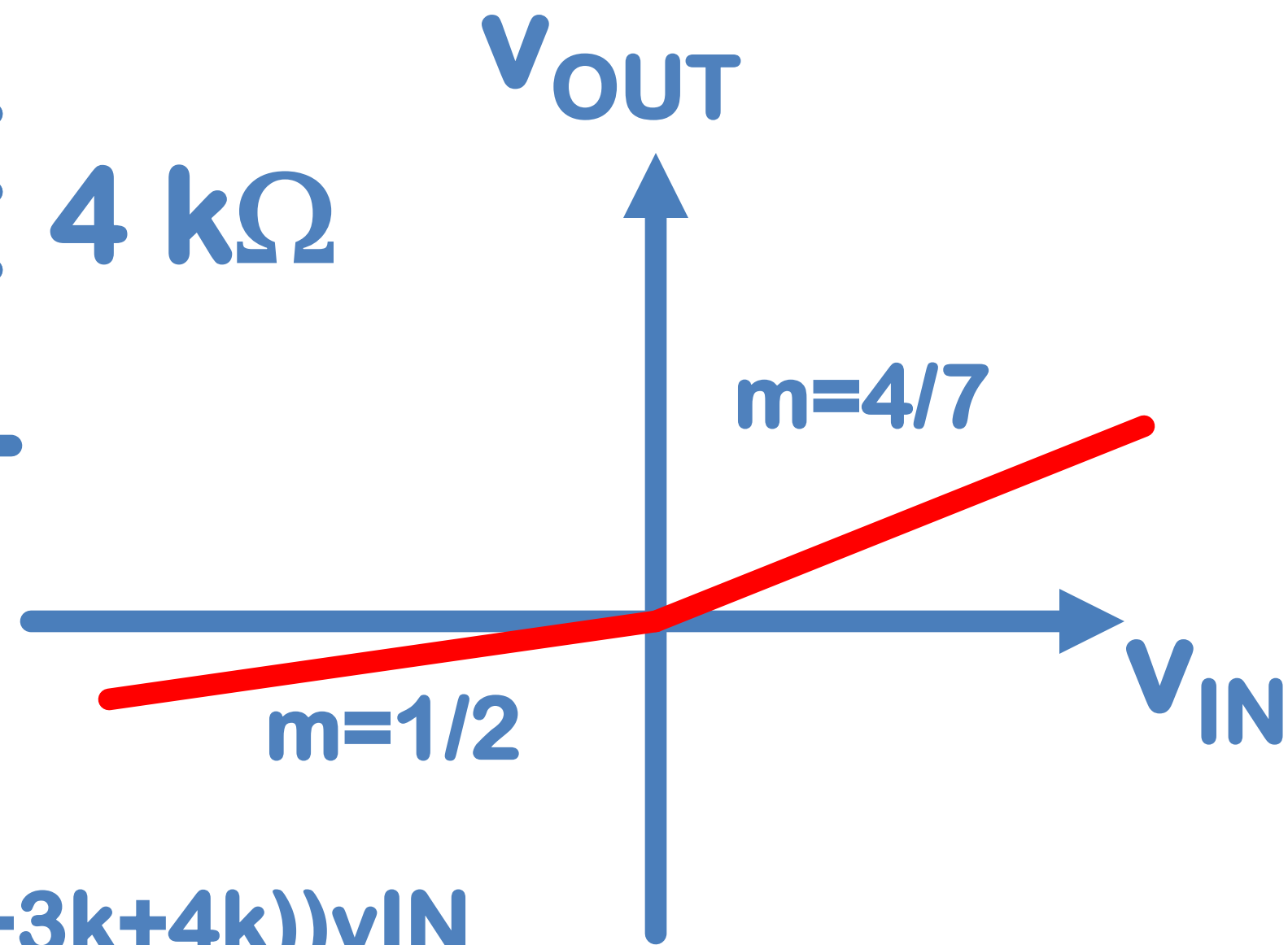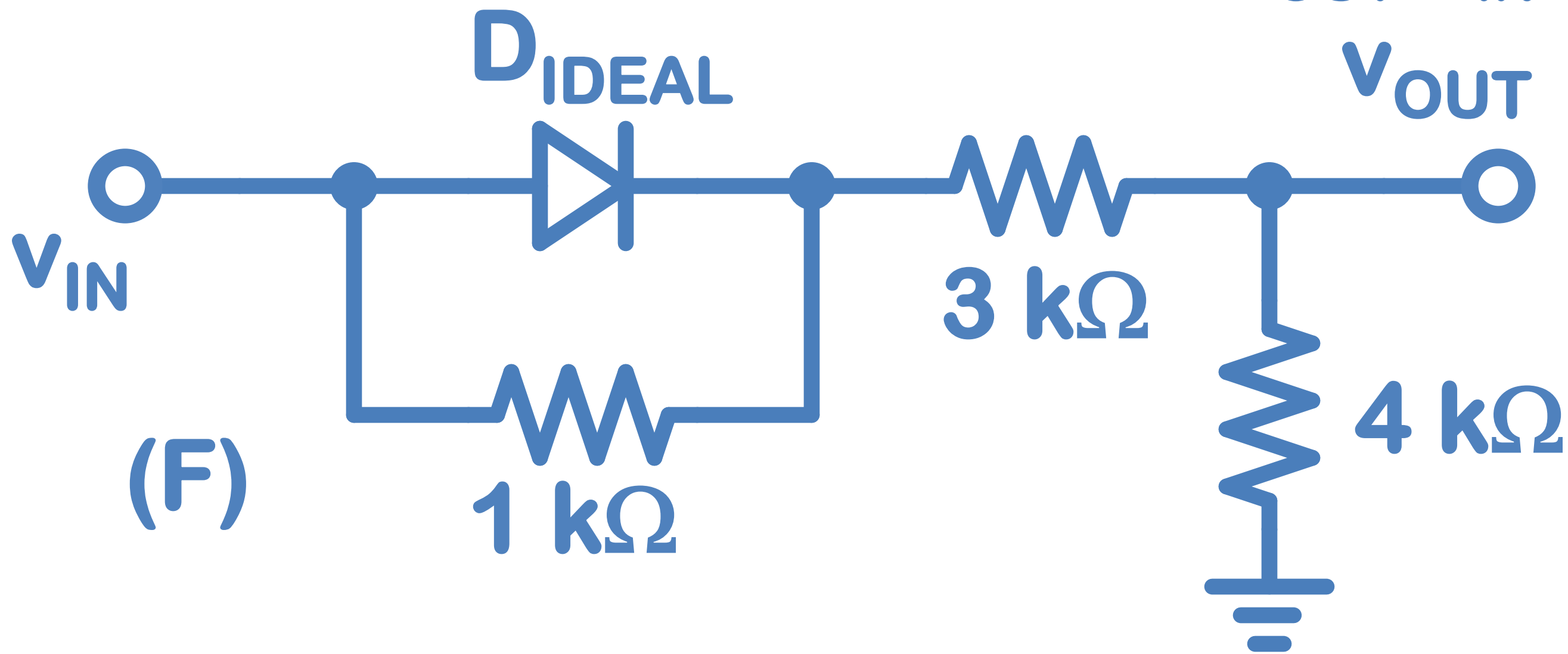a) Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



1. FB case:
2. short ($v_D=0$)
3. $v_{OUT}=(4k/(3k+4k))v_{IN}$
 $v_{OUT} = (4/7)v_{IN}$
 $i_D = (v_{IN})/(7k)$
4. apply $i_D > 0$, therefore
 $v_{IN} > 0$
5. Next

1. RB case:
2. open ($i_D=0$)
3. $v_{OUT}=(4k/(1k+3k+4k))v_{IN}$
 $v_{OUT} = (1/2)v_{IN}$
 $v_D = (7/8)v_{IN}$
4. apply $v_D < 0$, therefore
 $v_{IN} < 0$
5. Done

answer:

$$v_{OUT} = (4/7)v_{IN}, v_{IN} > 0$$


$$v_{OUT} = (1/2)v_{IN}, v_{IN} < 0$$

Problem 4.

a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.

1. don't to FB, FB case

Next

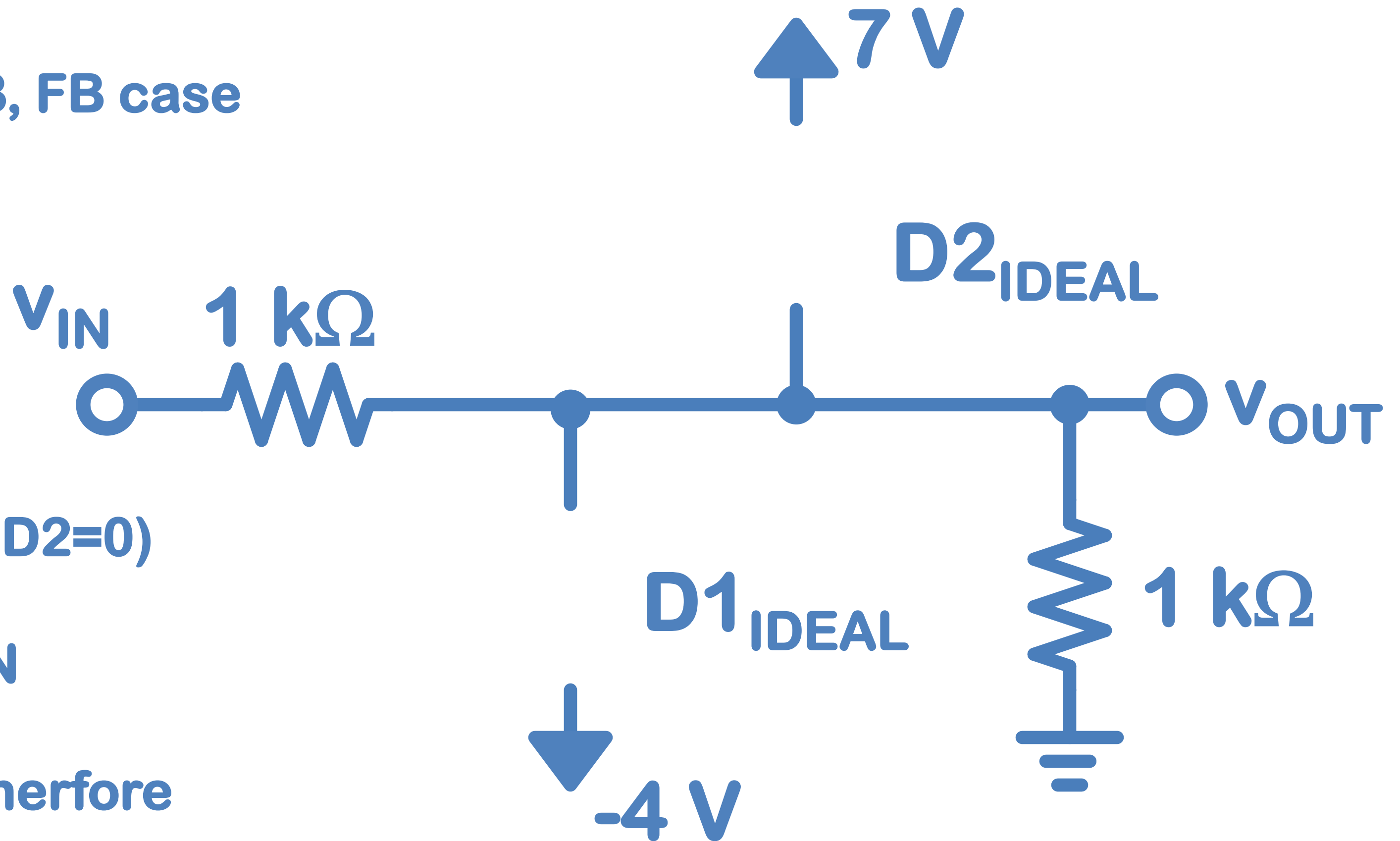

1. RB, RB case:

2. opens ($i_{D1}=0$, $i_{D2}=0$)

3. $v_{OUT}=(1/2)v_{IN}$

$v_{D1} = -4 - (1/2)v_{IN}$

$v_{D2} = (1/2)v_{IN}-7$

4. apply $v_{D1}<0$, therefore

$v_{IN} > -(8)$

apply $v_{D2}<0$, therefore

$v_{IN} < (14)$

Intersection is: $-(8) < v_{IN} < (14)$


5. Next

Problem 4.

a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.

1. don't to FB, FB case

Next

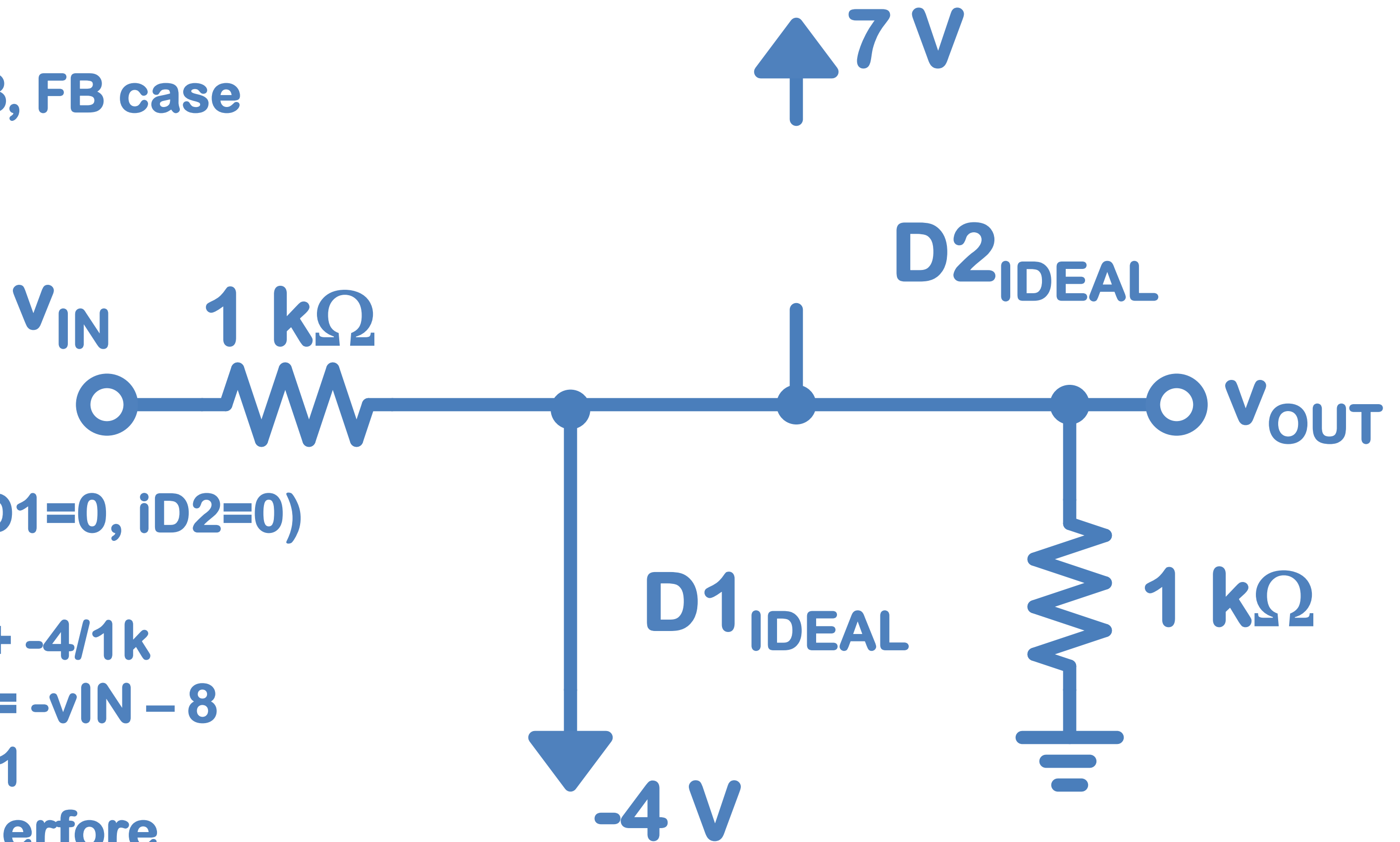

1. FB, RB case:

2. short, open ($v_{D1}=0$, $i_{D2}=0$)

3. $v_{OUT} = -4$

$$i_{D1} = (-4 - v_{IN})/1k + -4/1k$$

$$i_{D1} = -4 - v_{IN} - 4 = -v_{IN} - 8$$

$$v_{D2} = (-4 - 7) = -11$$

4. apply $i_{D1} > 0$, therefore

$$v_{IN} < -(8)$$

apply $v_{D2} < 0$, therefore

always

Intersection is: $v_{IN} < -(8)$


5. Next

Problem 4.

a) Find the equation and plot $v_{OUT}(v_{IN})$ for the circuit.

1. don't to FB, FB case

Next

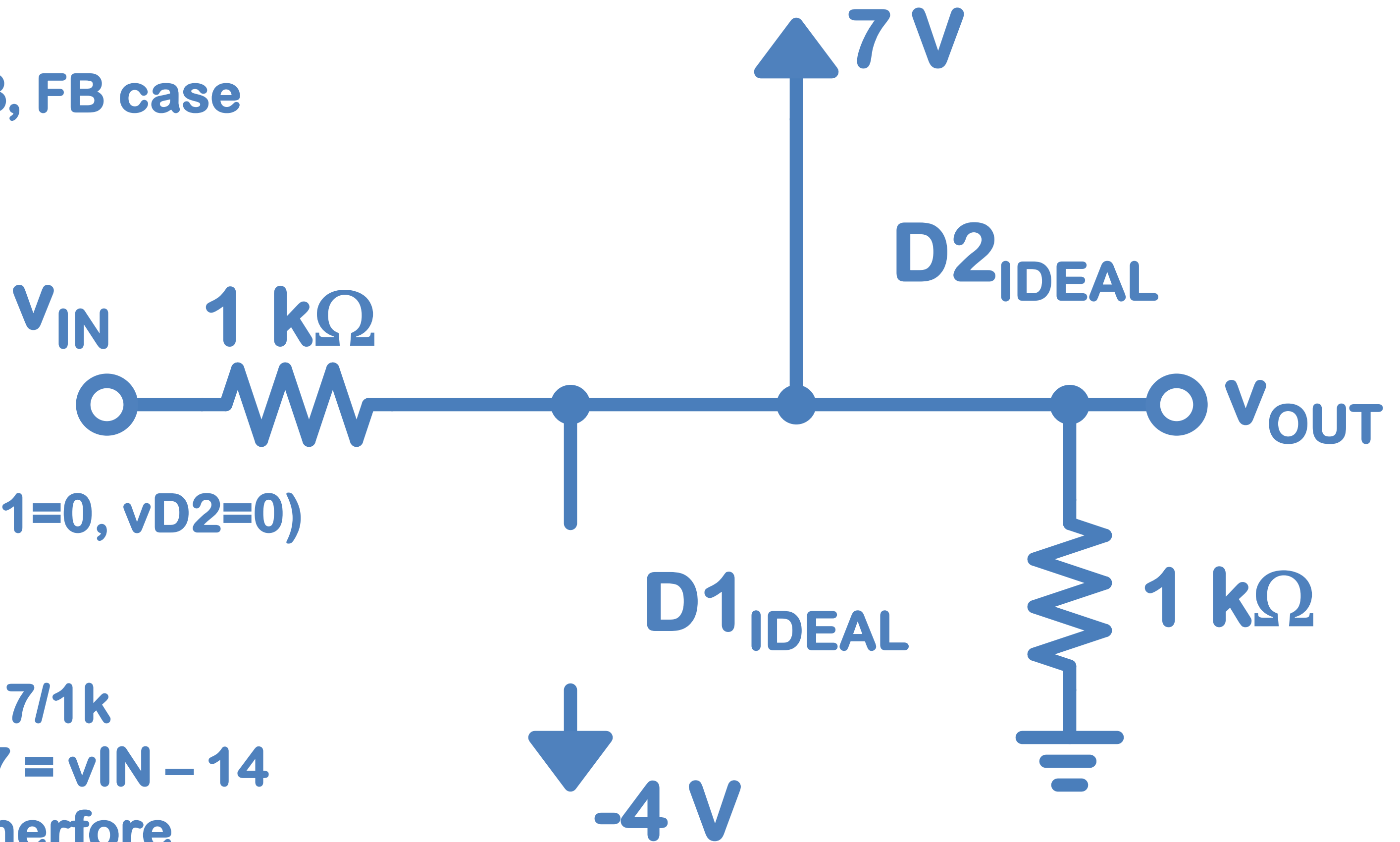

1. RB, FB case:

2. open, short ($i_{D1}=0$, $v_{D2}=0$)

3. $v_{OUT}=7$

$$v_{D1} = -4 - 7 = -11$$

$$i_{D2} = (v_{IN}-7)/1k - 7/1k$$

$$3 \cdot i_{D2} = v_{IN} - 7 - 7 = v_{IN} - 14$$


4. apply $v_{D1} < 0$, therefore
always

apply $i_{D2} > 0$, therefore

$$v_{IN} > 14$$

Intersection is: $v_{IN} > 14$

5. Next

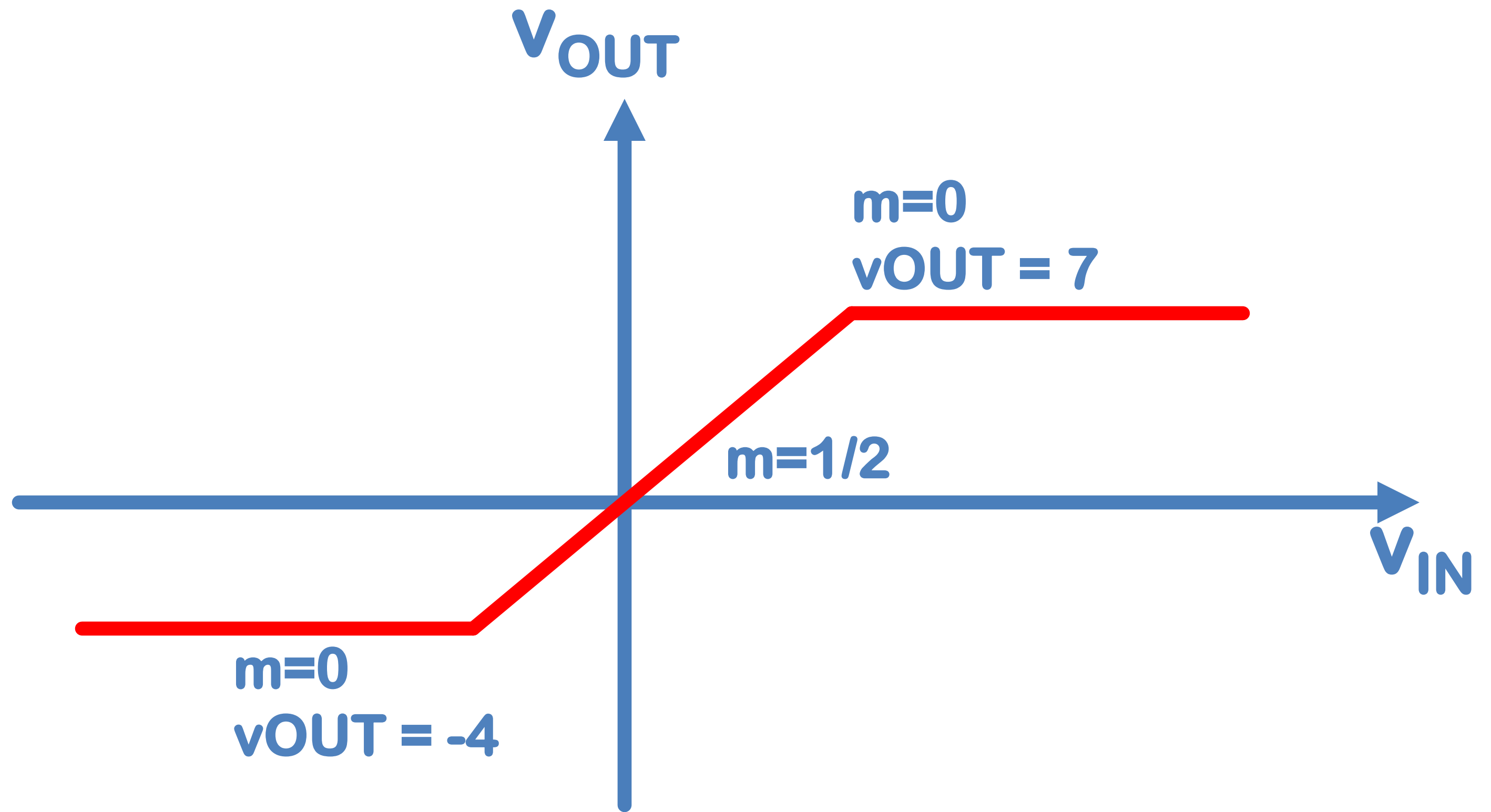

$v_{OUT} = (1/2)v_{IN}$,
 $v_{OUT} = -4$,
 $v_{OUT} = 7$,

$-(8) < v_{IN} < (14)$

$v_{IN} < -(8)$

$v_{IN} > (14)$