

EECS 312 – Electronic Circuits I – Homework 3
Carl Leuschen – Spring 2024

1. Fill in the missing values in the table. Diodes A to F are Junction Diodes. Assume $V_T=25\text{mV}$.

Diode	I_S (A)	n	V_D (V)	I_D (mA)	P_D (mW)
A	3×10^{-15}	1	0.65	.582	.382
B	2×10^{-9}	1.8	0.64	3	1.92
C	3×10^{-12}	1.38	0.7	2	1.4
D	9.36×10^{-11}	1.9	0.55	.01	.0055
E	9.51×10^{-15}	1.2	.769	1.3	1
F	1.2×10^{-13}	1.05	.68	17.65	12

2. A Junction Diode with $n=1.4$ conducts 0.3mA at 0.7V , $I_D(V_D=0.7\text{V})=0.3\text{mA}$.


a. How much does the device conduct (find I_D) at $V_D=0.8\text{V}$? 0.6V ? 0.5V ?

5.22mA, 17.23uA, 0.990uA

b. What voltage (find V_D) would produce a current of $I_D=50\text{uA}$? 5mA ? 50mA ?

0.637V, 0.798V, 0.879V

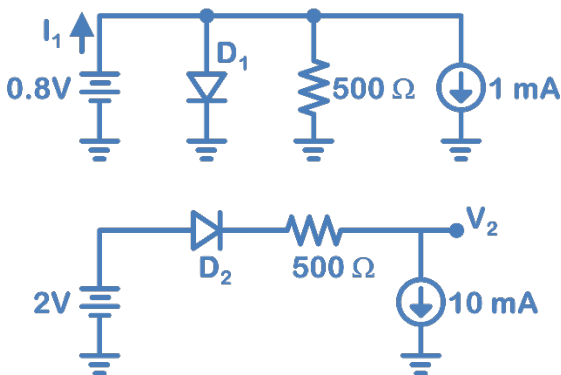3. Find the I_1 and V_2 in the following circuit. Use $I_S=4 \times 10^{-14}$ A and $n=1.4$ for the diodes.



$I_1 = 2.93\text{mA}$, $V_2 = -3.92\text{V}$