


Problem 1.

Find V_D and I_D for each circuit.



(A)

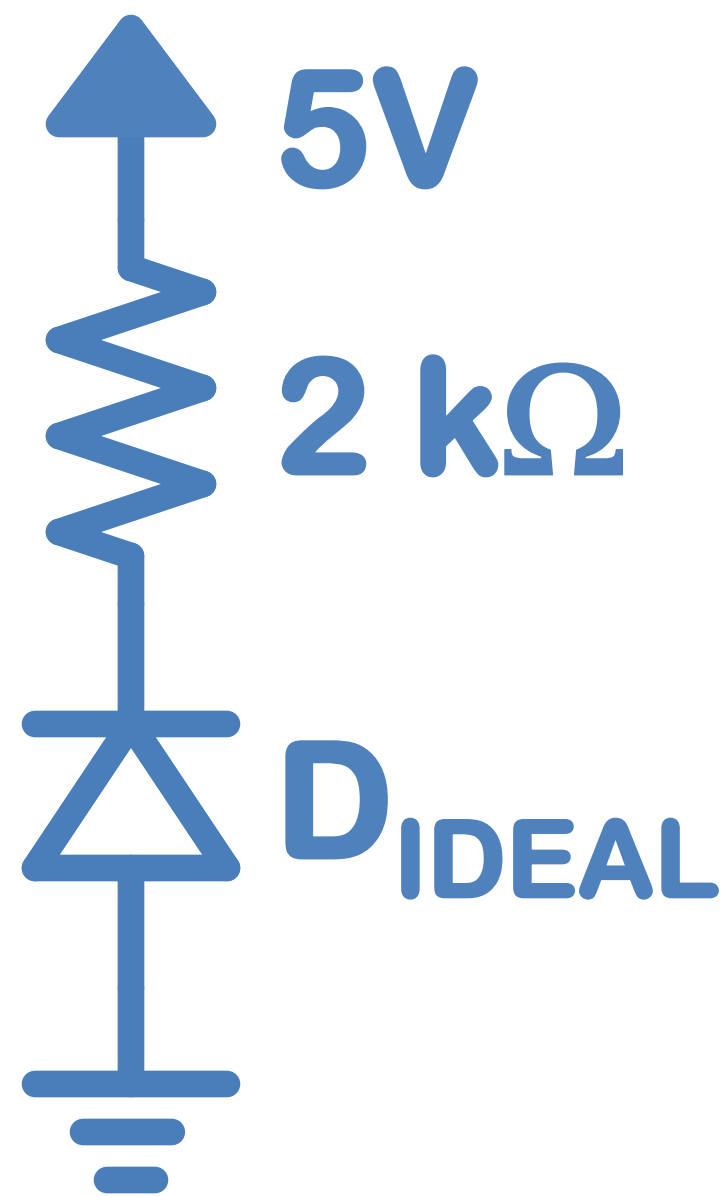1. FB:
2. short ($v_D=0$)
3. $i_D = 3.3/3.8k$
 $i_D = 0.87mA$
4. check $i_D > 0$
YES
5. Done




(B)

1. RB:
2. open ($i_D=0$)
3. $v_D = 0-5 = -5V$
4. check $v_D < 0.7$
YES
5. Done



(C)

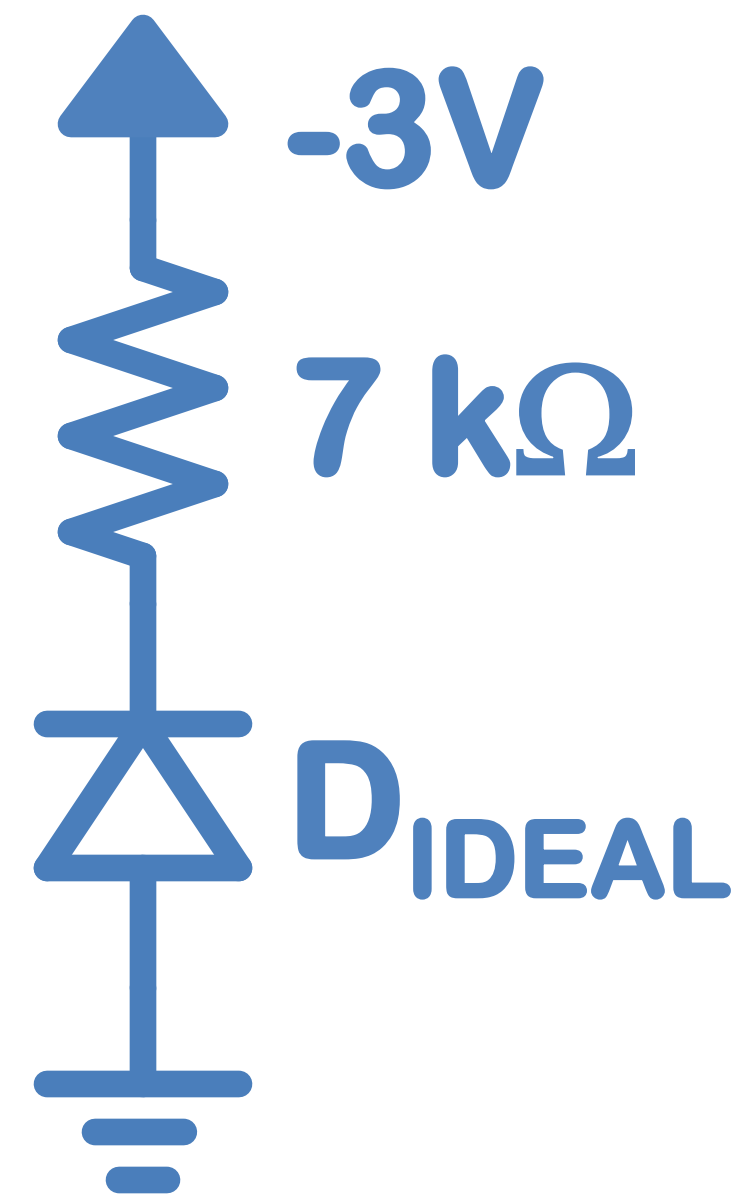1. RB:
2. open ($i_D=0$)
3. $v_D = -1-0 = -1V$
4. check $v_D < 0.7$
YES
5. Done



(D)

1. FB:
2. CVD ($v_D=0.7$)
3. $i_D = 2.3/7k$
 $i_D = 0.33mA$
4. check $i_D > 0$
YES
5. Done

Problem 1.

Find V_D and I_D for each circuit.



(E)

1. FB:
2. CVD ($v_D=0.7$)
3. $i_D = 7.3/12k$
 $i_D = 0.61mA$
4. check $i_D > 0$
YES
5. Done




(F)

1. FB:
2. CVD ($v_D=0.7$)
3. $i_D = 3.3/2.3k$
 $i_D = 1.43mA$
4. check $i_D > 0$
YES
5. Done



(G)

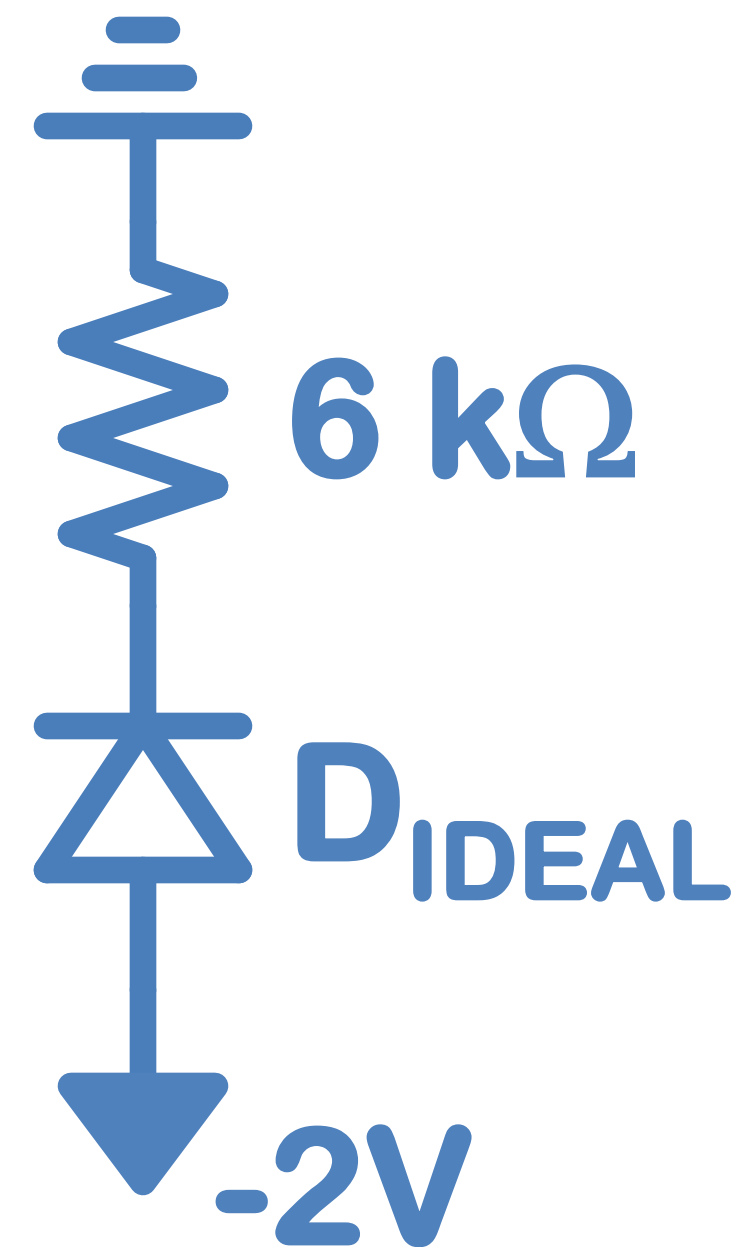
1. FB:
2. CVD ($v_D=0.7$)
3. $i_D = 4.3/11k$
 $i_D = 0.39mA$
4. check $i_D > 0$
YES
5. Done



(H)

1. RB:
2. open ($i_D=0$)
3. $v_D = -2-0 = -2V$
4. check $v_D < 0.7$
YES
5. Done

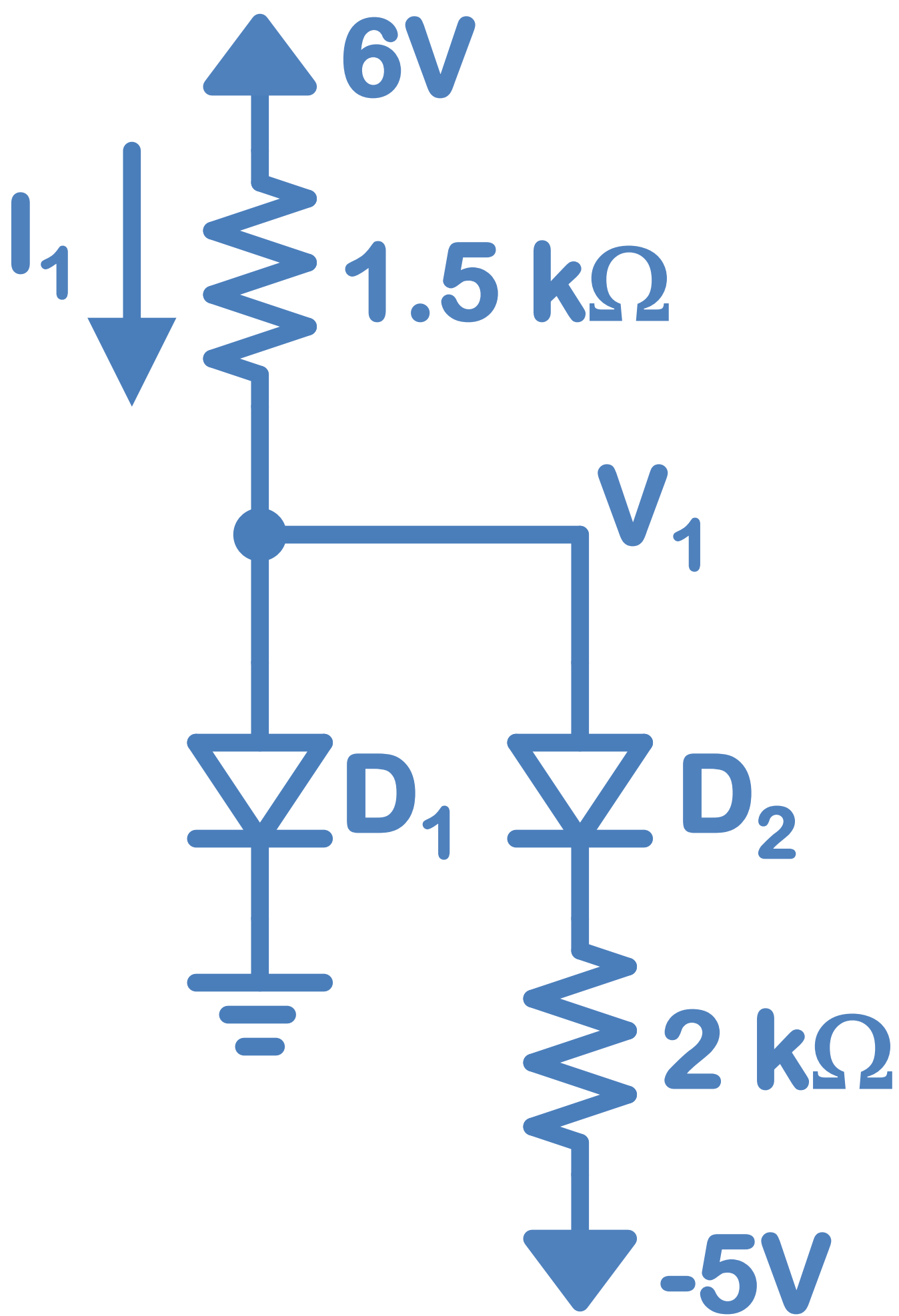Problem 2. Find $V_{1,2,3}$ and $I_{1,2,3}$ in the circuits below. All diodes are ideal.



(A)

1. FB, FB
2. CVD ($v_{D1}=0.7, v_{D2}=0.7$)
3. Find I_1, V_1, i_{D1}, i_{D2}

$$V_1 = 0.7$$

$$I_1 = 5.3/1.5k = 3.53mA$$


$$i_{D2} = 0 - -5/2k = 2.5mA$$

$$i_{D1} = 3.53 - 2.5 = 1.03mA$$

4. check
 $i_{D1} > 0$ Yes
 $i_{D2} > 0$ Yes

5. Done

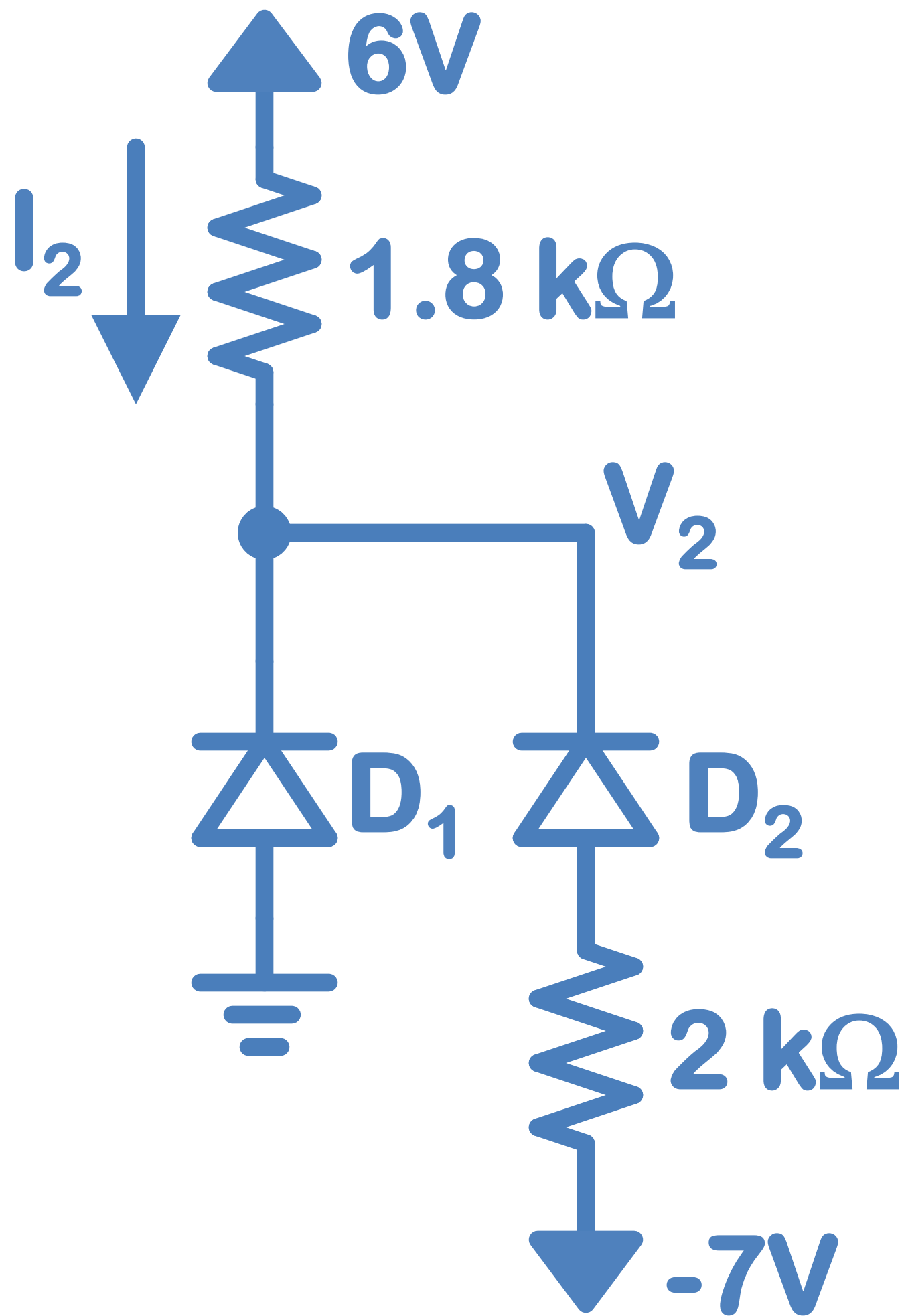Problem 2. Find $V_{1,2,3}$ and $I_{1,2,3}$ in the circuits below. All diodes are ideal.



(B)

1. RB, RB
2. opens ($i_{D1}=0, i_{D2}=0$)
3. Find I_2, V_2, v_{D1}, v_{D2}

$$V_2 = 6$$

$$I_2 = 0$$


$$v_{D1} = 0 - 6 = -6V$$

$$v_{D2} = -7 - 6 = -13V$$

4. check
 $v_{D1} < 0.7$ Yes
 $v_{D2} < 0.7$ Yes

5. Done

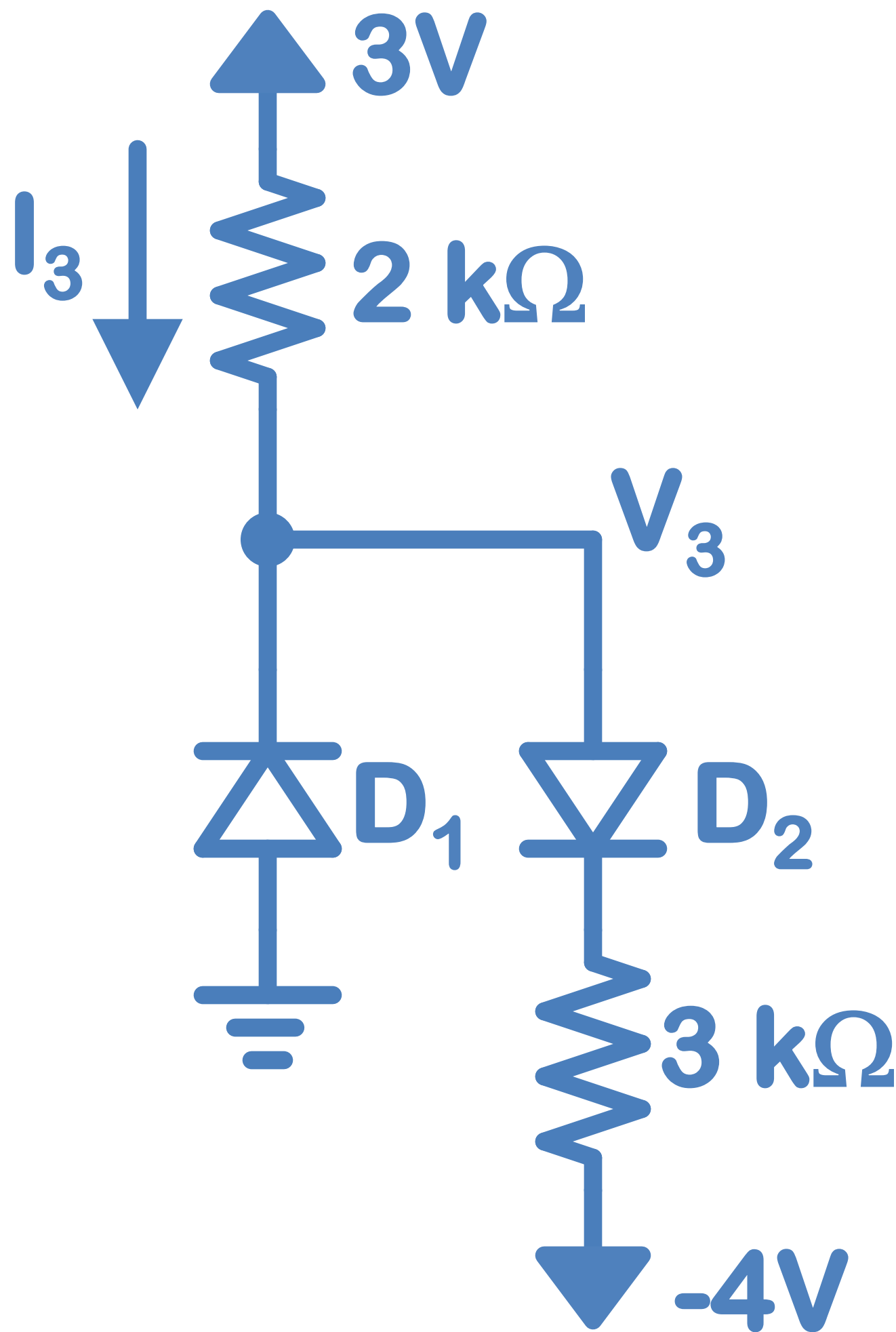Problem 2. Find $V_{1,2,3}$ and $I_{1,2,3}$ in the circuits below. All diodes are ideal.



(C)

1. RB, FB
2. open, CVD ($i_{D1}=0$, $v_{D2}=0.7$)
3. Find I_3 , V_3 , i_{D1} , i_{D2}

$$I_3 = (3 - -4 - 0.7) / (2k + 3k) = 6.3 / 5k = 1.26mA$$

$$V_3 = 3 - 2k * 1.26m = 0.48V$$



$$v_{D1} = 0 - 0.48 = -0.48V$$

$$i_{D2} = I_3 = 1.26mA$$

4. check
 $v_{D1} < 0.7$ Yes
 $i_{D2} > 0$ Yes

5. Done

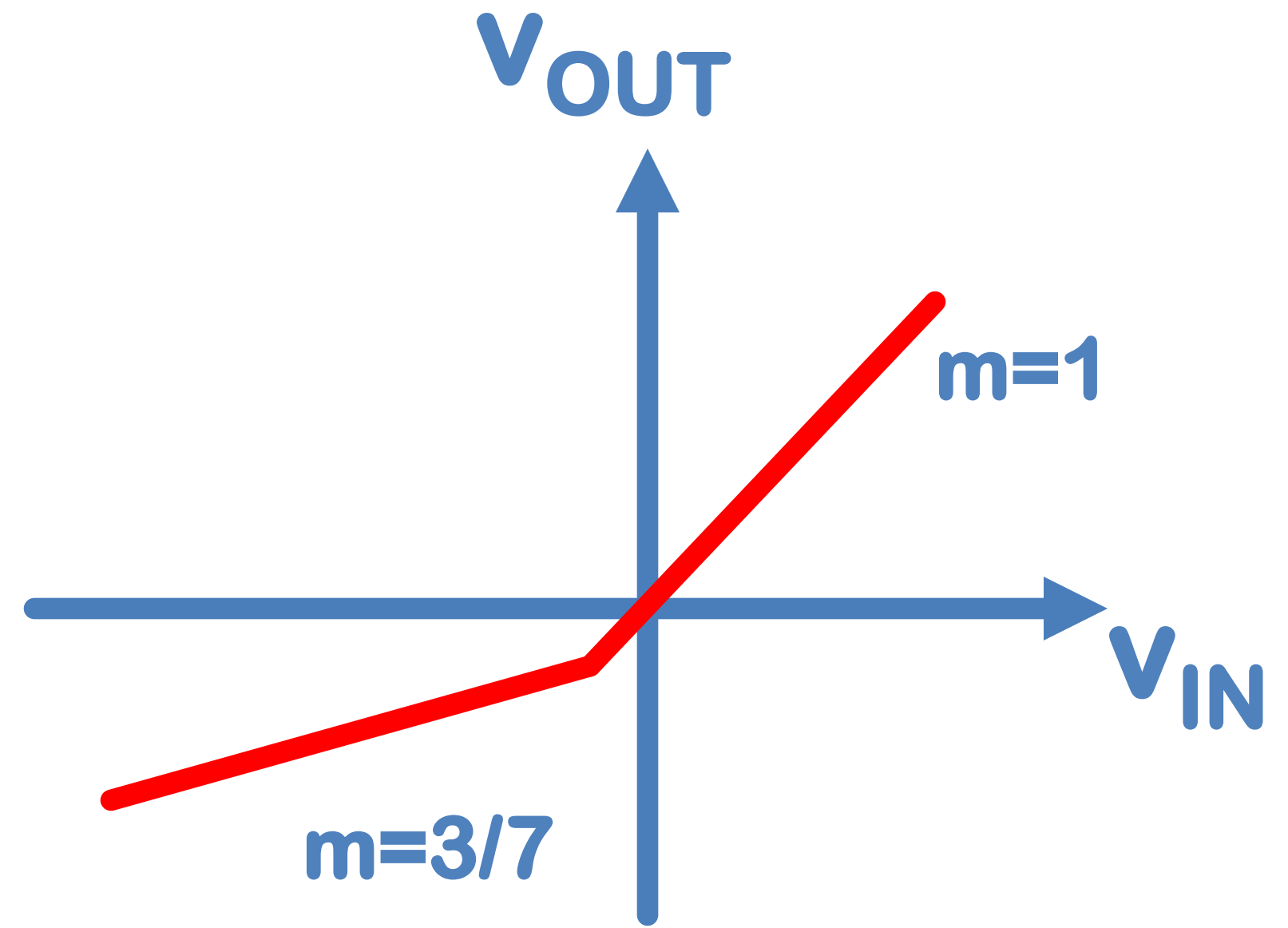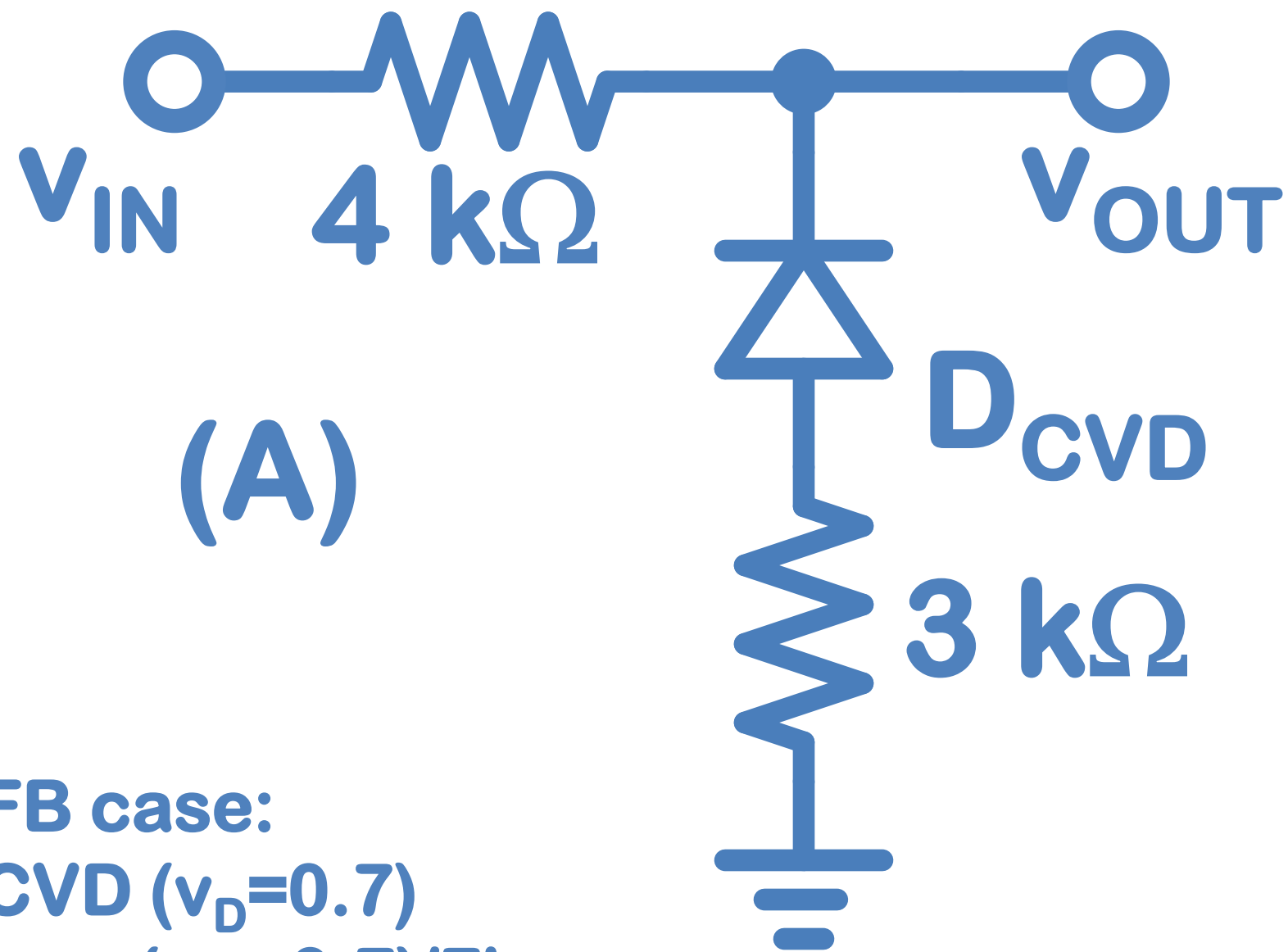Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.





1. FB case:
2. CVD ($v_D=0.7$)
3. $I_D = -(v_{IN}+0.7)/7k$
 $v_{OUT} = -0.7 - 3kI_D$
 $v_{OUT} = -0.7 + (3/7)(v_{IN}+0.7)$
 $v_{OUT} = (3/7)v_{IN} - (7/7)0.7 + (3/7)0.7$
 $v_{OUT} = (3/7)v_{IN} - .4$
4. apply $i_D > 0$, therefore
 $-(v_{IN}+0.7)/7k > 0$
 $v_{IN} < -0.7$
5. Next

1. RB case:
2. open ($i_D=0$)
3. $v_{OUT} = v_{IN}$
 $v_D = (0 - v_{IN})$
4. apply $v_D < 0.7$, therefore
 $-v_{IN} < 0.7$
 $v_{IN} > -0.7$
5. Done

answer:
 $v_{OUT} = (3/7)v_{IN} - 0.4, v_{IN} < -0.7$
 $v_{OUT} = v_{IN}, v_{IN} > -0.7$

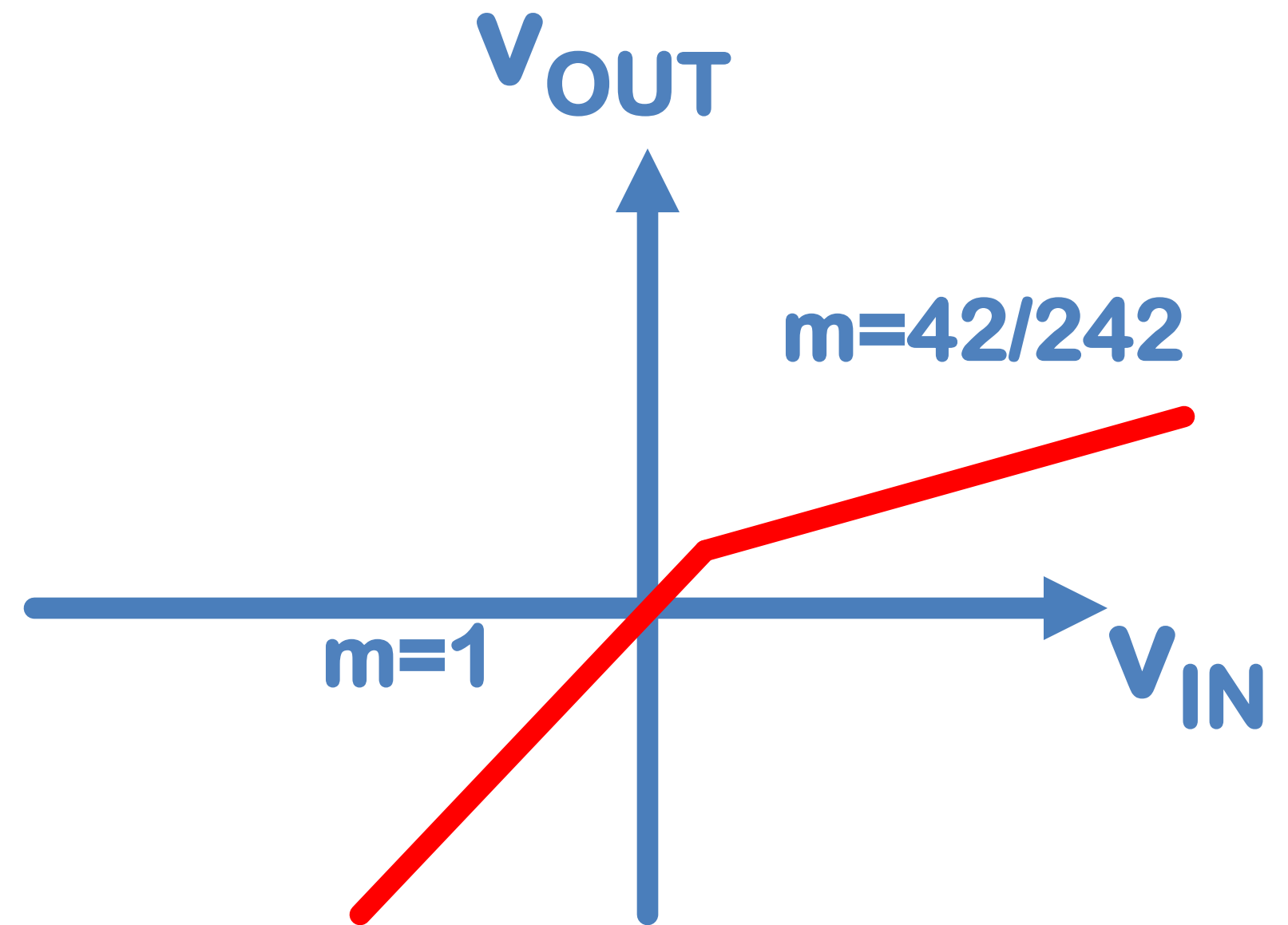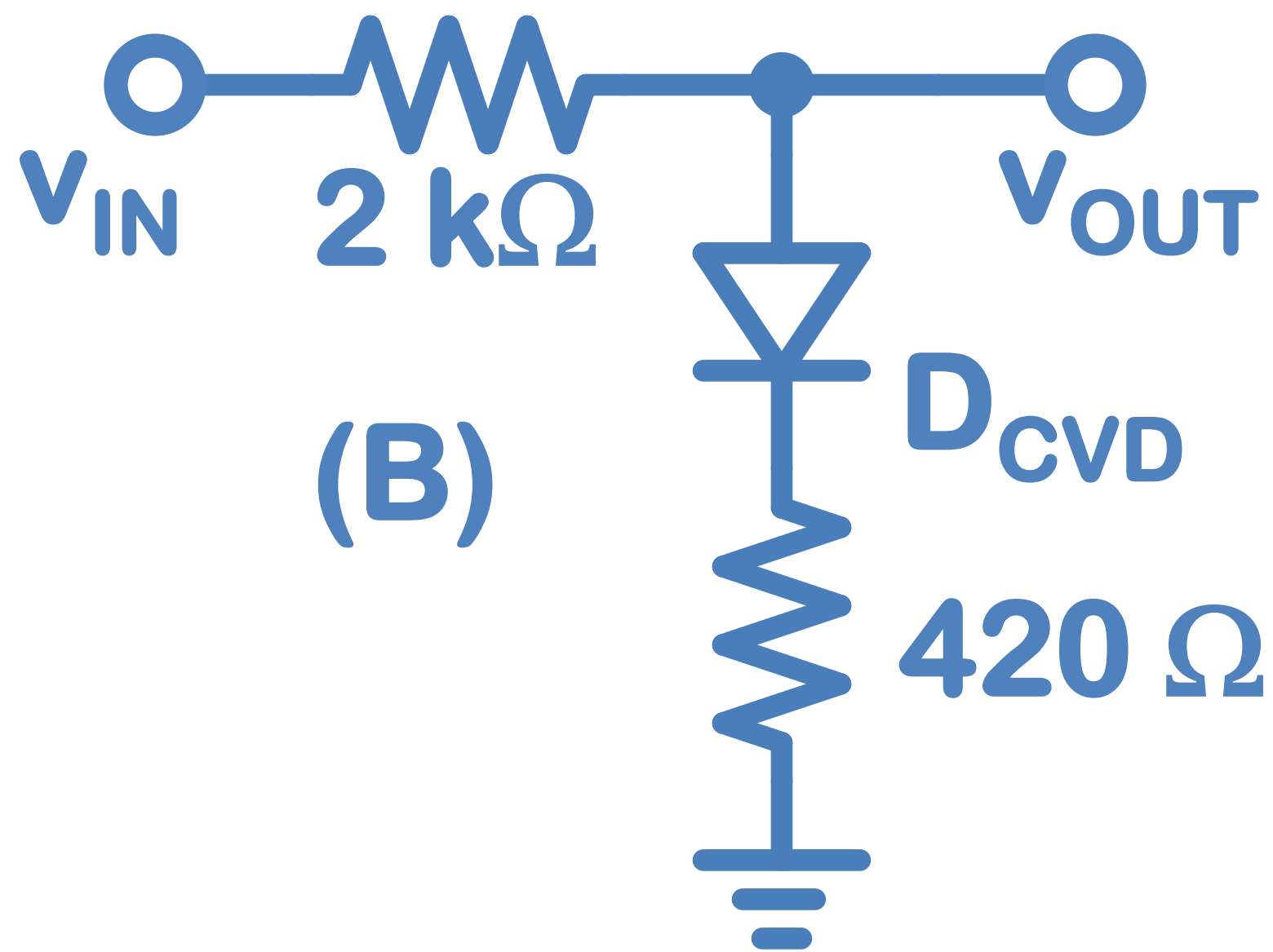Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



1. FB case:

2. CVD ($v_D=0.7$)

3. $i_D = (v_{IN}-0.7)/(2420)$

$v_{OUT}=0.7+(420/(420+2k))(v_{IN}-0.7)$

$v_{OUT} = (42/242)(v_{IN}-0.7) + 0.7$

4. apply $i_D > 0$, therefore

$v_{IN} > 0.7$

5. Next

1. RB case:

2. open ($i_D=0$)

3. $v_{OUT}=v_{IN}$

$v_D = (v_{IN}-0)$

4. apply $v_D < 0.7$, therefore

$v_{IN} < 0.7$



5. Done

answer:

$v_{OUT} = (42/242)(v_{IN}-0.7)+0.7, v_{IN} > 0.7$

$v_{OUT} = v_{IN}, v_{IN} < 0.7$

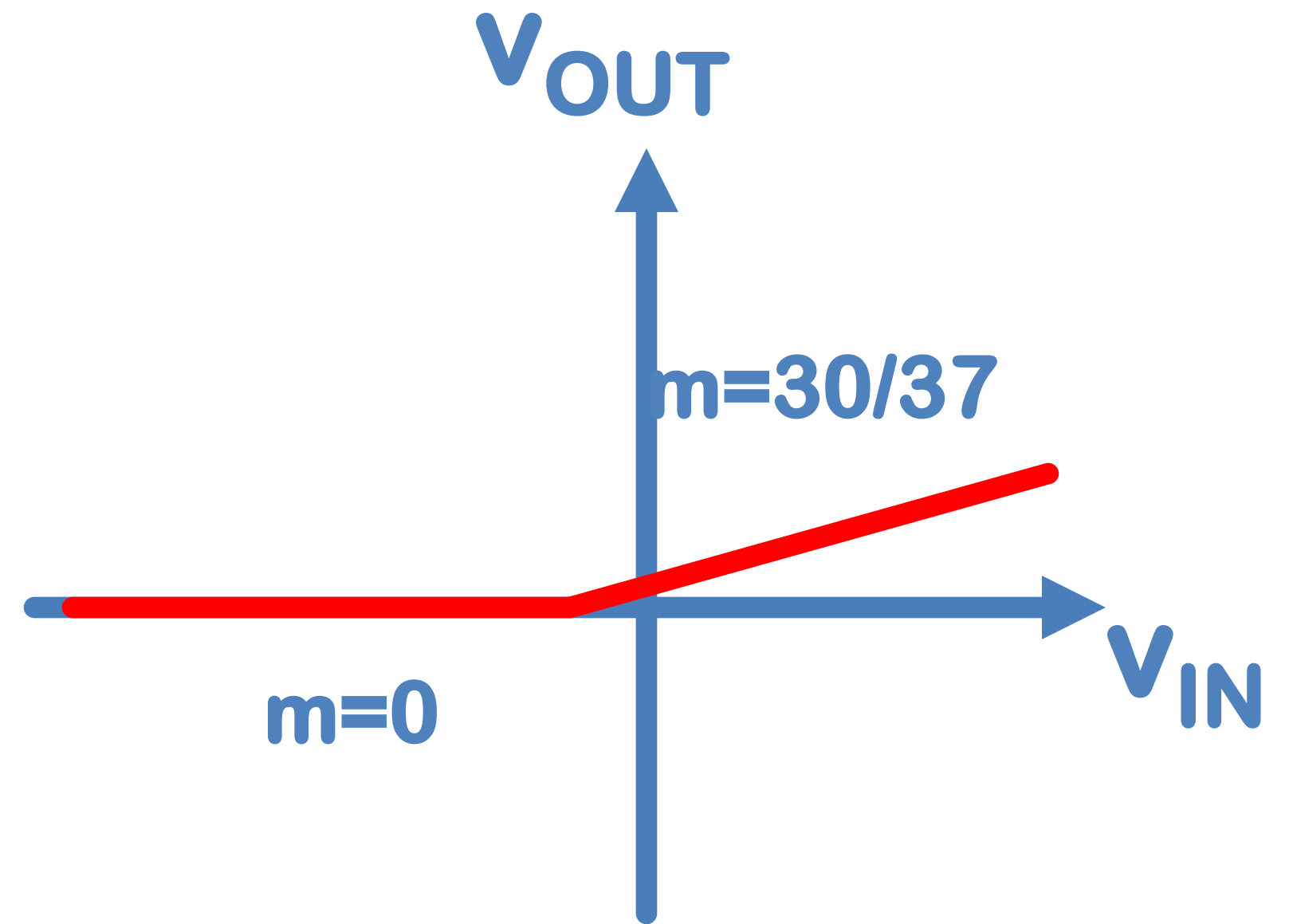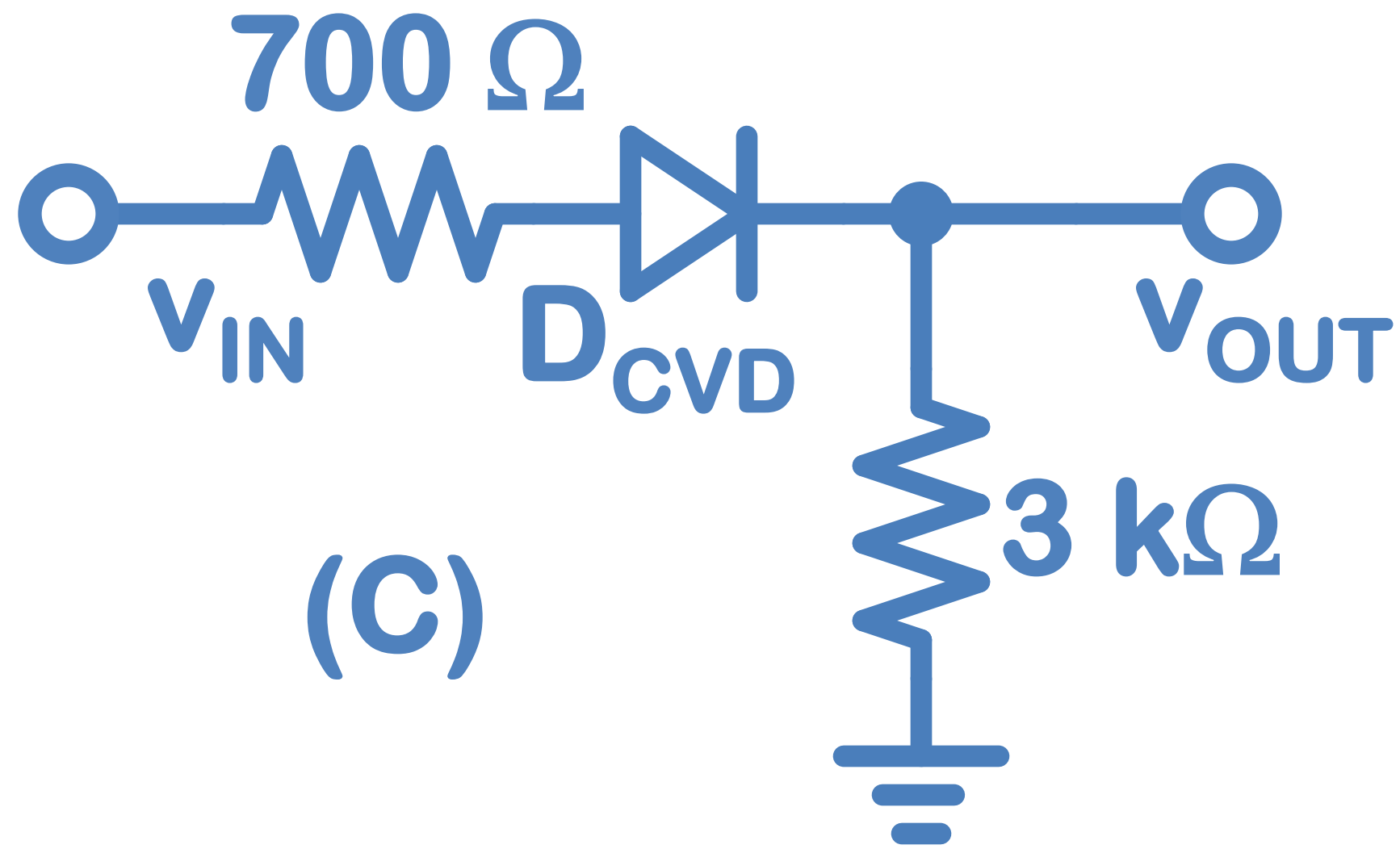Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



1. FB case:
2. CVD ($v_D=0.7$)
3. $i_D = (v_{IN}-0.7)/(3700)$
 $v_{OUT}=3k*i_D=(30/37)(v_{IN}-0.7)$
4. apply $i_D>0$, therefore
 $v_{IN} > 0.7$
5. Next



1. RB case:
2. open ($i_D=0$)
3. $v_{OUT}=0$
 $v_D = v_{IN}-v_{OUT}$
 $v_D = v_{IN}-0$
4. apply $v_D<0.7$, therefore
 $v_{IN} < 0.7$
5. Done

answer:

$$v_{OUT} = (30/37)(v_{IN}-0.7), v_{IN}>0.7$$

$$v_{OUT} = 0, v_{IN}<0.7$$

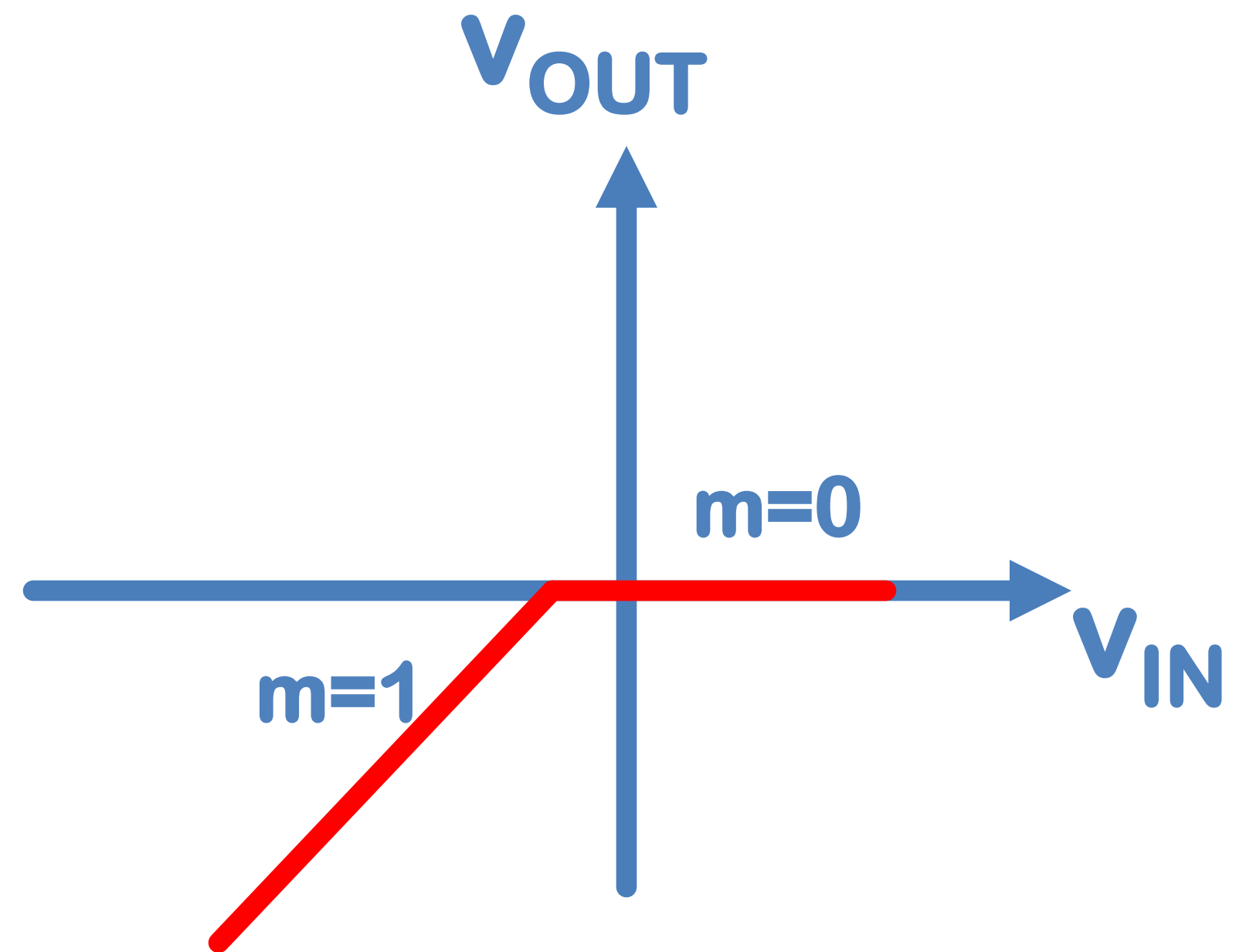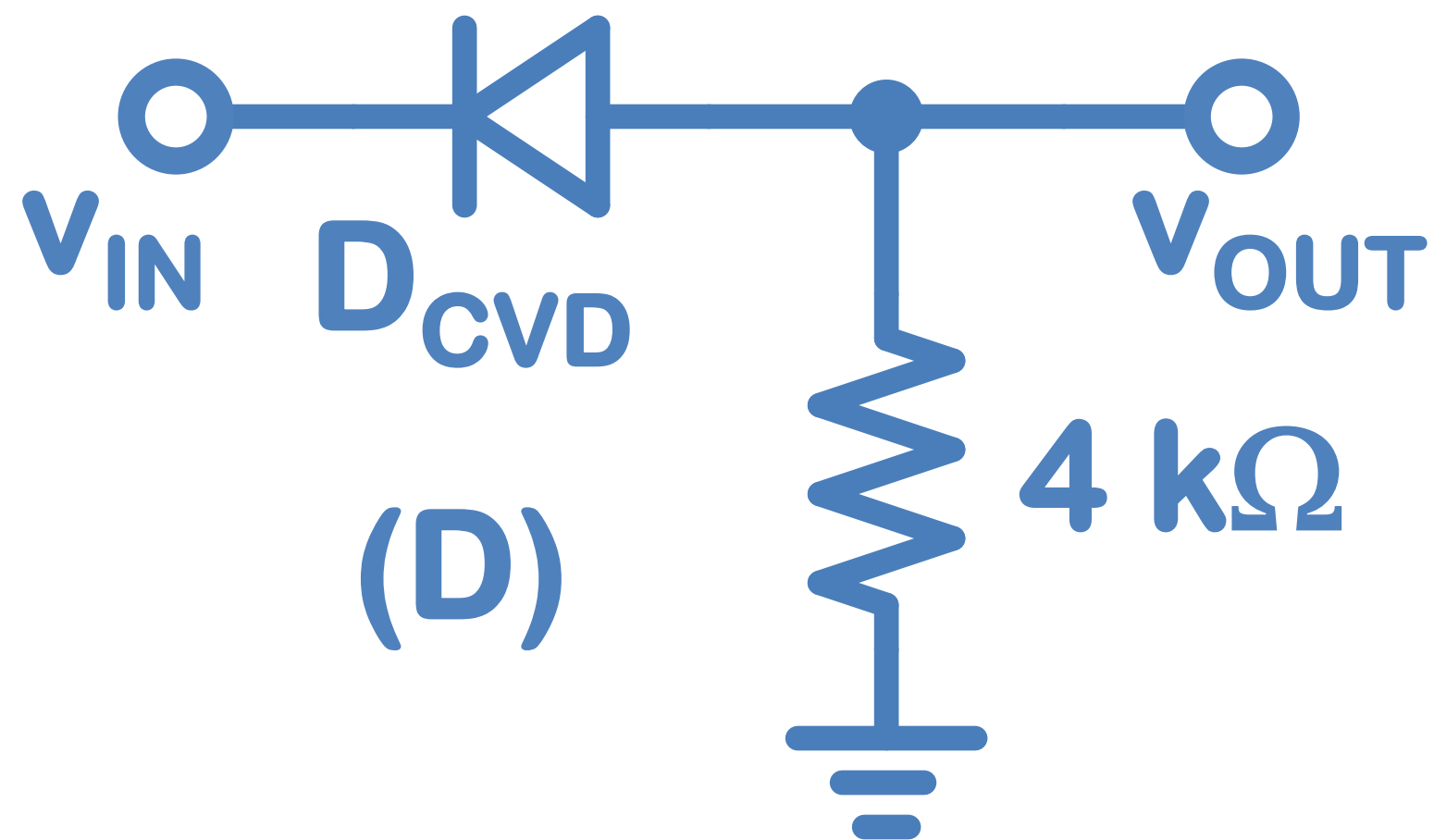Problem 3. Find the equations and plot $v_{OUT}(v_{IN})$ for each circuit.



answer:

$$v_{OUT} = v_{IN} + 0.7, v_{IN} < -0.7$$


$$v_{OUT} = 0, v_{IN} > -0.7$$

1. FB case:
2. CVD ($v_D = 0.7$)
3. $v_{OUT} = v_{IN} + 0.7$
 $i_D = -(v_{IN} + 0.7)/(4k)$
4. apply $i_D > 0$, therefore
 $-(v_{IN} + 0.7)/4k > 0$
 $v_{IN} < -0.7$
5. Next

1. RB case:
2. open ($i_D = 0$)
3. $v_{OUT} = 0$
 $v_D = v_{OUT} - v_{IN}$
 $v_D = -v_{IN}$
4. apply $v_D < 0.7$, therefore
 $v_{IN} > -0.7$
5. Done

Problem 3.

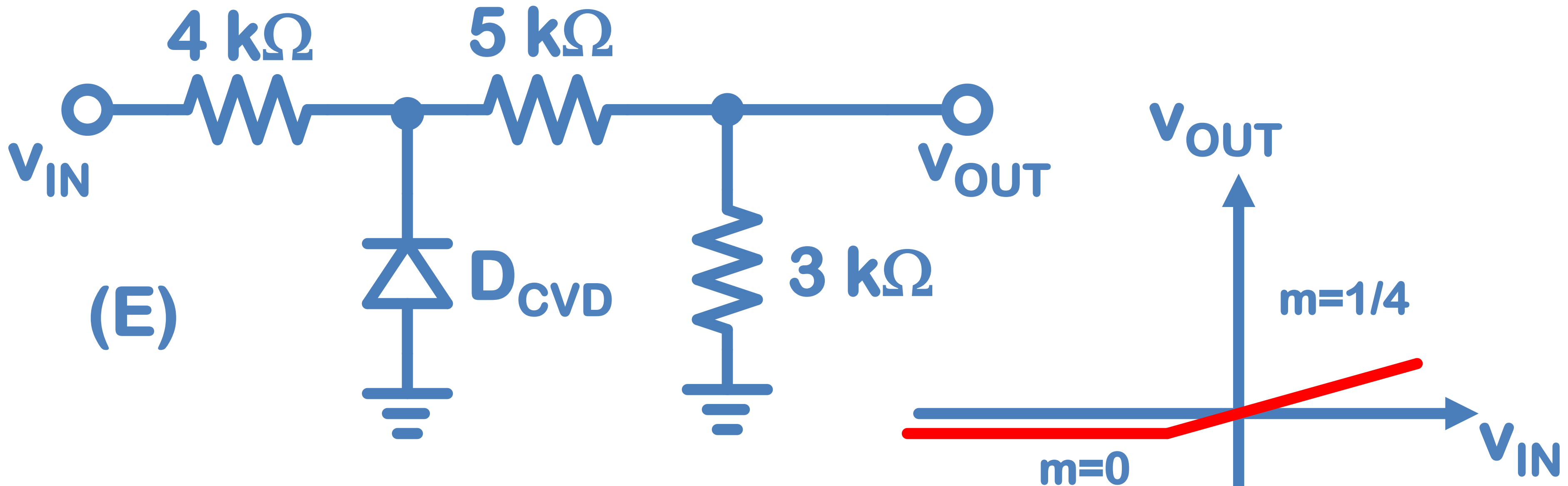a) Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.



(E)

1. FB case:
2. short ($v_D=0.7$)
3. $v_{OUT}=-0.7(3/8)$
 $i_D = (-0.7-v_{IN})/(4k)+-.7/8k$
4. apply $i_D>0$, therefore
 $(-0.7-v_{IN})/(4k)+-.7/8k > 0$
 $(-1.4-2v_{IN}) -.7 > 0$
 $-2v_{IN}>2.1$
 $v_{IN}<-1.05$
5. Next

1. RB case:
2. open ($i_D=0$)
3. $v_{OUT}=(3k/(4k+5k+3k))v_{IN}$
 $v_{OUT} = (1/4)v_{IN}$
 $v_D = 0-(8k/12k)v_{IN}$
 $v_D = 0-(2/3)v_{IN}$
4. apply $v_D<0.7$, therefore
 $v_{IN} > (-3/2).7 = -1.05$
5. Done



answer:

$$v_{OUT} = -(3/8)0.7, v_{IN}<-1.05$$

$$v_{OUT} = (1/4)v_{IN}, v_{IN}>1.05$$

Problem 3.

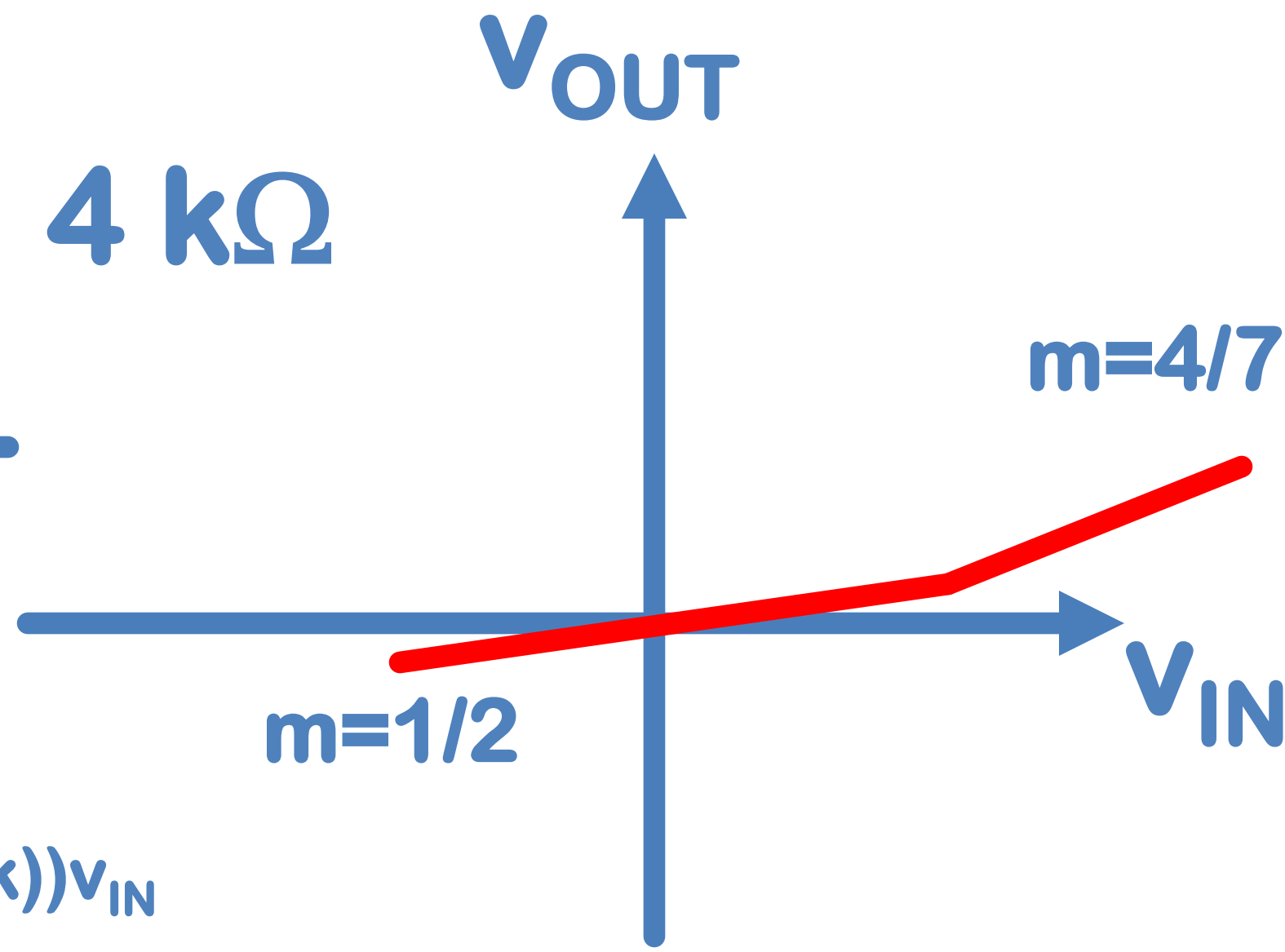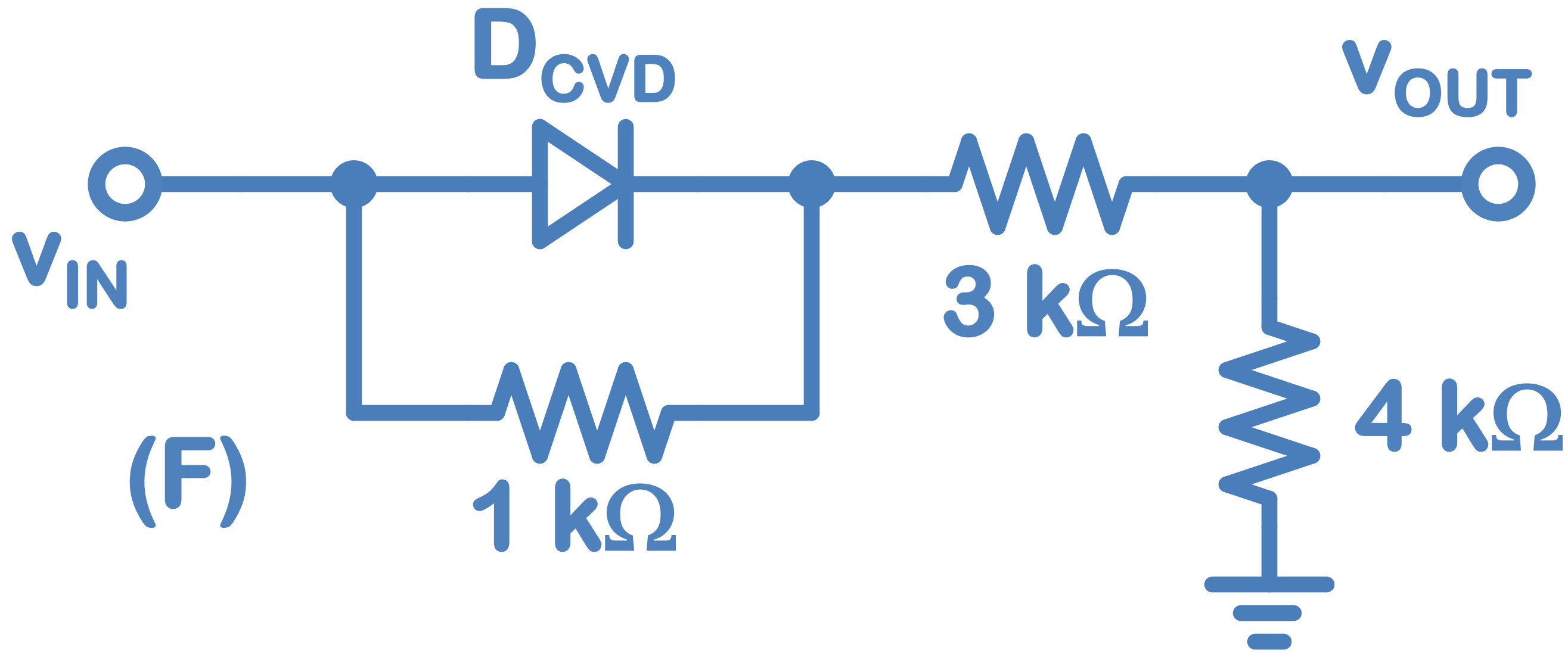a) Find the equation and plot $v_{OUT}(v_{IN})$ for each circuit.




1. FB case:
2. CVD ($v_D=0.7$)
3. $v_{OUT}=(4k/(3k+4k))(v_{IN}-0.7)$
 $v_{OUT} = (4/7)(v_{IN}-0.7)$
 $i_D = (v_{IN}-0.7)/(7k)-0.7/1k$
4. apply $i_D > 0$, therefore
 $(v_{IN}-0.7)/(7k) > 0.7/1k$
 $v_{IN} > 5.6$

1. RB case:
2. open ($i_D=0$)
3. $v_{OUT}=(4k/(1k+3k+4k))v_{IN}$
 $v_{OUT} = (1/2)v_{IN}$
 $v_D = (1/8)v_{IN}$
4. apply $v_D < 0.7$, therefore
 $v_{IN} < 5.6$
5. Done

answer:
 $v_{OUT} = (4/7)(v_{IN}-0.7), v_{IN} > 5.6$
 $v_{OUT} = (1/2)v_{IN}, v_{IN} < 5.6$

5. Next

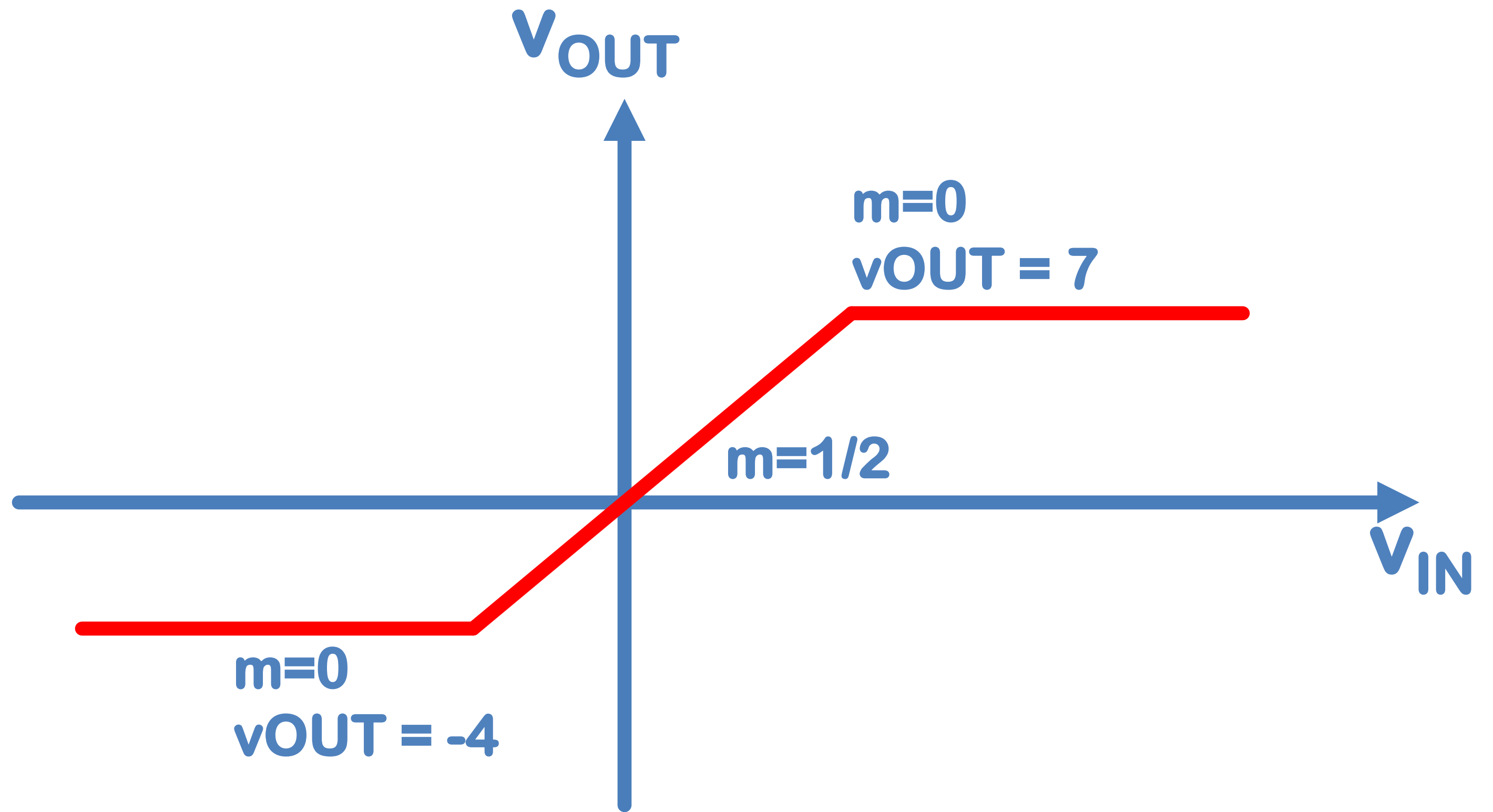

$$v_{OUT} = (1/2)v_{IN}, \quad -9.4 < v_{IN} < 15.4$$

$$v_{OUT} = -4.7, \quad v_{IN} < -9.4$$

$$v_{OUT} = 7.7, \quad v_{IN} > 15.4$$