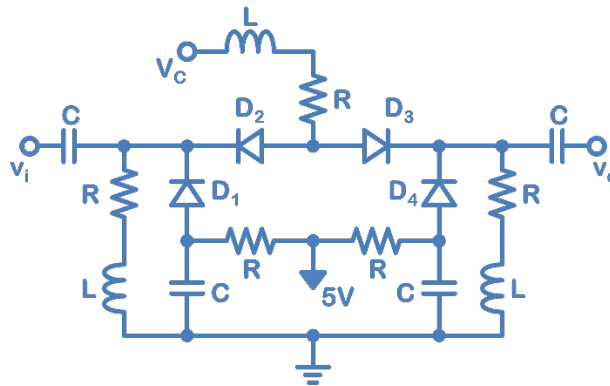


Small Signal Analysis

The figure below shows a circuit for an improved Waugh Voltage Controlled Attenuator, where V_C and $V_+(5V)$ are the large-signal voltage sources.

Reference: <https://www.microwaves101.com/encyclopedias/waugh-attenuator>



Large-Signal Sources.

V_C is the “constant” control voltage.

5V is a constant voltage.

Small-Signal Source.

The small signal input v_i is on the left.

Small-Signal probe.

The small signal output v_o is on the right.

Assume all capacitors and inductors are very large, $R=400\Omega$, and $n=2.32$ for all diodes.

1. Draw the large-signal circuit.
2. Using the 0.7V CVD model, find the large signal diode currents for large signal control voltages:
 $V_C = 3V, 5V, 7V, 9V, 11V, 13V$
 hint: The circuit is symmetrical, so you can just analyze half.
 Split the top resistor into two parallel resistors with values $2R=800\Omega$.
 $I_{D1}=I_{D4}$, and $I_{D2}=I_{D3}$
3. Calculate the small signal resistances for the diodes for each control voltage.
4. Draw the small-signal circuit.
5. Find the small signal ratio, v_o/v_i , for each control voltage.
6. Generate a plot of the small signal ratio in terms of V_C using your points.
7. Simulate the circuit using your favorite CAD tool to find and plot v_o/v_i vs. V_C .
 Use $I_S=2.27e-8$ Amps and $n=2.23$.